

SOLUTIONS

CHAPTER 1

Exercise 1.1

(a) Biologists study cells at many levels. The cells are built from organelles such as the mitochondria, ribosomes, and chloroplasts. Organelles are built of macromolecules such as proteins, lipids, nucleic acids, and carbohydrates. These biochemical macromolecules are built simpler molecules such as carbon chains and amino acids. When studying at one of these levels of abstraction, biologists are usually interested in the levels above and below: what the structures at that level are used to build, and how the structures themselves are built.

(b) The fundamental building blocks of chemistry are electrons, protons, and neutrons (physicists are interested in how the protons and neutrons are built). These blocks combine to form atoms. Atoms combine to form molecules. For example, when chemists study molecules, they can abstract away the lower levels of detail so that they can describe the general properties of a molecule such as benzene without having to calculate the motion of the individual electrons in the molecule.

Exercise 1.2

(a) Automobile designers use hierarchy to construct a car from major assemblies such as the engine, body, and suspension. The assemblies are constructed from subassemblies; for example, the engine contains cylinders, fuel injectors, the ignition system, and the drive shaft. Modularity allows components to be swapped without redesigning the rest of the car; for example, the seats can be cloth, leather, or leather with a built in heater depending on the model of the vehicle, so long as they all mount to the body in the same place. Regularity involves the use of interchangeable parts and the sharing of parts between different vehicles; a 65R14 tire can be used on many different cars.

(b) Businesses use hierarchy in their organization chart. An employee reports to a manager, who reports to a general manager who reports to a vice president who reports to the president. Modularity includes well-defined interfaces between divisions. The salesperson who spills a coke in his laptop calls a single number for technical support and does not need to know the detailed organization of the information systems department. Regularity includes the use of standard procedures. Accountants follow a well-defined set of rules to calculate profit and loss so that the finances of each division can be combined to determine the finances of the company and so that the finances of the company can be reported to investors who can make a straightforward comparison with other companies.

Exercise 1.3

Ben can use a hierarchy to design the house. First, he can decide how many bedrooms, bathrooms, kitchens, and other rooms he would like. He can then jump up a level of hierarchy to decide the overall layout and dimensions of the house. At the top-level of the hierarchy, he material he would like to use, what kind of roof, etc. He can then jump to an even lower level of hierarchy to decide the specific layout of each room, where he would like to place the doors, windows, etc. He can use the principle of regularity in planning the framing of the house. By using the same type of material, he can scale the framing depending on the dimensions of each room. He can also use regularity to choose the same (or a small set of) doors and windows for each room. That way, when he places a new door or window he need not redesign the size, material, layout specifications from scratch. This is also an example of modularity: once he has designed the specifications for the windows in one room, for example, he need not re-specify them when he uses the same windows in another room. This will save him both design time and, thus, money. He could also save by buying some items (like windows) in bulk.

Exercise 1.4

An accuracy of ± 50 mV indicates that the signal can be resolved to 100 mV intervals. There are 50 such intervals in the range of 0-5 volts, so the signal represents $\log_2 50 = 5.64$ bits of information.

Exercise 1.5

(a) The hour hand can be resolved to $12 * 4 = 48$ positions, which represents $\log_2 48 = 5.58$ bits of information. (b) Knowing whether it is before or after noon adds one more bit.

Exercise 1.6

Each digit conveys $\log_2 60 = 5.91$ bits of information. $4000_{10} = 1\ 6\ 40_{60}$ (1 in the 3600 column, 6 in the 60's column, and 40 in the 1's column).

Exercise 1.7

$$2^{16} = 65,536 \text{ numbers.}$$

Exercise 1.8

$$2^{32} - 1 = 4,294,967,295$$

Exercise 1.9

$$(a) 2^{16} - 1 = 65535; (b) 2^{15} - 1 = 32767; (c) 2^{15} - 1 = 32767$$

Exercise 1.10

$$(a) 2^{32} - 1 = 4,294,967,295; (b) 2^{31} - 1 = 2,147,483,647; (c) 2^{31} - 1 = 2,147,483,647$$

Exercise 1.11

$$(a) 0; (b) -2^{15} = -32768; (c) -(2^{15} - 1) = -32767$$

Exercise 1.12

$$(a) 0; (b) -2^{31} = -2,147,483,648; (c) -(2^{31} - 1) = -2,147,483,647;$$

Exercise 1.13

$$(a) 10; (b) 54; (c) 240; (d) 2215$$

Exercise 1.14

$$(a) 14; (b) 36; (c) 215; (d) 15,012$$

Exercise 1.15

$$(a) A; (b) 36; (c) F0; (d) 8A7$$

Exercise 1.16

(a) E; (b) 24; (c) D7; (d) 3AA4

Exercise 1.17

(a) 165; (b) 59; (c) 65535; (d) 3489660928

Exercise 1.18

(a) 78; (b) 124; (c) 60,730; (d) 1,077,915, 649

Exercise 1.19

(a) 10100101; (b) 00111011; (c) 1111111111111111;
(d) 11010000000000000000000000000000

Exercise 1.20

(a) 1001110; (b) 1111100; (c) 1110110100111010; (d) 100 0000 0011
1111 1011 0000 0000 0001

Exercise 1.21

(a) -6; (b) -10; (c) 112; (d) -97

Exercise 1.22

(a) -2 ($-8+4+2 = -2$ or magnitude = $0001+1 = 0010$: thus, -2); (b) -29 (-32
 $+2+1 = -29$ or magnitude = $011100+1 = 011101$: thus, -29); (c) 78; (d) -75

Exercise 1.23

(a) -2; (b) -22; (c) 112; (d) -31

Exercise 1.24

(a) -6; (b) -3; (c) 78; (d) -53

Exercise 1.25

(a) 101010; (b) 111111; (c) 11100101; (d) 1101001101

Exercise 1.26

(a) 1110; (b) 110100; (c) 101010011; (d) 1011000111

Exercise 1.27

(a) 2A; (b) 3F; (c) E5; (d) 34D

Exercise 1.28

(a) E; (b) 34; (c) 153; (d) 2C7;

Exercise 1.29

(a) 00101010; (b) 11000001; (c) 01111100; (d) 10000000; (e) overflow

Exercise 1.30

(a) 00011000; (b) 11000101; (c) overflow; (d) overflow; (e) 01111111\

Exercise 1.31

00101010; (b) 10111111; (c) 01111100; (d) overflow; (e) overflow

Exercise 1.32

(a) 00011000; (b) 10111011; (c) overflow; (d) overflow; (e) 01111111

Exercise 1.33

(a) 00000101; (b) 11111010

Exercise 1.34

(a) 00000111; (b) 11111001

Exercise 1.35

(a) 00000101; (b) 00001010

Exercise 1.36

(a) 00000111; (b) 00001001

Exercise 1.37

(a) 52; (b) 77; (c) 345; (d) 1515

Exercise 1.38

(a) 0o16; (b) 0o64; (c) 0o339; (d) 0o1307

Exercise 1.39

(a) 100010_2 , 22_{16} , 34_{10} ; (b) 110011_2 , 33_{16} , 51_{10} ; (c) 010101101_2 , AD_{16} , 173_{10} ; (d) 011000100111_2 , 627_{16} , 1575_{10}

Exercise 1.40

(a) 0b10011; 0x13; 19; (b) 0b100101; 0x25; 37; (c) 0b11111001; 0xF9; 249; (d) 0b10101110000; 0x570; 1392

Exercise 1.41

15 greater than 0, 16 less than 0; 15 greater and 15 less for sign/magnitude

Exercise 1.42

(26-1) are greater than 0; 26 are less than 0. For sign/magnitude numbers, (26-1) are still greater than 0, but (26-1) are less than 0.

Exercise 1.43

4, 8

Exercise 1.44

8

Exercise 1.45

5,760,000

Exercise 1.46

$(5 \times 10^9 \text{ bits/second})(60 \text{ seconds/minute})(1 \text{ byte/8 bits}) = 3.75 \times 10^{10}$ bytes

Exercise 1.47

46.566 gigabytes


Exercise 1.48

2 billion


Exercise 1.49

128 kbits

Exercise 1.50

 

Exercise 1.51

 

Exercise 1.52

(a) 1101; (b) 11000 (overflows)

Exercise 1.53

(a) 11011101; (b) 110001000 (overflows)

Exercise 1.54

(a) 11012, no overflow; (b) 10002, no overflow

Exercise 1.55

(a) 11011101; (b) 110001000

Exercise 1.56

- (a) $010000 + 001001 = 011001$;
- (b) $011011 + 011111 = 111010$ (overflow);
- (c) $111100 + 010011 = 001111$;
- (d) $000011 + 100000 = 100011$;
- (e) $110000 + 110111 = 100111$;
- (f) $100101 + 100001 = 000110$ (overflow)

Exercise 1.57

- (a) $000111 + 001101 = 010100$
- (b) $010001 + 011001 = 101010$, overflow
- (c) $100110 + 001000 = 101110$
- (d) $011111 + 110010 = 010001$
- (e) $101101 + 101010 = 010111$, overflow
- (f) $111110 + 100011 = 100001$

Exercise 1.58

(a) 10; (b) 3B; (c) E9; (d) 13C (overflow)

Exercise 1.59

(a) 0x2A; (b) 0x9F; (c) 0xFE; (d) 0x66, overflow

Exercise 1.60

(a) $01001 - 00111 = 00010$; (b) $01100 - 01111 = 11101$; (c) $11010 - 01011 = 01111$; (d) $00100 - 11000 = 01100$


Exercise 1.61

(a) $010010 + 110100 = 000110$; (b) $011110 + 110111 = 010101$; (c) $100100 + 111101 = 100001$; (d) $110000 + 101011 = 011011$, overflow

Exercise 1.62

(a) 3; (b) 01111111; (c) $00000000_2 = -127_{10}$; $11111111_2 = 128_{10}$

Exercise 1.63

 

Exercise 1.64

(a) 001010001001; (b) 951; (c) 1000101; (d) each 4-bit group represents one decimal digit, so conversion between binary and decimal is easy. BCD can also be used to represent decimal fractions exactly.

Exercise 1.65

(a) 0011 0111 0001

(b) 187

(c) $95 = 1011111$

(d) Addition of BCD numbers doesn't work directly. Also, the representation doesn't maximize the amount of information that can be stored; for example 2 BCD digits requires 8 bits and can store up to 100 values (0-99) - unsigned 8-bit binary can store 28 (256) values.

Exercise 1.66

Three on each hand, so that they count in base six.

Exercise 1.67

Both of them are full of it. $42_{10} = 101010_2$, which has 3 1's in its representation.

Exercise 1.68

Both are right.

Exercise 1.69

```
#include <stdio.h>
```

```
void main(void)
{
    char bin[80];
    int i = 0, dec = 0;

    printf("Enter binary number: ");
    scanf("%s", bin);

    while (bin[i] != 0) {
        if (bin[i] == '0') dec = dec * 2;
        else if (bin[i] == '1') dec = dec * 2 + 1;
        else printf("Bad character %c in the number.\n", bin[i]);
        i = i + 1;
    }
    printf("The decimal equivalent is %d\n", dec);
}
```

Exercise 1.70

```
/* This program works for numbers that don't overflow the
   range of an integer. */

#include <stdio.h>

void main(void)
{
    int b1, b2, digits1 = 0, digits2 = 0;
    char num1[80], num2[80], tmp, c;
    int digit, num = 0, j;

    printf ("Enter base #1: "); scanf("%d", &b1);
    printf ("Enter base #2: "); scanf("%d", &b2);
    printf ("Enter number in base %d ", b1); scanf("%s", num1);


    while (num1[digits1] != 0) {
        c = num1[digits1++];
        if (c >= 'a' && c <= 'z') c = c + 'A' - 'a';
        if (c >= '0' && c <= '9') digit = c - '0';
        else if (c >= 'A' && c <= 'F') digit = c - 'A' + 10;
        else printf("Illegal character %c\n", c);
        if (digit >= b1) printf("Illegal digit %c\n", c);
        num = num * b1 + digit;
    }
    while (num > 0) {
        digit = num % b2;
        num = num / b2;
        num2[digits2++] = digit < 10 ? digit + '0' : digit + 'A' -
10;
    }
    num2[digits2] = 0;

    for (j = 0; j < digits2/2; j++) { // reverse order of digits
        tmp = num2[j];
        num2[j] = num2[digits2-j-1];
        num2[digits2-j-1] = tmp;
    }

    printf("The base %d equivalent is %s\n", b2, num2);
}
```

Exercise 1.71

OR3

 


$$Y = A + B + C$$

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

(a)

XOR3

 


$$Y = A \oplus B \oplus C$$

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

(b)

XNOR4

 


$$Y = \overline{A \oplus B \oplus C \oplus D}$$

| A | C | B | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

(c)

Exercise 1.72


OR4

 

$Y = A+B+C+D$

| A | C | B | D | Y |
|-------|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| (a) 1 | 1 | 1 | 1 | 1 |


XNOR3

 

$Y = A \oplus B \oplus C$

| A | B | C | Y |
|-----|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |
| (b) | | | |

NAND5

 

$Y = \overline{ABCDE}$

| A | B | C | D | E | Y |
|-------|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |
| (c) 1 | 1 | 1 | 1 | 1 | 0 |

Exercise 1.73

| <i>A</i> | <i>B</i> | <i>C</i> | <i>Y</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Exercise 1.74

| <i>A</i> | <i>B</i> | <i>C</i> | <i>Y</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Exercise 1.75

| <i>A</i> | <i>B</i> | <i>C</i> | <i>Y</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Exercise 1.76

| | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|--|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|--|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>Zero</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>A NOR B</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>\overline{AB}</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>NOT A</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>$A\overline{B}$</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>NOT B</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>XOR</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <div>NAND</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>AND</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>XNOR</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>B</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>$\overline{A} + B$</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>A</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>$A + \overline{B}$</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>OR</div> | A | B | Y | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | <table><tr><td>A</td><td>B</td><td>Y</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <div>One</div> | A | B | Y | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| A | B | Y | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

Exercise 1.77

2^{2^N}

Exercise 1.78

$V_{IL} = 2.5; V_{IH} = 3; V_{OL} = 1.5; V_{OH} = 4; NM_L = 1; NM_H = 1$

Exercise 1.79

No, there is no legal set of logic levels. The slope of the transfer characteristic never is better than -1, so the system never has any gain to compensate for noise.

Exercise 1.80

$V_{IL} = 2; V_{IH} = 4; V_{OL} = 1; V_{OH} = 4.5; NM_L = 1; NM_H = 0.5$

Exercise 1.81

The circuit functions as a buffer with logic levels $V_{IL} = 1.5$; $V_{IH} = 1.8$; $V_{OL} = 1.2$; $V_{OH} = 3.0$. It can receive inputs from LVCMOS and LVTTL gates because their output logic levels are compatible with this gate's input levels. However, it cannot drive LVCMOS or LVTTL gates because the $1.2 V_{OL}$ exceeds the V_{IL} of LVCMOS and LVTTL.


Exercise 1.82

(a) AND gate; (b) $V_{IL} = 1.5$; $V_{IH} = 2.25$; $V_{OL} = 0$; $V_{OH} = 3$


Exercise 1.83

(a) XOR gate; (b) $V_{IL} = 1.25$; $V_{IH} = 2$; $V_{OL} = 0$; $V_{OH} = 3$


Exercise 1.84

 

Exercise 1.85

 

Exercise 1.86

 

Exercise 1.87


XOR

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


Exercise 1.88

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |


Exercise 1.89

 

Exercise 1.90

 

Question 1.1

 

Question 1.2

4 times. Place 22 coins on one side and 22 on the other. If one side rises, the fake is on that side. Otherwise, the fake is among the 20 remaining. From the group containing the fake, place 8 on one side and 8 on the other. Again, identify which group contains the fake. From that group, place 3 on one side and 3 on the other. Again, identify which group contains the fake. Finally, place 1 coin on each side. Now the fake coin is apparent.

Question 1.3

17 minutes: (1) designer and freshman cross (2 minutes); (2) freshman returns (1 minute); (3) professor and TA cross (10 minutes); (4) designer returns (2 minutes); (5) designer and freshman cross (2 minutes).

CHAPTER 2

Exercise 2.1

(a) $Y = \bar{A}\bar{B} + A\bar{B} + AB$

(b) $Y = \bar{A}\bar{B}\bar{C} + ABC$

(c) $Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$

(d)

$$Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$$

(e)

$$Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$$

Exercise 2.2

(a) $Y = \bar{A}B + A\bar{B} + AB$

(b) $Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$

(c) $Y = \bar{A}\bar{B}C + AB\bar{C} + ABC$

(d) $Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}BCD + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD$

(e) $Y = \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}CD + A\bar{B}\bar{C}D$

Exercise 2.3

(a) $Y = (A + \bar{B})$

(b)

$$Y = (A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

(c) $Y = (A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$

(d)

$$Y = (A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)(A + \bar{B} + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(\bar{A} + B + \bar{C} + D)(\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D)$$

(e)

$$Y = (A + B + C + \bar{D})(A + B + \bar{C} + D)(A + \bar{B} + C + D)(A + \bar{B} + \bar{C} + \bar{D})(\bar{A} + B + C + D)(\bar{A} + B + \bar{C} + D)(\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D)$$

Exercise 2.4

(a) $Y = A + B$

(b) $Y = (A + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + \bar{C})$

(c) $Y = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + B + \bar{C})$

(d)

$$Y = (A + B + C + \bar{D})(A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(\bar{A} + B + C + \bar{D})(\bar{A} + B + \bar{C} + \bar{D})(\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + \bar{C} + D)$$

(e)

$$Y = (A + B + C + D)(A + B + C + \bar{D})(A + B + \bar{C} + D)(A + \bar{B} + C + D)(\bar{A} + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + D)$$

Exercise 2.5

(a) $Y = A + \bar{B}$

(b) $Y = \bar{A}\bar{B}\bar{C} + ABC$

(c) $Y = \bar{A}\bar{C} + A\bar{B} + AC$

(d) $Y = \bar{A}\bar{B} + \bar{B}\bar{D} + ACD$

(e)

$$Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + ABC\bar{D} + ABCD$$

This can also be expressed as:

$$Y = \overline{(A \oplus B)}\overline{(C \oplus D)} + (A \oplus B)(C \oplus D)$$

Exercise 2.6

(a) $Y = A + B$

(b) $Y = A\bar{C} + \bar{A}C + B\bar{C}$ or $Y = A\bar{C} + \bar{A}C + \bar{A}B$


(c) $Y = AB + \bar{A}\bar{B}C$

(d) $Y = BC + \bar{B}\bar{D}$


(e) $Y = A\bar{B} + \bar{A}BC + \bar{A}CD$ or $Y = A\bar{B} + \bar{A}BC + \bar{B}CD$

Exercise 2.7


(a)

 


(b)

 


(c)

 






(d)

 

(e)

 


Exercise 2.8

     


Exercise 2.9

(a) Same as 2.7(a)


(b)

 


(c)

 


(d)

 

(e)

 


Exercise 2.10

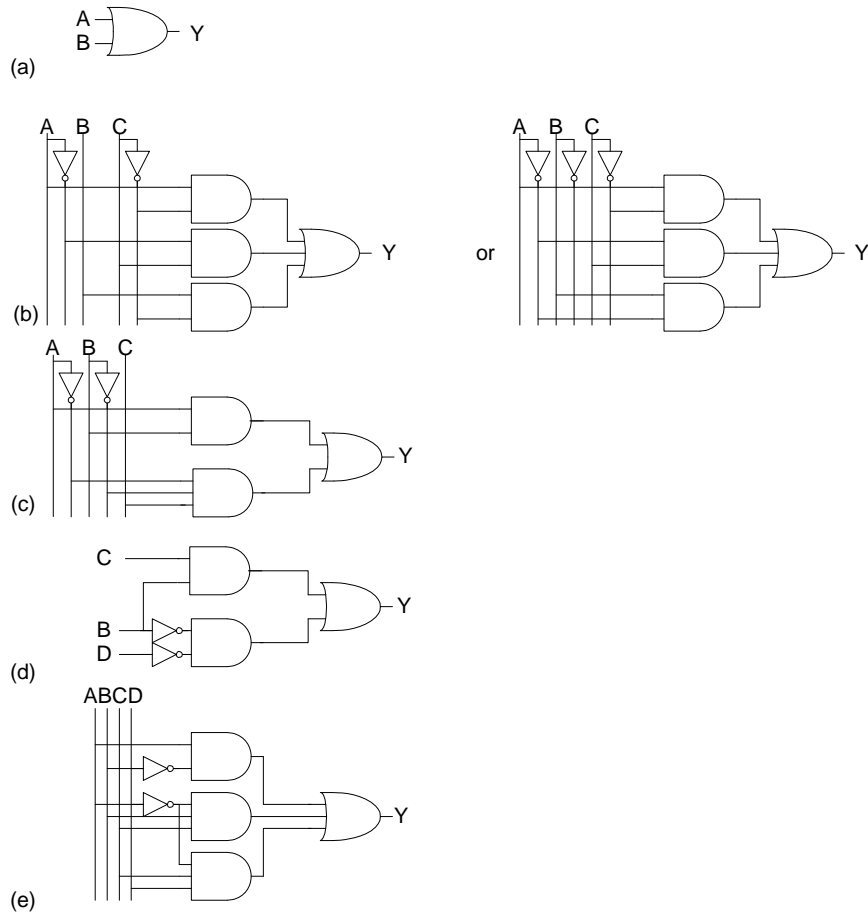


Exercise 2.11


(a)

 


(b)

 


(c)

 


(d)

 

(e)

 

Exercise 2.12

 

Exercise 2.13

- (a) $Y = AC + \overline{B}C$
 (b) $Y = \overline{A}$
 (c) $Y = \overline{A} + \overline{B}\overline{C} + \overline{B}\overline{D} + BD$


Exercise 2.14

- (a) $Y = \overline{A}B$
 (b) $Y = \overline{A} + \overline{B} + \overline{C} = \overline{ABC}$


$$(c) Y = A(\bar{B} + \bar{C} + \bar{D}) + \bar{B}\bar{C}\bar{D} = \overline{ABCD} + \bar{B}\bar{C}\bar{D}$$

Exercise 2.15


(a)

 


(b)

 


(c)

 


Exercise 2.16

 

(a)

 


(b)

 


(c)

Exercise 2.17


(a) $Y = B + \bar{A}\bar{C}$

 

(b) $Y = \bar{A}B$

 

(c) $Y = A + \bar{B}\bar{C} + \bar{D}\bar{E}$

 

Exercise 2.18

(a) $Y = \bar{B} + C$


(b) $Y = (A + \bar{C})D + B$

(c) $Y = B\bar{D}E + BD(\overline{A \oplus C})$

Exercise 2.19



4 gigarows = 4×2^{30} rows = 2^{32} rows, so the truth table has 32 inputs.

Exercise 2.20

 

Exercise 2.21

Ben is correct. For example, the following function, shown as a K-map, has two possible minimal sum-of-products expressions. Thus, although $\overline{A}\overline{C}\overline{D}$ and $\overline{B}\overline{C}\overline{D}$ are both prime implicants, the minimal sum-of-products expression does not have both of them.

  

Exercise 2.22

(a)

| B | $B \bullet B$ |
|-----|---------------|
| 0 | 0 |
| 1 | 1 |

(b)

| B | C | D | $(B \bullet C) + (B \bullet D)$ | $B \bullet (C + D)$ |
|-----|-----|-----|---------------------------------|---------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

(c)

| B | C | $(B \bullet C) + (B \bullet \bar{C})$ |
|-----|-----|---------------------------------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Exercise 2.23



| B_2 | B_1 | B_0 | $\overline{B_2 \bullet B_1 \bullet B_0}$ | $\overline{B_2} + \overline{B_1} + \overline{B_0}$ |
|-------|-------|-------|--|--|
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

Exercise 2.24


$$Y = \bar{A}D + \bar{A}\bar{B}C + \bar{A}\bar{C}D + ABCD$$

$$Z = \bar{A}\bar{C}D + BD$$

Exercise 2.25

  


Exercise 2.26

 

$$Y = (\bar{A} + \bar{B})(\bar{C} + \bar{D}) + \bar{E}$$

Exercise 2.27

 

$$Y = ABC + \bar{D} + (\bar{F} + \bar{G})\bar{E}$$

$$= ABC + \bar{D} + \bar{E}\bar{F} + \bar{E}\bar{G}$$

Exercise 2.28

Two possible options are shown below:

| Y CD \ AB | AB | | | |
|--------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | X | 0 | 1 | 1 |
| 01 | X | X | 1 | 0 |
| 11 | 0 | X | 1 | 1 |
| 10 | X | 0 | X | X |


(a) $Y = A\bar{D} + AC + BD$

| Y CD \ AB | AB | | | |
|--------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | X | 0 | 1 | 1 |
| 01 | X | X | 1 | 0 |
| 11 | 0 | X | 1 | 1 |
| 10 | X | 0 | X | X |

(b) $Y = A(B + C + \bar{D})$

Exercise 2.29

Two possible options are shown below:

 

Exercise 2.30


Option (a) could have a glitch when $A=1$, $B=1$, $C=0$, and D transitions from 1 to 0. The glitch could be removed by instead using the circuit in option (b).

Option (b) does not have a glitch. Only one path exists from any given input to the output.

Exercise 2.31

$$Y = \bar{A}D + A\bar{B}\bar{C}\bar{D} + BD + CD = A\bar{B}\bar{C}\bar{D} + D(\bar{A} + B + C)$$

Exercise 2.32

 

Exercise 2.33

The equation can be written directly from the description:

$$E = \bar{S}\bar{A} + AL + H$$

Exercise 2.34

(a)

| S_c $D_{1:0} \backslash D_{3:2}$ | | 00 | 01 | 11 | 10 |
|---------------------------------------|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 0 | 1 | |
| 01 | 1 | 1 | 0 | 1 | |
| 11 | 1 | 1 | 0 | 0 | |
| 10 | 0 | 1 | 0 | 0 | |

$$S_c = \bar{D}_3 D_0 + \bar{D}_3 D_2 + \bar{D}_2 \bar{D}_1$$

| S_d $D_{1:0} \backslash D_{3:2}$ | | 00 | 01 | 11 | 10 |
|---------------------------------------|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | 1 | 0 | 0 | 1 | |
| 01 | 0 | 1 | 0 | 0 | |
| 11 | 1 | 0 | 0 | 0 | |
| 10 | 1 | 1 | 0 | 0 | |

$$S_d = \bar{D}_3 D_1 \bar{D}_0 + \bar{D}_3 \bar{D}_2 D_1 + \bar{D}_2 \bar{D}_1 \bar{D}_0 + \bar{D}_3 D_2 \bar{D}_1 D_0$$

| S_e $D_{1:0} \backslash D_{3:2}$ | | 00 | 01 | 11 | 10 |
|---------------------------------------|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | 1 | 0 | 0 | 1 | |
| 01 | 0 | 0 | 0 | 0 | |
| 11 | 0 | 0 | 0 | 0 | |
| 10 | 1 | 1 | 0 | 0 | |

$$S_e = \bar{D}_2 \bar{D}_1 \bar{D}_0 + \bar{D}_3 D_1 \bar{D}_0$$

$L_{D_2 D_1 L_0} + L_{D_3 D_2 L_1 D_0}$

| S_f $D_{1:0} \backslash D_{3:2}$ | | 00 | 01 | 11 | 10 |
|---------------------------------------|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | 00 | 1 | 1 | 0 | 1 |
| | 01 | 0 | 1 | 0 | 1 |
| | 11 | 0 | 0 | 0 | 0 |
| | 10 | 0 | 1 | 0 | 0 |

$$S_f = \bar{D}_3 \bar{D}_1 \bar{D}_0 + \bar{D}_3 D_2 \bar{D}_1 + \bar{D}_3 D_2 \bar{D}_0 + D_3 \bar{D}_2 \bar{D}_1$$

| S_g $D_{1:0}$ | | $D_{3:2}$ | | | |
|--------------------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | 00 | 0 | 1 | 0 | 1 |
| | 01 | 0 | 1 | 0 | 1 |
| | 11 | 1 | 0 | 0 | 0 |
| | 10 | 1 | 1 | 0 | 0 |

$$S_g = \bar{D}_3 \bar{D}_2 D_1 + \bar{D}_3 D_1 \bar{D}_0 + \bar{D}_3 D_2 \bar{D}_1 + D_3 \bar{D}_2 \bar{D}_1$$

(b)

S_a

| $D_{3:2}$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| $D_{1:0}$ | | | | |
| 00 | 1 | 0 | X | 1 |
| 01 | 0 | 1 | X | 1 |
| 11 | 1 | 1 | X | X |
| 10 | 0 | 1 | X | X |

$$S_a = \bar{D}_2 \bar{D}_1 \bar{D}_0 + D_2 D_0 + D_3 + D_2 D_1 + D_1 D_0$$

S_b

| $D_{3:2}$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| $D_{1:0}$ | | | | |
| 00 | 1 | 1 | X | 1 |
| 01 | 1 | 0 | X | 1 |
| 11 | 1 | 1 | X | X |
| 10 | 1 | 0 | X | X |

$$S_b = \bar{D}_1 \bar{D}_0 + D_1 D_0 + \bar{D}_2$$

S_c

| $D_{3:2}$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| $D_{1:0}$ | | | | |
| 00 | 1 | 1 | X | 1 |
| 01 | 1 | 1 | X | 1 |
| 11 | 1 | 1 | X | X |
| 10 | 0 | 1 | X | X |

$$S_c = \bar{D}_1 + D_0 + D_2$$

S_d

| $D_{3:2}$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| $D_{1:0}$ | | | | |
| 00 | 1 | 0 | X | 1 |
| 01 | 0 | 1 | X | 0 |
| 11 | 1 | 0 | X | X |
| 10 | 1 | 1 | X | X |

$$S_d = D_2 \bar{D}_1 D_0 + \bar{D}_2 \bar{D}_0 + \bar{D}_2 D_1 + D_1 \bar{D}_0$$

S_e

| $D_{1:0} \backslash D_{3:2}$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00 | 1 | 0 | X | 1 |
| 01 | 0 | 0 | X | 0 |
| 11 | 0 | 0 | X | X |
| 10 | 1 | 1 | X | X |

$$S_e = \bar{D}_2 \bar{D}_0 + D_1 \bar{D}_0$$

S_f

| $D_{1:0} \backslash D_{3:2}$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00 | 1 | 1 | X | 1 |
| 01 | 0 | 1 | X | 1 |
| 11 | 0 | 0 | X | X |
| 10 | 0 | 1 | X | X |


$$S_f = \bar{D}_1 \bar{D}_0 + D_2 \bar{D}_1 + D_2 \bar{D}_0 + D_3$$

S_g

| $D_{1:0} \backslash D_{3:2}$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00 | 0 | 1 | X | 1 |
| 01 | 0 | 1 | X | 1 |
| 11 | 1 | 0 | X | X |
| 10 | 1 | 1 | X | X |

$$S_g = \bar{D}_2 D_1 + D_2 \bar{D}_0 + D_2 \bar{D}_1 + D_3$$

(c)

 

Exercise 2.35

| Decimal Value | A_3 | A_2 | A_1 | A_0 | D | P |
|---------------|-------|-------|-------|-------|-----|-----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 | 0 | 1 |
| 8 | 1 | 0 | 0 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 | 1 | 0 |
| 10 | 1 | 0 | 1 | 0 | 0 | 0 |
| 11 | 1 | 0 | 1 | 1 | 0 | 1 |
| 12 | 1 | 1 | 0 | 0 | 1 | 0 |
| 13 | 1 | 1 | 0 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 | 0 | 0 |
| 15 | 1 | 1 | 1 | 1 | 1 | 0 |

P has two possible minimal solutions:

D

$A_{3:2}$

$A_{1:0}$

| | | | | |
|----|----|----|----|---|
| 00 | 01 | 11 | 10 | |
| 00 | 0 | 0 | 1 | 0 |
| 01 | 0 | 0 | 0 | 1 |
| 11 | 1 | 0 | 1 | 0 |
| 10 | 0 | 1 | 0 | 0 |

$$D = \bar{A}_3\bar{A}_2A_1A_0 + \bar{A}_3A_2A_1\bar{A}_0 + A_3\bar{A}_2\bar{A}_1A_0 + A_3A_2\bar{A}_1\bar{A}_0 + A_3A_2A_1A_0$$

P


$A_{3:2}$

$A_{1:0}$

| | | | | |
|----|----|----|----|---|
| 00 | 01 | 11 | 10 | |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 1 | 1 | 0 |
| 11 | 1 | 1 | 0 | 1 |
| 10 | 1 | 0 | 0 | 0 |

$$P = \bar{A}_3\bar{A}_2A_0 + \bar{A}_3A_1A_0 + \bar{A}_3\bar{A}_2A_1 + \bar{A}_2A_1A_0$$
$$P = \bar{A}_3A_1A_0 + \bar{A}_3\bar{A}_2A_1 + \bar{A}_2A_1A_0 + \bar{A}_2\bar{A}_1A_0$$

Hardware implementations are below (implementing the first minimal equation given for P).

 

Exercise 2.36


| A_7 | A_6 | A_5 | A_4 | A_3 | A_2 | A_1 | A_0 | Y_2 | Y_1 | Y_0 | NONE |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | X | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | X | X | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | X | X | X | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 | X | X | X | X | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | X | X | X | X | X | 1 | 0 | 1 | 0 |
| 0 | 1 | X | X | X | X | X | X | 1 | 1 | 0 | 0 |
| 1 | X | X | X | X | X | X | X | 1 | 1 | 1 | 0 |

$$Y_2 = A_7 + A_6 + A_5 + A_4$$

$$Y_1 = A_7 + A_6 + \overline{A_5}\overline{A_4}A_3 + \overline{A_5}\overline{A_4}A_2$$

$$Y_0 = A_7 + \overline{A_6}A_5 + \overline{A_6}\overline{A_4}A_3 + \overline{A_6}\overline{A_4}\overline{A_2}A_1$$

$$NONE = \overline{A_7}\overline{A_6}\overline{A_5}\overline{A_4}\overline{A_3}\overline{A_2}\overline{A_1}\overline{A_0}$$

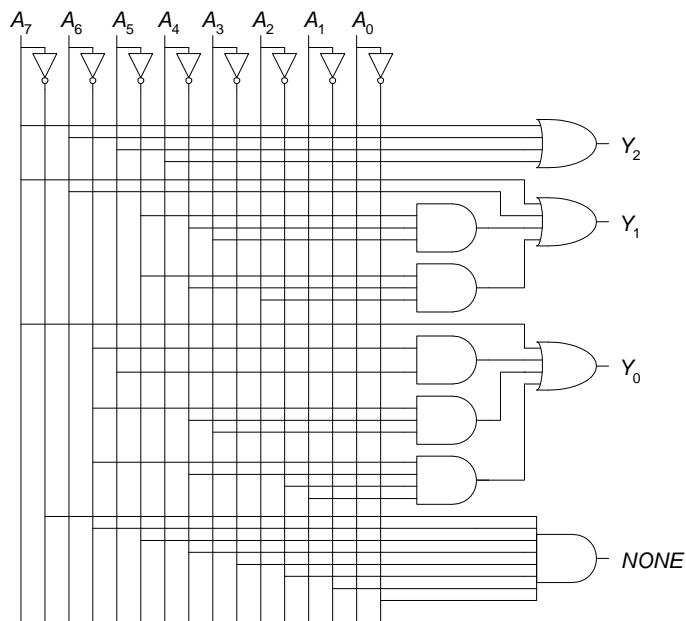

Exercise 2.37


The equations and circuit for $Y_{2:0}$ is the same as in Exercise 2.25, repeated here for convenience.

| A_7 | A_6 | A_5 | A_4 | A_3 | A_2 | A_1 | A_0 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | X | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 | X | X | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 1 | X | X | X | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | X | X | X | X | 1 | 0 | 0 |
| 0 | 0 | 1 | X | X | X | X | X | 1 | 0 | 1 |
| 0 | 1 | X | X | X | X | X | X | 1 | 1 | 0 |
| 1 | X | X | X | X | X | X | X | 1 | 1 | 1 |

$$Y_2 = A_7 + A_6 + A_5 + A_4$$

$$Y_1 = A_7 + A_6 + \overline{A_5}\overline{A_4}A_3 + \overline{A_5}\overline{A_4}A_2$$
 
$$Y_0 = A_7 + \overline{A_6}A_5 + \overline{A_6}\overline{A_4}A_3 + \overline{A_6}\overline{A_4}\overline{A_2}A_1$$




The truth table, equations, and circuit for $Z_{2:0}$ are as follows.

| A_7 | A_6 | A_5 | A_4 | A_3 | A_2 | A_1 | A_0 | Z_2 | Z_1 | Z_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | X | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 1 | X | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | X | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | X | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | X | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | X | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 1 | 1 | X | X | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | X | X | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | X | X | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | X | X | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | X | X | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | X | X | X | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | X | X | X | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | X | X | X | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | X | X | X | X | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | X | X | X | X | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | X | X | X | X | 1 | 0 | 0 |
| 0 | 1 | 1 | X | X | X | X | X | 1 | 0 | 1 |
| 1 | 0 | 1 | X | X | X | X | X | 1 | 0 | 1 |
| 1 | 1 | X | X | X | X | X | X | 1 | 1 | 0 |

$$Z_2 = A_4(A_5 + A_6 + A_7) + A_5(A_6 + A_7) + A_6A_7$$

$$Z_1 = A_2(A_3 + A_4 + A_5 + A_6 + A_7) + A_3(A_4 + A_5 + A_6 + A_7) + A_6A_7$$

$$Z_0 = A_1(A_2 + A_3 + A_4 + A_5 + A_6 + A_7) + A_3(A_4 + A_5 + A_6 + A_7) + A_5(A_6 + A_7)$$

 

Exercise 2.38

$$Y_6 = A_2 A_1 A_0$$

$$Y_5 = A_2 A_1$$


$$Y_4 = A_2 A_1 + A_2 A_0$$

$$Y_3 = A_2$$

$$Y_2 = A_2 + A_1 A_0$$

$$Y_1 = A_2 + A_1$$

$$Y_0 = A_2 + A_1 + A_0$$

 


Exercise 2.39

$$Y = A + \overline{C \oplus D} = A + CD + \overline{C}\overline{D}$$


Exercise 2.40

$$Y = \overline{\overline{C}}\overline{\overline{D}}(A \oplus B) + \overline{\overline{A}}\overline{\overline{B}} = \overline{\overline{A}}\overline{\overline{C}}\overline{\overline{D}} + \overline{\overline{B}}\overline{\overline{C}}\overline{\overline{D}} + \overline{\overline{A}}\overline{\overline{B}}$$

Exercise 2.41

 

Exercise 2.42

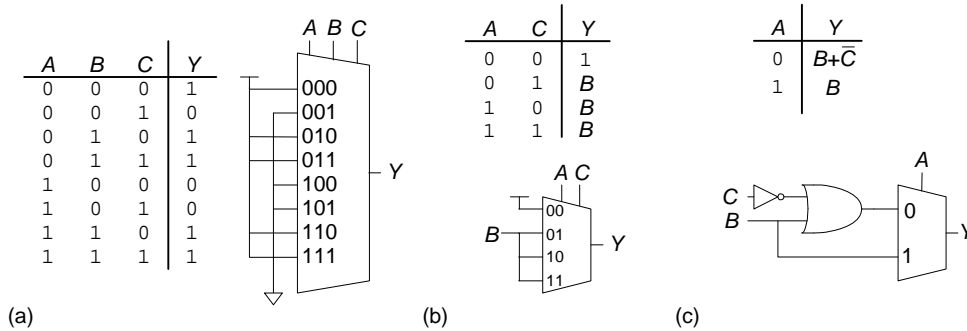

Exercise 2.43

$$t_{pd} = 3t_{pd_NAND2} = \mathbf{60\ ps}$$

$$t_{cd} = t_{cd_NAND2} = \mathbf{15\ ps}$$


Exercise 2.44

$$\begin{aligned} t_{pd} &= t_{pd_AND2} + 2t_{pd_NOR2} + t_{pd_NAND2} \\ &= [30 + 2(30) + 20]\ ps \\ &= \mathbf{110\ ps} \end{aligned}$$


$$\begin{aligned} t_{cd} &= 2t_{cd_NAND2} + t_{cd_NOR2} \\ &= [2(15) + 25]\ ps \\ &= \mathbf{55\ ps} \end{aligned}$$

Exercise 2.45

$$\begin{aligned}t_{pd} &= t_{pd_NOT} + t_{pd_AND3} \\&= 15 \text{ ps} + 40 \text{ ps} \\&= \mathbf{55 \text{ ps}} \\t_{cd} &= t_{cd_AND3} \\&= \mathbf{30 \text{ ps}}\end{aligned}$$

 


Exercise 2.46

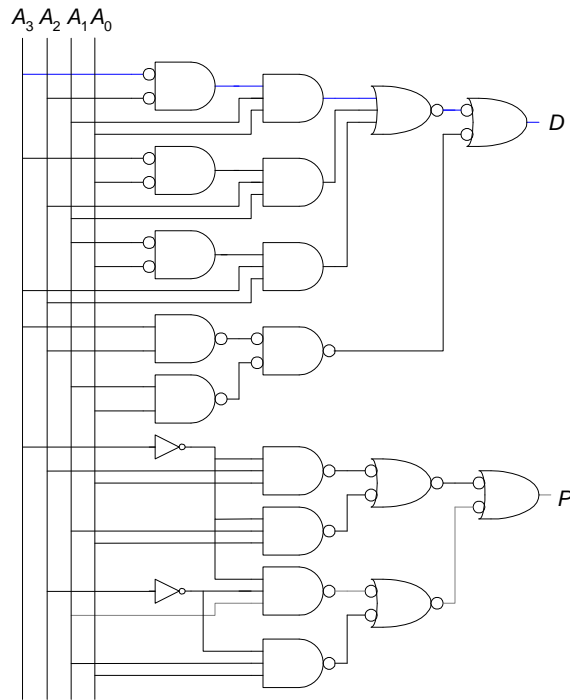

$$\begin{aligned}
 t_{pd} &= t_{pd_NOR2} + t_{pd_AND3} + t_{pd_NOR3} + t_{pd_NAND2} \\
 &= [30 + 40 + 45 + 20] \text{ ps} \\
 &= \mathbf{135 \text{ ps}}
 \end{aligned}$$

$$\begin{aligned}
 t_{cd} &= 2t_{cd_NAND2} + t_{cd_OR2} \\
 &= [2 (15) + 30] \text{ ps} \\
 &= \mathbf{60 \text{ ps}}
 \end{aligned}$$


Exercise 2.47

 

$$\begin{aligned}
 t_{pd} &= t_{pd_INV} + 3t_{pd_NAND2} + t_{pd_NAND3} \\
 &= [15 + 3(20) + 30] \text{ ps} \\
 &= \mathbf{105 \text{ ps}}
 \end{aligned}$$

$$\begin{aligned}
 t_{cd} &= t_{cd_NOT} + t_{cd_NAND2} \\
 &= [10 + 15] \text{ ps} \\
 &= \mathbf{25 \text{ ps}}
 \end{aligned}$$

Exercise 2.48

 


$$t_{pd_dy} = t_{pd_TRI_AY} \\ = \mathbf{50 \text{ ps}}$$

Note: the propagation delay from the control (select) input to the output is the circuit's critical path:

$$t_{pd_sy} = t_{pd_NOT} + t_{pd_AND3} + t_{pd_TRI_SY} \\ = [30 + 80 + 35] \text{ ps} \\ = \mathbf{145 \text{ ps}}$$

However, the problem specified to minimize the delay from data inputs to output, t_{pd_dy} .

Question 2.1

 

Question 2.2

| Month | A_3 | A_2 | A_1 | A_0 | Y |
|-------|-------|-------|-------|-------|---|
| Jan | 0 | 0 | 0 | 1 | 1 |
| Feb | 0 | 0 | 1 | 0 | 0 |
| Mar | 0 | 0 | 1 | 1 | 1 |
| Apr | 0 | 1 | 0 | 0 | 0 |
| May | 0 | 1 | 0 | 1 | 1 |
| Jun | 0 | 1 | 1 | 0 | 0 |
| Jul | 0 | 1 | 1 | 1 | 1 |
| Aug | 1 | 0 | 0 | 0 | 1 |
| Sep | 1 | 0 | 0 | 1 | 0 |
| Oct | 1 | 0 | 1 | 0 | 1 |
| Nov | 1 | 0 | 1 | 1 | 0 |
| Dec | 1 | 1 | 0 | 0 | 1 |

| $A_{3:2} \backslash A_{1:0}$ | 00 | 01 | 11 | 10 |
|------------------------------|----|----|----|----|
| 00 | X | 0 | 1 | 1 |
| 01 | 1 | 1 | X | 0 |
| 11 | 1 | 1 | X | 0 |
| 10 | 0 | 0 | X | 1 |

$$Y = \bar{A}_3 A_0 + A_3 \bar{A}_0 = A_3 \oplus A_0$$


```
graph LR
    A3 --- XOR[XOR]
    A0 --- XOR
    XOR --- Y
```

Question 2.3

A tristate buffer has two inputs and three possible outputs: 0, 1, and Z. One of the inputs is the data input and the other input is a control input, often called the *enable* input. When the enable input is 1, the tristate buffer transfers the data input to the output; otherwise, the output is high impedance, Z. Tristate buffers are used when multiple sources drive a single output at different times. One and only one tristate buffer is enabled at any given time.

Question 2.4

(a) An AND gate is not universal, because it cannot perform inversion (NOT).

(b) The set {OR, NOT} is universal. It can construct any Boolean function. For example, an OR gate with NOT gates on all of its inputs and output performs the AND operation. Thus, the set {OR, NOT} is equivalent to the set {AND, OR, NOT} and is universal.


(c) The NAND gate by itself is universal. A NAND gate with its inputs tied together performs the NOT operation. A NAND gate with a NOT gate on its output performs AND. And a NAND gate with NOT gates on its inputs performs OR. Thus, a NAND gate is equivalent to the set {AND, OR, NOT} and is universal.

Question 2.5


A circuit's contamination delay might be less than its propagation delay because the circuit may operate over a range of temperatures and supply voltages, for example, 3–3.6 V for LVCMOS (low voltage CMOS) chips. As temperature increases and voltage decreases, circuit delay increases. Also, the circuit may have different paths (critical and short paths) from the input to the output. A gate itself may have varying delays between different inputs and the output, affecting the gate's critical and short paths. For example, for a two-input NAND gate, a HIGH to LOW transition requires two nMOS transistor delays, whereas a LOW to HIGH transition requires a single pMOS transistor delay.

CHAPTER 3


Exercise 3.1

 


Exercise 3.2

 


Exercise 3.3

 


Exercise 3.4

 

Exercise 3.5

 

Exercise 3.6

 


Exercise 3.7

The circuit is sequential because it involves feedback and the output depends on previous values of the inputs. This is a SR latch. When $\bar{S} = 0$ and $\bar{R} = 1$, the circuit sets Q to 1. When $\bar{S} = 1$ and $\bar{R} = 0$, the circuit resets Q to 0. When both \bar{S} and \bar{R} are 1, the circuit remembers the old value. And when both \bar{S} and \bar{R} are 0, the circuit drives both outputs to 1.


Exercise 3.8

Sequential logic. This is a D flip-flop with active low asynchronous set and reset inputs. If \bar{S} and \bar{R} are both 1, the circuit behaves as an ordinary D flip-flop. If $\bar{S} = 0$, Q is immediately set to 0. If $\bar{R} = 0$, Q is immediately reset to 1. (This circuit is used in the commercial 7474 flip-flop.)

Exercise 3.9

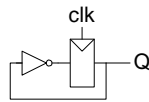

Exercise 3.10

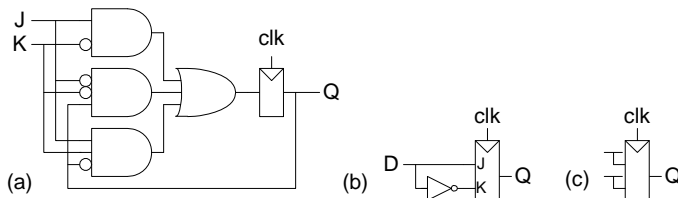


Exercise 3.11


If A and B have the same value, C takes on that value. Otherwise, C retains its old value.

Exercise 3.12


Make sure these next ones are correct too.

 


Exercise 3.13

 

Exercise 3.14

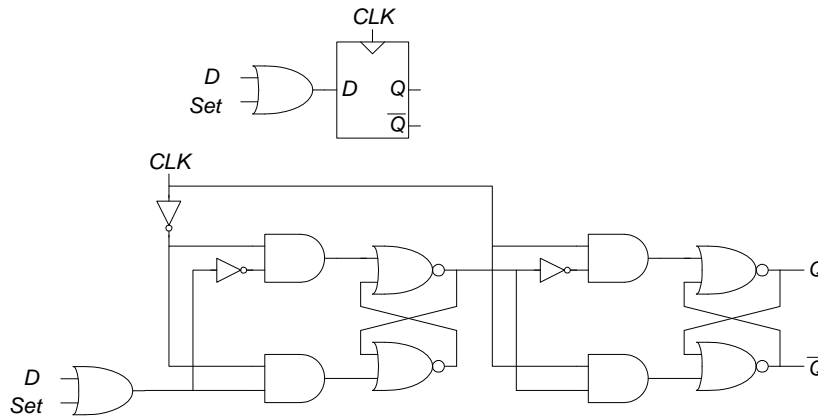

Exercise 3.15

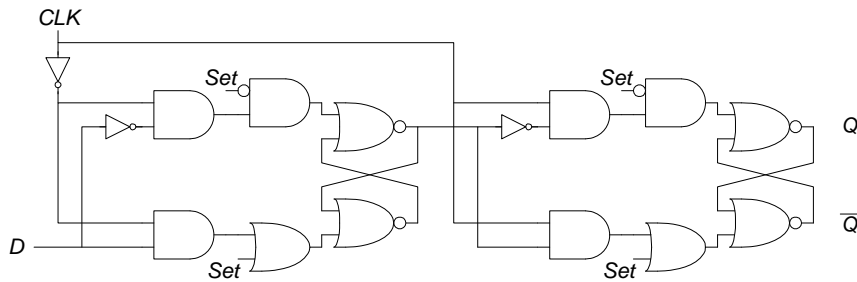

Exercise 3.16

From $\frac{1}{2Nt_{pd}}$ to $\frac{1}{2Nt_{cd}}$.

Exercise 3.17

If N is even, the circuit is stable and will not oscillate.

Exercise 3.18

(a) No: no register. (b) No: feedback without passing through a register. (c) Yes. Satisfies the definition. (d) Yes. Satisfies the definition.

Exercise 3.19

The system has at least five bits of state to represent the 24 floors that the elevator might be on.

Exercise 3.20

The FSM has $5^4 = 625$ states. This requires at least 10 bits to represent all the states.

Exercise 3.21

The FSM could be factored into four independent state machines, one for each student. Each of these machines has five states and requires 3 bits, so at least 12 bits of state are required for the factored design.

Exercise 3.22

This finite state machine asserts the output Q for one clock cycle if A is TRUE followed by B being TRUE.

| state | encoding $s_1:0$ |
|-------|---------------------|
| S0 | 00 |
| S1 | 01 |
| S2 | 10 |

TABLE 3.1 State encoding for Exercise 3.22

| current state | | inputs | | next state | |
|---------------|-------|--------|-----|------------|--------|
| s_1 | s_0 | a | b | s'_1 | s'_0 |
| 0 | 0 | 0 | X | 0 | 0 |
| 0 | 0 | 1 | X | 0 | 1 |

TABLE 3.2 State transition table with binary encodings for Exercise 3.22

| current state | | inputs | | next state | |
|---------------|-------|--------|-----|------------|--------|
| s_1 | s_0 | a | b | s'_1 | s'_0 |
| 0 | 1 | X | 0 | 0 | 0 |
| 0 | 1 | X | 1 | 1 | 0 |
| 1 | 0 | X | X | 0 | 0 |


TABLE 3.2 State transition table with binary encodings for Exercise 3.22

| current state | | output |
|---------------|-------|--------|
| s_1 | s_0 | q |
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |

TABLE 3.3 Output table with binary encodings for Exercise 3.22

$$S'_1 = S_0B$$
$$S'_0 = \overline{S_1}\overline{S_0}A$$

$$Q = S_1$$

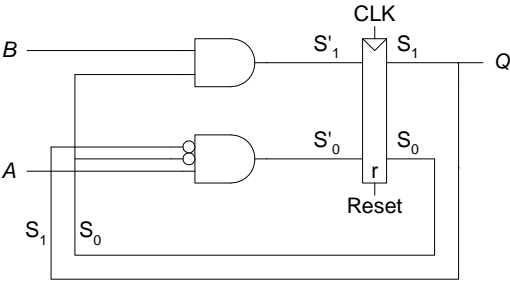

Exercise 3.23

This finite state machine asserts the output Q when A AND B is TRUE.

| state | encoding $s_{1:0}$ |
|-------|-----------------------|
| S0 | 00 |
| S1 | 01 |
| S2 | 10 |

TABLE 3.4 State encoding for Exercise 3.23


| current state | | inputs | | next state | | output |
|---------------|-------|--------|-----|------------|--------|--------|
| s_1 | s_0 | a | b | s'_1 | s'_0 | q |
| 0 | 0 | 0 | X | 0 | 0 | 0 |
| 0 | 0 | 1 | X | 0 | 1 | 0 |
| 0 | 1 | X | 0 | 0 | 0 | 0 |
| 0 | 1 | X | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 |

TABLE 3.5 Combined state transition and output table with binary encodings for Exercise 3.23


$$S'_1 = \overline{S_1}S_0B + S_1AB$$

$$S'_0 = \overline{S_1}\overline{S_0}A$$

$$Q' = S_1AB$$

 

Exercise 3.24

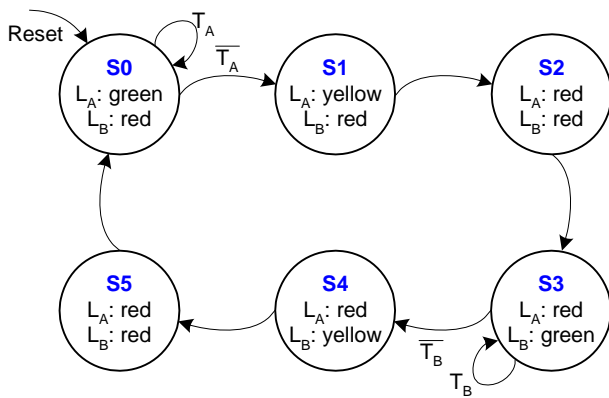

| state | encoding $s_{1:0}$ |
|-------|-----------------------|
| S0 | 000 |
| S1 | 001 |
| S2 | 010 |

TABLE 3.6 State encoding for Exercise 3.24

| state | encoding $s_{1:0}$ |
|-------|-----------------------|
| S3 | 100 |
| S4 | 101 |
| S5 | 110 |

TABLE 3.6 State encoding for Exercise 3.24

| current state | | | inputs | | next state | | |
|---------------|-------|-------|--------|-------|------------|--------|--------|
| s_2 | s_1 | s_0 | t_a | t_b | s'_2 | s'_1 | s'_0 |
| 0 | 0 | 0 | 0 | X | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | X | 0 | 0 | 0 |
| 0 | 0 | 1 | X | X | 0 | 1 | 0 |
| 0 | 1 | 0 | X | X | 1 | 0 | 0 |
| 1 | 0 | 0 | X | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | X | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | X | X | 1 | 1 | 0 |
| 1 | 1 | 0 | X | X | 0 | 0 | 0 |

TABLE 3.7 State transition table with binary encodings for Exercise 3.24

$$\begin{aligned} S'_2 &= S_2 \oplus S_1 \\ S'_1 &= \overline{S_1} S_0 \\ S'_0 &= \overline{S_1} \overline{S_0} (\overline{S_2} \overline{t_a} + S_2 \overline{t_b}) \end{aligned}$$

| current state | | | outputs | | | |
|----------------|----------------|----------------|-----------------|-----------------|-----------------|-----------------|
| s ₂ | s ₁ | s ₀ | l _{a1} | l _{a0} | l _{b1} | l _{b0} |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 |

TABLE 3.8 Output table for Exercise 3.24

$$\begin{aligned} L_{A1} &= S_1 \overline{S_0} + S_2 \overline{S_1} \\ L_{A0} &= \overline{S_2} S_0 \\ L_{B1} &= \overline{S_2} \overline{S_1} + S_1 \overline{S_0} \\ L_{B0} &= S_2 \overline{S_1} S_0 \end{aligned} \tag{3.1}$$


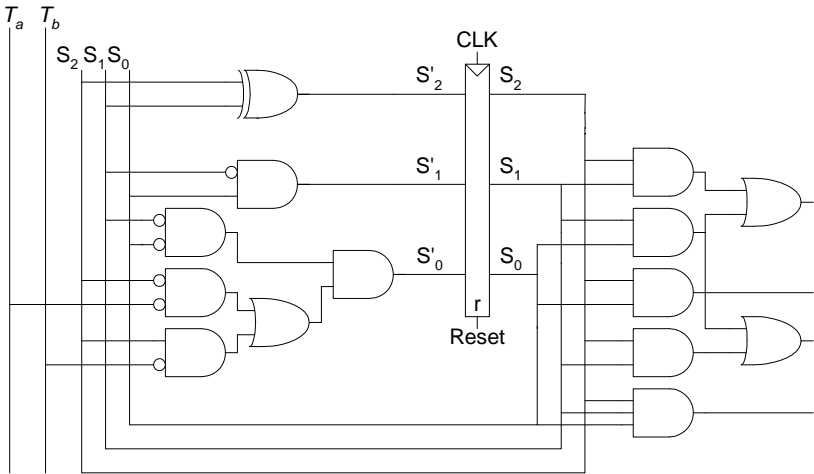


FIGURE 3.1 State machine circuit for traffic light controller for Exercise 3.21

Exercise 3.25

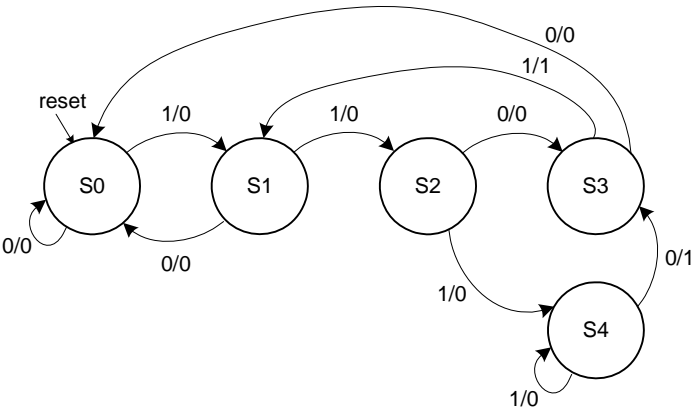

| state | encoding s_1s_0 |
|-------|----------------------|
| S0 | 000 |
| S1 | 001 |
| S2 | 010 |
| S3 | 100 |
| S4 | 101 |

TABLE 3.9 State encoding for Exercise 3.25

| current state | | | input | next state | | | output |
|---------------|-------|-------|-------|------------|--------|--------|--------|
| s_2 | s_1 | s_0 | a | s'_2 | s'_1 | s'_0 | q |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |

TABLE 3.10 Combined state transition and output table with binary encodings for Exercise 3.25

| current state | | | input | next state | | | output |
|---------------|-------|-------|-------|------------|--------|--------|--------|
| s_2 | s_1 | s_0 | a | s'_2 | s'_1 | s'_0 | q |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 |


TABLE 3.10 Combined state transition and output table with binary encodings for Exercise 3.25

$$s'_2 = \overline{s_2}s_1\overline{s_0} + s_2\overline{s_1}s_0$$


$$s'_1 = \overline{s_2}\overline{s_1}s_0A$$

$$s'_0 = A(\overline{s_2}\overline{s_0} + s_2\overline{s_1})$$

$$Q = s_2\overline{s_1}\overline{s_0}A + s_2\overline{s_1}s_0\overline{A}$$

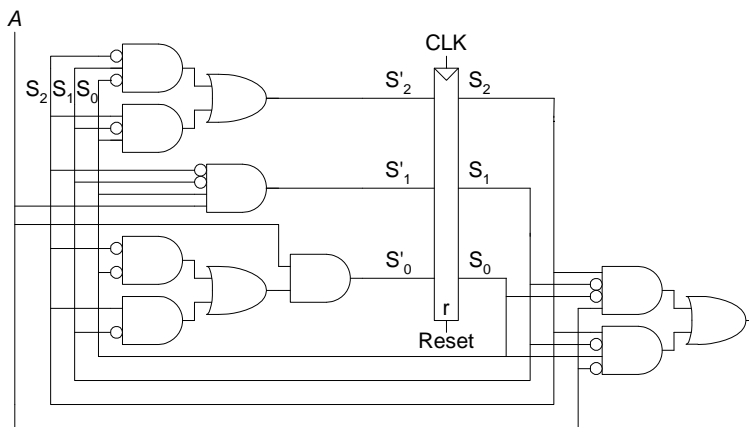

Exercise 3.26

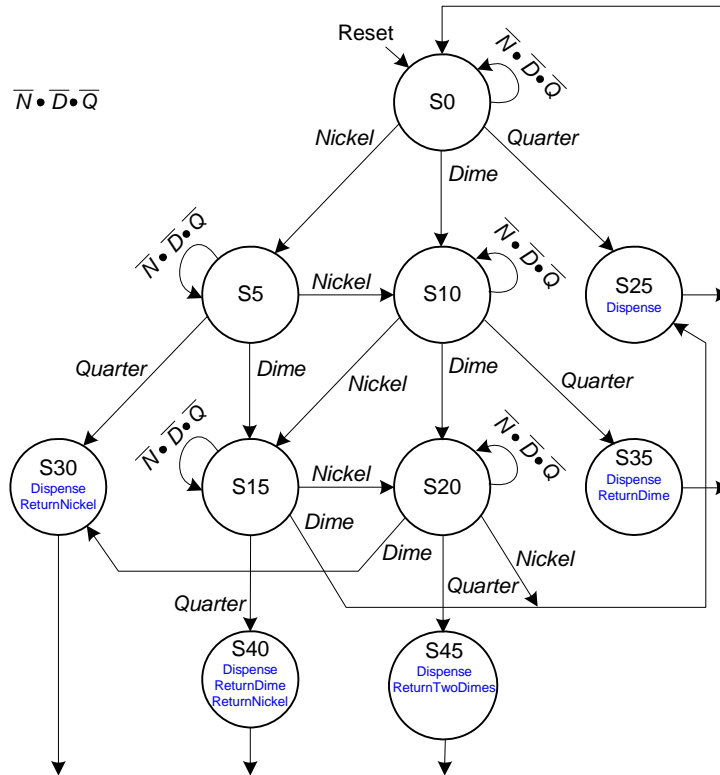

Note: $\overline{N} \cdot \overline{D} \cdot \overline{Q} = \overline{Nickel \cdot Dime \cdot Quarter}$

FIGURE 3.2 State transition diagram for soda machine dispensing of Exercise 3.23

| state | encoding s _{9:0} |
|-------|------------------------------|
| S0 | 0000000001 |
| S5 | 0000000010 |
| S10 | 0000000100 |
| S25 | 0000001000 |
| S30 | 0000010000 |
| S15 | 0000100000 |
| S20 | 0001000000 |
| S35 | 0010000000 |
| S40 | 0100000000 |
| S45 | 1000000000 |

FIGURE 3.3 State Encodings for Exercise 3.26

| current state <i>s</i> | inputs | | | next state <i>s'</i> |
|------------------------------|---------------|-------------|----------------|----------------------------|
| | <i>nickel</i> | <i>dime</i> | <i>quarter</i> | |
| S0 | 0 | 0 | 0 | S0 |
| S0 | 0 | 0 | 1 | S25 |
| S0 | 0 | 1 | 0 | S10 |
| S0 | 1 | 0 | 0 | S5 |
| S5 | 0 | 0 | 0 | S5 |
| S5 | 0 | 0 | 1 | S30 |
| S5 | 0 | 1 | 0 | S15 |
| S5 | 1 | 0 | 0 | S10 |
| S10 | 0 | 0 | 0 | S10 |

TABLE 3.11 State transition table for Exercise 3.26

| current state <i>s</i> | inputs | | | next state <i>s'</i> |
|------------------------------|---------------|-------------|----------------|----------------------------|
| | <i>nickel</i> | <i>dime</i> | <i>quarter</i> | |
| S10 | 0 | 0 | 1 | S35 |
| S10 | 0 | 1 | 0 | S20 |
| S10 | 1 | 0 | 0 | S15 |
| S25 | X | X | X | S0 |
| S30 | X | X | X | S0 |
| S15 | 0 | 0 | 0 | S15 |
| S15 | 0 | 0 | 1 | S40 |
| S15 | 0 | 1 | 0 | S25 |
| S15 | 1 | 0 | 0 | S20 |
| S20 | 0 | 0 | 0 | S20 |
| S20 | 0 | 0 | 1 | S45 |
| S20 | 0 | 1 | 0 | S30 |
| S20 | 1 | 0 | 0 | S25 |
| S35 | X | X | X | S0 |
| S40 | X | X | X | S0 |
| S45 | X | X | X | S0 |

TABLE 3.11 State transition table for Exercise 3.26

| current state <i>s</i> | inputs | | | next state <i>s'</i> |
|------------------------------|---------------|-------------|----------------|-------------------------|
| | <i>nickel</i> | <i>dime</i> | <i>quarter</i> | |
| 0000000001 | 0 | 0 | 0 | 0000000001 |
| 0000000001 | 0 | 0 | 1 | 0000001000 |
| 0000000001 | 0 | 1 | 0 | 0000000100 |
| 0000000001 | 1 | 0 | 0 | 0000000010 |

TABLE 3.12 State transition table for Exercise 3.26

| current state <i>s</i> | inputs | | | next state <i>s'</i> |
|------------------------------|---------------|-------------|----------------|-------------------------|
| | <i>nickel</i> | <i>dime</i> | <i>quarter</i> | |
| 0000000010 | 0 | 0 | 0 | 0000000010 |
| 0000000010 | 0 | 0 | 1 | 0000010000 |
| 0000000010 | 0 | 1 | 0 | 0000100000 |
| 0000000010 | 1 | 0 | 0 | 0000000100 |
| 0000000100 | 0 | 0 | 0 | 0000000100 |
| 0000000100 | 0 | 0 | 1 | 0010000000 |
| 0000000100 | 0 | 1 | 0 | 0001000000 |
| 0000000100 | 1 | 0 | 0 | 0000100000 |
| 0000001000 | X | X | X | 0000000001 |
| 0000010000 | X | X | X | 0000000001 |
| 0000100000 | 0 | 0 | 0 | 0000100000 |
| 0000100000 | 0 | 0 | 1 | 0100000000 |
| 0000100000 | 0 | 1 | 0 | 0000001000 |
| 0000100000 | 1 | 0 | 0 | 0001000000 |
| 0001000000 | 0 | 0 | 0 | 0001000000 |
| 0001000000 | 0 | 0 | 1 | 1000000000 |
| 0001000000 | 0 | 1 | 0 | 0000010000 |
| 0001000000 | 1 | 0 | 0 | 0000001000 |
| 0010000000 | X | X | X | 0000000001 |
| 0100000000 | X | X | X | 0000000001 |
| 1000000000 | X | X | X | 0000000001 |

TABLE 3.12 State transition table for Exercise 3.26

$s'_9 = s_6Q$

$s'_8 = s_5Q$

$$S'_7 = S_2Q$$

$$S'_6 = S_2D + S_5N + S_6\overline{N}\overline{D}\overline{Q}$$

$$S'_5 = S_1D + S_2N + S_5NDQ$$

$$S'_4 = S_1Q + S_6D$$

$$S'_3 = S_0Q + S_5D + S_6N$$

$$S'_2 = S_0D + S_1N + S_2\overline{N}\overline{D}\overline{Q}$$

$$S'_1 = S_0N + S_1NDQ$$


$$S'_0 = S_0\overline{N}\overline{D}\overline{Q} + S_3 + S_4 + S_7 + S_8 + S_9$$

$$Dispense = S_3 + S_4 + S_7 + S_8 + S_9$$

$$ReturnNickel = S_4 + S_8$$

$$ReturnDime = S_7 + S_8$$

$$ReturnTwoDimes = S_9$$

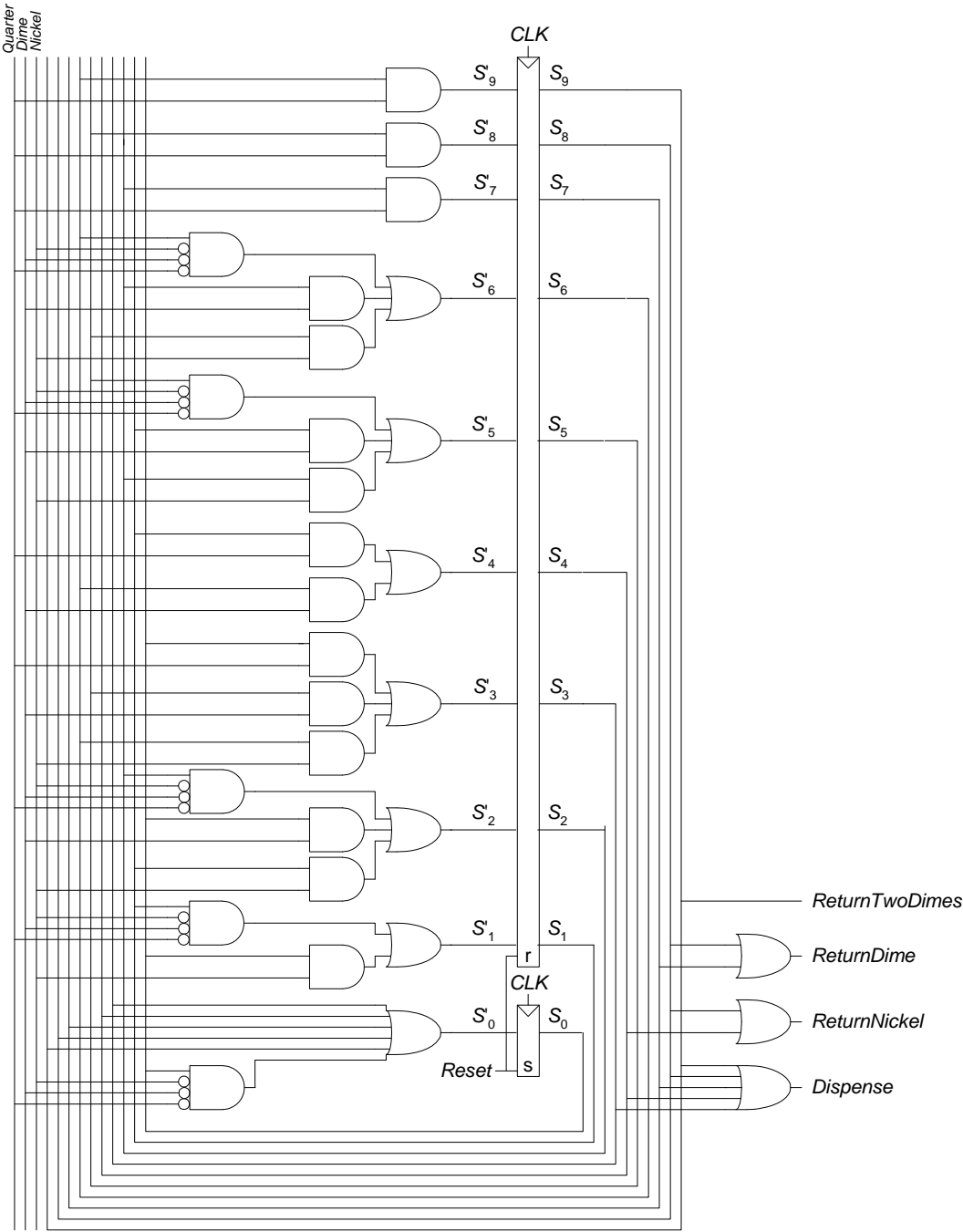

Exercise 3.27

 


FIGURE 3.4 State transition diagram for Exercise 3.27

| current state $s_{2:0}$ | next state $s'_{2:0}$ |
|-------------------------------|--------------------------|
| 000 | 001 |
| 001 | 011 |
| 011 | 010 |
| 010 | 110 |
| 110 | 111 |
| 111 | 101 |
| 101 | 100 |
| 100 | 000 |

TABLE 3.13 State transition table for Exercise 3.27

$$\begin{aligned} S'_2 &= S_1\overline{S_0} + S_2S_0 \\ S'_1 &= \overline{S_2}S_0 + S_1\overline{S_0} \\ S'_0 &= \overline{S_2 \oplus S_1} \\ Q_2 &= S_2 \\ Q_1 &= S_1 \\ Q_0 &= S_0 \end{aligned}$$

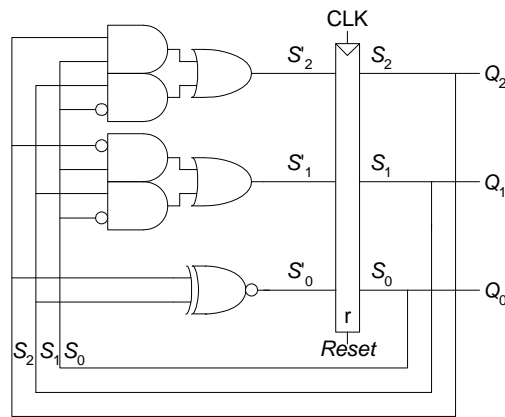


FIGURE 3.5 Hardware for Gray code counter FSM for Exercise 3.27

Exercise 3.28

 


FIGURE 3.6 State transition diagram for Exercise 3.28

| current state $s_{2:0}$ | input up | next state $s'_{2:0}$ |
|-------------------------------|-------------|--------------------------|
| 000 | 1 | 001 |
| 001 | 1 | 011 |
| 011 | 1 | 010 |
| 010 | 1 | 110 |
| 110 | 1 | 111 |
| 111 | 1 | 101 |
| 101 | 1 | 100 |
| 100 | 1 | 000 |
| 000 | 0 | 100 |
| 001 | 0 | 000 |
| 011 | 0 | 001 |
| 010 | 0 | 011 |
| 110 | 0 | 010 |
| 111 | 0 | 110 |
| 101 | 0 | 111 |
| 100 | 0 | 101 |

TABLE 3.14 State transition table for Exercise 3.28

$$S'_2 = UPS_1\overline{S_0} + \overline{UP}\overline{S_1}\overline{S_0} + S_2S_0$$

$$S'_1 = S_1\overline{S_0} + UPS_2\overline{S_0} + \overline{UP}S_2S_1$$

$$S'_0 = UP \oplus S_2 \oplus S_1$$

$$Q_2 = S_2$$

$$Q_1 = S_1$$

$$Q_0 = S_0$$

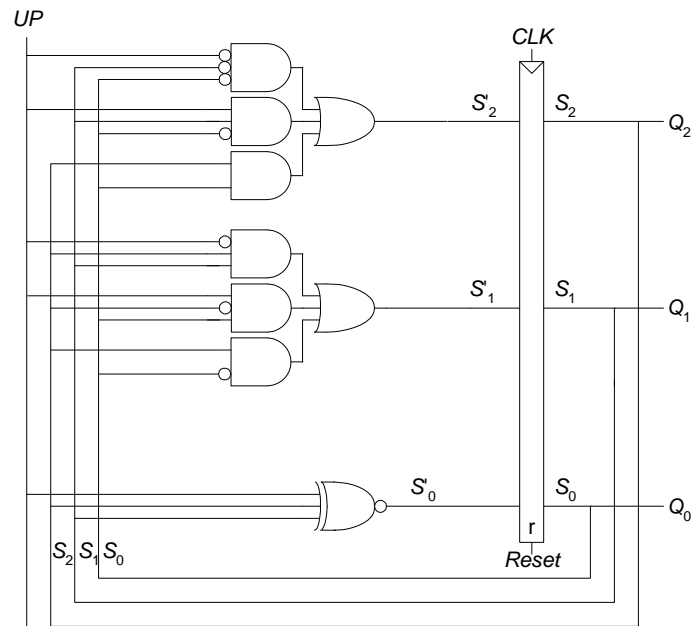


FIGURE 3.7 Finite state machine hardware for Exercise 3.28

Exercise 3.29

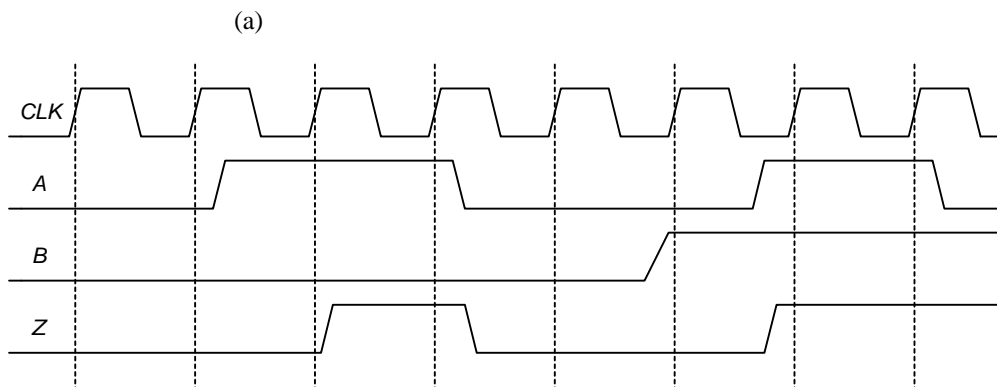


FIGURE 3.8 Waveform showing Z output for Exercise 3.29

(b) This FSM is a Mealy FSM because the output depends on the current value of the input as well as the current state.

(c)

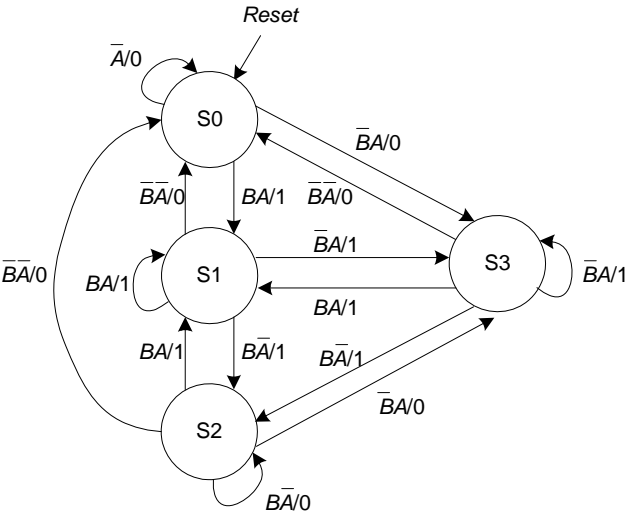


FIGURE 3.9 State transition diagram for Exercise 3.29

(Note: another viable solution would be to allow the state to transition from S0 to S1 on $\overline{B}\overline{A}/0$. The arrow from S0 to S0 would then be $\overline{B}\overline{A}/0$.)

| current state $s_{1:0}$ | inputs | | next state $s'_{1:0}$ | output z |
|----------------------------|--------|-----|--------------------------|---------------|
| | b | a | | |
| 00 | X | 0 | 00 | 0 |
| 00 | 0 | 1 | 11 | 0 |
| 00 | 1 | 1 | 01 | 1 |
| 01 | 0 | 0 | 00 | 0 |
| 01 | 0 | 1 | 11 | 1 |
| 01 | 1 | 0 | 10 | 1 |
| 01 | 1 | 1 | 01 | 1 |
| 10 | 0 | X | 00 | 0 |
| 10 | 1 | 0 | 10 | 0 |

TABLE 3.15 State transition table for Exercise 3.29

| current state $s_{1:0}$ | inputs | | next state $s'_{1:0}$ | output z |
|----------------------------|--------|-----|--------------------------|---------------|
| | b | a | | |
| 10 | 1 | 1 | 01 | 1 |
| 11 | 0 | 0 | 00 | 0 |
| 11 | 0 | 1 | 11 | 1 |
| 11 | 1 | 0 | 10 | 1 |
| 11 | 1 | 1 | 01 | 1 |

TABLE 3.15 State transition table for Exercise 3.29

$$S'_1 = \overline{B}A(\overline{S_1} + S_0) + B\overline{A}(S_1 + \overline{S_0})$$

$$S'_0 = A(\overline{S_1} + S_0 + B)$$

$$Z = BA + S_0(A + B)$$

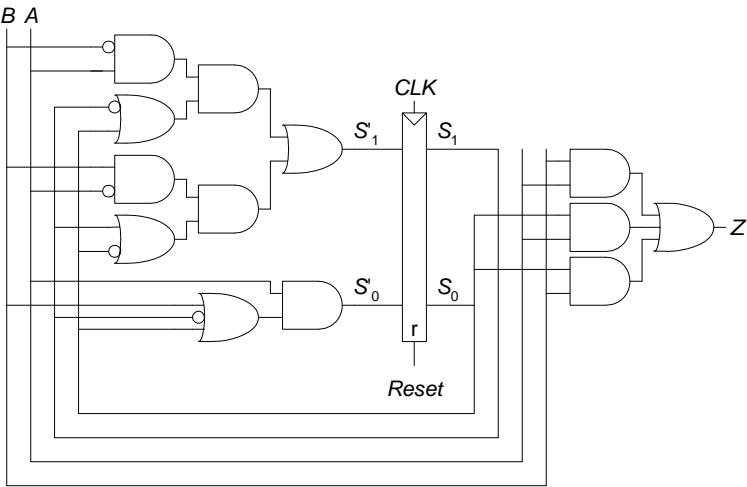


FIGURE 3.10 Hardware for FSM of Exercise 3.26

Note: One could also build this functionality by registering input A , producing both the logical AND and OR of input A and its previous (registered)

value, and then muxing the two operations using B . The output of the mux is Z :
 $Z = A\overline{A}_{\text{prev}}$ (if $B = 0$); $Z = A + A_{\text{prev}}$ (if $B = 1$).

Exercise 3.30

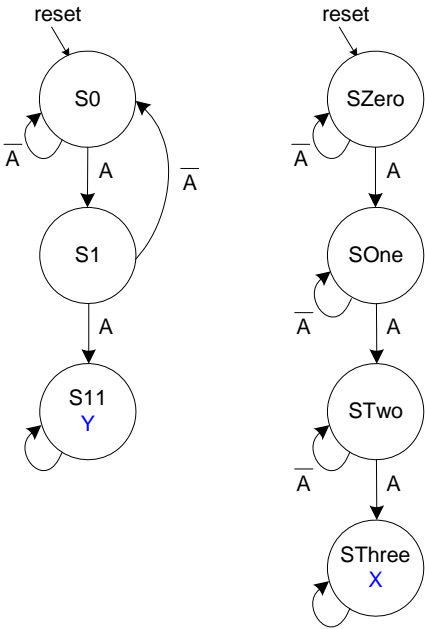


FIGURE 3.11 Factored state transition diagram for Exercise 3.30

| current state $s_{1:0}$ | input a | next state $s'_{1:0}$ |
|----------------------------|--------------|--------------------------|
| 00 | 0 | 00 |
| 00 | 1 | 01 |
| 01 | 0 | 00 |

TABLE 3.16 State transition table for output Y for Exercise 3.30

| current state $s_{1:0}$ | input a | next state $s'_{1:0}$ |
|-------------------------------|------------|--------------------------|
| 01 | 1 | 11 |
| 11 | X | 11 |

TABLE 3.16 State transition table for output Y for Exercise 3.30

| current state $t_{1:0}$ | input a | next state $t'_{1:0}$ |
|-------------------------------|------------|--------------------------|
| 00 | 0 | 00 |
| 00 | 1 | 01 |
| 01 | 0 | 01 |
| 01 | 1 | 10 |
| 10 | 0 | 10 |
| 10 | 1 | 11 |
| 11 | X | 11 |

TABLE 3.17 State transition table for output X for Exercise 3.30

$$S_1 = S_0(S_1 + A)$$
$$S_0 = \overline{S_1}A + S_0(S_1 + A)$$
$$Y = S_1$$

$$T_1 = T_1 + T_0A$$
$$T_0 = A(T_1 + \overline{T_0}) + \overline{A}T_0 + T_1T_0$$
$$X = T_1T_0$$

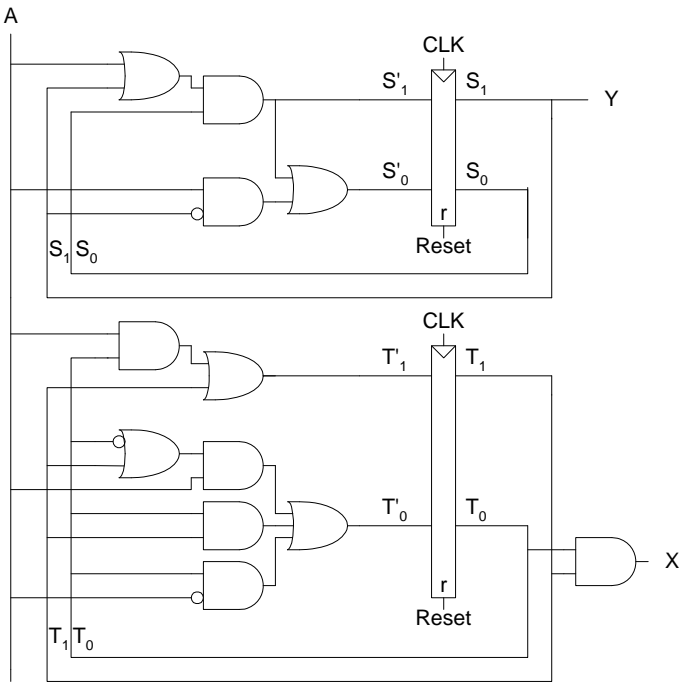


FIGURE 3.12 Finite state machine hardware for Exercise 3.30

Exercise 3.31

This finite state machine is a divide-by-two counter (see Section 3.4.2) when $X = 0$. When $X = 1$, the output, Q , is HIGH.

| current state | | input | next state | |
|---------------|-------|-------|------------|--------|
| s_1 | s_0 | x | s'_1 | s'_0 |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |


TABLE 3.18 State transition table with binary encodings for Exercise 3.31

| current state | | input | next state | |
|---------------|-------|-------|------------|--------|
| s_1 | s_0 | x | s'_1 | s'_0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | X | X | 0 | 1 |

TABLE 3.18 State transition table with binary encodings for Exercise 3.31

| current state | | output |
|---------------|-------|--------|
| s_1 | s_0 | q |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | X | 1 |

TABLE 3.19 Output table for Exercise 3.31

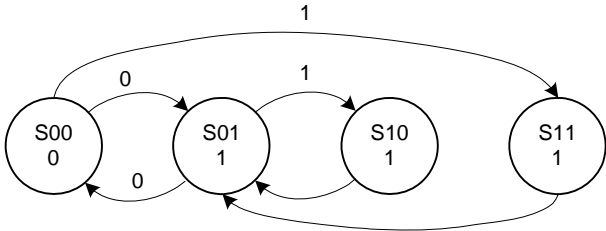

Exercise 3.32

| current state | | | input | next state | | |
|---------------|-------|-------|-------|------------|--------|--------|
| s_2 | s_1 | s_0 | a | s'_2 | s'_1 | s'_0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 |

TABLE 3.20 State transition table with binary encodings for Exercise 3.32

| current state | | | input | next state | | |
|---------------|-------|-------|-------|------------|--------|--------|
| s_2 | s_1 | s_0 | a | s'_2 | s'_1 | s'_0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 |

TABLE 3.20 State transition table with binary encodings for Exercise 3.32

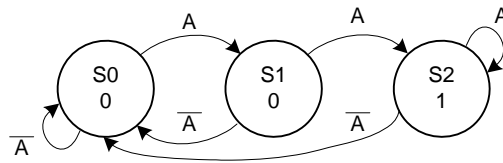


FIGURE 3.13 State transition diagram for Exercise 3.32

Q asserts whenever A is HIGH for two or more consecutive cycles.

Exercise 3.33

(a) First, we calculate the propagation delay through the combinational logic:

$$\begin{aligned}
 t_{pd} &= 3t_{pd_XOR} \\
 &= 3 \times 100 \text{ ps} \\
 &= \mathbf{300 \text{ ps}}
 \end{aligned}$$

Next, we calculate the cycle time:

$$\begin{aligned}
 T_c &\geq t_{pcq} + t_{pd} + t_{\text{setup}} \\
 &\geq [70 + 300 + 60] \text{ ps} \\
 &= 430 \text{ ps}
 \end{aligned}$$

$$f = 1 / 430 \text{ ps} = \mathbf{2.33 \text{ GHz}}$$

(b)

$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}} + t_{\text{skew}}$$

Thus,

$$\begin{aligned}
 t_{\text{skew}} &\leq T_c - (t_{pcq} + t_{pd} + t_{\text{setup}}), \text{ where } T_c = 1 / 2 \text{ GHz} = 500 \text{ ps} \\
 &\leq [500 - 430] \text{ ps} = \mathbf{70 \text{ ps}}
 \end{aligned}$$

(c)

First, we calculate the contamination delay through the combinational logic:

$$\begin{aligned} t_{cd} &= t_{cd_XOR} \\ &= 55 \text{ ps} \end{aligned}$$

$$t_{ccq} + t_{cd} > t_{\text{hold}} + t_{\text{skew}}$$

Thus,

$$\begin{aligned} t_{\text{skew}} &< (t_{ccq} + t_{cd}) - t_{\text{hold}} \\ &< (50 + 55) - 20 \\ &< \mathbf{85 \text{ ps}} \end{aligned}$$

(d)

 


FIGURE 3.14 Alyssa’s improved circuit for Exercise 3.33

First, we calculate the propagation and contamination delays through the combinational logic:

$$\begin{aligned} t_{pd} &= 2t_{pd_XOR} \\ &= 2 \times 100 \text{ ps} \\ &= \mathbf{200 \text{ ps}} \end{aligned}$$

$$\begin{aligned} t_{cd} &= 2t_{cd_XOR} \\ &= 2 \times 55 \text{ ps} \\ &= \mathbf{110 \text{ ps}} \end{aligned}$$

Next, we calculate the cycle time:

$$\begin{aligned} T_c &\geq t_{pcq} + t_{pd} + t_{\text{setup}} \\ &\geq [70 + 200 + 60] \text{ ps} \\ &= 330 \text{ ps} \end{aligned}$$

$$f = 1 / 330 \text{ ps} = \mathbf{3.03 \text{ GHz}}$$

$$\begin{aligned} t_{\text{skew}} &< (t_{ccq} + t_{cd}) - t_{\text{hold}} \\ &< (50 + 110) - 20 \\ &< \mathbf{140 \text{ ps}} \end{aligned}$$

Exercise 3.34

- (a) 9.09 GHz
- (b) 15 ps
- (c) 26 ps

Exercise 3.35

- (a) $T_c = 1 / 40 \text{ MHz} = 25 \text{ ns}$
 $T_c \geq t_{pcq} + Nt_{CLB} + t_{setup}$
 $25 \text{ ns} \geq [0.72 + N(0.61) + 0.53] \text{ ps}$
 Thus, $N < 38.9$
 $N = 38$

- (b)
 $t_{skew} < (t_{ccq} + t_{cd_CLB}) - t_{hold}$
 $< [(0.5 + 0.3) - 0] \text{ ns}$
 $< 0.8 \text{ ns} = 800 \text{ ps}$

Exercise 3.36

1.138 ns

Exercise 3.37

$P(\text{failure})/\text{sec} = 1/\text{MTBF} = 1/(50 \text{ years} * 3.15 \times 10^7 \text{ sec/year}) = \mathbf{6.34 \times 10^{-10}}$ (EQ 3.26)

$P(\text{failure})/\text{sec}$ waiting for one clock cycle: $N*(T_0/T_c)*e^{-(T_c-t_{setup})/\tau}$

$$= 0.5 * (110/1000) * e^{-(1000-70)/100} = 5.0 \times 10^{-6}$$

$P(\text{failure})/\text{sec}$ waiting for two clock cycles: $N*(T_0/T_c)*[e^{-(T_c-t_{setup})/\tau}]^2$

$$= 0.5 * (110/1000) * [e^{-(1000-70)/100}]^2 = 4.6 \times 10^{-10}$$

This is just less than the required probability of failure (6.34×10^{-10}). Thus, **2 cycles** of waiting is just adequate to meet the MTBF.

Exercise 3.38

(a) You know you've already entered metastability, so the probability that the sampled signal is metastable is 1. Thus,

$$P(\text{failure}) = 1 \times e^{-\frac{t}{\tau}}$$

Solving for the probability of still being metastable (failing) to be 0.01:

$$P(\text{failure}) = e^{-\frac{t}{\tau}} = 0.01$$

Thus,

$$t = -\tau \times \ln(P(\text{failure})) = -20 \times \ln((0.01)) = \mathbf{92 \text{ seconds}}$$

(b) The probability of death is the chance of still being metastable after 3 minutes

$$P(\text{failure}) = 1 \times e^{-(3 \text{ min} \times 60 \text{ sec}) / 20 \text{ sec}} = \mathbf{0.000123}$$

Exercise 3.39

We assume a two flip-flop synchronizer. The most significant impact on the probability of failure comes from the exponential component. If we ignore the T_0/T_c term in the probability of failure equation, assuming it changes little with increases in cycle time, we get:

$$P(\text{failure}) = e^{-\frac{t}{\tau}}$$

$$MTBF = \frac{1}{P(\text{failure})} = e^{\frac{T_c - t_{\text{setup}}}{\tau}}$$

$$\frac{MTBF_2}{MTBF_1} = 10 = e^{\frac{T_{c2} - T_{c1}}{30ps}}$$

Solving for $T_{c2} - T_{c1}$, we get:

$$T_{c2} - T_{c1} = 69ps$$

Thus, the clock cycle time must increase by **69 ps**. This holds true for cycle times much larger than T_0 (20 ps) and the increased time (69 ps).

Exercise 3.40

Alyssa is correct. Ben's circuit does not eliminate metastability. After the first transition on D, D2 is always 0 because as D2 transitions from 0 to 1 or 1 to 0, it enters the forbidden region and Ben's "metastability detector" resets the first flip-flop to 0. Even if Ben's circuit could correctly detect a metastable output, it would asynchronously reset the flip-flop which, if the reset occurred around the clock edge, this could cause the second flip-flop to sample a transitioning signal and become metastable.

Question 3.1

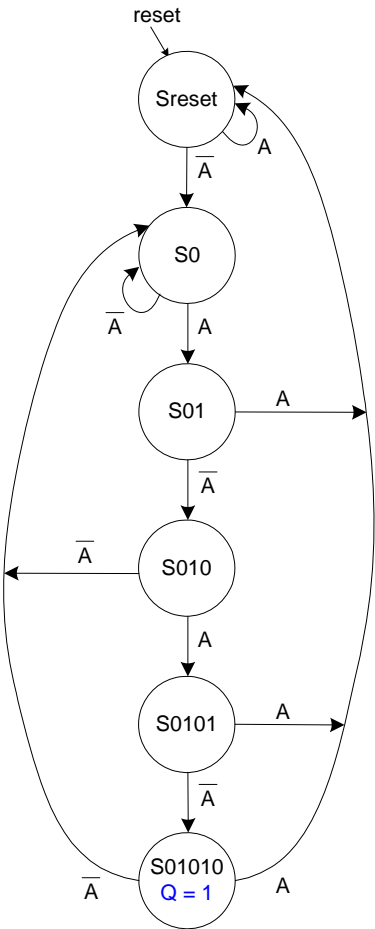


FIGURE 3.15 State transition diagram for Question 3.1

| current state $s_{5:0}$ | input | next state $s'_{5:0}$ |
|-------------------------------|-------|--------------------------|
| | a | |
| 000001 | 0 | 000010 |
| 000001 | 1 | 000001 |

TABLE 3.21 State transition table for Question 3.1

| current state $s_{5:0}$ | input | next state $s'_{5:0}$ |
|-------------------------------|-------|--------------------------|
| | a | |
| 000010 | 0 | 000010 |
| 000010 | 1 | 000100 |
| 000100 | 0 | 001000 |
| 000100 | 1 | 000001 |
| 001000 | 0 | 000010 |
| 001000 | 1 | 010000 |
| 010000 | 0 | 100000 |
| 010000 | 1 | 000001 |
| 100000 | 0 | 000010 |
| 100000 | 1 | 000001 |

TABLE 3.21 State transition table for Question 3.1

$S''_5 = S_4A$
 $S''_4 = S_3A$
 $S''_3 = S_2A$
 $S''_2 = S_1A$
 $S''_1 = A(S_1 + S_3 + S_5)$
 $S''_0 = A(S_0 + S_2 + S_4 + S_5)$
 $Q = S_5$

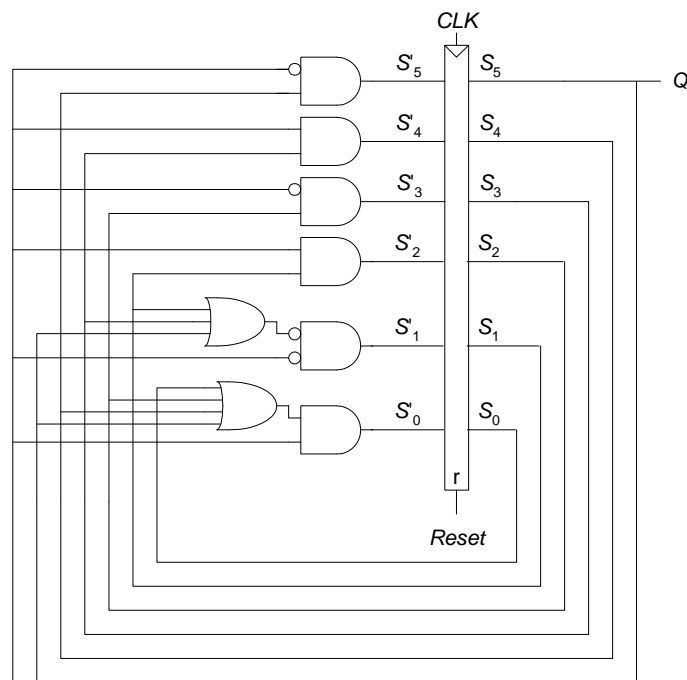


FIGURE 3.16 Finite state machine hardware for Question 3.1

Question 3.2

The FSM should output the value of A until after the first 1 is received. It then should output the inverse of A . For example, the 8-bit two's complement of the number 6 (00000110) is (1111010). Starting from the least significant bit on the far right, the two's complement is created by outputting the same value of the input until the first 1 is reached. Thus, the two least significant bits of the two's complement number are "10". Then the remaining bits are inverted, making the complete number 1111010.

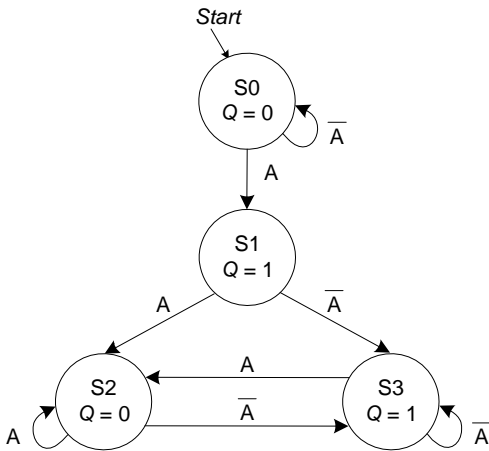


FIGURE 3.17 State transition diagram for Question 3.2

| current state $s_{1:0}$ | input | next state $s'_{1:0}$ |
|-------------------------------|-------|--------------------------|
| | a | |
| 00 | 0 | 00 |
| 00 | 1 | 01 |
| 01 | 0 | 11 |
| 01 | 1 | 10 |
| 10 | 0 | 11 |
| 10 | 1 | 10 |
| 11 | 0 | 11 |
| 11 | 1 | 10 |

TABLE 3.22 State transition table for Question 3.2

$$S'_1 = S_1 + S_0$$
$$S'_0 = A \oplus (S_1 + S_0)$$
$$Q = S_0$$

FIGURE 3.18 Finite state machine hardware for Question 3.2

Question 3.4

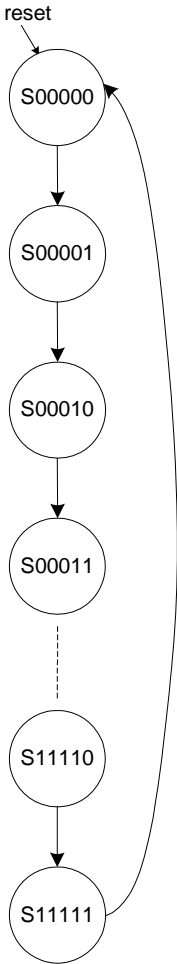


FIGURE 3.19 State transition diagram for Question 3.4

| current state $s_{4:0}$ | next state $s'_{4:0}$ |
|----------------------------|--------------------------|
| 00000 | 00001 |
| 00001 | 00010 |

TABLE 3.23 State transition table for Question 3.4

| current state $s_{4:0}$ | next state $s'_{4:0}$ |
|-------------------------------|--------------------------|
| 00010 | 00011 |
| 00011 | 00100 |
| 00100 | 00101 |
| ... | ... |
| 11110 | 11111 |
| 11111 | 00000 |

TABLE 3.23 State transition table for Question 3.4

$$s'_4 = s_4 \oplus s_3 s_2 s_1 s_0$$

$$s'_3 = s_3 \oplus s_2 s_1 s_0$$

$$s'_2 = s_2 \oplus s_1 s_0$$

$$s'_1 = s_1 \oplus s_0$$

$$s'_0 = \overline{s_0}$$

$$Q_{4:0} = s_{4:0}$$

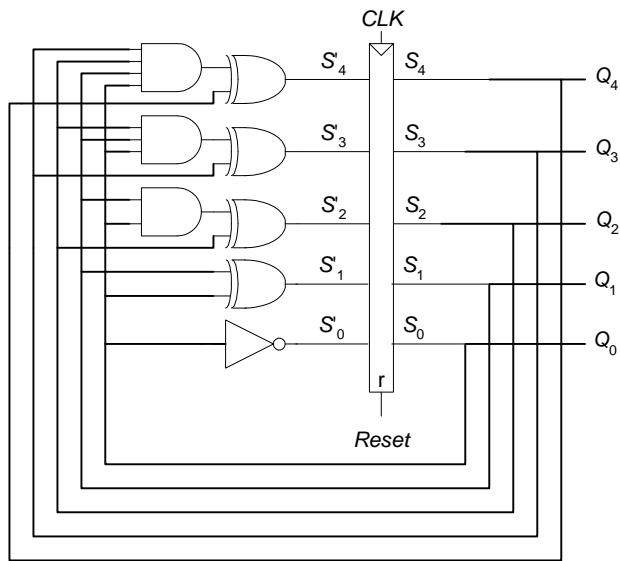


FIGURE 3.20 Finite state machine hardware for Question 3.4

Question 3.5

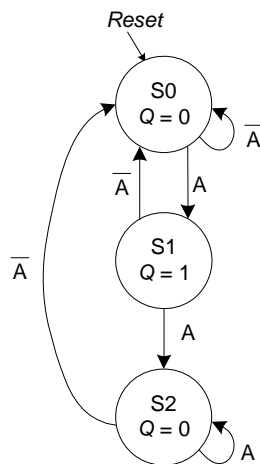


FIGURE 3.21 State transition diagram for edge detector circuit of Question 3.5

| current state $s_{1:0}$ | input | next state $s'_{1:0}$ |
|-------------------------------|-------|--------------------------|
| | a | |
| 00 | 0 | 00 |
| 00 | 1 | 01 |
| 01 | 0 | 00 |
| 01 | 1 | 10 |
| 10 | 0 | 00 |
| 10 | 1 | 10 |

TABLE 3.24 State transition table for Question 3.5

$$S'_1 = AS_1$$
$$S'_0 = AS_1S_0$$
$$Q = S_1$$

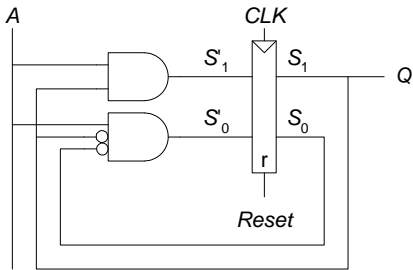


FIGURE 3.22 Finite state machine hardware for Question 3.5

Question 3.6

Pipelining divides a block of combinational logic into N stages, with a register between each stage. Pipelining increases throughput, the number of tasks that can be completed in a given amount of time. Ideally, pipelining increases throughput by a factor of N . But because of the following three reasons, the

speedup is usually less than N : (1) The combinational logic usually cannot be divided into N equal stages. (2) Adding registers between stages adds delay called the *sequencing overhead*, the time it takes to get the signal into and out of the register, $t_{\text{setup}} + t_{\text{pcq}}$. (3) The pipeline is not always operating at full capacity: at the beginning of execution, it takes time to fill up the pipeline, and at the end it takes time to drain the pipeline. However, pipelining offers significant speedup at the cost of little extra hardware.

Question 3.7

A flip-flop with a negative hold time allows D to start changing *before* the clock edge arrives.

Question 3.8

We use a divide-by-three counter (see Example 3.6 on page 155 of the text-book) with A as the clock input followed by a *negative edge-triggered* flip-flop, which samples the input, D , on the negative or falling edge of the clock, or in this case, A . The output is the output of the divide-by-three counter, S_0 , OR the output of the negative edge-triggered flip-flop, $N1$. Figure 3.24 shows the waveforms of the internal signals, S_0 and $N1$.

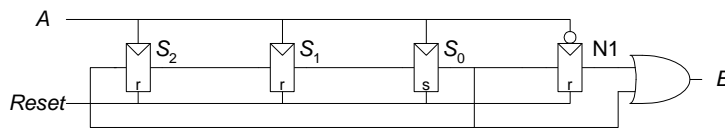


FIGURE 3.23 Hardware for Question 3.8

 


FIGURE 3.24 Waveforms for Question 3.8


Question 3.9

Without the added buffer, the propagation delay through the logic, t_{pd} , must be less than or equal to $T_c - (t_{pcq} + t_{setup})$. However, if you add a buffer to the clock input of the receiver, the clock arrives at the receiver later. The earliest that the clock edge arrives at the receiver is t_{cd_BUF} after the actual clock edge. Thus, the propagation delay through the logic is now given an extra t_{cd_BUF} . So, t_{pd} now must be less than $T_c + t_{cd_BUF} - (t_{pcq} + t_{setup})$.


CHAPTER 4

Note: the HDL files given in the following solutions are available on the textbook's companion website at:
<http://textbooks.elsevier.com/9780123704979>

Exercise 4.1

 

Exercise 4.2

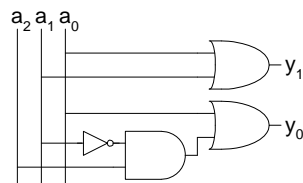

Exercise 4.3

SystemVerilog

```
module xor_4(input logic [3:0] a,
             output logic
               y);

    assign y = ^a;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity xor_4 is
    port(a: in  STD_LOGIC_VECTOR(3 downto 0);
          y: out STD_LOGIC);
end;

architecture synth of xor_4 is
begin
    y <= a(3) xor a(2) xor a(1) xor a(0);
end;
```

Exercise 4.4

ex4_4.tv file:

```
0000_0
0001_1
0010_1
0011_0
0100_1
0101_0
0110_0
0111_1
1000_1
1001_0
1010_0
1011_1
1100_0
1101_1
1110_1
1111_0
```

SystemVerilog

```

module ex4_4_testbench();
    logic      clk, reset;
    logic [3:0] a;
    logic      yexpected;
    logic      y;
    logic [31:0] vectornum, errors;
    logic [4:0] testvectors[10000:0];

    // instantiate device under test
    xor_4 dut(a, y);

    // generate clock
    always
    begin
        clk = 1; #5; clk = 0; #5;
    end

    // at start of test, load vectors
    // and pulse reset
    initial
    begin
        $readmemb("ex4_4.tv", testvectors);
        vectornum = 0; errors = 0;
        reset = 1; #27; reset = 0;
    end

    // apply test vectors on rising edge of clk
    always @(posedge clk)
    begin
        #1; {a, yexpected} =
            testvectors[vectornum];
    end

    // check results on falling edge of clk
    always @(negedge clk)
    if (~reset) begin // skip during reset
        if (y != yexpected) begin
            $display("Error: inputs = %h", a);
            $display("  outputs = %b (%b expected)",
                y, yexpected);
            errors = errors + 1;
        end
        vectornum = vectornum + 1;
        if (testvectors[vectornum] == 5'bxx) begin
            $display("%d tests completed with %d errors",
                vectornum, errors);
            $finish;
        end
    end
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;
use STD.TEXTIO.all;
use work.txt_util.all

entity ex4_4_testbench is -- no inputs or outputs
end;

architecture sim of ex4_4_testbench is
    component sillyfunction
        port(a: in  STD_LOGIC_VECTOR(3 downto 0);
             y: out STD_LOGIC);
    end component;
    signal a: STD_LOGIC_VECTOR(3 downto 0);
    signal y, clk, reset: STD_LOGIC;
    signal yexpected: STD_LOGIC;
    constant MEMSIZE: integer := 10000;
    type tvarchar is array(MEMSIZE downto 0) of
        STD_LOGIC_VECTOR(4 downto 0);
    signal testvectors: tvarchar;
    shared variable vectornum, errors: integer;
begin
    -- instantiate device under test
    dut: xor_4 port map(a, y);

    -- generate clock
    process begin
        clk <= '1'; wait for 5 ns;
        clk <= '0'; wait for 5 ns;
    end process;

    -- at start of test, load vectors
    -- and pulse reset
    process is
        file tv: TEXT;
        variable i, j: integer;
        variable L: line;
        variable ch: character;
    begin
        -- read file of test vectors
        i := 0;
        FILE_OPEN(tv, "ex4_4.tv", READ_MODE);
        while not endfile(tv) loop
            readline(tv, L);
            for j in 4 downto 0 loop
                read(L, ch);
                if (ch = '_') then read(L, ch);
                end if;
                if (ch = '0') then
                    testvectors(i)(j) <= '0';
                else testvectors(i)(j) <= '1';
                end if;
            end loop;
            i := i + 1;
        end loop;
        vectornum := 0; errors := 0;
        reset <= '1'; wait for 27 ns; reset <= '0';
        wait;
    end process;

```

(VHDL continued on next page)

(continued from previous page)

VHDL

```
-- apply test vectors on rising edge of clk
process (clk) begin
    if (clk'event and clk = '1') then

        a <= testvectors(vectornum)(4 downto 1)
        after 1 ns;
        yexpected <= testvectors(vectornum)(0)
        after 1 ns;
    end if;
end process;

-- check results on falling edge of clk
process (clk) begin
    if (clk'event and clk = '0' and reset = '0') then
        assert y = yexpected
            report "Error: y = " & STD_LOGIC'image(y);
        if (y /= yexpected) then
            errors := errors + 1;
        end if;
        vectornum := vectornum + 1;
        if (is_x(testvectors(vectornum))) then
            if (errors = 0) then
                report "Just kidding -- " &
                    integer'image(vectornum) &
                    " tests completed successfully."
                    severity failure;
            else
                report integer'image(vectornum) &
                    " tests completed, errors = " &
                    integer'image(errors)
                    severity failure;
            end if;
        end if;
    end if;
end process;
end;
```

Exercise 4.5

SystemVerilog

```
module minority(input  logic a, b, c
               output logic y);

    assign y = ~a & ~b | ~a & ~c | ~b & ~c;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity minority is
    port(a, b, c:  in  STD_LOGIC;
         y:        out STD_LOGIC);
end;

architecture synth of minority is
begin
    y <= ((not a) and (not b)) or ((not a) and (not c))
        or ((not b) and (not c));
end;
```

Exercise 4.6

SystemVerilog

```
module sevenseg(input  logic [3:0] data,
                output logic [6:0] segments);

    always_comb
    case (data)
        //          abc_defg
        4'h0: segments = 7'b111_1110;
        4'h1: segments = 7'b011_0000;
        4'h2: segments = 7'b110_1101;
        4'h3: segments = 7'b111_1001;
        4'h4: segments = 7'b011_0011;
        4'h5: segments = 7'b101_1011;
        4'h6: segments = 7'b101_1111;
        4'h7: segments = 7'b111_0000;
        4'h8: segments = 7'b111_1111;
        4'h9: segments = 7'b111_0011;
        4'ha: segments = 7'b111_0111;
        4'hb: segments = 7'b001_1111;
        4'hc: segments = 7'b000_1101;
        4'hd: segments = 7'b011_1101;
        4'he: segments = 7'b100_1111;
        4'hf: segments = 7'b100_0111;
    endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity seven_seg_decoder is
    port(data:      in  STD_LOGIC_VECTOR(3 downto 0);
          segments: out STD_LOGIC_VECTOR(6 downto 0));
end;

architecture synth of seven_seg_decoder is
begin
    process(all) begin
        case data is
            --          abcdefg
            when X"0" => segments <= "1111110";
            when X"1" => segments <= "0110000";
            when X"2" => segments <= "1101101";
            when X"3" => segments <= "1111001";
            when X"4" => segments <= "0110011";
            when X"5" => segments <= "1011011";
            when X"6" => segments <= "1011111";
            when X"7" => segments <= "1110000";
            when X"8" => segments <= "1111111";
            when X"9" => segments <= "1110011";
            when X"A" => segments <= "1110111";
            when X"B" => segments <= "0011111";
            when X"C" => segments <= "0001101";
            when X"D" => segments <= "0111101";
            when X"E" => segments <= "1001111";
            when X"F" => segments <= "1000111";
            when others => segments <= "0000000";
        end case;
    end process;
end;
```

Exercise 4.7

ex4_7.tv file:

```
0000_111_1110
0001_011_0000
0010_110_1101
0011_111_1001
0100_011_0011
0101_101_1011
0110_101_1111
0111_111_0000
1000_111_1111
1001_111_1011
1010_111_0111
1011_001_1111
1100_000_1101
1101_011_1101
1110_100_1111
1111_100_0111
```


Option 1:

SystemVerilog

```

module ex4_7_testbench();
    logic      clk, reset;
    logic [3:0] data;
    logic [6:0] s_expected;
    logic [6:0] s;
    logic [31:0] vectornum, errors;
    logic [10:0] testvectors[10000:0];

    // instantiate device under test
    sevenseg dut(data, s);

    // generate clock
    always
    begin
        clk = 1; #5; clk = 0; #5;
    end

    // at start of test, load vectors
    // and pulse reset
    initial
    begin
        $readmemb("ex4_7.tv", testvectors);
        vectornum = 0; errors = 0;
        reset = 1; #27; reset = 0;
    end

    // apply test vectors on rising edge of clk
    always @(posedge clk)
    begin
        #1; {data, s_expected} =
            testvectors[vectornum];
    end

    // check results on falling edge of clk
    always @(negedge clk)
    if (~reset) begin // skip during reset
        if (s != s_expected) begin
            $display("Error: inputs = %h", data);
            $display("  outputs = %b (%b expected)",
                s, s_expected);
            errors = errors + 1;
        end
        vectornum = vectornum + 1;
        if (testvectors[vectornum] == 11'bx) begin
            $display("%d tests completed with %d errors",
                vectornum, errors);
            $finish;
        end
    end
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;
use STD.TEXTIO.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;

entity ex4_7_testbench is -- no inputs or outputs
end;

architecture sim of ex4_7_testbench is
    component seven_seg_decoder
        port(data: in STD_LOGIC_VECTOR(3 downto 0);
             segments: out STD_LOGIC_VECTOR(6 downto 0));
    end component;
    signal data: STD_LOGIC_VECTOR(3 downto 0);
    signal s: STD_LOGIC_VECTOR(6 downto 0);
    signal clk, reset: STD_LOGIC;
    signal s_expected: STD_LOGIC_VECTOR(6 downto 0);
    constant MEMSIZE: integer := 10000;
    type tarray is array(MEMSIZE downto 0) of
        STD_LOGIC_VECTOR(10 downto 0);
    signal testvectors: tarray;
    shared variable vectornum, errors: integer;
begin
    -- instantiate device under test
    dut: seven_seg_decoder port map(data, s);

    -- generate clock
    process begin
        clk <= '1'; wait for 5 ns;
        clk <= '0'; wait for 5 ns;
    end process;

    -- at start of test, load vectors
    -- and pulse reset
    process is
        file tv: TEXT;
        variable i, j: integer;
        variable L: line;
        variable ch: character;
    begin
        -- read file of test vectors
        i := 0;
        FILE_OPEN(tv, "ex4_7.tv", READ_MODE);
        while not endfile(tv) loop
            readline(tv, L);
            for j in 10 downto 0 loop
                read(L, ch);
                if (ch = '_') then read(L, ch);
                end if;
                if (ch = '0') then
                    testvectors(i)(j) <= '0';
                else testvectors(i)(j) <= '1';
                end if;
            end loop;
            i := i + 1;
        end loop;
    end process;
end architecture

```

(VHDL continued on next page)

(continued from previous page)

VHDL

```
vectornum := 0; errors := 0;
reset <= '1'; wait for 27 ns; reset <= '0';
wait;
end process;

-- apply test vectors on rising edge of clk
process (clk) begin
    if (clk'event and clk = '1') then

        data <= testvectors(vectornum)(10 downto 7)
        after 1 ns;
        s_expected <= testvectors(vectornum)(6 downto 0)
        after 1 ns;
        end if;
    end process;

-- check results on falling edge of clk
process (clk) begin
    if (clk'event and clk = '0' and reset = '0') then
        assert s = s_expected
        report "data = " &
            integer'image(CONV_INTEGER(data)) &
            "; s = " &
            integer'image(CONV_INTEGER(s)) &
            "; s_expected = " &
            integer'image(CONV_INTEGER(s_expected));
        if (s /= s_expected) then
            errors := errors + 1;
        end if;
        vectornum := vectornum + 1;
        if (is_x(testvectors(vectornum))) then
            if (errors = 0) then
                report "Just kidding -- " &
                    integer'image(vectornum) &
                    " tests completed successfully."
                severity failure;
            else
                report integer'image(vectornum) &
                    " tests completed, errors = " &
                    integer'image(errors)
                severity failure;
            end if;
        end if;
    end process;
end;
```


Option 2 (VHDL only):

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;
use STD.TEXTIO.all;
use work.txt_util.all;

entity ex4_7_testbench is -- no inputs or outputs
end;

architecture sim of ex4_7_testbench is
  component seven_seg_decoder
    port(data: in STD_LOGIC_VECTOR(3 downto 0);
          segments: out STD_LOGIC_VECTOR(6 downto 0));
  end component;
  signal data: STD_LOGIC_VECTOR(3 downto 0);
  signal s: STD_LOGIC_VECTOR(6 downto 0);
  signal clk, reset: STD_LOGIC;
  signal s_expected: STD_LOGIC_VECTOR(6 downto 0);
  constant MEMSIZE: integer := 10000;
  type tarray is array(MEMSIZE downto 0) of
    STD_LOGIC_VECTOR(10 downto 0);
  signal testvectors: tarray;
  shared variable vectornum, errors: integer;
begin
  -- instantiate device under test
  dut: seven_seg_decoder port map(data, s);

  -- generate clock
  process begin
    clk <= '1'; wait for 5 ns;
    clk <= '0'; wait for 5 ns;
  end process;

  -- at start of test, load vectors
  -- and pulse reset
  process is
    file tv: TEXT;
    variable i, j: integer;
    variable L: line;
    variable ch: character;
  begin
    -- read file of test vectors
    i := 0;
    FILE_OPEN(tv, "ex4_7.tv", READ_MODE);
    while not endfile(tv) loop
      readline(tv, L);
      for j in 10 downto 0 loop
        read(L, ch);
        if (ch = '_') then read(L, ch);
        end if;
        if (ch = '0') then
          testvectors(i)(j) <= '0';
        else testvectors(i)(j) <= '1';
        end if;
      end loop;
      i := i + 1;
    end loop;

    vectornum := 0; errors := 0;
    reset <= '1'; wait for 27 ns; reset <= '0';
  end process;
end;

```

```

    wait;
  end process;

  -- apply test vectors on rising edge of clk
  process (clk) begin
    if (clk'event and clk = '1') then

      data <= testvectors(vectornum)(10 downto 7)
        after 1 ns;
      s_expected <= testvectors(vectornum)(6 downto 0)
        after 1 ns;
      end if;
    end process;

  -- check results on falling edge of clk
  process (clk) begin
    if (clk'event and clk = '0' and reset = '0') then
      assert s = s_expected
        report "data = " & str(data) &
          "; s = " & str(s) &
            "; s_expected = " & str(s_expected);
      if (s /= s_expected) then
        errors := errors + 1;
      end if;
      vectornum := vectornum + 1;
      if (is_x(testvectors(vectornum))) then
        if (errors = 0) then
          report "Just kidding -- " &
            integer'image(vectornum) &
              " tests completed successfully."
            severity failure;
        else
          report integer'image(vectornum) &
            " tests completed, errors = " &
              integer'image(errors)
            severity failure;
        end if;
      end if;
    end process;
  end;
end;

```

(see Web site for file: txt_util.vhd)

Exercise 4.8

SystemVerilog

```
module mux8
  #(parameter width = 4)
  (input logic [width-1:0] d0, d1, d2, d3,
   d4, d5, d6, d7,
   input logic [2:0] s,
   output logic [width-1:0] y);

  always_comb
  case (s)
    0: y = d0;
    1: y = d1;
    2: y = d2;
    3: y = d3;
    4: y = d4;
    5: y = d5;
    6: y = d6;
    7: y = d7;
  endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux8 is
  generic(width: integer := 4);
  port(d0,
        d1,
        d2,
        d3,
        d4,
        d5,
        d6,
        d7: in STD_LOGIC_VECTOR(width-1 downto 0);
        s: in STD_LOGIC_VECTOR(2 downto 0);
        y: out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture synth of mux8 is
begin
  with s select y <=
    d0 when "000",
    d1 when "001",
    d2 when "010",
    d3 when "011",
    d4 when "100",
    d5 when "101",
    d6 when "110",
    d7 when others;
end;
```

Exercise 4.9

SystemVerilog

```
module ex4_9
    (input  logic a, b, c,
     output logic y);

    mux8 #(1) mux8_1(1'b1, 1'b0, 1'b0, 1'b1,
                    1'b1, 1'b1, 1'b0, 1'b0,
                    {a,b,c}, y);

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_9 is
    port(a,
         b,
         c: in  STD_LOGIC;
         y: out STD_LOGIC_VECTOR(0 downto 0));
end;

architecture struct of ex4_9 is
    component mux8
        generic(width: integer);
        port(d0, d1, d2, d3, d4, d5, d6,
             d7: in  STD_LOGIC_VECTOR(width-1 downto 0);
             s:   in  STD_LOGIC_VECTOR(2 downto 0);
             y:   out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    signal sel: STD_LOGIC_VECTOR(2 downto 0);
begin
    sel <= a & b & c;

    mux8_1: mux8 generic map(1)
        port map("1", "0", "0", "1",
                "1", "1", "0", "0",
                sel, y);
end;
```

Exercise 4.10

SystemVerilog

```
module ex4_10
    (input  logic a, b, c,
     output logic y);

    mux4 #(1) mux4_1( ~c, c, 1'b1, 1'b0, {a, b}, y);
endmodule

module mux4
    #(parameter width = 4)
    (input  logic [width-1:0] d0, d1, d2, d3,
     input  logic [1:0]      s,
     output logic [width-1:0] y);

    always_comb
        case (s)
            0: y = d0;
            1: y = d1;
            2: y = d2;
            3: y = d3;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_10 is
    port(a,
         b,
         c: in  STD_LOGIC;
         y: out STD_LOGIC_VECTOR(0 downto 0));
end;

architecture struct of ex4_10 is
    component mux4
        generic(width: integer);
        port(d0, d1, d2,
             d3: in  STD_LOGIC_VECTOR(width-1 downto 0);
             s: in  STD_LOGIC_VECTOR(1 downto 0);
             y: out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    signal cb:      STD_LOGIC_VECTOR(0 downto 0);
    signal c_vect:  STD_LOGIC_VECTOR(0 downto 0);
    signal sel:     STD_LOGIC_VECTOR(1 downto 0);
begin
    c_vect(0) <= c;
    cb(0) <= not c;
    sel <= (a & b);
    mux4_1: mux4 generic map(1)
        port map(cb, c_vect, "1", "0", sel, y);
end;


library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux4 is
    generic(width: integer := 4);
    port(d0,
         d1,
         d2,
         d3: in  STD_LOGIC_VECTOR(width-1 downto 0);
         s: in  STD_LOGIC_VECTOR(1 downto 0);
         y: out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture synth of mux4 is
begin
    with s select y <=
        d0 when "00",
        d1 when "01",
        d2 when "10",
        d3 when others;
end;
```

Exercise 4.11

A shift register with feedback, shown below, cannot be correctly described with blocking assignments.

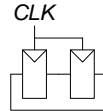

Exercise 4.12

SystemVerilog

```
module priority(input  logic [7:0] a,
               output logic [7:0] y);

    always_comb
    casez (a)
        8'b1??????? : y = 8'b10000000;
        8'b01?????? : y = 8'b01000000;
        8'b001????? : y = 8'b00100000;
        8'b0001???? : y = 8'b00010000;
        8'b00001??? : y = 8'b00001000;
        8'b000001?? : y = 8'b00000100;
        8'b0000001? : y = 8'b00000010;
        8'b000000001 : y = 8'b000000001;
        default:     y = 8'b000000000;
    endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity priority is
    port(a:      in  STD_LOGIC_VECTOR(7 downto 0);
          y: out  STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of priority is
begin
    process(all) begin
        if    a(7) = '1' then y <= "10000000";
        elsif a(6) = '1' then y <= "01000000";
        elsif a(5) = '1' then y <= "00100000";
        elsif a(4) = '1' then y <= "00010000";
        elsif a(3) = '1' then y <= "00001000";
        elsif a(2) = '1' then y <= "00000100";
        elsif a(1) = '1' then y <= "00000010";
        elsif a(0) = '1' then y <= "00000001";
        else
            y <= "00000000";
        end if;
    end process;
end;
```

Exercise 4.13

SystemVerilog

```
module decoder2_4(input  logic [1:0] a,
                  output logic [3:0] y);
    always_comb
        case (a)
            2'b00: y = 4'b0001;
            2'b01: y = 4'b0010;
            2'b10: y = 4'b0100;
            2'b11: y = 4'b1000;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity decoder2_4 is
    port(a: in  STD_LOGIC_VECTOR(1 downto 0);
          y: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of decoder2_4 is
begin
    process(all) begin
        case a is
            when "00"  => y <= "0001";
            when "01"  => y <= "0010";
            when "10"  => y <= "0100";
            when "11"  => y <= "1000";
            when others => y <= "0000";
        end case;
    end process;
end;
```

Exercise 4.14

SystemVerilog

```
module decoder6_64(input  logic [5:0] a,
                  output logic [63:0] y);

    logic [11:0] y2_4;

    decoder2_4 dec0(a[1:0], y2_4[3:0]);
    decoder2_4 dec1(a[3:2], y2_4[7:4]);
    decoder2_4 dec2(a[5:4], y2_4[11:8]);

    assign y[0] = y2_4[0] & y2_4[4] & y2_4[8];
    assign y[1] = y2_4[1] & y2_4[4] & y2_4[8];
    assign y[2] = y2_4[2] & y2_4[4] & y2_4[8];
    assign y[3] = y2_4[3] & y2_4[4] & y2_4[8];
    assign y[4] = y2_4[0] & y2_4[5] & y2_4[8];
    assign y[5] = y2_4[1] & y2_4[5] & y2_4[8];
    assign y[6] = y2_4[2] & y2_4[5] & y2_4[8];
    assign y[7] = y2_4[3] & y2_4[5] & y2_4[8];
    assign y[8] = y2_4[0] & y2_4[6] & y2_4[8];
    assign y[9] = y2_4[1] & y2_4[6] & y2_4[8];
    assign y[10] = y2_4[2] & y2_4[6] & y2_4[8];
    assign y[11] = y2_4[3] & y2_4[6] & y2_4[8];
    assign y[12] = y2_4[0] & y2_4[7] & y2_4[8];
    assign y[13] = y2_4[1] & y2_4[7] & y2_4[8];
    assign y[14] = y2_4[2] & y2_4[7] & y2_4[8];
    assign y[15] = y2_4[3] & y2_4[7] & y2_4[8];
    assign y[16] = y2_4[0] & y2_4[4] & y2_4[9];
    assign y[17] = y2_4[1] & y2_4[4] & y2_4[9];
    assign y[18] = y2_4[2] & y2_4[4] & y2_4[9];
    assign y[19] = y2_4[3] & y2_4[4] & y2_4[9];
    assign y[20] = y2_4[0] & y2_4[5] & y2_4[9];
    assign y[21] = y2_4[1] & y2_4[5] & y2_4[9];
    assign y[22] = y2_4[2] & y2_4[5] & y2_4[9];
    assign y[23] = y2_4[3] & y2_4[5] & y2_4[9];
    assign y[24] = y2_4[0] & y2_4[6] & y2_4[9];
    assign y[25] = y2_4[1] & y2_4[6] & y2_4[9];
    assign y[26] = y2_4[2] & y2_4[6] & y2_4[9];
    assign y[27] = y2_4[3] & y2_4[6] & y2_4[9];
    assign y[28] = y2_4[0] & y2_4[7] & y2_4[9];
    assign y[29] = y2_4[1] & y2_4[7] & y2_4[9];
    assign y[30] = y2_4[2] & y2_4[7] & y2_4[9];
    assign y[31] = y2_4[3] & y2_4[7] & y2_4[9];
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity decoder6_64 is
    port(a: in  STD_LOGIC_VECTOR(5 downto 0);
         y: out STD_LOGIC_VECTOR(63 downto 0));
end;

architecture struct of decoder6_64 is
    component decoder2_4
        port(a: in  STD_LOGIC_VECTOR(1 downto 0);
             y: out STD_LOGIC_VECTOR(3 downto 0));
    end component;
    signal y2_4: STD_LOGIC_VECTOR(11 downto 0);
begin
    dec0: decoder2_4 port map(a(1 downto 0),
                             y2_4(3 downto 0));
    dec1: decoder2_4 port map(a(3 downto 2),
                             y2_4(7 downto 4));
    dec2: decoder2_4 port map(a(5 downto 4),
                             y2_4(11 downto 8));

    y(0) <= y2_4(0) and y2_4(4) and y2_4(8);
    y(1) <= y2_4(1) and y2_4(4) and y2_4(8);
    y(2) <= y2_4(2) and y2_4(4) and y2_4(8);
    y(3) <= y2_4(3) and y2_4(4) and y2_4(8);
    y(4) <= y2_4(0) and y2_4(5) and y2_4(8);
    y(5) <= y2_4(1) and y2_4(5) and y2_4(8);
    y(6) <= y2_4(2) and y2_4(5) and y2_4(8);
    y(7) <= y2_4(3) and y2_4(5) and y2_4(8);
    y(8) <= y2_4(0) and y2_4(6) and y2_4(8);
    y(9) <= y2_4(1) and y2_4(6) and y2_4(8);
    y(10) <= y2_4(2) and y2_4(6) and y2_4(8);
    y(11) <= y2_4(3) and y2_4(6) and y2_4(8);
    y(12) <= y2_4(0) and y2_4(7) and y2_4(8);
    y(13) <= y2_4(1) and y2_4(7) and y2_4(8);
    y(14) <= y2_4(2) and y2_4(7) and y2_4(8);
    y(15) <= y2_4(3) and y2_4(7) and y2_4(8);
    y(16) <= y2_4(0) and y2_4(4) and y2_4(9);
    y(17) <= y2_4(1) and y2_4(4) and y2_4(9);
    y(18) <= y2_4(2) and y2_4(4) and y2_4(9);
    y(19) <= y2_4(3) and y2_4(4) and y2_4(9);
    y(20) <= y2_4(0) and y2_4(5) and y2_4(9);
    y(21) <= y2_4(1) and y2_4(5) and y2_4(9);
    y(22) <= y2_4(2) and y2_4(5) and y2_4(9);
    y(23) <= y2_4(3) and y2_4(5) and y2_4(9);
    y(24) <= y2_4(0) and y2_4(6) and y2_4(9);
    y(25) <= y2_4(1) and y2_4(6) and y2_4(9);
    y(26) <= y2_4(2) and y2_4(6) and y2_4(9);
    y(27) <= y2_4(3) and y2_4(6) and y2_4(9);
    y(28) <= y2_4(0) and y2_4(7) and y2_4(9);
    y(29) <= y2_4(1) and y2_4(7) and y2_4(9);
    y(30) <= y2_4(2) and y2_4(7) and y2_4(9);
    y(31) <= y2_4(3) and y2_4(7) and y2_4(9);
```

(continued on next page)

(continued from previous page)

SystemVerilog

VHDL

```
assign y[32] = y2_4[0] & y2_4[4] & y2_4[10];
assign y[33] = y2_4[1] & y2_4[4] & y2_4[10];
assign y[34] = y2_4[2] & y2_4[4] & y2_4[10];
assign y[35] = y2_4[3] & y2_4[4] & y2_4[10];
assign y[36] = y2_4[0] & y2_4[5] & y2_4[10];
assign y[37] = y2_4[1] & y2_4[5] & y2_4[10];
assign y[38] = y2_4[2] & y2_4[5] & y2_4[10];
assign y[39] = y2_4[3] & y2_4[5] & y2_4[10];
assign y[40] = y2_4[0] & y2_4[6] & y2_4[10];
assign y[41] = y2_4[1] & y2_4[6] & y2_4[10];
assign y[42] = y2_4[2] & y2_4[6] & y2_4[10];
assign y[43] = y2_4[3] & y2_4[6] & y2_4[10];
assign y[44] = y2_4[0] & y2_4[7] & y2_4[10];
assign y[45] = y2_4[1] & y2_4[7] & y2_4[10];
assign y[46] = y2_4[2] & y2_4[7] & y2_4[10];
assign y[47] = y2_4[3] & y2_4[7] & y2_4[10];
assign y[48] = y2_4[0] & y2_4[4] & y2_4[11];
assign y[49] = y2_4[1] & y2_4[4] & y2_4[11];
assign y[50] = y2_4[2] & y2_4[4] & y2_4[11];
assign y[51] = y2_4[3] & y2_4[4] & y2_4[11];
assign y[52] = y2_4[0] & y2_4[5] & y2_4[11];
assign y[53] = y2_4[1] & y2_4[5] & y2_4[11];
assign y[54] = y2_4[2] & y2_4[5] & y2_4[11];
assign y[55] = y2_4[3] & y2_4[5] & y2_4[11];
assign y[56] = y2_4[0] & y2_4[6] & y2_4[11];
assign y[57] = y2_4[1] & y2_4[6] & y2_4[11];
assign y[58] = y2_4[2] & y2_4[6] & y2_4[11];
assign y[59] = y2_4[3] & y2_4[6] & y2_4[11];
assign y[60] = y2_4[0] & y2_4[7] & y2_4[11];
assign y[61] = y2_4[1] & y2_4[7] & y2_4[11];
assign y[62] = y2_4[2] & y2_4[7] & y2_4[11];
assign y[63] = y2_4[3] & y2_4[7] & y2_4[11];
endmodule
```

```
y(32) <= y2_4(0) and y2_4(4) and y2_4(10);
y(33) <= y2_4(1) and y2_4(4) and y2_4(10);
y(34) <= y2_4(2) and y2_4(4) and y2_4(10);
y(35) <= y2_4(3) and y2_4(4) and y2_4(10);
y(36) <= y2_4(0) and y2_4(5) and y2_4(10);
y(37) <= y2_4(1) and y2_4(5) and y2_4(10);
y(38) <= y2_4(2) and y2_4(5) and y2_4(10);
y(39) <= y2_4(3) and y2_4(5) and y2_4(10);
y(40) <= y2_4(0) and y2_4(6) and y2_4(10);
y(41) <= y2_4(1) and y2_4(6) and y2_4(10);
y(42) <= y2_4(2) and y2_4(6) and y2_4(10);
y(43) <= y2_4(3) and y2_4(6) and y2_4(10);
y(44) <= y2_4(0) and y2_4(7) and y2_4(10);
y(45) <= y2_4(1) and y2_4(7) and y2_4(10);
y(46) <= y2_4(2) and y2_4(7) and y2_4(10);
y(47) <= y2_4(3) and y2_4(7) and y2_4(10);
y(48) <= y2_4(0) and y2_4(4) and y2_4(11);
y(49) <= y2_4(1) and y2_4(4) and y2_4(11);
y(50) <= y2_4(2) and y2_4(4) and y2_4(11);
y(51) <= y2_4(3) and y2_4(4) and y2_4(11);
y(52) <= y2_4(0) and y2_4(5) and y2_4(11);
y(53) <= y2_4(1) and y2_4(5) and y2_4(11);
y(54) <= y2_4(2) and y2_4(5) and y2_4(11);
y(55) <= y2_4(3) and y2_4(5) and y2_4(11);
y(56) <= y2_4(0) and y2_4(6) and y2_4(11);
y(57) <= y2_4(1) and y2_4(6) and y2_4(11);
y(58) <= y2_4(2) and y2_4(6) and y2_4(11);
y(59) <= y2_4(3) and y2_4(6) and y2_4(11);
y(60) <= y2_4(0) and y2_4(7) and y2_4(11);
y(61) <= y2_4(1) and y2_4(7) and y2_4(11);
y(62) <= y2_4(2) and y2_4(7) and y2_4(11);
y(63) <= y2_4(3) and y2_4(7) and y2_4(11);
end;
```


Exercise 4.15

(a) $Y = AC + \overline{A}\overline{B}C$

SystemVerilog

```
module ex4_15a(input  logic a, b, c,
              output logic y);

    assign y = (a & c) | (~a & ~b & c);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_15a is
    port(a, b, c: in  STD_LOGIC;
         y:      out STD_LOGIC);
end;

architecture behave of ex4_15a is
begin
    y <= (not a and not b and c) or (not b and c);
end;
```

(b) $Y = \overline{A}\overline{B} + \overline{A}B\overline{C} + \overline{\overline{A} + \overline{C}}$

SystemVerilog

```
module ex4_15b(input  logic a, b, c,
              output logic y);

    assign y = (~a & ~b) | (~a & b & ~c) | ~(a | ~c);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_15b is
    port(a, b, c: in  STD_LOGIC;
         y:      out STD_LOGIC);
end;

architecture behave of ex4_15b is
begin
    y <= ((not a) and (not b)) or ((not a) and b and
    (not c)) or (not(a or (not c)));
end;
```

(c) $Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD + \overline{B}\overline{C}\overline{D} + \overline{A}$

SystemVerilog

```
module ex4_15c(input  logic a, b, c, d,
              output logic y);

    assign y = (~a & ~b & ~c & ~d) | (a & ~b & ~c) |
    (a & ~b & c & ~d) | (a & b & d) |
    (~a & ~b & c & ~d) | (b & ~c & d) | ~a;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_15c is
    port(a, b, c, d: in  STD_LOGIC;
         y:      out STD_LOGIC);
end;

architecture behave of ex4_15c is
begin
    y <= ((not a) and (not b) and (not c) and (not d)) or
    (a and (not b) and (not c)) or
    (a and (not b) and c and (not d)) or
    (a and b and d) or
    ((not a) and (not b) and c and (not d)) or
    (b and (not c) and d) or (not a);
end;
```

Exercise 4.16

SystemVerilog

```
module ex4_16(input  logic a, b, c, d, e,
              output logic y);

    assign y = ~(~(a & b) & ~(c & d)) & e;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_16 is
    port(a, b, c, d, e: in  STD_LOGIC;
          y:              out STD_LOGIC);
end;

architecture behave of ex4_16 is
begin
    y <= not((not((not(a and b)) and
                  (not(c and d)))) and e);

end;
```

Exercise 4.17

SystemVerilog

```
module ex4_17(input logic a, b, c, d, e, f, g
              output logic y);

    logic n1, n2, n3, n4, n5;

    assign n1 = ~(a & b & c);
    assign n2 = ~(n1 & d);
    assign n3 = ~(f & g);
    assign n4 = ~(n3 | e);
    assign n5 = ~(n2 | n4);
    assign y = ~(n5 & n5);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_17 is
    port(a, b, c, d, e, f, g: in STD_LOGIC;
          y: out STD_LOGIC);
end;

architecture synth of ex4_17 is
    signal n1, n2, n3, n4, n5: STD_LOGIC;
begin
    n1 <= not(a and b and c);
    n2 <= not(n1 and d);
    n3 <= not(f and g);
    n4 <= not(n3 or e);
    n5 <= not(n2 or n4);
    y <= not (n5 or n5);
end;
```

Exercise 4.18

Verilog

```
module ex4_18(input  logic a, b, c, d,
              output logic y);

    always_comb
        casez ({a, b, c, d})
            // note: outputs cannot be assigned don't care
            0: y = 1'b0;
            1: y = 1'b0;
            2: y = 1'b0;
            3: y = 1'b0;
            4: y = 1'b0;
            5: y = 1'b0;
            6: y = 1'b0;
            7: y = 1'b0;
            8: y = 1'b1;
            9: y = 1'b0;
            10: y = 1'b0;
            11: y = 1'b1;
            12: y = 1'b1;
            13: y = 1'b1;
            14: y = 1'b0;
            15: y = 1'b1;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_18 is
    port(a, b, c, d: in  STD_LOGIC;
          y:          out STD_LOGIC);
end;

architecture synth of ex4_17 is
    signal vars: STD_LOGIC_VECTOR(3 downto 0);
begin
    vars <= (a & b & c & d);
    process(all) begin
        case vars is
            -- note: outputs cannot be assigned don't care
            when X"0" => y <= '0';
            when X"1" => y <= '0';
            when X"2" => y <= '0';
            when X"3" => y <= '0';
            when X"4" => y <= '0';
            when X"5" => y <= '0';
            when X"6" => y <= '0';
            when X"7" => y <= '0';
            when X"8" => y <= '1';
            when X"9" => y <= '0';
            when X"A" => y <= '0';
            when X"B" => y <= '1';
            when X"C" => y <= '1';
            when X"D" => y <= '1';
            when X"E" => y <= '0';
            when X"F" => y <= '1';
            when others => y <= '0';--should never happen
        end case;
    end process;
end;
```

Exercise 4.19

SystemVerilog

```
module ex4_18(input  logic [3:0] a,
             output logic      p, d);

    always_comb
        case (a)
            0: {p, d} = 2'b00;
            1: {p, d} = 2'b00;
            2: {p, d} = 2'b10;
            3: {p, d} = 2'b11;
            4: {p, d} = 2'b00;
            5: {p, d} = 2'b10;
            6: {p, d} = 2'b01;
            7: {p, d} = 2'b10;
            8: {p, d} = 2'b00;
            9: {p, d} = 2'b01;
            10: {p, d} = 2'b00;
            11: {p, d} = 2'b10;
            12: {p, d} = 2'b01;
            13: {p, d} = 2'b10;
            14: {p, d} = 2'b00;
            15: {p, d} = 2'b01;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_18 is
    port(a:   in  STD_LOGIC_VECTOR(3 downto 0);
         p, d: out STD_LOGIC);
end;

architecture synth of ex4_18 is
    signal vars: STD_LOGIC_VECTOR(1 downto 0);
begin
    p <= vars(1);
    d <= vars(0);
    process(all) begin
        case a is
            when X"0" => vars <= "00";
            when X"1" => vars <= "00";
            when X"2" => vars <= "10";
            when X"3" => vars <= "11";
            when X"4" => vars <= "00";
            when X"5" => vars <= "10";
            when X"6" => vars <= "01";
            when X"7" => vars <= "10";
            when X"8" => vars <= "00";
            when X"9" => vars <= "01";
            when X"A" => vars <= "00";
            when X"B" => vars <= "10";
            when X"C" => vars <= "01";
            when X"D" => vars <= "10";
            when X"E" => vars <= "00";
            when X"F" => vars <= "01";
            when others => vars <= "00";
        end case;
    end process;
end;
```

Exercise 4.20

SystemVerilog

```
module priority_encoder(input  logic [7:0] a,
                      output logic [2:0] y,
                      output logic      none);

    always_comb
        casez (a)
            8'b00000000: begin y = 3'd0;  none = 1'b1; end
            8'b00000001: begin y = 3'd0;  none = 1'b0; end
            8'b0000001?: begin y = 3'd1;  none = 1'b0; end
            8'b000001?: begin y = 3'd2;  none = 1'b0; end
            8'b00001?: begin y = 3'd3;  none = 1'b0; end
            8'b0001?: begin y = 3'd4;  none = 1'b0; end
            8'b001?: begin y = 3'd5;  none = 1'b0; end
            8'b01?: begin y = 3'd6;  none = 1'b0; end
            8'b1?: begin y = 3'd7;  none = 1'b0; end
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity priority_encoder is
    port(a:    in  STD_LOGIC_VECTOR(7 downto 0);
          y:    out STD_LOGIC_VECTOR(2 downto 0);
          none: out STD_LOGIC);
end;

architecture synth of priority_encoder is
begin
    process(all) begin
        case? a is
            when "00000000" => y <= "000"; none <= '1';
            when "00000001" => y <= "000"; none <= '0';
            when "0000001-" => y <= "001"; none <= '0';
            when "000001--" => y <= "010"; none <= '0';
            when "00001---" => y <= "011"; none <= '0';
            when "0001----" => y <= "100"; none <= '0';
            when "001-----" => y <= "101"; none <= '0';
            when "01-----" => y <= "110"; none <= '0';
            when "1-----" => y <= "111"; none <= '0';
            when others      => y <= "000"; none <= '0';
        end case?;
    end process;
end;
```

Exercise 4.21

SystemVerilog

```
module priority_encoder2(input  logic [7:0] a,
                        output logic [2:0] y, z,
                        output logic      none);

always_comb
begin
    casez (a)
        8'b00000000: begin y = 3'd0; none = 1'b1; end
        8'b00000001: begin y = 3'd0; none = 1'b0; end
        8'b0000001?: begin y = 3'd1; none = 1'b0; end
        8'b000001??: begin y = 3'd2; none = 1'b0; end
        8'b00001??: begin y = 3'd3; none = 1'b0; end
        8'b0001??: begin y = 3'd4; none = 1'b0; end
        8'b001??: begin y = 3'd5; none = 1'b0; end
        8'b01??: begin y = 3'd6; none = 1'b0; end
        8'b1??: begin y = 3'd7; none = 1'b0; end
    endcase

    casez (a)
        8'b00000011: z = 3'b000;
        8'b00000101: z = 3'b000;
        8'b00001001: z = 3'b000;
        8'b00010001: z = 3'b000;
        8'b00100001: z = 3'b000;
        8'b01000001: z = 3'b000;
        8'b10000001: z = 3'b000;
        8'b0000011?: z = 3'b001;
        8'b0000101?: z = 3'b001;
        8'b0001001?: z = 3'b001;
        8'b0010001?: z = 3'b001;
        8'b0100001?: z = 3'b001;
        8'b000011??: z = 3'b010;
        8'b000101??: z = 3'b010;
        8'b001001??: z = 3'b010;
        8'b010001??: z = 3'b010;
        8'b00011??: z = 3'b011;
        8'b00101??: z = 3'b011;
        8'b01001??: z = 3'b011;
        8'b10001??: z = 3'b011;
        8'b0011??: z = 3'b100;
        8'b0101??: z = 3'b100;
        8'b1001??: z = 3'b100;
        8'b011??: z = 3'b101;
        8'b101??: z = 3'b101;
        8'b11??: z = 3'b110;
        default: z = 3'b000;
    endcase
end
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity priority_encoder2 is
    port(a: in STD_LOGIC_VECTOR(7 downto 0);
          y, z: out STD_LOGIC_VECTOR(2 downto 0);
          none: out STD_LOGIC);
end entity;

architecture synth of priority_encoder is
begin
    process(all) begin
        case? a is
            when "00000000" => y <= "000"; none <= '1';
            when "00000001" => y <= "000"; none <= '0';
            when "0000001-" => y <= "001"; none <= '0';
            when "000001--" => y <= "010"; none <= '0';
            when "00001---" => y <= "011"; none <= '0';
            when "0001----" => y <= "100"; none <= '0';
            when "001-----" => y <= "101"; none <= '0';
            when "01-----" => y <= "110"; none <= '0';
            when "1-----" => y <= "111"; none <= '0';
            when others => y <= "000"; none <= '0';
        end case?;
        case? a is
            when "00000011" => z <= "000";
            when "00000101" => z <= "000";
            when "00001001" => z <= "000";
            when "00001001" => z <= "000";
            when "00010001" => z <= "000";
            when "00100001" => z <= "000";
            when "01000001" => z <= "000";
            when "10000001" => z <= "000";
            when "0000011-" => z <= "001";
            when "0000101-" => z <= "001";
            when "0001001-" => z <= "001";
            when "0010001-" => z <= "001";
            when "0100001-" => z <= "001";
            when "1000001-" => z <= "001";
            when "000011--" => z <= "010";
            when "000101--" => z <= "010";
            when "000101--" => z <= "010";
            when "001001--" => z <= "010";
            when "010001--" => z <= "010";
            when "100001--" => z <= "010";
            when "00011---" => z <= "011";
            when "00101---" => z <= "011";
            when "01001---" => z <= "011";
            when "10001---" => z <= "011";
            when "0011----" => z <= "100";
            when "0101----" => z <= "100";
            when "1001----" => z <= "100";
            when "011-----" => z <= "101";
            when "101-----" => z <= "101";
            when "11-----" => z <= "110";
            when others => z <= "000";
        end case?;
    end process;
end;
```

Exercise 4.22

SystemVerilog

```
module thermometer(input  logic [2:0] a,
                   output logic [6:0] y);

    always_comb
        case (a)
            0: y = 7'b0000000;
            1: y = 7'b0000001;
            2: y = 7'b0000011;
            3: y = 7'b0000111;
            4: y = 7'b0001111;
            5: y = 7'b0011111;
            6: y = 7'b0111111;
            7: y = 7'b1111111;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity thermometer is
    port(a:    in  STD_LOGIC_VECTOR(2 downto 0);
         y:    out STD_LOGIC_VECTOR(6 downto 0));
end;

architecture synth of thermometer is
begin
    process(all) begin
        case a is
            when "000" => y <= "0000000";
            when "001" => y <= "0000001";
            when "010" => y <= "0000011";
            when "011" => y <= "0000111";
            when "100" => y <= "0001111";
            when "101" => y <= "0011111";
            when "110" => y <= "0111111";
            when "111" => y <= "1111111";
            when others => y <= "0000000";
        end case;
    end process;
end;
```

Exercise 4.23

SystemVerilog

```
module month31days(input  logic [3:0] month,
                  output logic      y);

    always_comb
    casez (month)
        1:      y = 1'b1;
        2:      y = 1'b0;
        3:      y = 1'b1;
        4:      y = 1'b0;
        5:      y = 1'b1;
        6:      y = 1'b0;
        7:      y = 1'b1;
        8:      y = 1'b1;
        9:      y = 1'b0;
        10:     y = 1'b1;
        11:     y = 1'b0;
        12:     y = 1'b1;
        default: y = 1'b0;
    endcase
endmodule
```


VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity month31days is
    port(a:      in  STD_LOGIC_VECTOR(3 downto 0);
         y:      out STD_LOGIC);
end;

architecture synth of month31days is
begin
    process(all) begin
        case a is
            when X"1" => y <= '1';
            when X"2" => y <= '0';
            when X"3" => y <= '1';
            when X"4" => y <= '0';
            when X"5" => y <= '1';
            when X"6" => y <= '0';
            when X"7" => y <= '1';
            when X"8" => y <= '1';
            when X"9" => y <= '0';
            when X"A" => y <= '1';
            when X"B" => y <= '0';
            when X"C" => y <= '1';
            when others => y <= '0';
        end case;
    end process;
end;
```

Exercise 4.24

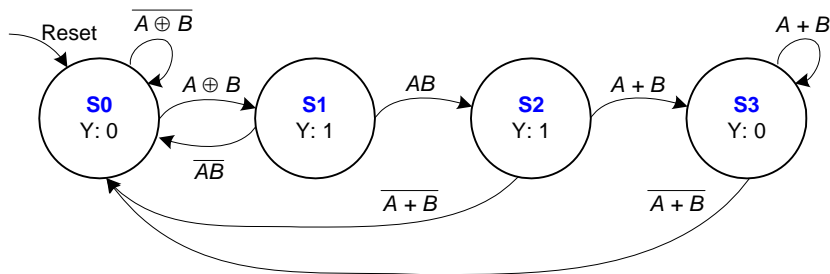

Exercise 4.25

 


FIGURE 4.1 State transition diagram for Exercise 4.25

Exercise 4.26

SystemVerilog

```

module srlatch(input logic s, r,
               output logic q, qbar);

    always_comb
        case ({s,r})
            2'b01: {q, qbar} = 2'b01;
            2'b10: {q, qbar} = 2'b10;
            2'b11: {q, qbar} = 2'b00;
        endcase
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity srlatch is
    port(s, r: in STD_LOGIC;
          q, qbar: out STD_LOGIC);
end;

architecture synth of srlatch is
    signal qqbar: STD_LOGIC_VECTOR(1 downto 0);
    signal sr: STD_LOGIC_VECTOR(1 downto 0);
begin
    q <= qqbar(1);
    qbar <= qqbar(0);
    sr <= s & r;
    process(all) begin
        if sr = '11' and sr = '00'
            then qqbar <= "10";
        elsif sr = '01' and sr = '10'
            then qqbar <= "01";
        elsif sr = '11' and sr = '11'
            then qqbar <= "00";
        end if;
    end process;
end;

```

Exercise 4.27

SystemVerilog

```
module jkflop(input logic j, k, clk,
             output logic q);

    always @(posedge clk)
        case ({j,k})
            2'b01: q <= 1'b0;
            2'b10: q <= 1'b1;
            2'b11: q <= ~q;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity jkflop is
    port(j, k, clk: in STD_LOGIC;
         q: inout STD_LOGIC);
end;

architecture synth of jkflop is
    signal jk: STD_LOGIC_VECTOR(1 downto 0);
begin
    jk <= j & k;
    process(clk) begin
        if rising_edge(clk) then
            if j = '1' and k = '0'
                then q <= '1';
            elsif j = '0' and k = '1'
                then q <= '0';
            elsif j = '1' and k = '1'
                then q <= not q;
            end if;
        end if;
    end process;
end;
```

Exercise 4.28

SystemVerilog

```
module latch3_18(input logic d, clk,
                 output logic q);

    logic n1, n2, clk_b;

    assign #1 n1 = clk & d;
    assign clk_b = ~clk;
    assign #1 n2 = clk_b & q;
    assign #1 q = n1 | n2;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity latch3_18 is
    port(d, clk: in STD_LOGIC;
         q: inout STD_LOGIC);
end;

architecture synth of latch3_18 is
    signal n1, clk_b, n2: STD_LOGIC;
begin
    n1 <= (clk and d) after 1 ns;
    clk_b <= (not clk);
    n2 <= (clk_b and q) after 1 ns;
    q <= (n1 or n2) after 1 ns;
end;
```

This circuit is in error with any delay in the inverter.

Exercise 4.29

SystemVerilog

```
module trafficFSM(input  logic clk, reset, ta, tb,
                 output logic [1:0] la, lb);

    typedef enum logic [1:0] {S0, S1, S2, S3}
        statetype;
    statetype [1:0] state, nextstate;

    parameter green  = 2'b00;
    parameter yellow = 2'b01;
    parameter red    = 2'b10;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (ta) nextstate = S0;
                else      nextstate = S1;
            S1:      nextstate = S2;
            S2: if (tb) nextstate = S2;
                else      nextstate = S3;
            S3:      nextstate = S0;
        endcase

    // Output Logic
    always_comb
        case (state)
            S0: {la, lb} = {green, red};
            S1: {la, lb} = {yellow, red};
            S2: {la, lb} = {red, green};
            S3: {la, lb} = {red, yellow};
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity trafficFSM is
    port(clk, reset, ta, tb: in  STD_LOGIC;
         la, lb: inout STD_LOGIC_VECTOR(1 downto 0));
end;

architecture behave of trafficFSM is
    type statetype is (S0, S1, S2, S3);
    signal state, nextstate: statetype;
    signal lalb: STD_LOGIC_VECTOR(3 downto 0);
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if ta then
                            nextstate <= S0;
                        else nextstate <= S1;
                        end if;
            when S1 => nextstate <= S2;
            when S2 => if tb then
                            nextstate <= S2;
                        else nextstate <= S3;
                        end if;
            when S3 => nextstate <= S0;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    la <= lalb(3 downto 2);
    lb <= lalb(1 downto 0);
    process(all) begin
        case state is
            when S0 => lalb <= "0010";
            when S1 => lalb <= "0110";
            when S2 => lalb <= "1000";
            when S3 => lalb <= "1001";
            when others => lalb <= "1010";
        end case;
    end process;
end;
```

Exercise 4.30

Mode Module

SystemVerilog

```
module mode(input  logic clk, reset, p, r,
            output logic m);

    typedef enum logic {S0, S1} statetype;
    statetype state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (p) nextstate = S1;
                else nextstate = S0;
            S1: if (r) nextstate = S0;
                else nextstate = S1;
        endcase

    // Output Logic
    assign m = state;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mode is
    port(clk, reset, p, r: in  STD_LOGIC;
          m: out STD_LOGIC);
end;

architecture synth of mode is
    type statetype is (S0, S1);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if p then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if r then
                            nextstate <= S0;
                        else nextstate <= S1;
                        end if;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    m <= '1' when state = S1 else '0';
end;
```

(continued on next page)

Lights Module

SystemVerilog

```
module lights(input logic clk, reset, ta, tb, m,
             output logic [1:0] la, lb);

    typedef enum logic [1:0] {S0, S1, S2, S3}
        statetype;

    statetype [1:0] state, nextstate;

    parameter green = 2'b00;
    parameter yellow = 2'b01;
    parameter red = 2'b10;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (ta) nextstate = S0;
                else nextstate = S1;
            S1: nextstate = S2;
            S2: if (tb | m) nextstate = S2;
                else nextstate = S3;
            S3: nextstate = S0;
        endcase

    // Output Logic
    always_comb
        case (state)
            S0: {la, lb} = {green, red};
            S1: {la, lb} = {yellow, red};
            S2: {la, lb} = {red, green};
            S3: {la, lb} = {red, yellow};
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity lights is
    port(clk, reset, ta, tb, m: in STD_LOGIC;
         la, lb: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of lights is
    type statetype is (S0, S1, S2, S3);
    signal state, nextstate: statetype;
    signal lalb: STD_LOGIC_VECTOR(3 downto 0);
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if ta then
                            nextstate <= S0;
                        else nextstate <= S1;
                        end if;
            when S1 => nextstate <= S2;
            when S2 => if ((tb or m) = '1') then
                            nextstate <= S2;
                        else nextstate <= S3;
                        end if;
            when S3 => nextstate <= S0;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    la <= lalb(3 downto 2);
    lb <= lalb(1 downto 0);
    process(all) begin
        case state is
            when S0 => lalb <= "0010";
            when S1 => lalb <= "0110";
            when S2 => lalb <= "1000";
            when S3 => lalb <= "1001";
            when others => lalb <= "1010";
        end case;
    end process;
end;
```

(continued on next page)

Controller Module

SystemVerilog

```
module controller(input  logic clk, reset, p,
                  r, ta, tb,
                  output logic [1:0] la, lb);

    mode modefsm(clk, reset, p, r, m);
    lights lightsfsm(clk, reset, ta, tb, m, la, lb);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity controller is
    port(clk, reset: in  STD_LOGIC;
          p, r, ta:   in  STD_LOGIC;
          tb:        in  STD_LOGIC;
          la, lb: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture struct of controller is
    component mode
        port(clk, reset, p, r: in  STD_LOGIC;
              m:          out STD_LOGIC);
    end component;
    component lights
        port(clk, reset, ta, tb, m: in  STD_LOGIC;
              la, lb: out STD_LOGIC_VECTOR(1 downto 0));
    end component;

    begin
        modefsm:  mode  port map(clk, reset, p, r, m);
        lightsfsm: lights port map(clk, reset, ta, tb,
                                   m, la, lb);
    end;
```

Exercise 4.31

SystemVerilog

```
module fig3_42(input  logic clk, a, b, c, d,
              output logic x, y);

    logic n1, n2;
    logic areg, breg, creg, dreg;

    always_ff @(posedge clk) begin
        areg <= a;
        breg <= b;
        creg <= c;
        dreg <= d;
        x <= n2;
        y <= ~(dreg | n2);
    end

    assign n1 = areg & breg;
    assign n2 = n1 | creg;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fig3_42 is
    port(clk, a, b, c, d: in  STD_LOGIC;
          x, y:           out STD_LOGIC);
end;

architecture synth of fig3_42 is
    signal n1, n2, areg, breg, creg, dreg: STD_LOGIC;
begin
    process(clk) begin
        if rising_edge(clk) then
            areg <= a;
            breg <= b;
            creg <= c;
            dreg <= d;
            x <= n2;
            y <= not (dreg or n2);
        end if;
    end process;

    n1 <= areg and breg;
    n2 <= n1 or creg;
end;
```

Exercise 4.32

SystemVerilog

```
module fig3_69(input  logic clk, reset, a, b,
              output logic q);
    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (a) nextstate = S1;
                else nextstate = S0;
            S1: if (b) nextstate = S2;
                else nextstate = S0;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase

    // Output Logic
    assign q = state[1];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fig3_69 is
    port(clk, reset, a, b: in  STD_LOGIC;
         q: out STD_LOGIC);
end;

architecture synth of fig3_69 is
    type statetype is (S0, S1, S2);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if b then
                            nextstate <= S2;
                        else nextstate <= S0;
                        end if;
            when S2 => nextstate <= S0;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    q <= '1' when state = S2 else '0';
end;
```

Exercise 4.33

SystemVerilog

```
module fig3_70(input logic clk, reset, a, b,
              output logic q);
    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (a)      nextstate = S1;
                else      nextstate = S0;
            S1: if (b)      nextstate = S2;
                else      nextstate = S0;
            S2: if (a & b)  nextstate = S2;
                else      nextstate = S0;
            default:      nextstate = S0;
        endcase

    // Output Logic
    always_comb
        case (state)
            S0:      q = 0;
            S1:      q = 0;
            S2: if (a & b) q = 1;
                else  q = 0;
            default:  q = 0;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fig3_70 is
    port(clk, reset, a, b: in  STD_LOGIC;
         q: out STD_LOGIC);
end;

architecture synth of fig3_70 is
    type statetype is (S0, S1, S2);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                           nextstate <= S1;
                       else nextstate <= S0;
                       end if;
            when S1 => if b then
                           nextstate <= S2;
                       else nextstate <= S0;
                       end if;
            when S2 => if (a = '1' and b = '1') then
                           nextstate <= S2;
                       else nextstate <= S0;
                       end if;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    q <= '1' when ( (state = S2) and
                   (a = '1' and b = '1'))
        else '0';
end;
```

Exercise 4.34

SystemVerilog

```

module ex4_34(input  logic clk, reset, ta, tb,
              output logic [1:0] la, lb);
    typedef enum logic [2:0] {S0, S1, S2, S3, S4, S5}
        statetype;
    statetype [2:0] state, nextstate;

    parameter green = 2'b00;
    parameter yellow = 2'b01;
    parameter red = 2'b10;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (ta) nextstate = S0;
                else nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S3;
            S3: if (tb) nextstate = S3;
                else nextstate = S4;
            S4: nextstate = S5;
            S5: nextstate = S0;
        endcase

    // Output Logic
    always_comb
        case (state)
            S0: {la, lb} = {green, red};
            S1: {la, lb} = {yellow, red};
            S2: {la, lb} = {red, red};
            S3: {la, lb} = {red, green};
            S4: {la, lb} = {red, yellow};
            S5: {la, lb} = {red, red};
        endcase
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_34 is
    port(clk, reset, ta, tb: in  STD_LOGIC;
          la, lb: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of ex4_34 is
    type statetype is (S0, S1, S2, S3, S4, S5);
    signal state, nextstate: statetype;
    signal lalb: STD_LOGIC_VECTOR(3 downto 0);
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if ta = '1' then
                            nextstate <= S0;
                        else nextstate <= S1;
                        end if;
            when S1 => nextstate <= S2;
            when S2 => nextstate <= S3;
            when S3 => if tb = '1' then
                            nextstate <= S3;
                        else nextstate <= S4;
                        end if;
            when S4 => nextstate <= S5;
            when S5 => nextstate <= S0;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    la <= lalb(3 downto 2);
    lb <= lalb(1 downto 0);
    process(all) begin
        case state is
            when S0 => lalb <= "0010";
            when S1 => lalb <= "0110";
            when S2 => lalb <= "1010";
            when S3 => lalb <= "1000";
            when S4 => lalb <= "1001";
            when S5 => lalb <= "1010";
            when others => lalb <= "1010";
        end case;
    end process;
end;

```

Exercise 4.35

SystemVerilog

```

module daughterfsm(input  logic clk, reset, a,
                  output logic smile);
    typedef enum logic [1:0] {S0, S1, S2, S3, S4}
        statetype;
    statetype [2:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (a) nextstate = S1;
                else nextstate = S0;
            S1: if (a) nextstate = S2;
                else nextstate = S0;
            S2: if (a) nextstate = S4;
                else nextstate = S3;
            S3: if (a) nextstate = S1;
                else nextstate = S0;
            S4: if (a) nextstate = S4;
                else nextstate = S3;
            default: nextstate = S0;
        endcase

    // Output Logic
    assign smile = ((state == S3) & a) |
                  ((state == S4) & ~a);
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity daughterfsm is
    port(clk, reset, a: in  STD_LOGIC;
         smile:      out STD_LOGIC);
end;

architecture synth of daughterfsm is
    type statetype is (S0, S1, S2, S3, S4);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if a then
                            nextstate <= S2;
                        else nextstate <= S0;
                        end if;
            when S2 => if a then
                            nextstate <= S4;
                        else nextstate <= S3;
                        end if;
            when S3 => if a then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S4 => if a then
                            nextstate <= S4;
                        else nextstate <= S3;
                        end if;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    smile <= '1' when ( ((state = S3) and (a = '1')) or
                       ((state = S4) and (a = '0')) )
              else '0';
end;

```

Exercise 4.36

(starting on next page)

SystemVerilog

```
module ex4_36(input  logic clk, reset, n, d, q,
             output logic dispense,
                    return5, return10,
                    return2_10);
    typedef enum logic [3:0] {S0 = 4'b0000,
                             S5 = 4'b0001,
                             S10 = 4'b0010,
                             S25 = 4'b0011,
                             S30 = 4'b0100,
                             S15 = 4'b0101,
                             S20 = 4'b0110,
                             S35 = 4'b0111,
                             S40 = 4'b1000,
                             S45 = 4'b1001}
    statetype;
    statetype [3:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0:      if (n) nextstate = S5;
                     else if (d) nextstate = S10;
                     else if (q) nextstate = S25;
                     else      nextstate = S0;
            S5:      if (n) nextstate = S10;
                     else if (d) nextstate = S15;
                     else if (q) nextstate = S30;
                     else      nextstate = S5;
            S10:     if (n) nextstate = S15;
                     else if (d) nextstate = S20;
                     else if (q) nextstate = S35;
                     else      nextstate = S10;
            S25:     nextstate = S0;
            S30:     nextstate = S0;
            S15:     if (n) nextstate = S20;
                     else if (d) nextstate = S25;
                     else if (q) nextstate = S40;
                     else      nextstate = S15;
            S20:     if (n) nextstate = S25;
                     else if (d) nextstate = S30;
                     else if (q) nextstate = S45;
                     else      nextstate = S20;
            S35:     nextstate = S0;
            S40:     nextstate = S0;
            S45:     nextstate = S0;
            default: nextstate = S0;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_36 is
    port(clk, reset, n, d, q: in  STD_LOGIC;
          dispense, return5, return10: out STD_LOGIC;
          return2_10: out STD_LOGIC);
end entity;

architecture synth of ex4_36 is
    type statetype is (S0, S5, S10, S25, S30, S15, S20,
                      S35, S40, S45);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 =>
                if n then nextstate <= S5;
                elsif d then nextstate <= S10;
                elsif q then nextstate <= S25;
                else      nextstate <= S0;
            end if;
            when S5 =>
                if n then nextstate <= S10;
                elsif d then nextstate <= S15;
                elsif q then nextstate <= S30;
                else      nextstate <= S5;
            end if;
            when S10 =>
                if n then nextstate <= S15;
                elsif d then nextstate <= S20;
                elsif q then nextstate <= S35;
                else      nextstate <= S10;
            end if;
            when S25 => nextstate <= S0;
            when S30 => nextstate <= S0;
            when S15 =>
                if n then nextstate <= S20;
                elsif d then nextstate <= S25;
                elsif q then nextstate <= S40;
                else      nextstate <= S15;
            end if;
            when S20 =>
                if n then nextstate <= S25;
                elsif d then nextstate <= S30;
                elsif q then nextstate <= S45;
                else      nextstate <= S20;
            end if;
            when S35 => nextstate <= S0;
            when S40 => nextstate <= S0;
            when S45 => nextstate <= S0;
            when others => nextstate <= S0;
        end case;
    end process;
end architecture;
```


(continued from previous page)

SystemVerilog

```
// Output Logic
assign dispense = (state == S25) |
                  (state == S30) |
                  (state == S35) |
                  (state == S40) |
                  (state == S45);
assign return5  = (state == S30) |
                  (state == S40);
assign return10 = (state == S35) |
                  (state == S40);
assign return2_10 = (state == S45);
endmodule
```

VHDL

```
-- output logic
dispense <= '1' when ((state = S25) or
                     (state = S30) or
                     (state = S35) or
                     (state = S40) or
                     (state = S45))
              else '0';
return5  <= '1' when ((state = S30) or
                     (state = S40))
              else '0';
return10 <= '1' when ((state = S35) or
                     (state = S40))
              else '0';
return2_10 <= '1' when (state = S45)
              else '0';
end;
```

Exercise 4.37

SystemVerilog

```
module ex4_37(input logic clk, reset,
              output logic [2:0] q);
    typedef enum logic [2:0] {S0 = 3'b000,
                             S1 = 3'b001,
                             S2 = 3'b011,
                             S3 = 3'b010,
                             S4 = 3'b110,
                             S5 = 3'b111,
                             S6 = 3'b101,
                             S7 = 3'b100}
        statetype;

    statetype [2:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S3;
            S3: nextstate = S4;
            S4: nextstate = S5;
            S5: nextstate = S6;
            S6: nextstate = S7;
            S7: nextstate = S0;
        endcase

    // Output Logic
    assign q = state;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_37 is
    port(clk: in STD_LOGIC;
         reset: in STD_LOGIC;
         q: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture synth of ex4_37 is
    signal state: STD_LOGIC_VECTOR(2 downto 0);
    signal nextstate: STD_LOGIC_VECTOR(2 downto 0);
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= "000";
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when "000" => nextstate <= "001";
            when "001" => nextstate <= "011";
            when "011" => nextstate <= "010";
            when "010" => nextstate <= "110";
            when "110" => nextstate <= "111";
            when "111" => nextstate <= "101";
            when "101" => nextstate <= "100";
            when "100" => nextstate <= "000";
            when others => nextstate <= "000";
        end case;
    end process;

    -- output logic
    q <= state;
end;
```

Exercise 4.38

SystemVerilog

```
module ex4_38(input logic clk, reset, up,
              output logic [2:0] q);

  typedef enum logic [2:0] {
    S0 = 3'b000,
    S1 = 3'b001,
    S2 = 3'b011,
    S3 = 3'b010,
    S4 = 3'b110,
    S5 = 3'b111,
    S6 = 3'b101,
    S7 = 3'b100} statetype;
  statetype [2:0] state, nextstate;

  // State Register
  always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;

  // Next State Logic
  always_comb
    case (state)
      S0: if (up) nextstate = S1;
          else nextstate = S7;
      S1: if (up) nextstate = S2;
          else nextstate = S0;
      S2: if (up) nextstate = S3;
          else nextstate = S1;
      S3: if (up) nextstate = S4;
          else nextstate = S2;
      S4: if (up) nextstate = S5;
          else nextstate = S3;
      S5: if (up) nextstate = S6;
          else nextstate = S4;
      S6: if (up) nextstate = S7;
          else nextstate = S5;
      S7: if (up) nextstate = S0;
          else nextstate = S6;
    endcase

  // Output Logic
  assign q = state;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_38 is
  port(clk: in STD_LOGIC;
        reset: in STD_LOGIC;
        up: in STD_LOGIC;
        q: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture synth of ex4_38 is
  signal state: STD_LOGIC_VECTOR(2 downto 0);
  signal nextstate: STD_LOGIC_VECTOR(2 downto 0);
begin
  -- state register
  process(clk, reset) begin
    if reset then state <= "000";
    elsif rising_edge(clk) then
      state <= nextstate;
    end if;
  end process;

  -- next state logic
  process(all) begin
    case state is
      when "000" => if up then
                      nextstate <= "001";
                    else
                      nextstate <= "100";
                    end if;
      when "001" => if up then
                      nextstate <= "011";
                    else
                      nextstate <= "000";
                    end if;
      when "011" => if up then
                      nextstate <= "010";
                    else
                      nextstate <= "001";
                    end if;
      when "010" => if up then
                      nextstate <= "110";
                    else
                      nextstate <= "011";
                    end if;
    end case;
  end process;
end;
```

(continued on next page)

(continued from previous page)

VHDL

```
when "110" => if up then
    nextstate <= "111";
else
    nextstate <= "010";
end if;
when "111" => if up then
    nextstate <= "101";
else
    nextstate <= "110";
end if;
when "101" => if up then
    nextstate <= "100";
else
    nextstate <= "111";
end if;
when "100" => if up then
    nextstate <= "000";
else
    nextstate <= "101";
end if;
when others => nextstate <= "000";
end case;
end process;

-- output logic
q <= state;
end;
```

Exercise 4.39

Option 1

SystemVerilog

```

module ex4_39(input  logic clk, reset, a, b,
              output logic z);
    typedef enum logic [1:0] {S0, S1, S2, S3}
        statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: case ({b,a})
                    2'b00: nextstate = S0;
                    2'b01: nextstate = S3;
                    2'b10: nextstate = S0;
                    2'b11: nextstate = S1;
                endcase
            S1: case ({b,a})
                    2'b00: nextstate = S0;
                    2'b01: nextstate = S3;
                    2'b10: nextstate = S2;
                    2'b11: nextstate = S1;
                endcase
            S2: case ({b,a})
                    2'b00: nextstate = S0;
                    2'b01: nextstate = S3;
                    2'b10: nextstate = S2;
                    2'b11: nextstate = S1;
                endcase
            S3: case ({b,a})
                    2'b00: nextstate = S0;
                    2'b01: nextstate = S3;
                    2'b10: nextstate = S2;
                    2'b11: nextstate = S1;
                endcase
            default: nextstate = S0;
        endcase

    // Output Logic
    always_comb
        case (state)
            S0: z = a & b;
            S1: z = a | b;
            S2: z = a & b;
            S3: z = a | b;
            default: z = 1'b0;
        endcase
    endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_39 is
    port(clk:   in   STD_LOGIC;
          reset: in   STD_LOGIC;
          a, b:  in   STD_LOGIC;
          z:     out  STD_LOGIC);
end;

architecture synth of ex4_39 is
    type statetype is (S0, S1, S2, S3);
    signal state, nextstate: statetype;
    signal ba: STD_LOGIC_VECTOR(1 downto 0);
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    ba <= b & a;
    process(all) begin
        case state is
            when S0 =>
                case (ba) is
                    when "00" => nextstate <= S0;
                    when "01" => nextstate <= S3;
                    when "10" => nextstate <= S0;
                    when "11" => nextstate <= S1;
                    when others => nextstate <= S0;
                end case;
            when S1 =>
                case (ba) is
                    when "00" => nextstate <= S0;
                    when "01" => nextstate <= S3;
                    when "10" => nextstate <= S2;
                    when "11" => nextstate <= S1;
                    when others => nextstate <= S0;
                end case;
            when S2 =>
                case (ba) is
                    when "00" => nextstate <= S0;
                    when "01" => nextstate <= S3;
                    when "10" => nextstate <= S2;
                    when "11" => nextstate <= S1;
                    when others => nextstate <= S0;
                end case;
            when S3 =>
                case (ba) is
                    when "00" => nextstate <= S0;
                    when "01" => nextstate <= S3;
                    when "10" => nextstate <= S2;
                    when "11" => nextstate <= S1;
                    when others => nextstate <= S0;
                end case;
            when others =>
                nextstate <= S0;
        end case;
    end process;
end process;

```

(continued from previous page)

VHDL

```
-- output logic
process(all) begin
  case state is
    when S0    => if (a = '1' and b = '1')
                  then z <= '1';
                  else z <= '0';
                  end if;
    when S1    => if (a = '1' or b = '1')
                  then z <= '1';
                  else z <= '0';
                  end if;
    when S2    => if (a = '1' and b = '1')
                  then z <= '1';
                  else z <= '0';
                  end if;
    when S3    => if (a = '1' or b = '1')
                  then z <= '1';
                  else z <= '0';
                  end if;
    when others => z <= '0';
  end case;
end process;
end;
```

Option 2

SystemVerilog

```
module ex4_37(input  logic clk, a, b,
              output logic z);

  logic aprev;

  // State Register
  always_ff @(posedge clk)
    aprev <= a;

  assign z = b ? (aprev | a) : (aprev & a);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_37 is
  port(clk:   in  STD_LOGIC;
        a, b: in  STD_LOGIC;
        z:    out STD_LOGIC);
end;

architecture synth of ex4_37 is
  signal aprev, nland, n2or: STD_LOGIC;
begin
  -- state register
  process(clk) begin
    if rising_edge(clk) then
      aprev <= a;
    end if;
  end process;

  z <= (a or aprev) when b = '1' else
      (a and aprev);
end;
```

Exercise 4.40

SystemVerilog

```
module fsm_y(input  clk, reset, a,
             output y);
    typedef enum logic [1:0] {S0=2'b00, S1=2'b01,
                             S11=2'b11} statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0:  if (a) nextstate = S1;
                  else nextstate = S0;
            S1:  if (a) nextstate = S11;
                  else nextstate = S0;
            S11: nextstate = S11;
            default: nextstate = S0;
        endcase

    // Output Logic
    assign y = state[1];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fsm_y is
    port(clk, reset, a: in  STD_LOGIC;
         y: out STD_LOGIC);
end;

architecture synth of fsm_y is
    type statetype is (S0, S1, S11);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                           nextstate <= S1;
                       else nextstate <= S0;
                       end if;
            when S1 => if a then
                           nextstate <= S11;
                       else nextstate <= S0;
                       end if;
            when S11 => nextstate <= S11;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    y <= '1' when (state = S11) else '0';
end;
```

(continued on next page)

(continued from previous page)

SystemVerilog

```
module fsm_x(input logic clk, reset, a,
            output logic x);
    typedef enum logic [1:0] {S0, S1, S2, S3}
        statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (a) nextstate = S1;
                else nextstate = S0;
            S1: if (a) nextstate = S2;
                else nextstate = S1;
            S2: if (a) nextstate = S3;
                else nextstate = S2;
            S3: nextstate = S3;
        endcase

    // Output Logic
    assign x = (state == S3);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fsm_x is
    port(clk, reset, a: in STD_LOGIC;
         x: out STD_LOGIC);
end;

architecture synth of fsm_x is
    type statetype is (S0, S1, S2, S3);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if a then
                            nextstate <= S2;
                        else nextstate <= S1;
                        end if;
            when S2 => if a then
                            nextstate <= S3;
                        else nextstate <= S2;
                        end if;
            when S3 => nextstate <= S3;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    x <= '1' when (state = S3) else '0';
end;
```

Exercise 4.41

SystemVerilog

```
module ex4_41(input  logic clk, start, a,
             output logic q);
    typedef enum logic [1:0] {S0, S1, S2, S3}
        statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge start)
        if (start) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (a) nextstate = S1;
                else      nextstate = S0;
            S1: if (a) nextstate = S2;
                else      nextstate = S3;
            S2: if (a) nextstate = S2;
                else      nextstate = S3;
            S3: if (a) nextstate = S2;
                else      nextstate = S3;
        endcase

    // Output Logic
    assign q = state[0];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_41 is
    port(clk, start, a: in  STD_LOGIC;
         q:      out STD_LOGIC);
end;

architecture synth of ex4_41 is
    type statetype is (S0, S1, S2, S3);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, start) begin
        if start then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if a then
                            nextstate <= S2;
                        else nextstate <= S3;
                        end if;
            when S2 => if a then
                            nextstate <= S2;
                        else nextstate <= S3;
                        end if;
            when S3 => if a then
                            nextstate <= S2;
                        else nextstate <= S3;
                        end if;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    q <= '1' when ((state = S1) or (state = S3))
        else '0';
end;
```

Exercise 4.42

SystemVerilog

```
module ex4_42(input  logic clk, reset, x,
              output logic q);
    typedef enum logic [1:0] {S0, S1, S2, S3}
        statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S00;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S00: if (x) nextstate = S11;
                 else  nextstate = S01;
            S01: if (x) nextstate = S10;
                 else  nextstate = S00;
            S10:      nextstate = S01;
            S11:      nextstate = S01;
        endcase

    // Output Logic
    assign q = state[0] | state[1];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_42 is
    port(clk, reset, x: in  STD_LOGIC;
          q:      out STD_LOGIC);
end;

architecture synth of ex4_42 is
    type statetype is (S00, S01, S10, S11);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S00;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S00 => if x then
                            nextstate <= S11;
                        else nextstate <= S01;
                        end if;
            when S01 => if x then
                            nextstate <= S10;
                        else nextstate <= S00;
                        end if;
            when S10 =>      nextstate <= S01;
            when S11 =>      nextstate <= S01;
            when others =>   nextstate <= S00;
        end case;
    end process;

    -- output logic
    q <= '0' when (state = S00) else '1';
end;
```

Exercise 4.43

SystemVerilog

```
module ex4_43(input  clk, reset, a,
              output q);
    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype [1:0] state, nextstate;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0: if (a) nextstate = S1;
                else nextstate = S0;
            S1: if (a) nextstate = S2;
                else nextstate = S0;
            S2: if (a) nextstate = S2;
                else nextstate = S0;
            default: nextstate = S0;
        endcase

    // Output Logic
    assign q = state[1];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_43 is
    port(clk, reset, a: in  STD_LOGIC;
          q:          out STD_LOGIC);
end;

architecture synth of ex4_43 is
    type statetype is (S0, S1, S2);
    signal state, nextstate: statetype;
begin
    -- state register
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when S0 => if a then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if a then
                            nextstate <= S2;
                        else nextstate <= S0;
                        end if;
            when S2 => if a then
                            nextstate <= S2;
                        else nextstate <= S0;
                        end if;
            when others => nextstate <= S0;
        end case;
    end process;

    -- output logic
    q <= '1' when (state = S2) else '0';
end;
```

Exercise 4.44

(a)

SystemVerilog

```
module ex4_44a(input logic clk, a, b, c, d,
              output logic q);

    logic areg, breg, creg, dreg;

    always_ff @(posedge clk)
    begin
        areg <= a;
        breg <= b;
        creg <= c;
        dreg <= d;
        q    <= ((areg ^ breg) ^ creg) ^ dreg;
    end
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_44a is
    port(clk, a, b, c, d: in  STD_LOGIC;
          q:                   out STD_LOGIC);
end;

architecture synth of ex4_44a is
    signal areg, breg, creg, dreg: STD_LOGIC;
begin
    process(clk) begin
        if rising_edge(clk) then
            areg <= a;
            breg <= b;
            creg <= c;
            dreg <= d;
            q <= ((areg xor breg) xor creg) xor dreg;
        end if;
    end process;
end;
```

(d)

SystemVerilog

```
module ex4_44d(input logic clk, a, b, c, d,
              output logic q);

    logic areg, breg, creg, dreg;

    always_ff @(posedge clk)
    begin
        areg <= a;
        breg <= b;
        creg <= c;
        dreg <= d;
        q    <= (areg ^ breg) ^ (creg ^ dreg);
    end
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_44d is
    port(clk, a, b, c, d: in  STD_LOGIC;
          q:                   out STD_LOGIC);
end;

architecture synth of ex4_44d is
    signal areg, breg, creg, dreg: STD_LOGIC;
begin
    process(clk) begin
        if rising_edge(clk) then
            areg <= a;
            breg <= b;
            creg <= c;
            dreg <= d;
            q <= (areg xor breg) xor (creg xor dreg);
        end if;
    end process;
end;
```

SystemVerilog

```
module ex4_45(input logic clk, c,
             input logic [1:0] a, b,
             output logic [1:0] s);

    logic [1:0] areg, breg;
    logic creg;
    logic [1:0] sum;
    logic cout;

    always_ff @(posedge clk)
        {areg, breg, creg, s} <= {a, b, c, sum};

    fulladder fulladd1(areg[0], breg[0], creg,
                     sum[0], cout);
    fulladder fulladd2(areg[1], breg[1], cout,
                     sum[1], );
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex4_45 is
    port(clk, c: in STD_LOGIC;
         a, b: in STD_LOGIC_VECTOR(1 downto 0);
         s: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of ex4_45 is
    component fulladder is
        port(a, b, cin: in STD_LOGIC;
             s, cout: out STD_LOGIC);
    end component;
    signal creg: STD_LOGIC;
    signal areg, breg, cout: STD_LOGIC_VECTOR(1 downto 0);
    signal sum: STD_LOGIC_VECTOR(1 downto 0);
begin
    process(clk) begin
        if rising_edge(clk) then
            areg <= a;
            breg <= b;
            creg <= c;
            s <= sum;
        end if;
    end process;

    fulladd1: fulladder
        port map(areg(0), breg(0), creg, sum(0), cout(0));
    fulladd2: fulladder
        port map(areg(1), breg(1), cout(0), sum(1),
        cout(1));
end;
```

Exercise 4.46

A signal declared as `tri` can have multiple drivers.

Exercise 4.47

SystemVerilog

```
module syncbad(input  logic clk,
               input  logic d,
               output logic q);

    logic n1;

    always_ff @(posedge clk)
        begin
            q  <= n1; // nonblocking
            n1 <= d;  // nonblocking
        end
endmodule
```

VHDL


```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity syncbad is
    port(clk: in  STD_LOGIC;
          d:   in  STD_LOGIC;
          q:   out STD_LOGIC);
end;

architecture bad of syncbad is
begin
    process(clk)
        variable n1: STD_LOGIC;
    begin
        if rising_edge(clk) then
            q <= n1; -- nonblocking
            n1 <= d; -- nonblocking
        end if;
    end process;
end;
```


Exercise 4.48

They have the same function.

 

Exercise 4.49

They do not have the same function.

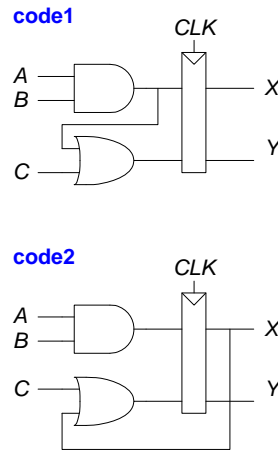

Exercise 4.50

(a) Problem: Signal `d` is not included in the sensitivity list of the `always` statement. Correction shown below (changes are in bold).

```
module latch(input  logic    clk,
             input  logic [3:0] d,
             output logic [3:0] q);

    always_latch
        if (clk) q <= d;
endmodule
```

(b) Problem: Signal `b` is not included in the sensitivity list of the `always` statement. Correction shown below (changes are in bold).

```
module gates(input  logic [3:0] a, b,
             output logic [3:0] y1, y2, y3, y4, y5);

    always_comb
    begin
        y1 = a & b;
        y2 = a | b;
        y3 = a ^ b;
        y4 = ~(a & b);
        y5 = ~(a | b);
    end
endmodule
```

(c) Problem: The sensitivity list should not include the word “posedge”. The `always` statement needs to respond to any changes in `s`, not just the positive edge. Signals `d0` and `d1` need to be added to the sensitivity list. Also, the `always` statement implies combinational logic, so blocking assignments should be used.

```
module mux2(input logic [3:0] d0, d1,
            input logic s,
            output logic [3:0] y);

    always_comb
        if (s) y = d1;
        else y = d0;
endmodule
```

(d) Problem: This module will actually work in this case, but it's good practice to use nonblocking assignments in `always` statements that describe sequential logic. Because the `always` block has more than one statement in it, it requires a `begin` and `end`.

```
module twoflops(input logic clk,
                input logic d0, d1,
                output logic q0, q1);

    always_ff @(posedge clk)
    begin
        q1 <= d1;           // nonblocking assignment
        q0 <= d0;           // nonblocking assignment
    end
endmodule
```

(e) Problem: `out1` and `out2` are not assigned for all cases. Also, it would be best to separate the next state logic from the state register. `reset` is also missing in the input declaration.

```
module FSM(input logic clk,
            input logic reset,
            input logic a,
            output logic out1, out2);

    logic state, nextstate;

    // state register
    always_ff @(posedge clk, posedge reset)
        if (reset)
            state <= 1'b0;
        else
            state <= nextstate;

    // next state logic
    always_comb
        case (state)
            1'b0: if (a) nextstate = 1'b1;
                  else nextstate = 1'b0;
            1'b1: if (~a) nextstate = 1'b0;
                  else nextstate = 1'b1;
        endcase

    // output logic (combinational)
    always_comb
        if (state == 0) {out1, out2} = {1'b1, 1'b0};
        else
            {out1, out2} = {1'b0, 1'b1};
endmodule
```

(f) Problem: A priority encoder is made from combinational logic, so the HDL must completely define what the outputs are for all possible input combinations. So, we must add an `else` statement at the end of the `always` block.

```
module priority(input logic [3:0] a,
```



```

        output logic [3:0] y);

always_comb
    if      (a[3]) y = 4'b1000;
    else if (a[2]) y = 4'b0100;
    else if (a[1]) y = 4'b0010;
    else if (a[0]) y = 4'b0001;
    else       y = 4'b0000;
endmodule

```

(g) Problem: the next state logic block has no default statement. Also, state S2 is missing the S.

```

module divideby3FSM(input  logic clk,
                   input  logic reset,
                   output logic out);

    logic [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;

    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else       state <= nextstate;

    // Next State Logic
    always_comb
        case (state)
            S0:    nextstate = S1;
            S1:    nextstate = S2;
            S2:    nextstate = S0;
            default: nextstate = S0;
        endcase

    // Output Logic
    assign out = (state == S2);
endmodule

```

(h) Problem: the ~ is missing on the first tristate.

```

module mux2tri(input  logic [3:0] d0, d1,
              input  logic s,
              output logic [3:0] y);

    tristate t0(d0, ~s, y);
    tristate t1(d1, s, y);

endmodule

```

(i) Problem: an output, in this case, q , cannot be assigned in multiple always or assignment statements. Also, the flip-flop does not include an enable, so it should not be named `floprsen`.

```

module floprs(input  logic clk,
              input  logic reset,
              input  logic set,
              input  logic [3:0] d,
              output logic [3:0] q);

    always_ff @(posedge clk, posedge reset, posedge set)

```

```
        if (reset)    q <= 0;
        else if (set) q <= 1;
        else         q <= d;
    endmodule
```

(j) **Problem:** this is a combinational module, so nonconcurrent (blocking) assignment statements (=) should be used in the always statement, not concurrent assignment statements (<=). Also, it's safer to use always @(*) for combinational logic to make sure all the inputs are covered.

```
module and3(input  logic a, b, c,
            output logic y);

    logic tmp;

    always_comb
    begin
        tmp = a & b;
        y   = tmp & c;
    end
endmodule
```

Exercise 4.51

It is necessary to write

```
q <= '1' when state = S0 else '0';
```

rather than simply

```
q <= (state = S0);
```

because the result of the comparison (state = S0) is of type Boolean (true and false) and q must be assigned a value of type STD_LOGIC ('1' and '0').

Exercise 4.52

(a) **Problem:** both clk and d must be in the process statement.

```
architecture synth of latch is
begin
    process(clk, d) begin
        if clk = '1' then q <= d;
        end if;
    end process;
end;
```

(b) **Problem:** both a and b must be in the process statement.

```
architecture proc of gates is
begin
    process(all) begin
        y1 <= a and b;
        y2 <= a or b;
        y3 <= a xor b;
    end process;
end;
```

```

    y4 <= a nand b;
    y5 <= a nor b;
end process;
end;
```

(c) **Problem:** The end if and end process statements are missing.

```

architecture synth of flop is
begin
    process(clk)
        if clk'event and clk = '1' then
            q <= d;
        end if;
    end process;
end;
```

(d) **Problem:** The final else statement is missing. Also, it's better to use "process(all)" instead of "process(a)"

```

architecture synth of priority is
begin
    process(all) begin
        if a(3) = '1' then y <= "1000";
        elsif a(2) = '1' then y <= "0100";
        elsif a(1) = '1' then y <= "0010";
        elsif a(0) = '1' then y <= "0001";
        else y <= "0000";
        end if;
    end process;
end;
```

(e) **Problem:** The default statement is missing in the nextstate case statement. Also, it's better to use the updated statements: "if reset", "rising_edge(clk)", and "process(all)".

```

architecture synth of divideby3FSM is
    type statetype is (S0, S1, S2);
    signal state, nextstate: statetype;
begin
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    process(all) begin
        case state is
            when S0 => nextstate <= S1;
            when S1 => nextstate <= S2;
            when S2 => nextstate <= S0;
            when others => nextstate <= S0;
        end case;
    end process;

    q <= '1' when state = S0 else '0';
end;
```

(f) **Problem:** The select signal on tristate instance t0 must be inverted. However, VHDL does not allow logic to be performed within an instance declaration. Thus, an internal signal, sbar, must be declared.

```

architecture struct of mux2 is
    component tristate
```

```
        port(a: in  STD_LOGIC_VECTOR(3 downto 0);
              en: in  STD_LOGIC;
              y: out STD_LOGIC_VECTOR(3 downto 0));
    end component;
    signal sbar: STD_LOGIC;
begin
    sbar <= not s;
    t0: tristate port map(d0, sbar, y);
    t1: tristate port map(d1, s, y);
end;
```

(g) **Problem:** The q output cannot be assigned in two process or assignment statements. Also, it's better to use the updated statements: "if reset", and "rising_edge(clk)".

```
architecture asynchronous of flopr is
begin
    process(clk, reset, set) begin
        if reset then
            q <= '0';
        elsif set then
            q <= '1';
        elsif rising_edge(clk) then
            q <= d;
        end if;
    end process;
end;
```

Question 4.1

SystemVerilog

```
assign result = sel ? data : 32'b0;
```

VHDL

```
result <= data when sel = '1' else X"00000000";
```

Question 4.2

HDLs support *blocking* and *nonblocking assignments* in an always / process statement. A group of blocking assignments are evaluated in the order they appear in the code, just as one would expect in a standard programming

language. A group of nonblocking assignments are evaluated concurrently; all of the statements are evaluated before any of the left hand sides are updated.

SystemVerilog

In a SystemVerilog `always` statement, `=` indicates a blocking assignment and `<=` indicates a nonblocking assignment.

Do not confuse either type with continuous assignment using the `assign` statement. `assign` statements are normally used outside `always` statements and are also evaluated concurrently.

VHDL

In a VHDL `process` statement, `:=` indicates a blocking assignment and `<=` indicates a nonblocking assignment (also called a concurrent assignment). This is the first section where `:=` is introduced.

Nonblocking assignments are made to outputs and to signals. Blocking assignments are made to variables, which are declared in `process` statements (see the next example).

`<=` can also appear outside `process` statements, where it is also evaluated concurrently.

See HDL Examples 4.24 and 4.29 for comparisons of blocking and nonblocking assignments. Blocking and nonblocking assignment guidelines are given on page 206.

Question 4.3

The SystemVerilog statement performs the bit-wise AND of the 16 least significant bits of data with 0xC820. It then ORs these 16 bits to produce the 1-bit result.

CHAPTER 5

Note: the HDL files given in the following solutions are available on the textbook's companion website at:

<http://textbooks.elsevier.com/9780123704979> .

Exercise 5.1

(a) From Equation 5.1, we find the 64-bit ripple-carry adder delay to be:

$$t_{\text{ripple}} = Nt_{\text{FA}} = 64(450 \text{ ps}) = 28.8 \text{ ns}$$

(b) From Equation 5.6, we find the 64-bit carry-lookahead adder delay to be:

$$t_{\text{CLA}} = t_{\text{pg}} + t_{\text{pg_block}} + \left(\frac{N}{k} - 1\right)t_{\text{AND_OR}} + kt_{\text{FA}}$$

$$t_{\text{CLA}} = \left[150 + (6 \times 150) + \left(\frac{64}{4} - 1\right)300 + (4 \times 450)\right] = 7.35 \text{ ns}$$

(Note: the actual delay is only 7.2 ns because the first AND_OR gate only has a 150 ps delay.)

(c) From Equation 5.11, we find the 64-bit prefix adder delay to be:

$$t_{\text{PA}} = t_{\text{pg}} + \log_2 N(t_{\text{pg_prefix}}) + t_{\text{XOR}}$$

$$t_{\text{PA}} = [150 + 6(300) + 150] = 2.1 \text{ ns}$$

Exercise 5.2

(a) The fundamental building block of both the ripple-carry and carry-lookahead adders is the full adder. We use the full adder from Figure 4.8, shown again here for convenience:

 


FIGURE 5.1 Full adder implementation

The full adder delay is three two-input gates.

$$t_{FA} = 3(50) \text{ ps} = 150 \text{ ps}$$

The full adder area is five two-input gates.

$$A_{FA} = 5(15 \mu m^2) = 75 \mu m^2$$

The full adder capacitance is five two-input gates.

$$C_{FA} = 5(20 \text{ fF}) = 100 \text{ fF}$$

Thus, the ripple-carry adder delay, area, and capacitance are:

$$t_{\text{ripple}} = N t_{FA} = 64(150 \text{ ps}) = 9.6 \text{ ns}$$

$$A_{\text{ripple}} = N A_{FA} = 64(75 \mu m^2) = 4800 \mu m^2$$

$$C_{\text{ripple}} = N C_{FA} = 64(100 \text{ fF}) = 6.4 \text{ pF}$$

Using the carry-lookahead adder from Figure 5.6, we can calculate delay, area, and capacitance. Using Equation 5.6:

$$t_{CLA} = [50 + 6(50) + 15(100) + 4(150)] \text{ ps} = 2.45 \text{ ns}$$

(The actual delay is only 2.4 ns because the first AND_OR gate only contributes one gate delay.)

For each 4-bit block of the 64-bit carry-lookahead adder, there are 4 full adders, 8 two-input gates to generate P_i and G_i , and 11 two-input gates to generate $P_{i:j}$ and $G_{i:j}$. Thus, the area and capacitance are:

$$A_{CLAblock} = [4(75) + 19(15)] \mu m^2 = 585 \mu m^2$$

$$A_{CLA} = 16(585) \mu m^2 = 9360 \mu m^2$$

$$C_{CLAblock} = [4(100) + 19(20)] \text{ fF} = 780 \text{ fF}$$

$$C_{CLA} = 16(780) \text{ fF} = 12.48 \text{ pF}$$

Now solving for power using Equation 1.4,

$$P_{\text{dynamic_ripple}} = \frac{1}{2} CV_{DD}^2 f = \frac{1}{2} (6.4 \text{ pF}) (1.2 \text{ V})^2 (100 \text{ MHz}) = 0.461 \text{ mW}$$

$$P_{\text{dynamic_CLA}} = \frac{1}{2} CV_{DD}^2 f = \frac{1}{2} (12.48 \text{ pF}) (1.2 \text{ V})^2 (100 \text{ MHz}) = 0.899 \text{ mW}$$

| | ripple- carry | carry-lookahead | cla/ripple |
|--------------------|------------------|-----------------|------------|
| Area (μm^2) | 4800 | 9360 | 1.95 |
| Delay (ns) | 9.6 | 2.45 | 0.26 |
| Power (mW) | 0.461 | 0.899 | 1.95 |

TABLE 5.1 CLA and ripple-carry adder comparison

(b) Compared to the ripple-carry adder, the carry-lookahead adder is almost twice as large and uses almost twice the power, but is almost four times as fast. Thus for performance-limited designs where area and power are not constraints, the carry-lookahead adder is the clear choice. On the other hand, if either area or power are the limiting constraints, one would choose a ripple-carry adder if performance were not a constraint.

Exercise 5.3

A designer might choose to use a ripple-carry adder instead of a carry-lookahead adder if chip area is the critical resource and delay is not the critical constraint.

Exercise 5.4

SystemVerilog

```

module prefixaddl6(input  logic [15:0] a, b,
                  input  logic      cin,
                  output logic [15:0] s,
                  output logic      cout);

    logic [14:0] p, g;
    logic [7:0]  pij_0, gij_0, pij_1, gij_1,
                pij_2, gij_2, pij_3, gij_3;
    logic [15:0] gen;

    pgblock pgblock_top(a[14:0], b[14:0], p, g);
    pgblackblock pgblackblock_0({p[14], p[12], p[10],
                                p[8], p[6], p[4], p[2], p[0]},
                                {g[14], g[12], g[10], g[8], g[6], g[4], g[2], g[0]},
                                {p[13], p[11], p[9], p[7], p[5], p[3], p[1], 1'b0},
                                {g[13], g[11], g[9], g[7], g[5], g[3], g[1], cin},
                                pij_0, gij_0);

    pgblackblock pgblackblock_1({pij_0[7], p[13],
                                pij_0[5], p[9], pij_0[3], p[5], pij_0[1], p[1]},
                                {gij_0[7], g[13], gij_0[5], g[9], gij_0[3],
                                 g[5], gij_0[1], g[1]},
                                { {2{pij_0[6]}}, {2{pij_0[4]}}, {2{pij_0[2]}},
                                  {2{pij_0[0]}} },
                                { {2{gij_0[6]}}, {2{gij_0[4]}}, {2{gij_0[2]}},
                                  {2{gij_0[0]}} },
                                pij_1, gij_1);

    pgblackblock pgblackblock_2({pij_1[7], pij_1[6],
                                pij_0[6], p[11], pij_1[3], pij_1[2], pij_0[2], p[3]},
                                {gij_1[7], gij_1[6], gij_0[6], g[11], gij_1[3],
                                 gij_1[2], gij_0[2], g[3]},
                                { {4{pij_1[5]}}, {4{pij_1[1]}} },
                                { {4{gij_1[5]}}, {4{gij_1[1]}} },
                                pij_2, gij_2);

    pgblackblock pgblackblock_3({pij_2[7], pij_2[6],
                                pij_2[5], pij_2[4], pij_1[5], pij_1[4],
                                pij_0[4], p[7]},
                                {gij_2[7], gij_2[6], gij_2[5],
                                 gij_2[4], gij_1[5], gij_1[4], gij_0[4], g[7]},
                                { 8{pij_2[3]} }, { 8{gij_2[3]} },
                                pij_3, gij_3);

    sumblock sum_out(a, b, gen, s);

    assign gen = {gij_3, gij_2[3:0],
                  gij_1[1:0], gij_0[0], cin};
    assign cout = (a[15] & b[15]) |
                  (gen[15] & (a[15] | b[15]));

endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity prefixaddl6 is
    port(a, b: in  STD_LOGIC_VECTOR(15 downto 0);
          cin: in  STD_LOGIC;
          s:  out STD_LOGIC_VECTOR(15 downto 0);
          cout: out STD_LOGIC);
end;

architecture synth of prefixaddl6 is
    component pgblock
        port(a, b: in  STD_LOGIC_VECTOR(14 downto 0);
              p, g: out STD_LOGIC_VECTOR(14 downto 0));
    end component;

    component pgblackblock is
        port (pik, gik: in  STD_LOGIC_VECTOR(7 downto 0);
              pkj, gkj: in  STD_LOGIC_VECTOR(7 downto 0);
              pij: out STD_LOGIC_VECTOR(7 downto 0);
              gij: out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    component sumblock is
        port (a, b, g: in  STD_LOGIC_VECTOR(15 downto 0);
              s:  out STD_LOGIC_VECTOR(15 downto 0));
    end component;

    signal p, g: STD_LOGIC_VECTOR(14 downto 0);
    signal pij_0, gij_0, pij_1, gij_1,
            pij_2, gij_2, gij_3:
        STD_LOGIC_VECTOR(7 downto 0);
    signal gen: STD_LOGIC_VECTOR(15 downto 0);
    signal pik_0, pik_1, pik_2, pik_3,
            gik_0, gik_1, gik_2, gik_3,
            pkj_0, pkj_1, pkj_2, pkj_3,
            gkj_0, gkj_1, gkj_2, gkj_3, dummy:
        STD_LOGIC_VECTOR(7 downto 0);

begin
    pgblock_top: pgblock
        port map(a(14 downto 0), b(14 downto 0), p, g);

    pik_0 <=
        (p(14)&p(12)&p(10)&p(8)&p(6)&p(4)&p(2)&p(0));
    gik_0 <=
        (g(14)&g(12)&g(10)&g(8)&g(6)&g(4)&g(2)&g(0));
    pkj_0 <=
        (p(13)&p(11)&p(9)&p(7)&p(5)&p(3)&p(1)&'0');
    gkj_0 <=
        (g(13)&g(11)&g(9)&g(7)&g(5)&g(3)&g(1)&cin);

    pgblackblock_0: pgblackblock
        port map(pik_0, gik_0, pkj_0, gkj_0,
                pij_0, gij_0);

```

(continued from previous page)

Verilog

VHDL

```

pik_1 <= (pij_0(7)&p(13)&pij_0(5)&p(9)&
          pij_0(3)&p(5)&pij_0(1)&p(1));
gik_1 <= (gij_0(7)&g(13)&gij_0(5)&g(9)&
          gij_0(3)&g(5)&gij_0(1)&g(1));
pkj_1 <= (pij_0(6)&pij_0(6)&pij_0(4)&pij_0(4)&
          pij_0(2)&pij_0(2)&pij_0(0)&pij_0(0));
gkj_1 <= (gij_0(6)&gij_0(6)&gij_0(4)&gij_0(4)&
          gij_0(2)&gij_0(2)&gij_0(0)&gij_0(0));

pgblackblock_1: pgblackblock
  port map(pik_1, gik_1, pkj_1, gkj_1,
           pij_1, gij_1);

pik_2 <= (pij_1(7)&pij_1(6)&pij_0(6)&
          p(11)&pij_1(3)&pij_1(2)&
          pij_0(2)&p(3));
gik_2 <= (gij_1(7)&gij_1(6)&gij_0(6)&
          g(11)&gij_1(3)&gij_1(2)&
          gij_0(2)&g(3));
pkj_2 <= (pij_1(5)&pij_1(5)&pij_1(5)&pij_1(5)&
          pij_1(1)&pij_1(1)&pij_1(1)&pij_1(1));
gkj_2 <= (gij_1(5)&gij_1(5)&gij_1(5)&gij_1(5)&
          gij_1(1)&gij_1(1)&gij_1(1)&gij_1(1));

pgblackblock_2: pgblackblock
  port map(pik_2, gik_2, pkj_2, gkj_2, pij_2, gij_2);

pik_3 <= (pij_2(7)&pij_2(6)&pij_2(5)&
          pij_2(4)&pij_1(5)&pij_1(4)&
          pij_0(4)&p(7));
gik_3 <= (gij_2(7)&gij_2(6)&gij_2(5)&
          gij_2(4)&gij_1(5)&gij_1(4)&
          gij_0(4)&g(7));
pkj_3 <= (pij_2(3),pij_2(3),pij_2(3),pij_2(3),
          pij_2(3),pij_2(3),pij_2(3),pij_2(3));
gkj_3 <= (gij_2(3),gij_2(3),gij_2(3),gij_2(3),
          gij_2(3),gij_2(3),gij_2(3),gij_2(3));

pgblackblock_3: pgblackblock
  port map(pik_3, gik_3, pkj_3, gkj_3, dummy,
           gij_3);

sum_out: sumblock
  port map(a, b, gen, s);

gen <= (gij_3&gij_2(3 downto 0)&gij_1(1 downto 0)&
        gij_0(0)&cin);
cout <= (a(15) and b(15)) or
        (gen(15) and (a(15) or b(15)));
end;
```

(continued from previous page)

SystemVerilog

```
module pgblock(input  logic [14:0] a, b,
              output logic [14:0] p, g);

    assign p = a | b;
    assign g = a & b;

endmodule

module pgblackblock(input  logic [7:0] pik, gik,
                   pkj, gkj,
                   output logic [7:0] pij, gij);

    assign pij = pik & pkj;
    assign gij = gik | (pik & gkj);

endmodule

module sumblock(input  logic [15:0] a, b, g,
               output logic [15:0] s);

    assign s = a ^ b ^ g;

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity pgblock is
    port(a, b: in  STD_LOGIC_VECTOR(14 downto 0);
          p, g: out STD_LOGIC_VECTOR(14 downto 0));
end;

architecture synth of pgblock is
begin
    p <= a or b;
    g <= a and b;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity pgblackblock is
    port(pik, gik, pkj, gkj:
          in  STD_LOGIC_VECTOR(7 downto 0);
          pij, gij:
          out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of pgblackblock is
begin
    pij <= pik and pkj;
    gij <= gik or (pik and gkj);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity sumblock is
    port(a, b, g: in  STD_LOGIC_VECTOR(15 downto 0);
          s:      out STD_LOGIC_VECTOR(15 downto 0));
end;

architecture synth of sumblock is
begin
    s <= a xor b xor g;
end;
```

Exercise 5.5

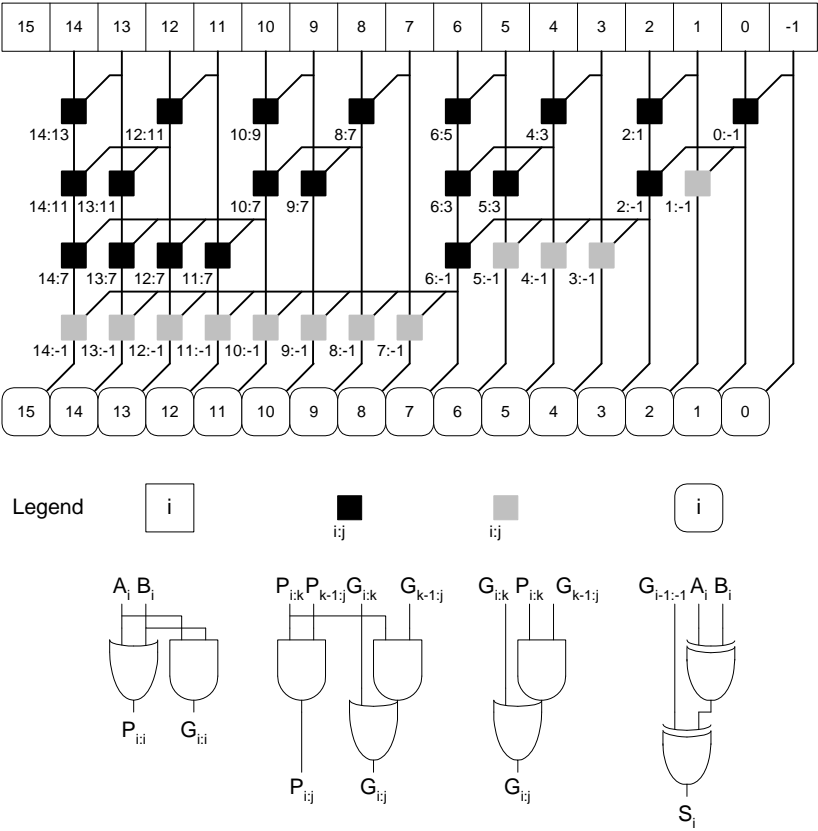


FIGURE 5.2 16-bit prefix adder with “gray cells”

Exercise 5.6

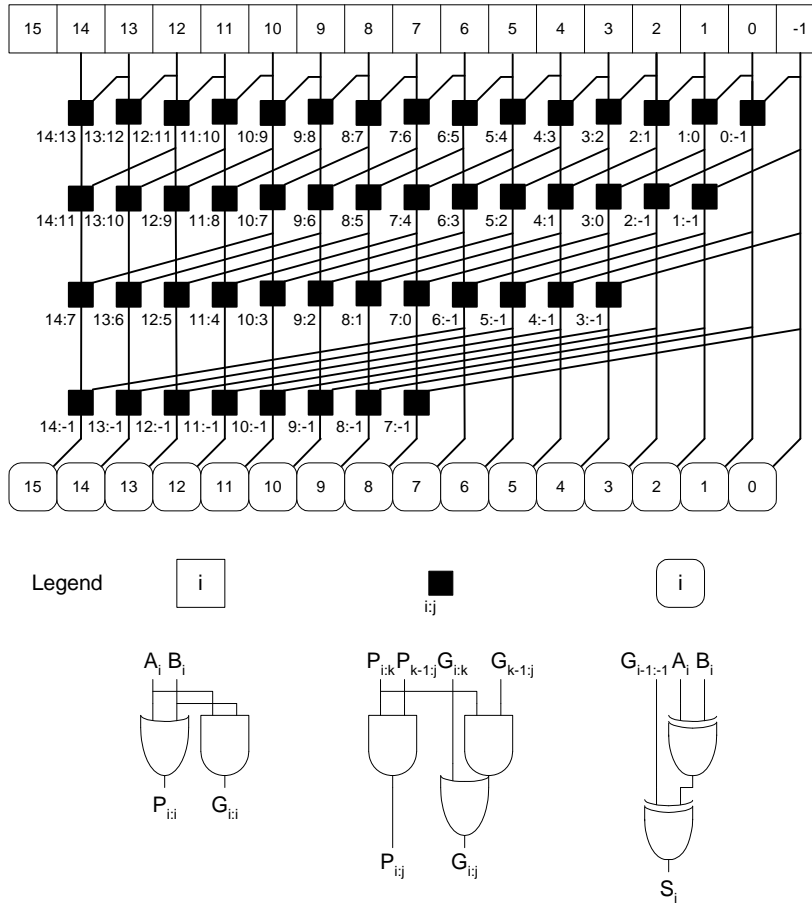


FIGURE 5.3 Schematic of a 16-bit Kogge-Stone adder

Exercise 5.7

(a) We show an 8-bit priority circuit in Figure 5.4. In the figure $X_7 = \bar{A}_7$, $X_{7:6} = \bar{A}_7\bar{A}_6$, $X_{7:5} = \bar{A}_7\bar{A}_6\bar{A}_5$, and so on. The priority encoder's delay is $\log_2 N$ 2-input AND gates followed by a final row of 2-input AND gates. The final stage is an $(N/2)$ -input OR gate. Thus, in general, the delay of an N -input priority encoder is:

$$t_{pd_priority} = (\log_2 N + 1)t_{pd_AND2} + t_{pd_ORN/2}$$

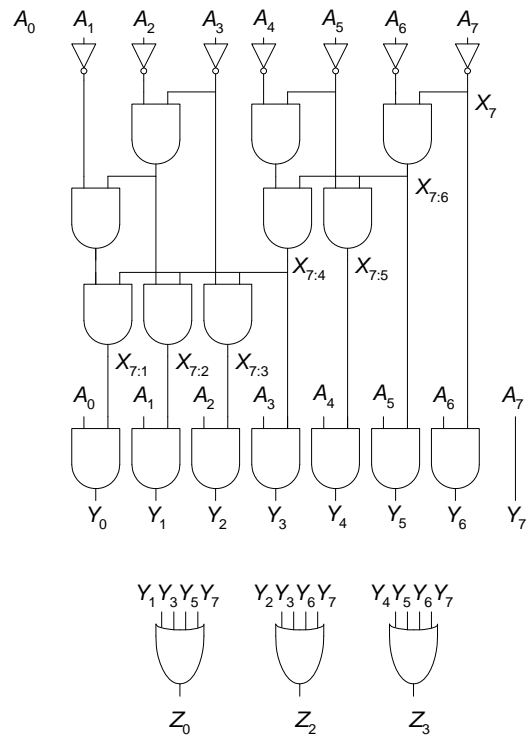


FIGURE 5.4 8-input priority encoder

SystemVerilog

```
module priorityckt(input  logic [7:0] a,
                  output logic [2:0] z);
    logic [7:0] y;
    logic      x7, x76, x75, x74, x73, x72, x71;
    logic      x32, x54, x31;
    logic [7:0] abar;

    // row of inverters
    assign abar = ~a;

    // first row of AND gates
    assign x7  = abar[7];
    assign x76 = abar[6] & x7;
    assign x54 = abar[4] & abar[5];
    assign x32 = abar[2] & abar[3];

    // second row of AND gates
    assign x75 = abar[5] & x76;
    assign x74 = x54 & x76;
    assign x31 = abar[1] & x32;

    // third row of AND gates
    assign x73 = abar[3] & x74;
    assign x72 = x32 & x74;
    assign x71 = x31 & x74;

    // fourth row of AND gates
    assign y = {a[7],      a[6] & x7,  a[5] & x76,
                a[4] & x75, a[3] & x74, a[2] & x73,
                a[1] & x72, a[0] & x71};

    // row of OR gates
    assign z = { |{y[7:4]},
                |{y[7:6], y[3:2]},
                |{y[1], y[3], y[5], y[7]} };
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity priorityckt is
    port(a: in  STD_LOGIC_VECTOR(7 downto 0);
          z: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture synth of priorityckt is
    signal y, abar:  STD_LOGIC_VECTOR(7 downto 0);
    signal x7, x76, x75, x74, x73, x72, x71,
            x32, x54, x31: STD_LOGIC;
begin
    -- row of inverters
    abar <= not a;

    -- first row of AND gates
    x7 <= abar(7);
    x76 <= abar(6) and x7;
    x54 <= abar(4) and abar(5);
    x32 <= abar(2) and abar(3);

    -- second row of AND gates
    x75 <= abar(5) and x76;
    x74 <= x54 and x76;
    x31 <= abar(1) and x32;

    -- third row of AND gates
    x73 <= abar(3) and x74;
    x72 <= x32 and x74;
    x71 <= x31 and x74;


    -- fourth row of AND gates
    y <= (a(7) & (a(6) and x7) & (a(5) and x76) &
          (a(4) and x75) & (a(3) and x74) & (a(2) and
x73) &
          (a(1) and x72) & (a(0) and x71));

    -- row of OR gates
    z <= ( (y(7) or y(6) or y(5) or y(4)) &
          (y(7) or y(6) or y(3) or y(2)) &
          (y(1) or y(3) or y(5) or y(7)) );


end;
```

Exercise 5.8


(a)

 

(b)

 

(c)

 

Exercise 5.9

SystemVerilog

```
module alu32(input  logic [31:0] A, B,
            input  logic [2:0] F,
            output logic [31:0] Y);

    logic [31:0] S, Bout;

    assign Bout = F[2] ? ~B : B;
    assign S = A + Bout + F[2];

    always_comb
        case (F[1:0])
            2'b00: Y <= A & Bout;
            2'b01: Y <= A | Bout;
            2'b10: Y <= S;
            2'b11: Y <= S[31];
        endcase

endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity alu32 is
    port(A, B: in  STD_LOGIC_VECTOR(31 downto 0);
          F:   in  STD_LOGIC_VECTOR(2 downto 0);
          Y:   out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture synth of alu32 is
    signal S, Bout:      STD_LOGIC_VECTOR(31 downto 0);
begin
    Bout <= (not B) when (F(2) = '1') else B;
    S <= A + Bout + F(2);

    process(all) begin
        case F(1 downto 0) is
            when "00" => Y <= A and Bout;
            when "01" => Y <= A or Bout;
            when "10" => Y <= S;
            when "11" => Y <=
                ("00000000000000000000000000000000" & S(31));
            when others => Y <= X"000000000";
        end case;
    end process;
end;
```

Exercise 5.10

(a)

When adding:

- If both operands are positive and output is negative, overflow occurred.
- If both operands are negative and the output is positive, overflow occurred.

When subtracting:

- If the first operand is positive and the second is negative, if the output of the adder unit is negative, overflow occurred.
- If first operand is negative and second operand is positive, if the output of the adder unit is positive, overflow occurred.

In equation form:

Overflow = ADD & (A & B & ~S[31] | ~A & ~B & S[31]) |

$\text{SUB } \& (A \& \sim B \& \sim S[31] \mid \sim A \& B \& S[31]);$
 // note: S is the output of the adder

When the ALU is performing addition, $F[2] = 0$. With subtraction, $F[2] =$
 1. Thus,

$\text{Overflow} = \sim F[2] \& (A \& B \& \sim S[31] \mid \sim A \& \sim B \& S[31]) \mid$
 $F[2] \& (\sim A \& B \& S[31] \mid A \& \sim B \& \sim S[31]);$

(b)

 


FIGURE 5.5 Overflow circuit

(c)

SystemVerilog

```
module alu32(input  logic [31:0] A, B,
            input  logic [2:0] F,
            output logic [31:0] Y,
            output logic Overflow);
    logic [31:0] S, Bout;

    assign Bout = F[2] ? ~B : B;
    assign S = A + Bout + F[2];

    always_comb
        case (F[1:0])
            2'b00: Y = A & Bout;
            2'b01: Y = A | Bout;
            2'b10: Y = S;
            2'b11: Y = S[31];
        endcase

    always_comb
        case (F[2])
            1'b0: Overflow = A[31] & B[31] & ~S[31] |
                            ~A[31] & ~B[31] & S[31];
            1'b1: Overflow = ~A[31] & B[31] & S[31] |
                            A[31] & ~B[31] & ~S[31];
            default: Overflow = 1'b0;
        endcase

endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity alu32 is
    port(A, B: in  STD_LOGIC_VECTOR(31 downto 0);
          F:      in  STD_LOGIC_VECTOR(2 downto 0);
          Y:      out STD_LOGIC_VECTOR(31 downto 0);
          Overflow: out STD_LOGIC);
end;

architecture synth of alu32 is
    signal S, Bout: STD_LOGIC_VECTOR(31 downto 0);
begin
    Bout <= (not B) when (F(2) = '1') else B;
    S <= A + Bout + F(2);

    -- alu function
    process(all) begin
        case F(1 downto 0) is
            when "00" => Y <= A and Bout;
            when "01" => Y <= A or Bout;
            when "10" => Y <= S;
            when "11" => Y <=
                ("00000000000000000000000000000000" & S(31));
            when others => Y <= X"00000000";
        end case;
    end process;

    -- overflow circuit
    process(all) begin
        case F(2 downto 1) is
            when "01" => Overflow <=
                (A(31) and B(31) and (not (S(31)))) or
                ((not A(31)) and (not B(31)) and S(31));
            when "11" => Overflow <=
                ((not A(31)) and B(31) and S(31)) or
                (A(31) and (not B(31)) and (not S(31)));
            when others => Overflow <= '0';
        end case;
    end process;
end;
```

Exercise 5.11

SystemVerilog

```
module alu32(input  logic [31:0] A, B,
            input  logic [2:0] F,
            output logic [31:0] Y,
            output logic Zero, Overflow);
    logic [31:0] S, Bout;

    assign Bout = F[2] ? ~B : B;
    assign S = A + Bout + F[2];

    always_comb
        case (F[1:0])
            2'b00: Y <= A & Bout;
            2'b01: Y <= A | Bout;
            2'b10: Y <= S;
            2'b11: Y <= S[31];
        endcase

    assign Zero = (Y == 32'b0);

    always_comb
        case (F[2:1])
            2'b01: Overflow <= A[31] & B[31] & ~S[31] |
                            ~A[31] & ~B[31] & S[31];
            2'b11: Overflow <= ~A[31] & B[31] & S[31] |
                            A[31] & ~B[31] & ~S[31];
            default: Overflow <= 1'b0;
        endcase
endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity alu32 is
    port(A, B:      in      STD_LOGIC_VECTOR(31 downto 0);
          F:        in      STD_LOGIC_VECTOR(2 downto 0);
          Y:        inout  STD_LOGIC_VECTOR(31 downto 0);
          Overflow: out     STD_LOGIC;
          Zero:     out     STD_LOGIC);
end;

architecture synth of alu32 is
    signal S, Bout:      STD_LOGIC_VECTOR(31 downto 0);
begin
    Bout <= (not B) when (F(2) = '1') else B;
    S <= A + Bout + F(2);

    -- alu function
    process(all) begin
        case F(1 downto 0) is
            when "00" => Y <= A and Bout;
            when "01" => Y <= A or Bout;
            when "10" => Y <= S;
            when "11" => Y <=
                ("00000000000000000000000000000000" & S(31));
            when others => Y <= X"00000000";
        end case;
    end process;

    Zero <= '1' when (Y = X"00000000") else '0';

    -- overflow circuit
    process(all) begin
        case F(2 downto 1) is
            when "01" => Overflow <=
                (A(31) and B(31) and (not (S(31)))) or
                ((not A(31)) and (not B(31)) and S(31));
            when "11" => Overflow <=
                ((not A(31)) and B(31) and S(31)) or
                (A(31) and (not B(31)) and (not S(31)));
            when others => Overflow <= '0';
        end case;
    end process;
end;
```

Exercise 5.12

The following shows the contents of the file test_alu32.tv and test_alu32_vhdl.tv. Note that VHDL does not use underscores (“_”) to separate the hex digits.

test_alu32.tv

```
0_A_00000000_00000000_00000000
0_2_00000000_FFFFFFFF_FFFFFFFF
0_A_00000001_FFFFFFFF_00000000
0_2_000000FF_00000001_00000100
0_E_00000000_00000000_00000000
0_6_00000000_FFFFFFFF_00000001
0_E_00000001_00000001_00000000
0_6_00000100_00000001_000000FF
0_F_00000000_00000000_00000000
0_7_00000000_00000001_00000001
0_F_00000000_FFFFFFFF_00000000
0_F_00000001_00000000_00000000
0_7_FFFFFFFF_00000000_00000001
0_0_FFFFFFFF_FFFFFFFF_FFFFFFFF
0_0_FFFFFFFF_12345678_12345678
0_0_12345678_87654321_02244220
0_8_00000000_FFFFFFFF_00000000
0_1_FFFFFFFF_FFFFFFFF_FFFFFFFF
0_1_12345678_87654321_97755779
0_1_00000000_FFFFFFFF_FFFFFFFF
0_9_00000000_00000000_00000000
1_2_FFFFFFFF_80000000_7FFFFFFF
1_2_00000001_7FFFFFFF_80000000
1_6_80000000_00000001_7FFFFFFF
1_6_7FFFFFFF_FFFFFFFF_80000000
```

test_alu32_vhdl.tv

```
0a000000000000000000000000000000
0200000000ffffffffffffffffffffff
0a00000001ffffffff00000000
02000000ff0000000100000100
0e0000000000000000000000000000
0600000000ffffffff00000001
0e000000010000000100000000
060000010000000001000000ff
0f0000000000000000000000000000
0700000000000000000100000001
0f00000000ffffffff00000000
0f00000001000000000000000000
07fffffffff0000000000000001
00ffffffffffffffffffffffffffff
00fffffffff1234567812345678
00123456788765432102244220
0800000000ffffffff00000000
01ffffffffffffffffffffffffffff
01123456788765432197755779
0100000000ffffffffffffffffffff
090000000000000000000000000000
12fffffffff8000000007fffffffff
12000000017fffffffff80000000
1680000000000000017fffffffff
167fffffffffffffffffff80000000
```

(continued on next page)

Testbench

SystemVerilog

```
module test_alu32_v;  
  
    // Inputs  
    logic [31:0] A;  
    logic [31:0] B;  
    logic [2:0] F;  
  
    // Outputs  
    logic [31:0] Y;  
    logic Zero, Overflow;  
  
    // Internal signals  
    reg clk;  
  
    // Simulation variables  
    logic [31:0] vectornum, errors;  
    logic [100:0] testvectors[10000:0];  
    logic [31:0] ExpectedY;  
    logic ExpectedZero;  
    logic ExpectedOverflow;  
  
    // Instantiate the Unit Under Test (UUT)  
    alu32 uut (A, B, F, Y, Zero, Overflow);  
  
    // generate clock  
    always  
    begin  
        clk = 1; #5; clk = 0; #5;  
    end
```

VHDL

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all; use STD.TEXTIO.all;  
use IEEE.STD_LOGIC_UNSIGNED.all;  
use IEEE.STD_LOGIC_ARITH.all;  
  
entity test_alu32_vhd is -- no inputs or outputs  
end;  
  
architecture sim of test_alu32_vhd is  
    component alu32  
        port(a, b:      in      STD_LOGIC_VECTOR(31 downto 0);  
             f:         in      STD_LOGIC_VECTOR(2 downto 0);  
             y:         inout   STD_LOGIC_VECTOR(31 downto 0);  
             zero:      out     STD_LOGIC;  
             overflow:  out     STD_LOGIC);  
    end component;  
  
    signal a, b:          STD_LOGIC_VECTOR(31 downto 0);  
    signal f:             STD_LOGIC_VECTOR(2 downto 0);  
    signal y:             STD_LOGIC_VECTOR(31 downto 0);  
    signal zero:          STD_LOGIC;  
    signal overflow:      STD_LOGIC;  
    signal clk, reset:    STD_LOGIC;  
    signal yexpected:     STD_LOGIC_VECTOR(31 downto 0);  
    signal oexpected:     STD_LOGIC;  
    signal zexpected:     STD_LOGIC;  
    constant MEMSIZE: integer := 25;  
    type tarray is array(MEMSIZE downto 0) of  
        STD_LOGIC_VECTOR(100 downto 0);  
    shared variable testvectors: tarray;  
    shared variable vectornum, errors: integer;  
begin  
  
    -- instantiate device under test  
    dut: alu32 port map(a, b, f, y, zero, overflow);  
  
    -- generate clock  
    process begin  
        clk <= '1'; wait for 5 ns;  
        clk <= '0'; wait for 5 ns;  
    end process;
```

(continued on next page)

*(continued from previous page)***SystemVerilog**

```
// at start of test, load vectors
initial
begin
    $readmemh("test_alu32.tv", testvectors);
    vectornum = 0; errors = 0;
end
```

VHDL

```
-- at start of test, load vectors
-- and pulse reset
process is
    file tv: TEXT;
    variable i, index, count: integer;
    variable L: line;
    variable ch: character;
    variable result: integer;
begin
    -- read file of test vectors
    i := 0;
    index := 0;
    FILE_OPEN(tv, "test_alu32_vhdl.tv", READ_MODE);
    report "Opening file\n";
    while not endfile(tv) loop
        readline(tv, L);
        result := 0;
        count := 3;
        for i in 1 to 26 loop
            read(L, ch);
            if '0' <= ch and ch <= '9' then
                result := result*16 + character'pos(ch)
                    - character'pos('0');
            elsif 'a' <= ch and ch <= 'f' then
                result := result*16 + character'pos(ch)
                    - character'pos('a')+10;
            else report "Format error on line " &
                integer'image(index) & " i = " &
                integer'image(i) & " char = " &
                character'image(ch)
                severity error;
            end if;

            -- load vectors
            -- assign first 5 bits
            if (i = 2) then
                testvectors(index)( 100 downto 96) :=
                    CONV_STD_LOGIC_VECTOR(result, 5);
                count := count - 1;
                result := 0;          -- reset result
            -- assign the rest of testvectors in
            -- 32-bit increments
            elsif ((i = 10) or (i = 18) or (i = 26)) then
                testvectors(index)( (count*32 + 31)
                    downto (count*32)) :=
                    CONV_STD_LOGIC_VECTOR(result, 32);
                count := count - 1;
                result := 0;          -- reset result
            end if;
        end loop;

        index := index + 1;
    end loop;

    vectornum := 0; errors := 0;
    reset <= '1'; wait for 27 ns; reset <= '0';
    wait;

end process;
```

(continued on next page)

(continued from previous page)

SystemVerilog

```
// apply test vectors on rising edge of clk

always @(posedge clk)
begin
    #1; {ExpectedOverflow, ExpectedZero, F, A, B,
        ExpectedY} = testvectors(vectornum);
    end

// check results on falling edge of clk
always @(negedge clk)
begin
    if ({Y, Zero, Overflow} !==
        {ExpectedY, ExpectedZero, ExpectedOverflow})
    begin
        $display("Error: inputs: F = %h, A = %h,
            B = %h", F, A, B);
        $display("  Y = %h, Zero = %b
            Overflow = %b\n (Expected Y = %h,
            Expected Zero = %b, Expected Overflow
            = %b)", Y, Zero, Overflow,
            ExpectedY, ExpectedZero,
            ExpectedOverflow);
        errors = errors + 1;
    end
    end
    vectornum = vectornum + 1;
    if (testvectors(vectornum) === 101'hx)
    begin
        $display("%d tests completed with %d
            errors", vectornum, errors);
        $finish;
    end
end

endmodule
```

VHDL

```
-- apply test vectors on rising edge of clk
process (clk) begin
    if (clk'event and clk = '1') then
        oexpected <= testvectors(vectornum)(100)
            after 1 ns;
        zexpected <= testvectors(vectornum)(99)
            after 1 ns;
        f
            <= testvectors(vectornum)(98 downto 96)
            after 1 ns;
        a
            <= testvectors(vectornum)(95 downto 64)
            after 1 ns;
        b
            <= testvectors(vectornum)(63 downto 32)
            after 1 ns;
        yexpected <= testvectors(vectornum)(31 downto 0)
            after 1 ns;
    end if;
end process;

-- check results on falling edge of clk
process (clk) begin
    if (clk'event and clk = '0' and reset = '0') then
        assert y = yexpected
            report "Error: vectornum = " &
                integer'image(vectornum) &
                "y = " & integer'image(CONV_INTEGER(y)) &
                ", a = " & integer'image(CONV_INTEGER(a)) &
                ", b = " & integer'image(CONV_INTEGER(b)) &
                ", f = " & integer'image(CONV_INTEGER(f));
        assert overflow = oexpected
            report "Error: overflow = " &
                STD_LOGIC'image(overflow);
        assert zero = zexpected
            report "Error: zero = " &
                STD_LOGIC'image(zero);
        if ( (y /= yexpected) or
            (overflow /= oexpected) or
            (zero /= zexpected) ) then
            errors := errors + 1;
        end if;
        vectornum := vectornum + 1;
        if (is_x(testvectors(vectornum))) then
            if (errors = 0) then
                report "Just kidding -- " &
                    integer'image(vectornum) &
                    " tests completed successfully."
                    severity failure;
            else
                report integer'image(vectornum) &
                    " tests completed, errors = " &
                    integer'image(errors)
                    severity failure;
            end if;
        end if;
    end if;
end process;
end;
```

A 2-bit left shifter creates the output by appending two zeros to the least significant bits of the input and dropping the two most significant bits.

 


FIGURE 5.6 2-bit left shifter, 32-bit input and output

2-bit Left Shifter

SystemVerilog

```
module leftshift2_32(input  logic [31:0] a,
                    output logic [31:0] y);
    assign y = {a[29:0], 2'b0};
endmodule
```


VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity leftshift2_32 is
    port(a: in  STD_LOGIC_VECTOR(31 downto 0);
         y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture synth of leftshift2_32 is
begin
    y <= a(29 downto 0) & "00";
end;
```

Exercise 5.14

 

4-bit Left and Right Rotator

SystemVerilog

```
module ex5_14(a, right_rotated, left_rotated,
shamt);
    input logic [3:0] a;
    output logic [3:0] right_rotated;
    output logic [3:0] left_rotated;
    input logic [1:0] shamt;

    // right rotated
    always_comb
        case(shamt)
            2'b00: right_rotated = a;
            2'b01: right_rotated =
                {a[0], a[3], a[2], a[1]};
            2'b10: right_rotated =
                {a[1], a[0], a[3], a[2]};
            2'b11: right_rotated =
                {a[2], a[1], a[0], a[3]};
            default: right_rotated = 4'bxxxx;
        endcase

    // left rotated
    always_comb
        case(shamt)
            2'b00: left_rotated = a;
            2'b01: left_rotated =
                {a[2], a[1], a[0], a[3]};
            2'b10: left_rotated =
                {a[1], a[0], a[3], a[2]};
            2'b11: left_rotated =
                {a[0], a[3], a[2], a[1]};
            default: left_rotated = 4'bxxxx;
        endcase
endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity ex5_14 is
    port(a: in STD_LOGIC_VECTOR(3 downto 0);
         right_rotated, left_rotated: out
             STD_LOGIC_VECTOR(3 downto 0);
         shamt: in STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of ex5_14 is
begin

    -- right-rotated
    process(all) begin
        case shamt is
            when "00" => right_rotated <= a;
            when "01" => right_rotated <=
                (a(0), a(3), a(2), a(1));
            when "10" => right_rotated <=
                (a(1), a(0), a(3), a(2));
            when "11" => right_rotated <=
                (a(2), a(1), a(0), a(3));
            when others => right_rotated <= "XXXX";
        end case;
    end process;

    -- left-rotated
    process(all) begin
        case shamt is
            when "00" => left_rotated <= a;
            when "01" => left_rotated <=
                (a(2), a(1), a(0), a(3));
            when "10" => left_rotated <=
                (a(1), a(0), a(3), a(2));
            when "11" => left_rotated <=
                (a(0), a(3), a(2), a(1));
            when others => left_rotated <= "XXXX";
        end case;
    end process;
end;
```

Exercise 5.15

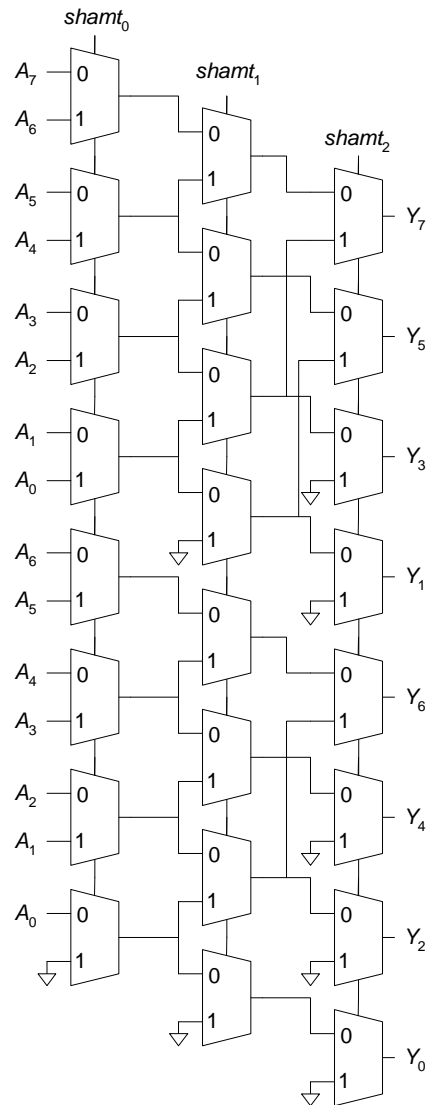


FIGURE 5.7 8-bit left shifter using 24 2:1 multiplexers

Exercise 5.16

Any N -bit shifter can be built by using $\log_2 N$ columns of 2-bit shifters. The first column of multiplexers shifts or rotates 0 to 1 bit, the second column shifts or rotates 0 to 3 bits, the following 0 to 7 bits, etc. until the final column shifts or rotates 0 to $N-1$ bits. The second column of multiplexers takes its inputs from the first column of multiplexers, the third column takes its input from the second column, and so forth. The 1-bit select input of each column is a single bit of the *shamt* (shift amount) control signal, with the least significant bit for the left-most column and the most significant bit for the right-most column.

Exercise 5.17

- (a) $B = 0, C = A, k = \text{shamt}$
- (b) $B = A_{N-1}$ (the most significant bit of A), repeated N times to fill all N bits of B
- (c) $B = A, C = 0, k = N - \text{shamt}$
- (d) $B = A, C = A, k = \text{shamt}$
- (e) $B = A, C = A, k = N - \text{shamt}$

Exercise 5.18

$$t_{pd_MULT4} = t_{AND} + 6t_{FA}$$

An $N \times N$ multiplier has N -bit operands, N partial products, and $N-1$ stages of 1-bit adders. So the propagation is:

$$t_{pd_MULTN} = t_{AND} + 2(N-1)t_{FA}$$

Exercise 5.19

$$t_{pd_DIV4} = 4(4t_{FA} + t_{MUX}) = 16t_{FA} + 4t_{MUX}$$

$$t_{pd_DIVN} = N^2 t_{FA} + N t_{MUX}$$

Exercise 5.20

Recall that a two's complement number has the same weights for the least significant $N-1$ bits, regardless of the sign. The sign bit has a weight of -2^{N-1} . Thus, the product of two N -bit complement numbers, y and x is:

$$P = \left(-y_{N-1}2^{N-1} + \sum_{j=0}^{N-2} y_j2^j \right) \left(-x_{N-1}2^{N-1} + \sum_{i=0}^{N-2} x_i2^i \right)$$

Thus,

$$\sum_{i=0}^{N-2} \sum_{j=0}^{N-2} x_i y_j 2^{i+j} + x_{N-1} y_{N-1} 2^{2N-2} - \sum_{i=0}^{N-2} x_i y_{N-1} 2^{i+N-1} - \sum_{j=0}^{N-2} x_{N-1} y_j 2^{j+N-1}$$

The two negative partial products are formed by taking the two's complement (inverting the bits and adding 1). Figure 5.8 shows a 4 x 4 multiplier. Figure 5.8 (b) shows the partial products using the above equation. Figure 5.8 (c) shows a simplified version, pushing through the 1's. This is known as a *modified Baugh-Wooley multiplier*. It can be built using a hierarchy of adders.

 


FIGURE 5.8 Multiplier: (a) symbol, (b) function, (c) simplified function

Exercise 5.21

 


FIGURE 5.9 Sign extension unit (a) symbol, (b) underlying hardware

SystemVerilog

```
module signext4_8(input  logic [3:0] a,
                  output logic [7:0] y);

    assign y = { 4{a[3]}, a};

endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity signext4_8 is
    port(a: in  STD_LOGIC_VECTOR(3 downto 0);
          y: out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of signext4_8 is
begin
```

Exercise 5.22

 


FIGURE 5.10 Zero extension unit (a) symbol, (b) underlying hardware

SystemVerilog

```
module zeroext4_8(input  logic [3:0] a,
                  output logic [7:0] y);

    assign y = {4'b0, a};

endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity zeroext4_8 is
    port(a: in  STD_LOGIC_VECTOR(3 downto 0);
         y: out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of zeroext4_8 is
begin
    y <= "0000" & a(3 downto 0);
end;
```

Exercise 5.23

$$\begin{array}{r}
 100.110 \\
 1100 \overline{) 111001.000} \\
 \underline{-1100} \\
 00100 \\
 \underline{-1100} \\
 1100 \\
 \underline{-1100} \\
 0
 \end{array}$$

Exercise 5.24

$$\begin{aligned} \text{(a)} \quad & \left[0, \left(2^{12} - 1 + \frac{2^{12} - 1}{2^{12}} \right) \right] \\ \text{(b)} \quad & \left[- \left(2^{11} - 1 + \frac{2^{12} - 1}{2^{12}} \right), \left(2^{11} - 1 + \frac{2^{12} - 1}{2^{12}} \right) \right] \\ \text{(c)} \quad & \left[- \left(2^{11} + \frac{2^{12} - 1}{2^{12}} \right), \left(2^{11} - 1 + \frac{2^{12} - 1}{2^{12}} \right) \right] \end{aligned}$$

Exercise 5.25

- (a) $1000\ 1101\ .\ 1001\ 0000 = 0x8D90$
- (b) $0010\ 1010\ .\ 0101\ 0000 = 0x2A50$
- (c) $1001\ 0001\ .\ 0010\ 1000 = 0x9128$

Exercise 5.26

- (a) $111110.100000 = 0xFA0$
- (b) $010000.010000 = 0x410$
- (c) $101000.000101 = 0xA05$

Exercise 5.27

- (a) $1111\ 0010\ .\ 0111\ 0000 = 0xF270$
- (b) $0010\ 1010\ .\ 0101\ 0000 = 0x2A50$
- (c) $1110\ 1110\ .\ 1101\ 1000 = 0xEED8$

Exercise 5.28

- (a) $100001.100000 = 0x860$
- (b) $010000.010000 = 0x410$
- (c) $110111.111011 = 0xDFB$

Exercise 5.29

- (a) $-1101.1001 = -1.1011001 \times 2^3$
Thus, the biased exponent $= 127 + 3 = 130 = 1000\ 0010_2$
In IEEE 754 single-precision floating-point format:
 $1\ 1000\ 0010\ 101\ 1001\ 0000\ 0000\ 0000\ 0000 = \mathbf{0xC1590000}$
- (b) $101010.0101 = 1.010100101 \times 2^5$
Thus, the biased exponent $= 127 + 5 = 132 = 1000\ 0100_2$
In IEEE 754 single-precision floating-point format:
 $0\ 1000\ 0100\ 010\ 1001\ 0100\ 0000\ 0000\ 0000 = \mathbf{0x42294000}$
- (c) $-10001.00101 = -1.000100101 \times 2^4$
Thus, the biased exponent $= 127 + 4 = 131 = 1000\ 0011_2$
In IEEE 754 single-precision floating-point format:
 $1\ 1000\ 0011\ 000\ 1001\ 0100\ 0000\ 0000\ 0000 = \mathbf{0xC1894000}$

Exercise 5.30

(a) $-11110.1 = -1.111101 \times 2^4$

Thus, the biased exponent = $127 + 4 = 131 = 1000\ 0011_2$

In IEEE 754 single-precision floating-point format:

1 1000 0011 111 1010 0000 0000 0000 0000 = **0xC1F40000**

(b) $10000.01 = 1.000001 \times 2^4$

Thus, the biased exponent = $127 + 4 = 131 = 1000\ 0011_2$

In IEEE 754 single-precision floating-point format:

0 1000 0011 000 0010 0100 0000 0000 0000 = **0x41820000**

(c) $-1000.000101 = -1.000000101 \times 2^3$

Thus, the biased exponent = $127 + 3 = 130 = 1000\ 0010_2$

In IEEE 754 single-precision floating-point format:

1 1000 0010 000 0001 0100 0000 0000 0000 = **0xC1014000**

Exercise 5.31

(a) 5.5

(b) $-0000.0001_2 = -0.0625$

(c) -8

Exercise 5.32

(a) 29.65625

(b) -25.1875

(c) -23.875

Exercise 5.33

When adding two floating point numbers, the number with the smaller exponent is shifted to preserve the most significant bits. For example, suppose we were adding the two floating point numbers 1.0×2^0 and 1.0×2^{-27} . We make the two exponents equal by shifting the second number right by 27 bits. Because the mantissa is limited to 24 bits, the second number ($1.000\ 0000\ 0000\ 0000\ 0000 \times 2^{-27}$) becomes $0.000\ 0000\ 0000\ 0000\ 0000 \times 2^0$, because the 1 is shifted off to the right. If we had shifted the number with the larger exponent (1.0×2^0) to the left, we would have shifted off the more significant bits (on the order of 2^0 instead of on the order of 2^{-27}).

Exercise 5.34

- (a) C0123456
- (b) D1E072C3
- (c) 5F19659A

Exercise 5.35

- (a)
- $$\begin{aligned} 0xC0D20004 &= 1\ 1000\ 0001\ 101\ 0010\ 0000\ 0000\ 0000\ 0100 \\ &= -1.101\ 0010\ 0000\ 0000\ 0000\ 01 \times 2^2 \\ 0x72407020 &= 0\ 1110\ 0100\ 100\ 0000\ 0111\ 0000\ 0010\ 0000 \\ &= 1.100\ 0000\ 0111\ 0000\ 001 \times 2^{101} \end{aligned}$$

When adding these two numbers together, 0xC0D20004 becomes:
 0×2^{101} because all of the significant bits shift off the right when making the exponents equal. Thus, the result of the addition is simply the second number:

0x72407020

- (b)
- $$\begin{aligned} 0xC0D20004 &= 1\ 1000\ 0001\ 101\ 0010\ 0000\ 0000\ 0000\ 0100 \\ &= -1.101\ 0010\ 0000\ 0000\ 0000\ 01 \times 2^2 \\ 0x40DC0004 &= 0\ 1000\ 0001\ 101\ 1100\ 0000\ 0000\ 0000\ 0100 \\ &= 1.101\ 1100\ 0000\ 0000\ 0000\ 01 \times 2^2 \end{aligned}$$

$$\begin{aligned} &1.101\ 1100\ 0000\ 0000\ 0000\ 01 \times 2^2 \\ &- 1.101\ 0010\ 0000\ 0000\ 0000\ 01 \times 2^2 \\ &= 0.000\ 1010 \qquad \qquad \qquad \times 2^2 \\ &= 1.010 \times 2^{-2} \\ &= 0\ 0111\ 1101\ 010\ 0000\ 0000\ 0000\ 0000\ 0000 \\ &= 0x3EA00000 \end{aligned}$$

- (c)
- $$\begin{aligned} 0x5FBE4000 &= 0\ 1011\ 1111\ 011\ 1110\ 0100\ 0000\ 0000\ 0000\ 0000 \\ &= 1.011\ 1110\ 01 \times 2^{64} \\ 0x3FF80000 &= 0\ 0111\ 1111\ 111\ 1000\ 0000\ 0000\ 0000\ 0000 \\ &= 1.111\ 1 \times 2^0 \\ 0xDFDE4000 &= 1\ 1011\ 1111\ 101\ 1110\ 0100\ 0000\ 0000\ 0000\ 0000 \\ &= -1.101\ 1110\ 01 \times 2^{64} \end{aligned}$$

$$\text{Thus, } (1.011\ 1110\ 01 \times 2^{64} + 1.111\ 1 \times 2^0) = 1.011\ 1110\ 01 \times 2^{64}$$

$$\begin{aligned} \text{And, } (1.011\ 1110\ 01 \times 2^{64} + 1.111\ 1 \times 2^0) - 1.101\ 1110\ 01 \times 2^{64} &= \\ -0.01 \times 2^{64} &= -1.0 \times 2^{64} \\ &= 1\ 1011\ 1101\ 000\ 0000\ 0000\ 0000\ 0000\ 0000 \\ &= \mathbf{0xDE800000} \end{aligned}$$

This is counterintuitive because the second number (0x3FF80000) does not affect the result because its order of magnitude is less than 2^{23} of the other numbers. This second number's significant bits are shifted off when the exponents are made equal.

Exercise 5.36

We only need to change step 5.

1. Extract exponent and fraction bits.
2. Prepend leading 1 to form the mantissa.
3. Compare exponents.
4. Shift smaller mantissa if necessary.
5. If one number is negative: Subtract it from the other number. If the result is negative, take the absolute value of the result and make the sign bit 1.
If both numbers are negative: Add the numbers and make the sign bit 1.
If both numbers are positive: Add the numbers and make the sign bit 0.
6. Normalize mantissa and adjust exponent if necessary.
7. Round result
8. Assemble exponent and fraction back into floating-point number

Exercise 5.37

$$(a) \ 2(2^{31} - 1 - 2^{23}) = 2^{32} - 2 - 2^{24} = 4,278,190,078$$

$$(b) \ 2(2^{31} - 1) = 2^{32} - 2 = 4,294,967,294$$

(c) $\pm\infty$ and NaN are given special representations because they are often used in calculations and in representing results. These values also give useful information to the user as return values, instead of returning garbage upon overflow, underflow, or divide by zero.

Exercise 5.38

$$\begin{aligned} \text{(a) } 245 &= 11110101 = 1.1110101 \times 2^7 \\ &= 0\ 1000\ 0110\ 111\ 0101\ 0000\ 0000\ 0000\ 0000 \\ &= 0x43750000 \\ 0.0625 &= 0.0001 = 1.0 \times 2^{-4} \\ &= 0\ 0111\ 1011\ 000\ 0000\ 0000\ 0000\ 0000\ 0000 \\ &= 0x3D800000 \end{aligned}$$

(b) 0x43750000 is greater than 0x3D800000, so magnitude comparison gives the correct result.

$$\begin{aligned} \text{(c)} \\ 1.1110101 \times 2^7 &= 0\ 0000\ 0111\ 111\ 0101\ 0000\ 0000\ 0000\ 0000 \\ &= 0x03F50000 \\ 1.0 \times 2^{-4} &= 0\ 1111\ 1100\ 000\ 0000\ 0000\ 0000\ 0000\ 0000 \\ &= 0x7E000000 \end{aligned}$$

(d) No, integer comparison no longer works. $7E000000 > 03F50000$ (indicating that 1.0×2^{-4} is greater than 1.1110101×2^7 , which is incorrect.)

(e) It is convenient for integer comparison to work with floating-point numbers because then the computer can compare numbers without needing to extract the mantissa, exponent, and sign.

Exercise 5.39

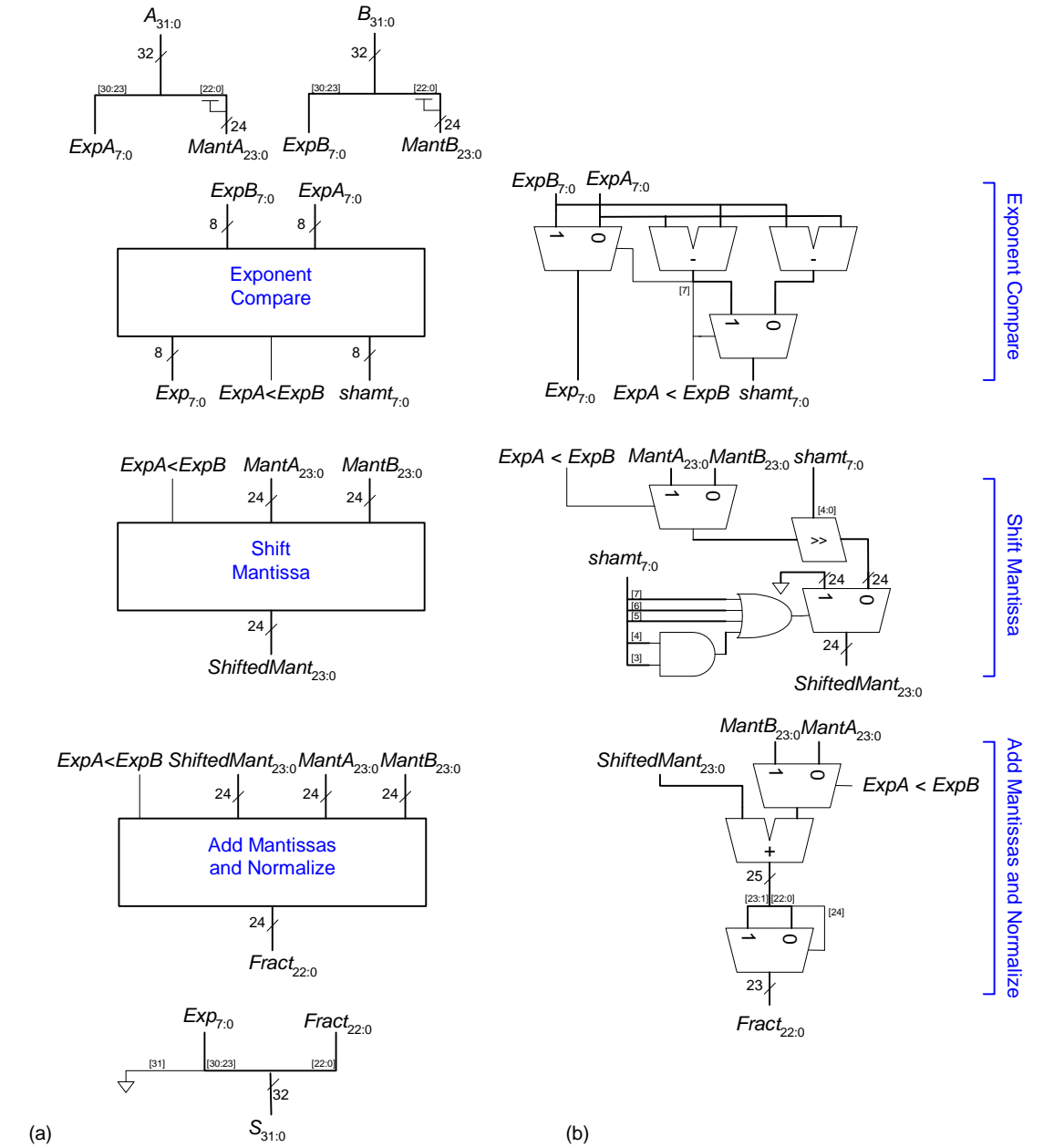


FIGURE 5.11 Floating-point adder hardware: (a) block diagram, (b) underlying hardware

SystemVerilog

```
module fpadd(input logic [31:0] a, b,
            output logic [31:0] s);

    logic [7:0] expa, expb, exp_pre, exp, shamt;
    logic alessb;
    logic [23:0] manta, mantb, shmant;
    logic [22:0] fract;

    assign {expa, manta} = {a[30:23], 1'b1, a[22:0]};
    assign {expb, mantb} = {b[30:23], 1'b1, b[22:0]};
    assign s = {1'b0, exp, fract};

    expcomp expcompl(expa, expb, alessb, exp_pre,
                    shamt);
    shiftmant shiftmant1(alessb, manta, mantb,
                        shamt, shmant);
    addmant addmant1(alessb, manta, mantb,
                    shmant, exp_pre, fract, exp);

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;

entity fpadd is
    port(a, b: in STD_LOGIC_VECTOR(31 downto 0);
         s: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture synth of fpadd is
    component expcomp
        port(expa, expb: in STD_LOGIC_VECTOR(7 downto 0);
             alessb: inout STD_LOGIC;
             exp,shamt: out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    component shiftmant
        port(alessb: in STD_LOGIC;
             manta: in STD_LOGIC_VECTOR(23 downto 0);
             mantb: in STD_LOGIC_VECTOR(23 downto 0);
             shamt: in STD_LOGIC_VECTOR(7 downto 0);
             shmant: out STD_LOGIC_VECTOR(23 downto 0));
    end component;

    component addmant
        port(alessb: in STD_LOGIC;
             manta: in STD_LOGIC_VECTOR(23 downto 0);
             mantb: in STD_LOGIC_VECTOR(23 downto 0);
             shmant: in STD_LOGIC_VECTOR(23 downto 0);
             exp_pre: in STD_LOGIC_VECTOR(7 downto 0);
             fract: out STD_LOGIC_VECTOR(22 downto 0);
             exp: out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    signal expa, expb: STD_LOGIC_VECTOR(7 downto 0);
    signal exp_pre, exp: STD_LOGIC_VECTOR(7 downto 0);
    signal shamt: STD_LOGIC_VECTOR(7 downto 0);
    signal alessb: STD_LOGIC;
    signal manta: STD_LOGIC_VECTOR(23 downto 0);
    signal mantb: STD_LOGIC_VECTOR(23 downto 0);
    signal shmant: STD_LOGIC_VECTOR(23 downto 0);
    signal fract: STD_LOGIC_VECTOR(22 downto 0);

begin

    expa <= a(30 downto 23);
    manta <= '1' & a(22 downto 0);
    expb <= b(30 downto 23);
    mantb <= '1' & b(22 downto 0);

    s <= '0' & exp & fract;

    expcomp1: expcomp
        port map(expa, expb, alessb, exp_pre, shamt);
    shiftmant1: shiftmant
        port map(alessb, manta, mantb, shamt, shmant);
    addmant1: addmant
        port map(alessb, manta, mantb, shmant,
                exp_pre, fract, exp);

end;
```

(continued from previous page)

SystemVerilog

```
module expcomp(input  logic [7:0] expa, expb,
               output logic      alessb,
               output logic [7:0] exp, shamt);
    logic [7:0] aminusb, bminusa;

    assign aminusb = expa - expb;
    assign bminusa = expb - expa;
    assign alessb  = aminusb[7];

    always_comb
        if (alessb) begin
            exp = expb;
            shamt = bminusa;
        end
        else begin
            exp = expa;
            shamt = aminusb;
        end
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;

entity expcomp is
    port(expa, expb: in  STD_LOGIC_VECTOR(7 downto 0);
          alessb:      inout STD_LOGIC;
          exp,shamt:   out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of expcomp is
    signal aminusb: STD_LOGIC_VECTOR(7 downto 0);
    signal bminusa: STD_LOGIC_VECTOR(7 downto 0);
begin
    aminusb <= expa - expb;
    bminusa <= expb - expa;
    alessb <= aminusb(7);

    exp <= expb when alessb = '1' else expa;
    shamt <= bminusa when alessb = '1' else aminusb;

end;
```

(continued on next page)

(continued from previous page)

SystemVerilog

```
module shiftmant(input  logic alessb,
                 input  logic [23:0] manta, mantb,
                 input  logic [7:0] shamt,
                 output logic [23:0] shmant);

    logic [23:0] shiftedval;

    assign shiftedval = alessb ?
        (manta >> shamt) : (mantb >> shamt);

    always_comb
        if (shamt[7] | shamt[6] | shamt[5] |
            (shamt[4] & shamt[3]))
            shmant = 24'b0;
        else
            shmant = shiftedval;

endmodule

module addmant(input  logic      alessb,
               input  logic [23:0] manta,
               input  logic [23:0] mantb, shmant,
               input  logic [7:0]  exp_pre,
               output logic [22:0] fract,
               output logic [7:0]  exp);

    logic [24:0] addresult;
    logic [23:0] addval;

    assign addval    = alessb ? mantb : manta;
    assign addresult = shmant + addval;
    assign fract     = addresult[24] ?
        addresult[23:1] :
        addresult[22:0];

    assign exp       = addresult[24] ?
        (exp_pre + 1) :
        exp_pre;

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use ieee.numeric_std.all;
use IEEE.std_logic_unsigned.all;

entity shiftmant is
    port(alessb: in  STD_LOGIC;
          manta: in  STD_LOGIC_VECTOR(23 downto 0);
          mantb: in  STD_LOGIC_VECTOR(23 downto 0);
          shamt: in  STD_LOGIC_VECTOR(7 downto 0);
          shmant: out STD_LOGIC_VECTOR(23 downto 0));
end;

architecture synth of shiftmant is
    signal shiftedval: unsigned (23 downto 0);
    signal shiftamt_vector: STD_LOGIC_VECTOR (7 downto 0);
begin

    shiftedval <= SHIFT_RIGHT( unsigned(manta), to_in-
        teger(unsigned(shamt))) when alessb = '1'
        else SHIFT_RIGHT( unsigned(mantb), to_in-
        teger(unsigned(shamt)));

    shmant <= X"000000" when (shamt > 22)
        else STD_LOGIC_VECTOR(shiftedval);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;

entity addmant is
    port(alessb: in  STD_LOGIC;
          manta: in  STD_LOGIC_VECTOR(23 downto 0);
          mantb: in  STD_LOGIC_VECTOR(23 downto 0);
          shmant: in  STD_LOGIC_VECTOR(23 downto 0);
          exp_pre: in  STD_LOGIC_VECTOR(7 downto 0);
          fract: out  STD_LOGIC_VECTOR(22 downto 0);
          exp: out  STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of addmant is
    signal addresult: STD_LOGIC_VECTOR(24 downto 0);
    signal addval: STD_LOGIC_VECTOR(23 downto 0);
begin
    addval <= mantb when alessb = '1' else manta;
    addresult <= ('0' & shmant) + addval;
    fract <= addresult(23 downto 1)
        when addresult(24) = '1'
        else addresult(22 downto 0);
    exp <= (exp_pre + 1)
        when addresult(24) = '1'
        else exp_pre;

end;
```

Exercise 5.40

(a)

- Extract exponent and fraction bits.
- Prepend leading 1 to form the mantissa.
- Add exponents.
- Multiply mantissas.
- Round result and truncate mantissa to 24 bits.
- Assemble exponent and fraction back into floating-point number

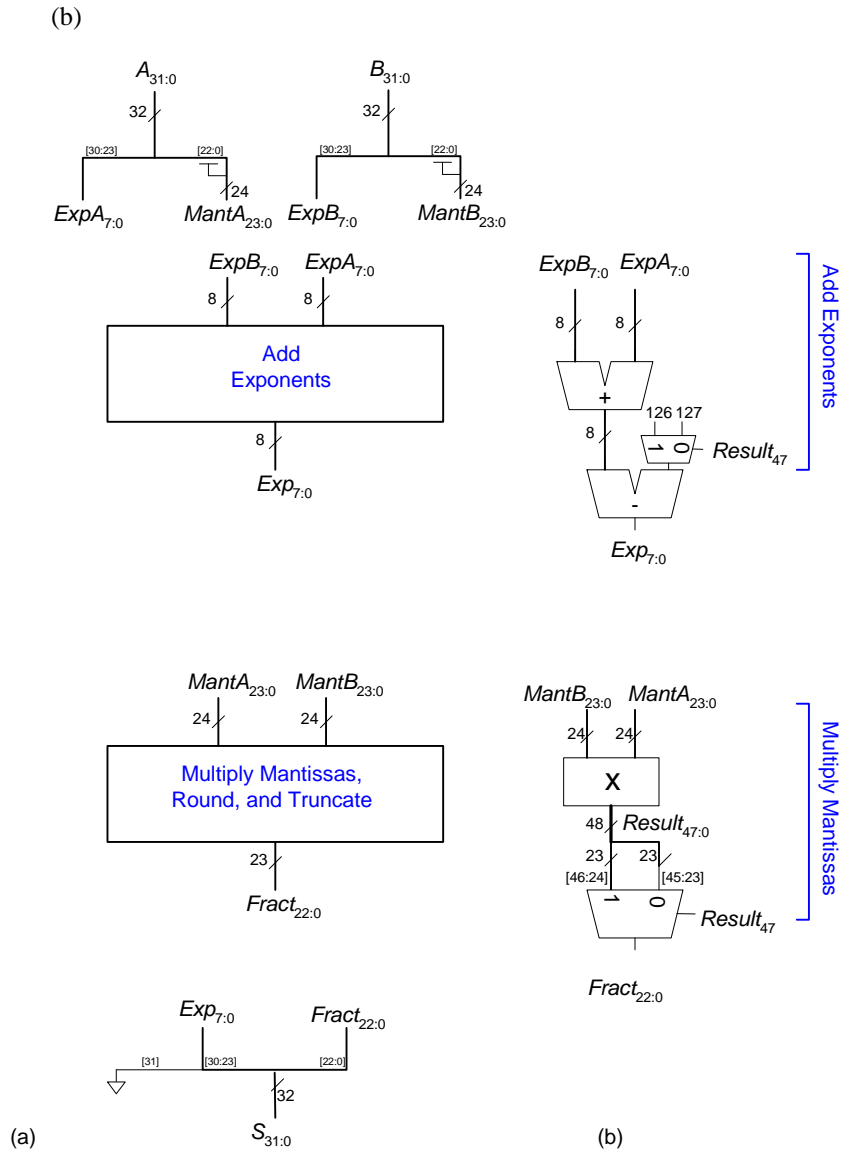


FIGURE 5.12 Floating-point multiplier block diagram

(c)

SystemVerilog

```
module fpmult(input  logic [31:0] a, b,
             output logic [31:0] m);

    logic [7:0]  expa, expb, exp;
    logic [23:0] manta, mantb;
    logic [22:0] fract;
    logic [47:0] result;

    assign {expa, manta} = {a[30:23], 1'b1, a[22:0]};
    assign {expb, mantb} = {b[30:23], 1'b1, b[22:0]};
    assign m           = {1'b0, exp, fract};

    assign result = manta * mantb;
    assign fract = result[47] ?
                    result[46:24] :
                    result[45:23];

    assign exp = result[47] ?
                (expa + expb - 126) :
                (expa + expb - 127);

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;

entity fpmult is
    port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
          m:      out STD_LOGIC_VECTOR(31 downto 0));
end;


architecture synth of fpmult is
    signal expa, expb, exp:
        STD_LOGIC_VECTOR(7 downto 0);
    signal manta, mantb:
        STD_LOGIC_VECTOR(23 downto 0);
    signal fract:
        STD_LOGIC_VECTOR(22 downto 0);
    signal result:
        STD_LOGIC_VECTOR(47 downto 0);
begin
    expa  <= a(30 downto 23);
    manta <= '1' & a(22 downto 0);
    expb  <= b(30 downto 23);
    mantb <= '1' & b(22 downto 0);

    m      <= '0' & exp & fract;
    result <= manta * mantb;
    fract  <= result(46 downto 24)
                when (result(47) = '1')
            else result(45 downto 23);
    exp    <= (expa + expb - 126)
                when (result(47) = '1')
            else (expa + expb - 127);

end;
```

Exercise 5.41

(a) Figure on next page

 

5.41 (b)

SystemVerilog

```
module prefixadd(input  logic [31:0] a, b,
                 input  logic      cin,
                 output logic [31:0] s,
                 output logic      cout);

    logic [30:0] p, g;
    // p and g prefixes for rows 1 - 5
    logic [15:0] p1, p2, p3, p4, p5;
    logic [15:0] g1, g2, g3, g4, g5;

    pandg row0(a, b, p, g);
    blackbox row1({p[30],p[28],p[26],p[24],p[22],
                  p[20],p[18],p[16],p[14],p[12],
                  p[10],p[8],p[6],p[4],p[2],p[0]},
                 {p[29],p[27],p[25],p[23],p[21],
                  p[19],p[17],p[15],p[13],p[11],
                  p[9],p[7],p[5],p[3],p[1],1'b0},
                 {g[30],g[28],g[26],g[24],g[22],
                  g[20],g[18],g[16],g[14],g[12],
                  g[10],g[8],g[6],g[4],g[2],g[0]},
                 {g[29],g[27],g[25],g[23],g[21],
                  g[19],g[17],g[15],g[13],g[11],
                  g[9],g[7],g[5],g[3],g[1],cin},
                 p1, g1);
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity prefixadd is
    port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
          cin: in  STD_LOGIC;
          s:  out STD_LOGIC_VECTOR(31 downto 0);
          cout: out STD_LOGIC);
end;

architecture synth of prefixadd is
    component pgblock
        port(a, b: in  STD_LOGIC_VECTOR(30 downto 0);
              p, g: out STD_LOGIC_VECTOR(30 downto 0));
    end component;

    component pgblackblock is
        port (pik, gik: in  STD_LOGIC_VECTOR(15 downto 0);
              pkj, gkj: in  STD_LOGIC_VECTOR(15 downto 0);
              pij: out STD_LOGIC_VECTOR(15 downto 0);
              gij: out STD_LOGIC_VECTOR(15 downto 0));
    end component;

    component subblock is
        port (a, b, g: in  STD_LOGIC_VECTOR(31 downto 0);
              s:  out STD_LOGIC_VECTOR(31 downto 0));
    end component;

    signal p, g: STD_LOGIC_VECTOR(30 downto 0);
    signal pik_1, pik_2, pik_3, pik_4, pik_5,
           gik_1, gik_2, gik_3, gik_4, gik_5,
           pkj_1, pkj_2, pkj_3, pkj_4, pkj_5,
           gkj_1, gkj_2, gkj_3, gkj_4, gkj_5,
           p1, p2, p3, p4, p5,
           g1, g2, g3, g4, g5:
        STD_LOGIC_VECTOR(15 downto 0);
    signal g6:  STD_LOGIC_VECTOR(31 downto 0);

begin
    row0: pgblock
        port map(a(30 downto 0), b(30 downto 0), p, g);

    pik_1 <=
        (p(30)&p(28)&p(26)&p(24)&p(22)&p(20)&p(18)&p(16)&
         p(14)&p(12)&p(10)&p(8)&p(6)&p(4)&p(2)&p(0));
    gik_1 <=
        (g(30)&g(28)&g(26)&g(24)&g(22)&g(20)&g(18)&g(16)&
         g(14)&g(12)&g(10)&g(8)&g(6)&g(4)&g(2)&g(0));
    pkj_1 <=
        (p(29)&p(27)&p(25)&p(23)&p(21)&p(19)&p(17)&p(15)&
         p(13)&p(11)&p(9)&p(7)&p(5)&p(3)&p(1)&'0');
    gkj_1 <=
        (g(29)&g(27)&g(25)&g(23)&g(21)&g(19)&g(17)&g(15)&
         g(13)&g(11)&g(9)&g(7)&g(5)&g(3)&g(1)&cin);

    row1: pgblackblock
        port map(pik_1, gik_1, pkj_1, gkj_1,
                p1, g1);
```

(continued on next page)
(continued from previous page)

SystemVerilog

```

blackbox row2({p1[15],p1[29],p1[13],p1[25],p1[11],
              p1[21],p1[9],p1[17],p1[7],p1[13],
              p1[5],p1[9],p1[3],p1[5],p1[1],p1[1]},
              {{2{p1[14]}},{2{p1[12]}},{2{p1[10]}},
               {2{p1[8]}},{2{p1[6]}},{2{p1[4]}},
               {2{p1[2]}},{2{p1[0]}}},
              {g1[15],g1[29],g1[13],g1[25],g1[11],
               g1[21],g1[9],g1[17],g1[7],g1[13],
               g1[5],g1[9],g1[3],g1[5],g1[1],g1[1]},
              {{2{g1[14]}},{2{g1[12]}},{2{g1[10]}},
               {2{g1[8]}},{2{g1[6]}},{2{g1[4]}},
               {2{g1[2]}},{2{g1[0]}}},
              p2, g2);

blackbox row3({p2[15],p2[14],p1[14],p1[27],p2[11],
              p2[10],p1[10],p1[19],p2[7],p2[6],
              p1[6],p1[11],p2[3],p2[2],p1[2],p1[3]},
              {{4{p2[13]}},{4{p2[9]}},{4{p2[5]}},
               {4{p2[1]}},
               {g2[15],g2[14],g1[14],g1[27],g2[11],
                g2[10],g1[10],g1[19],g2[7],g2[6],
                g1[6],g1[11],g2[3],g2[2],g1[2],g1[3]},
               {{4{g2[13]}},{4{g2[9]}},{4{g2[5]}},
                {4{g2[1]}},
                p3, g3);

```

VHDL

```

pik_2 <= p1(15)&p(29)&p1(13)&p(25)&p1(11)&
         p(21)&p1(9)&p(17)&p1(7)&p(13)&
         p1(5)&p(9)&p1(3)&p(5)&p1(1)&p(1);

gik_2 <= g1(15)&g(29)&g1(13)&g(25)&g1(11)&
         g(21)&g1(9)&g(17)&g1(7)&g(13)&
         g1(5)&g(9)&g1(3)&g(5)&g1(1)&g(1);

pkj_2 <=
         p1(14)&p1(14)&p1(12)&p1(12)&p1(10)&p1(10)&
         p1(8)&p1(8)&p1(6)&p1(6)&p1(4)&p1(4)&
         p1(2)&p1(2)&p1(0)&p1(0);

gkj_2 <=
         g1(14)&g1(14)&g1(12)&g1(12)&g1(10)&g1(10)&
         g1(8)&g1(8)&g1(6)&g1(6)&g1(4)&g1(4)&
         g1(2)&g1(2)&g1(0)&g1(0);

row2: pgblackblock
port map(pik_2, gik_2, pkj_2, gkj_2,
         p2, g2);

pik_3 <= p2(15)&p2(14)&p1(14)&p(27)&p2(11)&
         p2(10)&p1(10)&p(19)&p2(7)&p2(6)&
         p1(6)&p(11)&p2(3)&p2(2)&p1(2)&p(3);

gik_3 <= g2(15)&g2(14)&g1(14)&g(27)&g2(11)&
         g2(10)&g1(10)&g(19)&g2(7)&g2(6)&
         g1(6)&g(11)&g2(3)&g2(2)&g1(2)&g(3);

pkj_3 <= p2(13)&p2(13)&p2(13)&p2(13)&
         p2(9)&p2(9)&p2(9)&p2(9)&
         p2(5)&p2(5)&p2(5)&p2(5)&
         p2(1)&p2(1)&p2(1)&p2(1);

gkj_3 <= g2(13)&g2(13)&g2(13)&g2(13)&
         g2(9)&g2(9)&g2(9)&g2(9)&
         g2(5)&g2(5)&g2(5)&g2(5)&
         g2(1)&g2(1)&g2(1)&g2(1);

row3: pgblackblock
port map(pik_3, gik_3, pkj_3, gkj_3, p3, g3);

```

(continued on next page)

SystemVerilog

```

blackbox row4({p3[15:12],p2[13:12],
              p1[12],p[23],p3[7:4],
              p2[5:4],p1[4],p[7]},
              {{8{p3[11]}},{8{p3[3]}},
              {g3[15:12],g2[13:12],
              g1[12],g[23],g3[7:4],
              g2[5:4],g1[4],g[7]},
              {{8{g3[11]}},{8{g3[3]}},
              p4, g4};

blackbox row5({p4[15:8],p3[11:8],p2[9:8],
              p1[8],p[15]},
              {{16{p4[7]}},
              {g4[15:8],g3[11:8],g2[9:8],
              g1[8],g[15]},
              {{16{g4[7]}},
              p5,g5});

sum row6({g5,g4[7:0],g3[3:0],g2[1:0],g1[0],cin},
        a, b, s);

// generate cout
assign cout = (a[31] & b[31]) |
              (g5[15] & (a[31] | b[31]));

endmodule

```

VHDL

```

pik_4 <= p3(15 downto 12)&p2(13 downto 12)&
         p1(12)&p(23)&p3(7 downto 4)&
         p2(5 downto 4)&p1(4)&p(7);
gik_4 <= g3(15 downto 12)&g2(13 downto 12)&
         g1(12)&g(23)&g3(7 downto 4)&
         g2(5 downto 4)&g1(4)&g(7);
pkj_4 <= p3(11)&p3(11)&p3(11)&p3(11)&
         p3(11)&p3(11)&p3(11)&p3(11)&
         p3(3)&p3(3)&p3(3)&p3(3)&
         p3(3)&p3(3)&p3(3)&p3(3);
gkj_4 <= g3(11)&g3(11)&g3(11)&g3(11)&
         g3(11)&g3(11)&g3(11)&g3(11)&
         g3(3)&g3(3)&g3(3)&g3(3)&
         g3(3)&g3(3)&g3(3)&g3(3);

row4: pgblackblock
      port map(pik_4, gik_4, pkj_4, gkj_4, p4, g4);

pik_5 <= p4(15 downto 8)&p3(11 downto 8)&
         p2(9 downto 8)&p1(8)&p(15);
gik_5 <= g4(15 downto 8)&g3(11 downto 8)&
         g2(9 downto 8)&g1(8)&g(15);
pkj_5 <= p4(7)&p4(7)&p4(7)&p4(7)&
         p4(7)&p4(7)&p4(7)&p4(7)&
         p4(7)&p4(7)&p4(7)&p4(7)&
         p4(7)&p4(7)&p4(7)&p4(7);
gkj_5 <= g4(7)&g4(7)&g4(7)&g4(7)&
         g4(7)&g4(7)&g4(7)&g4(7)&
         g4(7)&g4(7)&g4(7)&g4(7)&
         g4(7)&g4(7)&g4(7)&g4(7);

row5: pgblackblock
      port map(pik_5, gik_5, pkj_5, gkj_5, p5, g5);

g6 <= (g5 & g4(7 downto 0) & g3(3 downto 0) &
      g2(1 downto 0) & g1(0) & cin);

row6: subblock
      port map(g6, a, b, s);

-- generate cout
cout <= (a(31) and b(31)) or
        (g6(31) and (a(31) or b(31)));

end;

```

(continued on next page)

(continued from previous page)

SystemVerilog

```
module pandg(input  logic [30:0] a, b,
             output logic [30:0] p, g);

    assign p = a | b;
    assign g = a & b;

endmodule

module blackbox(input  logic [15:0] pleft, pright,
                gleft, gright,
                output logic [15:0] pnext, gnext);

    assign pnext = pleft & pright;
    assign gnext = pleft & gright | gleft;

endmodule

module sum(input  logic [31:0] g, a, b,
           output logic [31:0] s);

    assign s = a ^ b ^ g;

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity pgblock is
    port(a, b: in  STD_LOGIC_VECTOR(30 downto 0);
          p, g: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of pgblock is
begin
    p <= a or b;
    g <= a and b;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity pgblackblock is
    port(pik, gik, pkj, gkj:
          in  STD_LOGIC_VECTOR(15 downto 0);
          pij, gij:
          out STD_LOGIC_VECTOR(15 downto 0));
end;

architecture synth of pgblackblock is
begin
    pij <= pik and pkj;
    gij <= gik or (pik and gkj);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity sumblock is
    port(g, a, b: in  STD_LOGIC_VECTOR(31 downto 0);
          s:      out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture synth of sumblock is
begin
    s <= a xor b xor g;
end;
```

5.41 (c) Using Equation 5.11 to find the delay of the prefix adder:

$$t_{PA} = t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR}$$

We find the delays for each block:

$$t_{pg} = 100 \text{ ps}$$

$$t_{pg_prefix} = 200 \text{ ps}$$


$$t_{XOR} = 100 \text{ ps}$$

Thus,

$$t_{PA} = [100 + 5(200) + 100] \text{ ps} = 1200 \text{ ps} = \mathbf{1.2 \text{ ns}}$$

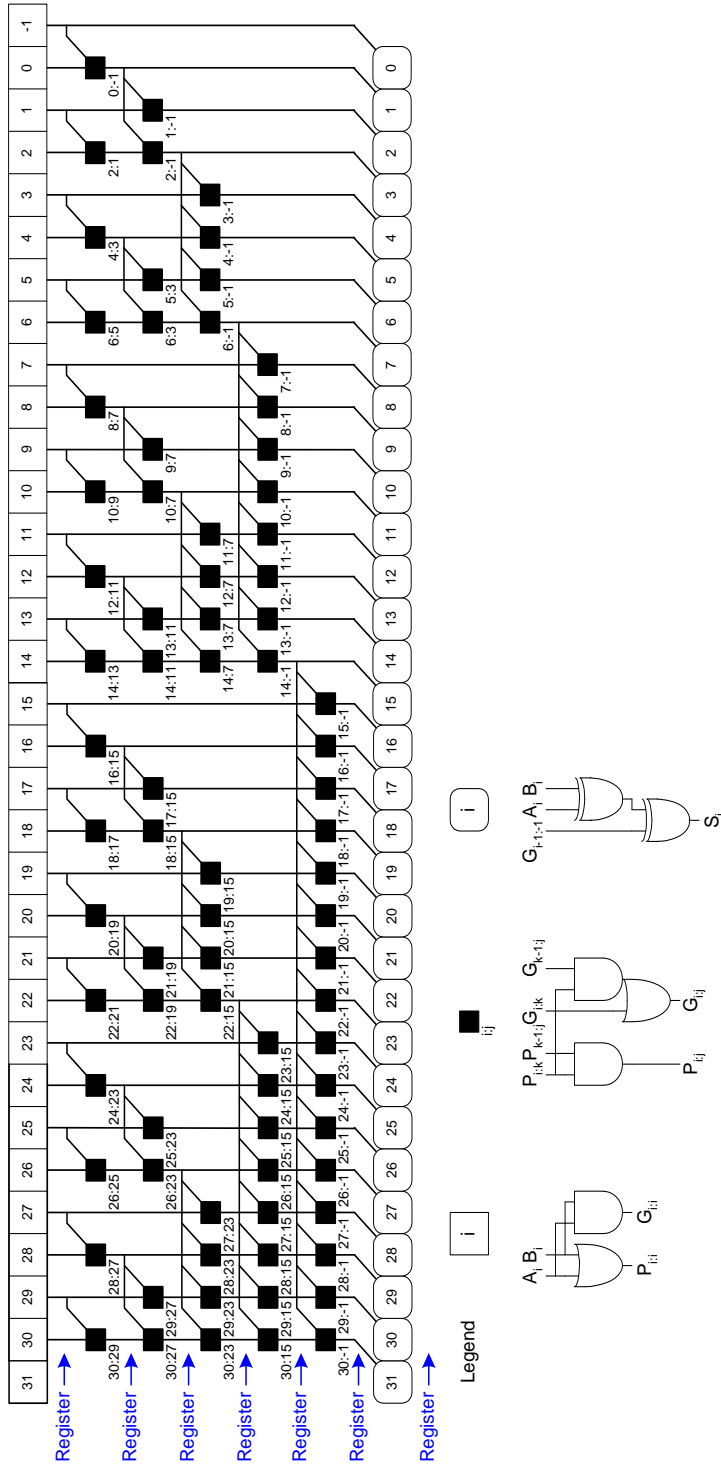5.41 (d) To make a pipelined prefix adder, add pipeline registers between each of the rows of the prefix adder. Now each stage will take 200 ps plus the

sequencing overhead, $t_{pq} + t_{\text{setup}} = 80\text{ps}$. Thus each cycle is 280 ps and the design can run at 3.57 GHz.



5.41 (e)

SystemVerilog

```

module prefixaddpipe(input  logic      clk, cin,
                    input  logic [31:0] a, b,
                    output logic [31:0] s, output cout);

    // p and g prefixes for rows 0 - 5
    logic [30:0] p0, p1, p2, p3, p4, p5;
    logic [30:0] g0, g1, g2, g3, g4, g5;
    logic p_1_0, p_1_1, p_1_2, p_1_3, p_1_4, p_1_5,
          g_1_0, g_1_1, g_1_2, g_1_3, g_1_4, g_1_5;

    // pipeline values for a and b
    logic [31:0] a0, a1, a2, a3, a4, a5,
                b0, b1, b2, b3, b4, b5;

    // row 0
    flop #(2) flop0_pg_1(clk, {1'b0,cin}, {p_1_0,g_1_0});
    pandg row0(clk, a[30:0], b[30:0], p0, g0);

    // row 1
    flop #(2) flop1_pg_1(clk, {p_1_0,g_1_0}, {p_1_1,g_1_1});
    flop #(30) flop1_pg(clk,
    {p0[29],p0[27],p0[25],p0[23],p0[21],p0[19],p0[17],p0[15],
     p0[13],p0[11],p0[9],p0[7],p0[5],p0[3],p0[1],
    g0[29],g0[27],g0[25],g0[23],g0[21],g0[19],g0[17],g0[15],
     g0[13],g0[11],g0[9],g0[7],g0[5],g0[3],g0[1]},
    {p1[29],p1[27],p1[25],p1[23],p1[21],p1[19],p1[17],p1[15],
     p1[13],p1[11],p1[9],p1[7],p1[5],p1[3],p1[1],
    g1[29],g1[27],g1[25],g1[23],g1[21],g1[19],g1[17],g1[15],
     g1[13],g1[11],g1[9],g1[7],g1[5],g1[3],g1[1]});

    blackbox row1(clk,
    {p0[30],p0[28],p0[26],p0[24],p0[22],
     p0[20],p0[18],p0[16],p0[14],p0[12],
     p0[10],p0[8],p0[6],p0[4],p0[2],p0[0]},
    {p0[29],p0[27],p0[25],p0[23],p0[21],
     p0[19],p0[17],p0[15],p0[13],p0[11],
     p0[9],p0[7],p0[5],p0[3],p0[1],1'b0},
    {g0[30],g0[28],g0[26],g0[24],g0[22],
     g0[20],g0[18],g0[16],g0[14],g0[12],
     g0[10],g0[8],g0[6],g0[4],g0[2],g0[0]},
    {g0[29],g0[27],g0[25],g0[23],g0[21],
     g0[19],g0[17],g0[15],g0[13],g0[11],
     g0[9],g0[7],g0[5],g0[3],g0[1],g_1_0},
    {p1[30],p1[28],p1[26],p1[24],p1[22],p1[20],
     p1[18],p1[16],p1[14],p1[12],p1[10],p1[8],
     p1[6],p1[4],p1[2],p1[0]},
    {g1[30],g1[28],g1[26],g1[24],g1[22],g1[20],
     g1[18],g1[16],g1[14],g1[12],g1[10],g1[8],
     g1[6],g1[4],g1[2],g1[0]});

    // row 2
    flop #(2) flop2_pg_1(clk, {p_1_1,g_1_1}, {p_1_2,g_1_2});
    flop #(30) flop2_pg(clk,
    {p1[28:27],p1[24:23],p1[20:19],p1[16:15],p1[12:11],

```



```

        p1[8:7],p1[4:3],p1[0],
g1[28:27],g1[24:23],g1[20:19],g1[16:15],g1[12:11],
g1[8:7],g1[4:3],g1[0]},
    {p2[28:27],p2[24:23],p2[20:19],p2[16:15],p2[12:11],
        p2[8:7],p2[4:3],p2[0]},
g2[28:27],g2[24:23],g2[20:19],g2[16:15],g2[12:11],
g2[8:7],g2[4:3],g2[0]}};
    blackbox row2(clk,

{p1[30:29],p1[26:25],p1[22:21],p1[18:17],p1[14:13],p1[10:9],p1[6:5],p1[2:1]
},

    { {2{p1[28]}}, {2{p1[24]}}, {2{p1[20]}}, {2{p1[16]}}, {2{p1[12]}},
    {2{p1[8]}},
    {2{p1[4]}}, {2{p1[0]}} },

{g1[30:29],g1[26:25],g1[22:21],g1[18:17],g1[14:13],g1[10:9],g1[6:5],g1[2:1]
},

    { {2{g1[28]}}, {2{g1[24]}}, {2{g1[20]}}, {2{g1[16]}}, {2{g1[12]}},
    {2{g1[8]}},
    {2{g1[4]}}, {2{g1[0]}} },

{p2[30:29],p2[26:25],p2[22:21],p2[18:17],p2[14:13],p2[10:9],p2[6:5],p2[2:1]
},

{g2[30:29],g2[26:25],g2[22:21],g2[18:17],g2[14:13],g2[10:9],g2[6:5],g2[2:1]
} );

// row 3
flop #(2) flop3_pg_1(clk, {p_1_2,g_1_2}, {p_1_3,g_1_3});
flop #(30) flop3_pg(clk, {p2[26:23],p2[18:15],p2[10:7],p2[2:0],
g2[26:23],g2[18:15],g2[10:7],g2[2:0]},
{p3[26:23],p3[18:15],p3[10:7],p3[2:0],
g3[26:23],g3[18:15],g3[10:7],g3[2:0]});
    blackbox row3(clk,
        {p2[30:27],p2[22:19],p2[14:11],p2[6:3]},
    { {4{p2[26]}}, {4{p2[18]}}, {4{p2[10]}}, {4{p2[2]}} },
    {g2[30:27],g2[22:19],g2[14:11],g2[6:3]},
    { {4{g2[26]}}, {4{g2[18]}}, {4{g2[10]}}, {4{g2[2]}} },
    {p3[30:27],p3[22:19],p3[14:11],p3[6:3]},
    {g3[30:27],g3[22:19],g3[14:11],g3[6:3]}});

// row 4
flop #(2) flop4_pg_1(clk, {p_1_3,g_1_3}, {p_1_4,g_1_4});
flop #(30) flop4_pg(clk, {p3[22:15],p3[6:0],
g3[22:15],g3[6:0]},
        {p4[22:15],p4[6:0]},
g4[22:15],g4[6:0]});

    blackbox row4(clk,
        {p3[30:23],p3[14:7]},
    { {8{p3[22]}}, {8{p3[6]}} },
        {g3[30:23],g3[14:7]},
    { {8{g3[22]}}, {8{g3[6]}} },
    {p4[30:23],p4[14:7]},
    {g4[30:23],g4[14:7]}});

// row 5
flop #(2) flop5_pg_1(clk, {p_1_4,g_1_4}, {p_1_5,g_1_5});
flop #(30) flop5_pg(clk, {p4[14:0],g4[14:0]},
        {p5[14:0],g5[14:0]});

```

190 SOLUTIONS chapter 5

```

        blackbox row5(clk,
                      p4[30:15],
                      {16{p4[14]}}},
                      g4[30:15],
                      {16{g4[14]}}},
                      p5[30:15], g5[30:15]);

    // pipeline registers for a and b
    flop #(64) flop0_ab(clk, {a,b}, {a0,b0});
    flop #(64) flop1_ab(clk, {a0,b0}, {a1,b1});
    flop #(64) flop2_ab(clk, {a1,b1}, {a2,b2});
    flop #(64) flop3_ab(clk, {a2,b2}, {a3,b3});
    flop #(64) flop4_ab(clk, {a3,b3}, {a4,b4});
    flop #(64) flop5_ab(clk, {a4,b4}, {a5,b5});

    sum row6(clk, {g5,g_1_5}, a5, b5, s);
    // generate cout
    assign cout = (a5[31] & b5[31]) | (g5[30] & (a5[31] | b5[31]));
endmodule

// submodules
module pandg(input  logic      clk,
             input  logic [30:0] a, b,
             output logic [30:0] p, g);

    always_ff @(posedge clk)
    begin
        p <= a | b;
        g <= a & b;
    end

endmodule

module blackbox(input  logic clk,
                input  logic [15:0] pleft, pright, gleft, gright,
                output logic [15:0] pnext, gnext);

    always_ff @(posedge clk)
    begin
        pnext <= pleft & pright;
        gnext <= pleft & gright | gleft;
    end

endmodule

module sum(input  logic      clk,
           input  logic [31:0] g, a, b,
           output logic [31:0] s);

    always_ff @(posedge clk)
        s <= a ^ b ^ g;
endmodule

module flop
#(parameter width = 8)
(input  logic      clk,
 input  logic [width-1:0] d,
 output logic [width-1:0] q);

    always_ff @(posedge clk)
        q <= d;
endmodule

```

5.41 (e)

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity prefixaddpipe is
  port(clk: in  STD_LOGIC;
        a, b: in  STD_LOGIC_VECTOR(31 downto 0);
        cin: in  STD_LOGIC;
        s:   out STD_LOGIC_VECTOR(31 downto 0);
        cout: out STD_LOGIC);
end;

architecture synth of prefixaddpipe is
  component pgblock
    port(clk: in  STD_LOGIC;
          a, b: in  STD_LOGIC_VECTOR(30 downto 0);
          p, g: out STD_LOGIC_VECTOR(30 downto 0));
  end component;
  component sumblock is
    port (clk:      in  STD_LOGIC;
          a, b, g: in  STD_LOGIC_VECTOR(31 downto 0);
          s:        out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component flop is generic(width: integer);
    port(clk: in  STD_LOGIC;
          d:   in  STD_LOGIC_VECTOR(width-1 downto 0);
          q:   out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  component flop1 is
    port(clk:      in  STD_LOGIC;
          d:        in  STD_LOGIC;
          q:        out STD_LOGIC);
  end component;
  component row1 is
    port(clk: in  STD_LOGIC;
          p0, g0: in  STD_LOGIC_VECTOR(30 downto 0);
          p_1_0, g_1_0: in STD_LOGIC;
          p1, g1: out STD_LOGIC_VECTOR(30 downto 0));
  end component;
  component row2 is
    port(clk: in  STD_LOGIC;
          p1, g1: in  STD_LOGIC_VECTOR(30 downto 0);
          p2, g2: out STD_LOGIC_VECTOR(30 downto 0));
  end component;
  component row3 is
    port(clk: in  STD_LOGIC;
          p2, g2: in  STD_LOGIC_VECTOR(30 downto 0);
          p3, g3: out STD_LOGIC_VECTOR(30 downto 0));
  end component;
  component row4 is
    port(clk: in  STD_LOGIC;
          p3, g3: in  STD_LOGIC_VECTOR(30 downto 0);
          p4, g4: out STD_LOGIC_VECTOR(30 downto 0));
  end component;
  component row5 is
    port(clk: in  STD_LOGIC;
          p4, g4: in  STD_LOGIC_VECTOR(30 downto 0);
          p5, g5: out STD_LOGIC_VECTOR(30 downto 0));
  end component;
```

```
-- p and g prefixes for rows 0 - 5
signal p0, p1, p2, p3, p4, p5: STD_LOGIC_VECTOR(30 downto 0);
signal g0, g1, g2, g3, g4, g5: STD_LOGIC_VECTOR(30 downto 0);

-- p and g prefixes for column -1, rows 0 - 5
signal p_l_0, p_l_1, p_l_2, p_l_3, p_l_4, p_l_5,
       g_l_0, g_l_1, g_l_2, g_l_3, g_l_4, g_l_5: STD_LOGIC;

-- pipeline values for a and b
signal a0, a1, a2, a3, a4, a5,
       b0, b1, b2, b3, b4, b5: STD_LOGIC_VECTOR(31 downto 0);

-- final generate signal
signal g5_all: STD_LOGIC_VECTOR(31 downto 0);

begin

-- p and g calculations
row0_reg: pgblock port map(clk, a(30 downto 0), b(30 downto 0), p0, g0);
row1_reg: row1 port map(clk, p0, g0, p_l_0, g_l_0, p1, g1);
row2_reg: row2 port map(clk, p1, g1, p2, g2);
row3_reg: row3 port map(clk, p2, g2, p3, g3);
row4_reg: row4 port map(clk, p3, g3, p4, g4);
row5_reg: row5 port map(clk, p4, g4, p5, g5);

-- pipeline registers for a and b
flop0_a: flop generic map(32) port map (clk, a, a0);
flop0_b: flop generic map(32) port map (clk, b, b0);
flop1_a: flop generic map(32) port map (clk, a0, a1);
flop1_b: flop generic map(32) port map (clk, b0, b1);
flop2_a: flop generic map(32) port map (clk, a1, a2);
flop2_b: flop generic map(32) port map (clk, b1, b2);
flop3_a: flop generic map(32) port map (clk, a2, a3);
flop3_b: flop generic map(32) port map (clk, b2, b3);
flop4_a: flop generic map(32) port map (clk, a3, a4);
flop4_b: flop generic map(32) port map (clk, b3, b4);
flop5_a: flop generic map(32) port map (clk, a4, a5);
flop5_b: flop generic map(32) port map (clk, b4, b5);

-- pipeline p and g for column -1
p_l_0 <= '0'; flop_l_g0: flop1 port map (clk, cin, g_l_0);
flop_l_p1: flop1 port map (clk, p_l_0, p_l_1);
flop_l_g1: flop1 port map (clk, g_l_0, g_l_1);
flop_l_p2: flop1 port map (clk, p_l_1, p_l_2);
flop_l_g2: flop1 port map (clk, g_l_1, g_l_2);
flop_l_p3: flop1 port map (clk, p_l_2, p_l_3); flop_l_g3:
flop1 port map (clk, g_l_2, g_l_3);
flop_l_p4: flop1 port map (clk, p_l_3, p_l_4);
flop_l_g4: flop1 port map (clk, g_l_3, g_l_4);
flop_l_p5: flop1 port map (clk, p_l_4, p_l_5);
flop_l_g5: flop1 port map (clk, g_l_4, g_l_5);

-- generate sum and cout
g5_all <= (g5&g_l_5);
row6: sumblock port map(clk, g5_all, a5, b5, s);

-- generate cout
cout <= (a5(31) and b5(31)) or (g5(30) and (a5(31) or b5(31)));
end;
```

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity pgblock is
  port(clk: in STD_LOGIC;
```

```

        a, b: in  STD_LOGIC_VECTOR(30 downto 0);
        p, g: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of pgblock is
begin
    process(clk) begin
        if rising_edge(clk) then
            p <= a or b;
            g <= a and b;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity blackbox is
    port(clk: in  STD_LOGIC;
          pik, pkj, gik, gkj:
              in  STD_LOGIC_VECTOR(15 downto 0);
          pij, gij:
              out STD_LOGIC_VECTOR(15 downto 0));
end;

architecture synth of blackbox is
begin
    process(clk) begin
        if rising_edge(clk) then
            pij <= pik and pkj;
            gij <= gik or (pik and gkj);
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity sumblock is
    port(clk: in  STD_LOGIC;
          g, a, b: in  STD_LOGIC_VECTOR(31 downto 0);
          s:      out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture synth of sumblock is
begin
    process(clk) begin
        if rising_edge(clk) then
            s <= a xor b xor g;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity flop is -- parameterizable flip flop
    generic(width: integer);
    port(clk:      in  STD_LOGIC;
          d:        in  STD_LOGIC_VECTOR(width-1 downto 0);
          q:        out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture synth of flop is
begin
    process(clk) begin
        if rising_edge(clk) then
            q <= d;
        end if;
    end process;
end;

```

```

        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity flop1 is -- 1-bit flip flop
    port(clk:      in  STD_LOGIC;
          d:        in  STD_LOGIC;
          q:        out STD_LOGIC);
end;

architecture synth of flop1 is
begin
    process(clk) begin
        if rising_edge(clk) then
            q <= d;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity row1 is
    port(clk:      in  STD_LOGIC;
          p0, g0: in  STD_LOGIC_VECTOR(30 downto 0);
          p_l_0, g_l_0: in STD_LOGIC;
          p1, g1: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of row1 is
    component blackbox is
        port (clk:      in  STD_LOGIC;
              pik, pkj: in STD_LOGIC_VECTOR(15 downto 0);
              gik, gkj: in STD_LOGIC_VECTOR(15 downto 0);
              pij:      out STD_LOGIC_VECTOR(15 downto 0);
              gij:      out STD_LOGIC_VECTOR(15 downto 0));
    end component;
    component flop is generic(width: integer);
        port(clk: in  STD_LOGIC;
              d:   in  STD_LOGIC_VECTOR(width-1 downto 0);
              q:   out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;

    -- internal signals for calculating p, g
    signal pik_0, gik_0, pkj_0, gkj_0,
           pij_0, gij_0: STD_LOGIC_VECTOR(15 downto 0);

    -- internal signals for pipeline registers
    signal pg0_in, pgl_out: STD_LOGIC_VECTOR(29 downto 0);

begin
    pg0_in <= (p0(29)&p0(27)&p0(25)&p0(23)&p0(21)&p0(19)&p0(17)&p0(15)&
               p0(13)&p0(11)&p0(9)&p0(7)&p0(5)&p0(3)&p0(1)&
               g0(29)&g0(27)&g0(25)&g0(23)&g0(21)&g0(19)&g0(17)&g0(15)&
               g0(13)&g0(11)&g0(9)&g0(7)&g0(5)&g0(3)&g0(1));
    flop1_pg: flop generic map(30) port map (clk, pg0_in, pgl_out);

    p1(29) <= pgl_out(29); p1(27) <= pgl_out(28); p1(25) <= pgl_out(27);
    p1(23) <= pgl_out(26);
    p1(21) <= pgl_out(25); p1(19) <= pgl_out(24); p1(17) <= pgl_out(23);
    p1(15) <= pgl_out(22); p1(13) <= pgl_out(21); p1(11) <= pgl_out(20);
    p1(9)  <= pgl_out(19); p1(7)  <= pgl_out(18); p1(5)  <= pgl_out(17);
    p1(3)  <= pgl_out(16); p1(1)  <= pgl_out(15);
    g1(29) <= pgl_out(14); g1(27) <= pgl_out(13); g1(25) <= pgl_out(12);
    g1(23) <= pgl_out(11); g1(21) <= pgl_out(10); g1(19) <= pgl_out(9);
    g1(17) <= pgl_out(8); g1(15) <= pgl_out(7); g1(13) <= pgl_out(6);

```

```

g1(11) <= pgl_out(5); g1(9) <= pgl_out(4); g1(7) <= pgl_out(3);
g1(5) <= pgl_out(2); g1(3) <= pgl_out(1); g1(1) <= pgl_out(0);

-- pg calculations
pik_0 <= (p0(30)&p0(28)&p0(26)&p0(24)&p0(22)&p0(20)&p0(18)&p0(16)&
p0(14)&p0(12)&p0(10)&p0(8)&p0(6)&p0(4)&p0(2)&p0(0));
gik_0 <= (g0(30)&g0(28)&g0(26)&g0(24)&g0(22)&g0(20)&g0(18)&g0(16)&
g0(14)&g0(12)&g0(10)&g0(8)&g0(6)&g0(4)&g0(2)&g0(0));
pkj_0 <= (p0(29)&p0(27)&p0(25)&p0(23)&p0(21)&p0(19)&p0(17)&p0(15)&
p0(13)&p0(11)&p0(9)&p0(7)&p0(5)&p0(3)&p0(1)&p_1_0);
gkj_0 <= (g0(29)&g0(27)&g0(25)&g0(23)&g0(21)&g0(19)&g0(17)&g0(15)&
g0(13)&g0(11)&g0(9)&g0(7)&g0(5)&g0(3)&g0(1)&g_1_0);

row1: blackbox port map(clk, pik_0, pkj_0, gik_0, gkj_0, pij_0, gij_0);

p1(30) <= pij_0(15); p1(28) <= pij_0(14); p1(26) <= pij_0(13);
p1(24) <= pij_0(12); p1(22) <= pij_0(11); p1(20) <= pij_0(10);
p1(18) <= pij_0(9); p1(16) <= pij_0(8); p1(14) <= pij_0(7);
p1(12) <= pij_0(6); p1(10) <= pij_0(5); p1(8) <= pij_0(4);
p1(6) <= pij_0(3); p1(4) <= pij_0(2); p1(2) <= pij_0(1); p1(0) <= pij_0(0);

g1(30) <= gij_0(15); g1(28) <= gij_0(14); g1(26) <= gij_0(13);
g1(24) <= gij_0(12); g1(22) <= gij_0(11); g1(20) <= gij_0(10);
g1(18) <= gij_0(9); g1(16) <= gij_0(8); g1(14) <= gij_0(7);
g1(12) <= gij_0(6); g1(10) <= gij_0(5); g1(8) <= gij_0(4);
g1(6) <= gij_0(3); g1(4) <= gij_0(2); g1(2) <= gij_0(1); g1(0) <= gij_0(0);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity row2 is
  port(clk:      in  STD_LOGIC;
        p1, g1: in  STD_LOGIC_VECTOR(30 downto 0);
        p2, g2: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of row2 is
  component blackbox is
    port (clk:      in  STD_LOGIC;
          pik, pkj: in  STD_LOGIC_VECTOR(15 downto 0);
          gik, gkj: in  STD_LOGIC_VECTOR(15 downto 0);
          pij:      out STD_LOGIC_VECTOR(15 downto 0);
          gij:      out STD_LOGIC_VECTOR(15 downto 0));
  end component;
  component flop is generic(width: integer);
    port(clk: in  STD_LOGIC;
          d:   in  STD_LOGIC_VECTOR(width-1 downto 0);
          q:   out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;

  -- internal signals for calculating p, g
  signal pik_l, gik_l, pkj_l, gkj_l,
        pij_l, gij_l: STD_LOGIC_VECTOR(15 downto 0);

  -- internal signals for pipeline registers
  signal pgl_in, pg2_out: STD_LOGIC_VECTOR(29 downto 0);

begin
  pgl_in <= (p1(28 downto 27)&p1(24 downto 23)&p1(20 downto 19)&
p1(16 downto 15)&
p1(12 downto 11)&p1(8 downto 7)&p1(4 downto 3)&p1(0)&
g1(28 downto 27)&g1(24 downto 23)&g1(20 downto 19)&
g1(16 downto 15)&
g1(12 downto 11)&g1(8 downto 7)&g1(4 downto 3)&g1(0));
  flop2_pg: flop generic map(30) port map (clk, pgl_in, pg2_out);

```

```

p2(28 downto 27) <= pg2_out(29 downto 28);
p2(24 downto 23) <= pg2_out(27 downto 26);
p2(20 downto 19) <= pg2_out( 25 downto 24);
p2(16 downto 15) <= pg2_out(23 downto 22);
p2(12 downto 11) <= pg2_out(21 downto 20);
p2(8  downto 7)  <= pg2_out(19 downto 18);
p2(4  downto 3)  <= pg2_out(17 downto 16);
p2(0) <= pg2_out(15);
g2(28 downto 27) <= pg2_out(14 downto 13);
g2(24 downto 23) <= pg2_out(12 downto 11);
g2(20 downto 19) <= pg2_out(10 downto 9);
g2(16 downto 15) <= pg2_out(8  downto 7);
g2(12 downto 11) <= pg2_out(6  downto 5);
g2(8  downto 7)  <= pg2_out(4  downto 3);
g2(4  downto 3)  <= pg2_out(2  downto 1); g2(0) <= pg2_out(0);

-- pg calculations
pik_1 <= (p1(30 downto 29)&p1(26 downto 25)&p1(22 downto 21)&
         p1(18 downto 17)&p1(14 downto 13)&p1(10 downto 9)&
         p1(6  downto 5)&p1(2  downto 1));
gik_1 <= (g1(30 downto 29)&g1(26 downto 25)&g1(22 downto 21)&
         g1(18 downto 17)&g1(14 downto 13)&g1(10 downto 9)&
         g1(6  downto 5)&g1(2  downto 1));
pkj_1 <= (p1(28)&p1(28)&p1(24)&p1(24)&p1(24)&p1(20)&p1(16)&p1(16)&
         p1(12)&p1(12)&p1(8)&p1(8)&p1(8)&p1(4)&p1(4)&p1(0)&p1(0));
gkj_1 <= (g1(28)&g1(28)&g1(24)&g1(24)&g1(24)&g1(20)&g1(20)&g1(16)&g1(16)&
         g1(12)&g1(12)&g1(8)&g1(8)&g1(8)&g1(4)&g1(4)&g1(0)&g1(0));

row2: blackbox
    port map(clk, pik_1, pkj_1, gik_1, gkj_1, pij_1, gij_1);

p2(30 downto 29) <= pij_1(15 downto 14);
p2(26 downto 25) <= pij_1(13 downto 12);
p2(22 downto 21) <= pij_1(11 downto 10);
p2(18 downto 17) <= pij_1(9  downto 8);
p2(14 downto 13) <= pij_1(7  downto 6); p2(10 downto 9) <= pij_1(5 downto 4);
p2(6  downto 5)  <= pij_1(3  downto 2); p2(2  downto 1) <= pij_1(1 downto 0);

g2(30 downto 29) <= gij_1(15 downto 14);
g2(26 downto 25) <= gij_1(13 downto 12);
g2(22 downto 21) <= gij_1(11 downto 10);
g2(18 downto 17) <= gij_1(9  downto 8);
g2(14 downto 13) <= gij_1(7  downto 6); g2(10 downto 9) <= gij_1(5 downto 4);
g2(6  downto 5)  <= gij_1(3  downto 2); g2(2  downto 1) <= gij_1(1 downto 0);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity row3 is
    port(clk:      in  STD_LOGIC;
          p2, g2: in  STD_LOGIC_VECTOR(30 downto 0);
          p3, g3: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of row3 is
    component blackbox is
        port (clk:      in  STD_LOGIC;
              pik, pkj: in  STD_LOGIC_VECTOR(15 downto 0);
              gik, gkj: in  STD_LOGIC_VECTOR(15 downto 0);
              pij:      out STD_LOGIC_VECTOR(15 downto 0);
              gij:      out STD_LOGIC_VECTOR(15 downto 0));
    end component;
    component flop is generic(width: integer);
        port(clk: in  STD_LOGIC;
              d:   in  STD_LOGIC_VECTOR(width-1 downto 0);

```



```
        q:   out STD_LOGIC_VECTOR(width-1 downto 0));
end component;

-- internal signals for calculating p, g
signal pik_2, gik_2, pkj_2, gkj_2,
       pij_2, gij_2: STD_LOGIC_VECTOR(15 downto 0);

-- internal signals for pipeline registers
signal pg2_in, pg3_out: STD_LOGIC_VECTOR(29 downto 0);

begin
    pg2_in <= (p2(26 downto 23)&p2(18 downto 15)&p2(10 downto 7)&
              p2(2 downto 0)&
              g2(26 downto 23)&g2(18 downto 15)&g2(10 downto 7)&g2(2 downto 0));
    flop3_pg: flop_generic map(30) port map (clk, pg2_in, pg3_out);
    p3(26 downto 23) <= pg3_out(29 downto 26);
    p3(18 downto 15) <= pg3_out(25 downto 22);
    p3(10 downto 7)  <= pg3_out(21 downto 18);
    p3(2 downto 0)   <= pg3_out(17 downto 15);
    g3(26 downto 23) <= pg3_out(14 downto 11);
    g3(18 downto 15) <= pg3_out(10 downto 7);
    g3(10 downto 7)  <= pg3_out(6 downto 3);
    g3(2 downto 0)   <= pg3_out(2 downto 0);

    -- pg calculations
    pik_2 <= (p2(30 downto 27)&p2(22 downto 19)&
              p2(14 downto 11)&p2(6 downto 3));
    gik_2 <= (g2(30 downto 27)&g2(22 downto 19)&
              g2(14 downto 11)&g2(6 downto 3));
    pkj_2 <= (p2(26)&p2(26)&p2(26)&p2(26)&
              p2(18)&p2(18)&p2(18)&p2(18)&
              p2(10)&p2(10)&p2(10)&p2(10)&
              p2(2)&p2(2)&p2(2)&p2(2));
    gkj_2 <= (g2(26)&g2(26)&g2(26)&g2(26)&
              g2(18)&g2(18)&g2(18)&g2(18)&
              g2(10)&g2(10)&g2(10)&g2(10)&
              g2(2)&g2(2)&g2(2)&g2(2));

    row3: blackbox
        port map(clk, pik_2, pkj_2, gik_2, gkj_2, pij_2, gij_2);

    p3(30 downto 27) <= pij_2(15 downto 12);
    p3(22 downto 19) <= pij_2(11 downto 8);
    p3(14 downto 11) <= pij_2(7 downto 4); p3(6 downto 3) <= pij_2(3 downto 0);
    g3(30 downto 27) <= gij_2(15 downto 12);
    g3(22 downto 19) <= gij_2(11 downto 8);
    g3(14 downto 11) <= gij_2(7 downto 4); g3(6 downto 3) <= gij_2(3 downto 0);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity row4 is
    port(clk:   in STD_LOGIC;
          p3, g3: in STD_LOGIC_VECTOR(30 downto 0);
          p4, g4: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of row4 is
    component blackbox is
        port (clk:   in STD_LOGIC;
              pik, pkj: in STD_LOGIC_VECTOR(15 downto 0);
              gik, gkj: in STD_LOGIC_VECTOR(15 downto 0);
              pij:   out STD_LOGIC_VECTOR(15 downto 0);
              gij:   out STD_LOGIC_VECTOR(15 downto 0));
    end component;
end architecture;
```

```

component flop is generic(width: integer);
  port(clk: in  STD_LOGIC;
        d:  in  STD_LOGIC_VECTOR(width-1 downto 0);
        q:  out STD_LOGIC_VECTOR(width-1 downto 0));
end component;

-- internal signals for calculating p, g
signal pik_3, gik_3, pkj_3, gkj_3,
       pij_3, gij_3: STD_LOGIC_VECTOR(15 downto 0);

-- internal signals for pipeline registers
signal pg3_in, pg4_out: STD_LOGIC_VECTOR(29 downto 0);

begin
  pg3_in <= (p3(22 downto 15)&p3(6 downto 0)&g3(22 downto 15)&g3(6 downto 0));
  flop4_pg: flop generic map(30) port map (clk, pg3_in, pg4_out);
  p4(22 downto 15) <= pg4_out(29 downto 22);
  p4(6 downto 0) <= pg4_out(21 downto 15);
  g4(22 downto 15) <= pg4_out(14 downto 7);
  g4(6 downto 0) <= pg4_out(6 downto 0);

  -- pg calculations
  pik_3 <= (p3(30 downto 23)&p3(14 downto 7));
  gik_3 <= (g3(30 downto 23)&g3(14 downto 7));
  pkj_3 <= (p3(22)&p3(22)&p3(22)&p3(22)&p3(22)&p3(22)&p3(22)&p3(22)&
            p3(6)&p3(6)&p3(6)&p3(6)&p3(6)&p3(6)&p3(6)&p3(6));
  gkj_3 <= (g3(22)&g3(22)&g3(22)&g3(22)&g3(22)&g3(22)&g3(22)&g3(22)&g3(22)&
            g3(6)&g3(6)&g3(6)&g3(6)&g3(6)&g3(6)&g3(6)&g3(6));

  row4: blackbox
    port map(clk, pik_3, pkj_3, gik_3, gkj_3, pij_3, gij_3);

  p4(30 downto 23) <= pij_3(15 downto 8);
  p4(14 downto 7) <= pij_3(7 downto 0);
  g4(30 downto 23) <= gij_3(15 downto 8);
  g4(14 downto 7) <= gij_3(7 downto 0);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity row5 is
  port(clk: in  STD_LOGIC;
        p4, g4: in  STD_LOGIC_VECTOR(30 downto 0);
        p5, g5: out STD_LOGIC_VECTOR(30 downto 0));
end;

architecture synth of row5 is
  component blackbox is
    port (clk: in  STD_LOGIC;
          pik, pkj: in  STD_LOGIC_VECTOR(15 downto 0);
          gik, gkj: in  STD_LOGIC_VECTOR(15 downto 0);
          pij: out STD_LOGIC_VECTOR(15 downto 0);
          gij: out STD_LOGIC_VECTOR(15 downto 0));
  end component;
  component flop is generic(width: integer);
    port(clk: in  STD_LOGIC;
          d:  in  STD_LOGIC_VECTOR(width-1 downto 0);
          q:  out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;

  -- internal signals for calculating p, g
  signal pik_4, gik_4, pkj_4, gkj_4,
       pij_4, gij_4: STD_LOGIC_VECTOR(15 downto 0);

  -- internal signals for pipeline registers
  signal pg4_in, pg5_out: STD_LOGIC_VECTOR(29 downto 0);

```

```
begin

  pg4_in <= (p4(14 downto 0)&g4(14 downto 0));
  flop4_pg: flop generic map(30) port map (clk, pg4_in, pg5_out);
  p5(14 downto 0) <= pg5_out(29 downto 15); g5(14 downto 0) <= pg5_out(14
downto 0);

  -- pg calculations
  pik_4 <= p4(30 downto 15);
  gik_4 <= g4(30 downto 15);
  pkj_4 <= p4(14)&p4(14)&p4(14)&p4(14)&
    p4(14)&p4(14)&p4(14)&p4(14)&
    p4(14)&p4(14)&p4(14)&p4(14)&
    p4(14)&p4(14)&p4(14)&p4(14);
  gkj_4 <= g4(14)&g4(14)&g4(14)&g4(14)&
    g4(14)&g4(14)&g4(14)&g4(14)&
    g4(14)&g4(14)&g4(14)&g4(14)&
    g4(14)&g4(14)&g4(14)&g4(14);

  row5: blackbox
    port map(clk, pik_4, gik_4, pkj_4, gkj_4, pij_4, gij_4);
    p5(30 downto 15) <= pij_4; g5(30 downto 15) <= gij_4;

end;
```

Exercise 5.42


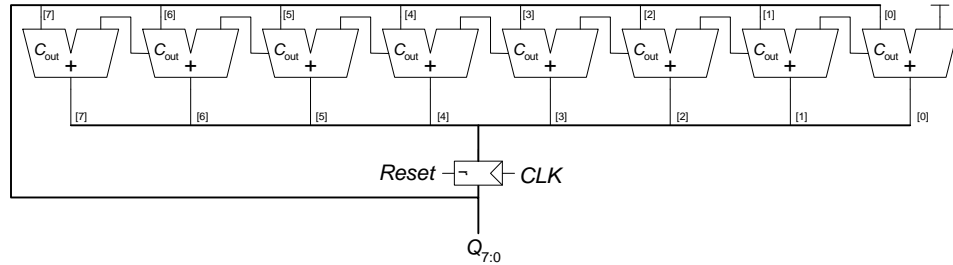


FIGURE 5.13 Incrementer built using half adders

Exercise 5.43

Exercise 5.44

 

Exercise 5.45

 


FIGURE 5.16 32-bit counter that increments by 4 or loads a new value, D

Exercise 5.46

(a)

0000

1000

1100

1110

1111

0111

0011

0001

(repeat)

(b)

$2N$. 1's shift into the left-most bit for N cycles, then 0's shift into the left bit for N cycles. Then the process repeats.

5.46 (c)

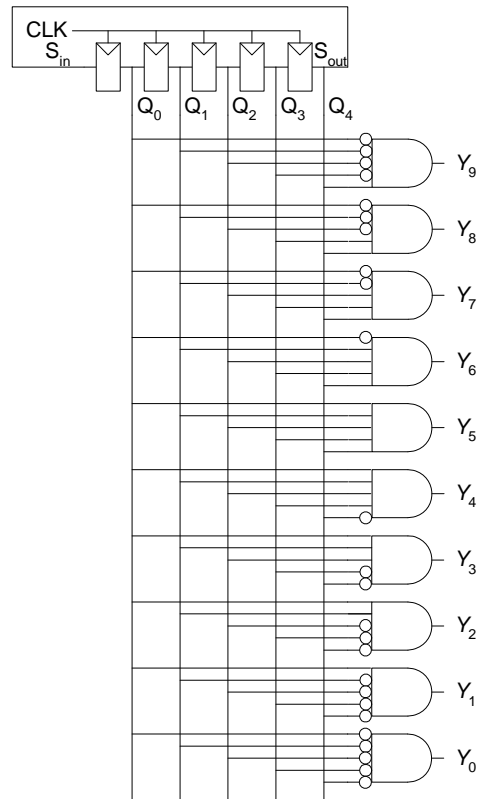


FIGURE 5.17 10-bit decimal counter using a 5-bit Johnson counter

(d) The counter uses less hardware and could be faster because it has a short critical path (a single inverter delay).

Exercise 5.47

SystemVerilog

```
module scanflop4(input logic clk, test, sin,
                 input logic [3:0] d,
                 output logic [3:0] q,
                 output logic sout);

    always_ff @(posedge clk)
        if (test)
            q <= d;
        else
            q <= {q[2:0], sin};

    assign sout = q[3];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity scanflop4 is
    port(clk, test, sin: in STD_LOGIC;
          d: in STD_LOGIC_VECTOR(3 downto 0);
          q: inout STD_LOGIC_VECTOR(3 downto 0);
          sout: out STD_LOGIC);
end;

architecture synth of scanflop4 is
begin
    process(clk, test) begin
        if rising_edge(clk) then
            if test then
                q <= d;
            else
                q <= q(2 downto 0) & sin;
            end if;
        end if;
    end process;

    sout <= q(3);
end;
```

Exercise 5.48

(a)

| value <i>a</i> _{1:0} | encoding <i>y</i> _{4:0} |
|----------------------------------|-------------------------------------|
| 00 | 00001 |
| 01 | 01010 |
| 10 | 10100 |
| 11 | 11111 |

TABLE 5.2 Possible encodings

The first two pairs of bits in the bit encoding repeat the value. The last bit is the XNOR of the two input values.

5.48 (b) This circuit can be built using a 16×2 -bit memory array, with the contents given in Table 5.3.

| address <i>a</i> _{4:0} | data <i>d</i> _{1:0} |
|------------------------------------|---------------------------------|
| 00001 | 00 |
| 00000 | 00 |
| 00011 | 00 |
| 00101 | 00 |
| 01001 | 00 |
| 10001 | 00 |
| 01010 | 01 |
| 01011 | 01 |
| 01000 | 01 |
| 01110 | 01 |
| 00010 | 01 |
| 11010 | 01 |
| 10100 | 10 |
| 10101 | 10 |
| 10110 | 10 |
| 10000 | 10 |
| 11100 | 10 |
| 00100 | 10 |
| 11111 | 11 |
| 11110 | 11 |
| 11101 | 11 |
| 11011 | 11 |
| 10111 | 11 |

TABLE 5.3 Memory array values for Exercise 5.48

| address $a_{4:0}$ | data $d_{1:0}$ |
|----------------------|-------------------|
| 01111 | 11 |
| others | XX |

TABLE 5.3 Memory array values for Exercise 5.48

5.48 (c) The implementation shown in part (b) allows the encoding to change easily. Each memory address corresponds to an encoding, so simply store different data values at each memory address to change the encoding.

Exercise 5.49

<http://www.intel.com/design/flash/articles/what.htm>

Flash memory is a nonvolatile memory because it retains its contents after power is turned off. Flash memory allows the user to electrically program and erase information. Flash memory uses memory cells similar to an EEPROM, but with a much thinner, precisely grown oxide between a floating gate and the substrate (see Figure 5.18).

Flash programming occurs when electrons are placed on the floating gate. This is done by forcing a large voltage (usually 10 to 12 volts) on the control gate. Electrons quantum-mechanically tunnel from the source through the thin oxide onto the control gate. Because the floating gate is completely insulated by oxide, the charges are trapped on the floating gate during normal operation. If electrons are stored on the floating gate, it blocks the effect of the control gate. The electrons on the floating gate can be removed by reversing the procedure, i.e., by placing a large negative voltage on the control gate.

The default state of a flash bitcell (when there are no electrons on the floating gate) is ON, because the channel will conduct when the wordline is HIGH. After the bitcell is programmed (i.e., when there are electrons on the floating gate), the state of the bitcell is OFF, because the floating gate blocks the effect of the control gate. Flash memory is a key element in thumb drives, cell phones, digital cameras, Blackberries, and other low-power devices that must retain their memory when turned off.

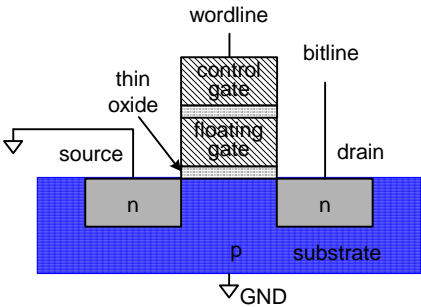


FIGURE 5.18 Flash EEPROM

Exercise 5.50

 


FIGURE 5.19 4 x 4 x 3 PLA implementing Exercise 5.44

5.50 (b)

 


FIGURE 5.20 16 x 3 ROM implementation of Exercise 5.44

5.50 (c)

SystemVerilog

```
module ex5_44c(input logic u, b, s, g,
               output logic m, j, v);

    assign m = s&g | u&b&s;
    assign j = ~u&b&~s | s&g;
    assign v = u&b&s | ~u&~s&g;
endmodule
```


VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity ex5_44c is
    port(u, b, s, g: in STD_LOGIC;
         m, j, v: out STD_LOGIC);
end;

architecture synth of ex5_44c is
begin
    m <= (s and g) or (u and b and s);
    j <= ((not u) and b and (not s)) or (s and g);
    v <= (u and b and s) or ((not u) and (not s) and g);
end;
```

Exercise 5.51

 

Exercise 5.52

 


FIGURE 5.21 4 x 8 x 3 PLA for Exercise 5.52

Exercise 5.53

- (a) Number of inputs = $2 \times 16 + 1 = 33$
Number of outputs = $16 + 1 = 17$

Thus, this would require a $2^{33} \times 17$ -bit ROM.

- (b) Number of inputs = 16
Number of outputs = 16

Thus, this would require a $2^{16} \times 16$ -bit ROM.

- (c) Number of inputs = 16
Number of outputs = 4

Thus, this would require a 2^{16} x 4-bit ROM.

All of these implementations are not good design choices. They could all be implemented in a smaller amount of hardware using discrete gates.


Exercise 5.54

- (a) Yes. Both circuits can compute any function of K inputs and K outputs.
- (b) No. The second circuit can only represent 2^K states. The first can represent more.
- (c) Yes. Both circuits compute any function of 1 input, N outputs, and 2^K states.
- (d) No. The second circuit forces the output to be the same as the state encoding, while the first one allows outputs to be independent of the state encoding.

Exercise 5.55


(a) 1 LE

| (A) | (B) | (C) | (D) | (Y) |
|--------|--------|--------|--------|------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 



(b) 2 LEs

| (B) data 1 | (C) data 2 | (D) data 3 | (E) data 4 | (X) LUT output | (A) data 1 | (X) data 2 | data 3 | data 4 | (Y) LUT output |
|---------------|---------------|---------------|---------------|-------------------|---------------|---------------|--------|--------|-------------------|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | X | X | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 | X | X | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | X | X | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | X | X | 1 |
| 0 | 1 | 0 | 0 | 1 | | | | | |
| 0 | 1 | 0 | 1 | 0 | | | | | |
| 0 | 1 | 1 | 0 | 0 | | | | | |
| 0 | 1 | 1 | 1 | 0 | | | | | |
| 1 | 0 | 0 | 0 | 1 | | | | | |
| 1 | 0 | 0 | 1 | 0 | | | | | |
| 1 | 0 | 1 | 0 | 0 | | | | | |
| 1 | 0 | 1 | 1 | 0 | | | | | |
| 1 | 1 | 0 | 0 | 1 | | | | | |
| 1 | 1 | 0 | 1 | 0 | | | | | |
| 1 | 1 | 1 | 0 | 0 | | | | | |
| 1 | 1 | 1 | 1 | 0 | | | | | |
| 1 | 1 | 1 | 1 | 0 | | | | | |

 



(c) 2 LEs

| (A) | (B) | (C) | (D) | (Y) | (A) | (B) | (C) | (D) | (Z) |
|---------------|---------------|---------------|---------------|------------|---------------|---------------|---------------|---------------|------------|
| <i>data 1</i> | <i>data 2</i> | <i>data 3</i> | <i>data 4</i> | LUT output | <i>data 1</i> | <i>data 2</i> | <i>data 3</i> | <i>data 4</i> | LUT output |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

  



(d) 2 LEs

| (A ₃) data 1 | (A ₂) data 2 | (A ₁) data 3 | (A ₀) data 4 | (D) LUT output | (A ₃) data 1 | (A ₂) data 2 | (A ₁) data 3 | (A ₀) data 4 | (P) LUT output |
|-----------------------------|-----------------------------|-----------------------------|-----------------------------|-------------------|-----------------------------|-----------------------------|-----------------------------|-----------------------------|-------------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |

  

(e) 2 LEs

| (A ₃) | (A ₂) | (A ₁) | (A ₀) | (Y ₀) | (A ₃) | (A ₂) | (A ₁) | (A ₀) | (Y ₁) |
|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output | data 1 | data 2 | data 3 | data 4 | LUT output |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

  

Exercise 5.56

(a) 8 LEs (see next page for figure)

LE 1

| | (A ₂) | (A ₁) | (A ₀) | (Y ₀) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 1 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 2

| | (A ₂) | (A ₁) | (A ₀) | (Y ₁) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 1 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 3

| | (A ₂) | (A ₁) | (A ₀) | (Y ₃) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 4

| | (A ₂) | (A ₁) | (A ₀) | (Y ₂) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 1 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 5

| | (A ₂) | (A ₁) | (A ₀) | (Y ₄) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 1 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 6









| | (A ₂) | (A ₁) | (A ₀) | (Y ₅) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 1 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 7

| | (A ₂) | (A ₁) | (A ₀) | (Y ₆) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 1 |
| X | 1 | 1 | 1 | 0 |

LE 8

| | (A ₂) | (A ₁) | (A ₀) | (Y ₇) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 1 |

        

(b) 8 LEs (see next page for figure)

LE 7

| | (A ₂) | (A ₁) | (A ₀) | (Y ₇) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 1 |

LE 6

| | (A ₂) | (A ₁) | (A ₀) | (Y ₆) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 1 |
| X | 1 | 1 | 1 | 0 |

LE 5

| | (A ₂) | (A ₁) | (A ₀) | (Y ₅) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 1 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 4

| | (A ₂) | (A ₁) | (A ₀) | (Y ₄) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 1 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 3

| | (A ₂) | (A ₁) | (A ₀) | (Y ₃) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 1 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 2









| | (A ₂) | (A ₁) | (A ₀) | (Y ₂) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 1

| | (A ₂) | (A ₁) | (A ₀) | (Y ₁) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 1 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

LE 0

| | (A ₂) | (A ₁) | (A ₀) | (Y ₀) |
|--------|-------------------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | 0 | 0 | 0 | 1 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

        

(c) 6 LEs (see next page for figure)

LE 1

| data 1 | data 2 | (A ₀) data 3 | (B ₀) data 4 | (S ₀) LUT output |
|--------|--------|-----------------------------|-----------------------------|---------------------------------|
| X | X | 0 | 0 | 0 |
| X | X | 0 | 1 | 1 |
| X | X | 1 | 0 | 1 |
| X | X | 1 | 1 | 1 |

LE 2

| data 1 | data 2 | (A ₀) data 3 | (B ₀) data 4 | (S ₁) LUT output |
|--------|--------|-----------------------------|-----------------------------|---------------------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

LE 3

| data 1 | data 2 | (A ₀) data 3 | (B ₀) data 4 | (C ₁) LUT output |
|--------|--------|-----------------------------|-----------------------------|---------------------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

LE 4







| data 1 | data 2 | (A ₂) data 3 | (B ₂) data 4 | (C ₁) LUT output |
|--------|--------|-----------------------------|-----------------------------|---------------------------------|
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 1 |
| X | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 1 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 1 |

LE 5

| data 1 | data 2 | data 3 | (B ₂) data 4 | (C ₂) LUT output |
|--------|--------|--------|-----------------------------|---------------------------------|
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 1 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 1 |
| X | 1 | 1 | 0 | 1 |
| X | 1 | 1 | 1 | 1 |


LE 6

| data 1 | data 2 | (A ₃) data 3 | (B ₃) data 4 | (S ₃) LUT output |
|--------|--------|-----------------------------|-----------------------------|---------------------------------|
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 1 |
| X | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 1 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 1 |

      


(d) 2 LEs

| | (A) | (S ₀) | (S ₁) | (S ₀ ') |
|---------------|---------------|-------------------|-------------------|--------------------|
| <i>data 1</i> | <i>data 2</i> | <i>data 3</i> | <i>data 4</i> | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 0 |
| X | 1 | 0 | 0 | 1 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 0 |
| X | 1 | 1 | 1 | 0 |

 


| | | (B) | (S ₀) | (S ₁) |
|--------|--------|--------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | X | 0 | 0 | 0 |
| X | X | 0 | 1 | 0 |
| X | X | 1 | 0 | 0 |
| X | X | 1 | 1 | 1 |

 


(e) 3 LEs


| | (S ₀) | (S ₂) | (S ₁) | (S ₂ ¹) |
|---------------|-------------------|-------------------|-------------------|--------------------------------|
| <i>data 1</i> | <i>data 2</i> | <i>data 3</i> | <i>data 4</i> | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 1 |
| X | 0 | 1 | 0 | 0 |
| X | 0 | 1 | 1 | 1 |
| X | 1 | 0 | 0 | 0 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 1 |
| X | 1 | 1 | 1 | 1 |

 

| | (S ₀) | (S ₁) | (S ₂) | (S ₁) |
|---------------|-------------------|-------------------|-------------------|-------------------|
| <i>data 1</i> | <i>data 2</i> | <i>data 3</i> | <i>data 4</i> | LUT output |
| X | 0 | 0 | 0 | 0 |
| X | 0 | 0 | 1 | 0 |
| X | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 1 | 1 |
| X | 1 | 0 | 0 | 1 |
| X | 1 | 0 | 1 | 0 |
| X | 1 | 1 | 0 | 1 |
| X | 1 | 1 | 1 | 0 |

 

| | | (S ₁) | (S ₂) | (S ₀) |
|--------|--------|-------------------|-------------------|-------------------|
| data 1 | data 2 | data 3 | data 4 | LUT output |
| X | X | 0 | 0 | 1 |
| X | X | 0 | 1 | 0 |
| X | X | 1 | 0 | 0 |
| X | X | 1 | 1 | 1 |

 

Exercise 5.57

(a) 5 LEs (2 for next state logic and state registers, 3 for output logic)

(b)

$$\begin{aligned} t_{pd} &= t_{pd_LE} + t_{wire} \\ &= (381 + 246) \text{ ps} \\ &= 627 \text{ ps} \end{aligned}$$

$$\begin{aligned} T_c &\geq t_{pcq} + t_{pd} + t_{setup} \\ &\geq [199 + 627 + 76] \text{ ps} \\ &= 902 \text{ ps} \end{aligned}$$

$$f = 1 / 902 \text{ ps} = \mathbf{1.1 \text{ GHz}}$$

(c)

First, we check that there is no hold time violation with this amount of clock skew.

$$\begin{aligned} t_{cd_LE} &= t_{pd_LE} = 381 \text{ ps} \\ t_{cd} &= t_{cd_LE} + t_{wire} = 627 \text{ ps} \end{aligned}$$

$$\begin{aligned} t_{skew} &< (t_{ccq} + t_{cd}) - t_{hold} \\ &< [(199 + 627) - 0] \text{ ps} \\ &< \mathbf{826 \text{ ps}} \end{aligned}$$

3 ns is less than 826 ps, so there is no hold time violation.

Now we find the fastest frequency at which it can run.

$$\begin{aligned} T_c &\geq t_{pcq} + t_{pd} + t_{setup} + t_{skew} \\ &\geq [0.902 + 3] \text{ ns} \\ &= 3.902 \text{ ns} \end{aligned}$$

$$f = 1 / 3.902 \text{ ns} = \mathbf{256 \text{ MHz}}$$

Exercise 5.58

(a) 2 LEs (1 for next state logic and state register, 1 for output logic)

(b) Same as answer for Exercise 5.57(b)

(c) Same as answer for Exercise 5.57(c)

Exercise 5.59

First, we find the cycle time:

$$T_c = 1/f = 1/100 \text{ MHz} = 10 \text{ ns}$$

$$\begin{aligned} T_c &\geq t_{pcq} + N t_{LE+wire} + t_{setup} \\ 10 \text{ ns} &\geq [0.199 + N(0.627) + 0.076] \text{ ns} \end{aligned}$$

Thus, $N \leq 15.5$

The maximum number of LEs on the critical path is **15**.

With at most one LE on the critical path and no clock skew, the fastest the FSM will run is:

$$\begin{aligned} T_c &\geq [0.199 + 0.627 + 0.076] \text{ ns} \\ &\geq 0.902 \text{ ns} \\ f &= 1 / 0.902 \text{ ns} = \mathbf{1.1 \text{ GHz}} \end{aligned}$$

Question 5.1

$$(2^N - 1)(2^N - 1) = 2^{2N} - 2^{N+1} + 1$$

Question 5.2

A processor might use BCD representation so that decimal numbers, such as 1.7, can be represented exactly.

Question 5.3

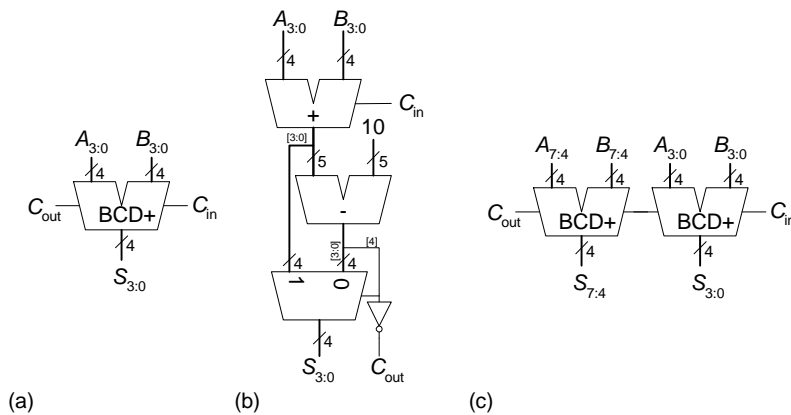


FIGURE 5.22 BCD adder: (a) 4-bit block, (b) underlying hardware, (c) 8-bit BCD adder

(continued from previous page)

SystemVerilog

```
module bcdadd_8(input  logic [7:0] a, b,
               input  logic      cin,
               output logic [7:0] s,
               output logic      cout);

    logic c0;

    bcdadd_4 bcd0(a[3:0], b[3:0], cin, s[3:0], c0);
    bcdadd_4 bcd1(a[7:4], b[7:4], c0, s[7:4], cout);

endmodule

module bcdadd_4(input  logic [3:0] a, b,
               input  logic      cin,
               output logic [3:0] s,
               output logic      cout);

    logic [4:0] result, sub10;

    assign result = a + b + cin;
    assign sub10 = result - 10;

    assign cout = ~sub10[4];
    assign s = sub10[4] ? result[3:0] : sub10[3:0];

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity bcdadd_8 is
    port(a, b: in  STD_LOGIC_VECTOR(7 downto 0);
          cin: in  STD_LOGIC;
          s:   out STD_LOGIC_VECTOR(7 downto 0);
          cout: out STD_LOGIC);
end;

architecture synth of bcdadd_8 is
    component bcdadd_4
        port(a, b: in  STD_LOGIC_VECTOR(3 downto 0);
              cin: in  STD_LOGIC;
              s:   out STD_LOGIC_VECTOR(3 downto 0);
              cout: out STD_LOGIC);
    end component;
    signal c0: STD_LOGIC;
begin

    bcd0: bcdadd_4
        port map(a(3 downto 0), b(3 downto 0), cin, s(3
downto 0), c0);
    bcd1: bcdadd_4
        port map(a(7 downto 4), b(7 downto 4), c0, s(7
downto 4), cout);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;

entity bcdadd_4 is
    port(a, b: in  STD_LOGIC_VECTOR(3 downto 0);
          cin: in  STD_LOGIC;
          s:   out STD_LOGIC_VECTOR(3 downto 0);
          cout: out STD_LOGIC);
end;

architecture synth of bcdadd_4 is
    signal result, sub10, a5, b5: STD_LOGIC_VECTOR(4
downto 0);
begin
    a5 <= '0' & a;
    b5 <= '0' & b;
    result <= a5 + b5 + cin;
    sub10 <= result - "01010";

    cout <= not (sub10(4));
    s <= result(3 downto 0) when sub10(4) = '1'
        else sub10(3 downto 0);

end;
```

CHAPTER 6

Exercise 6.1

(1) Simplicity favors regularity:

- Each instruction has a 6-bit opcode.
- MIPS has only 3 instruction formats (R-Type, I-Type, J-Type).
- Each instruction format has the same number and order of operands (they differ only in the opcode).
- Each instruction is the same size, making decoding hardware simple.

(2) Make the common case fast.

- Registers make the access to most recently accessed variables fast.
- The RISC (reduced instruction set computer) architecture, makes the common/simple instructions fast because the computer must handle only a small number of simple instructions.
- Most instructions require all 32 bits of an instruction, so all instructions are 32 bits (even though some would have an advantage of a larger instruction size and others a smaller instruction size). The instruction size is chosen to make the common instructions fast.

(3) Smaller is faster.

- The register file has only 32 registers.

- The ISA (instruction set architecture) includes only a small number of commonly used instructions. This keeps the hardware small and, thus, fast.
 - The instruction size is kept small to make instruction fetch fast.
- (4) Good design demands good compromises.
- MIPS uses three instruction formats (instead of just one).
 - Ideally all accesses would be as fast as a register access, but MIPS architecture also supports main memory accesses to allow for a compromise between fast access time and a large amount of memory.
 - Because MIPS is a RISC architecture, it includes only a set of simple instructions, it provides pseudocode to the user and compiler for commonly used operations, like moving data from one register to another (`move`) and loading a 32-bit immediate (`li`).

Exercise 6.2

Yes, it is possible to design a computer architecture without a register set. For example, an architecture could use memory as a very large register set. Each instruction would require a memory access. For example, an add instruction might look like this:


```
add 0x10, 0x20, 0x24
```

This would add the values stored at memory addresses 0x20 and 0x24 and place the result in memory address 0x10. Other instructions would follow the same pattern, accessing memory instead of registers. Some advantages of the architecture are that it would require fewer instructions. Load and store operations are now unnecessary. This would make the decoding hardware simpler and faster.

Some disadvantages of this architecture over the MIPS architecture is that each operation would require a memory access. Thus, either the processor would need to be slow or the memory small. Also, because the instructions must encode memory addresses instead of register numbers, the instruction size would be large in order to access all memory addresses. Or, alternatively, each instruction can only access a smaller number of memory addresses. For example, the architecture might require that one of the source operands is also a destination operand, reducing the number of memory addresses that must be encoded.


Exercise 6.3

- (a) $42 \times 4 = 42 \times 2^2 = 101010_2 \ll 2 = 10101000_2 = 0xA8$
(b) 0xA8 through 0xAB
(c)

 

Exercise 6.4

- (a) $15 \times 4 = 42 \times 2^2 = 1111_2 \ll 2 = 111100_2 = 0x3C$
(b) 0x3C through 0x3F
(c)

 

Exercise 6.5

```
# Big-endian
li    $t0, 0xABCD9876
sw    $t0, 100($0)
lb    $s5, 101($0) # the LSB of $s5 = 0xCD

# Little-endian
li    $t0, 0xABCD9876
sw    $t0, 100($0)
lb    $s5, 101($0) # the LSB of $s5 = 0x98
```

In big-endian format, the bytes are numbered from 100 to 103 from left to right. In little-endian format, the bytes are numbered from 100 to 103 from right to left. Thus, the final load byte (lb) instruction returns a different value depending on the endianness of the machine.

Exercise 6.6

- (a) 0x53 4F 53 00
(b) 0x43 6F 6F 6C 21 00


(c) 0x41 6C 79 73 73 61 00 (depends on the persons name)

Exercise 6.7


- (a) 0x68 6F 77 64 79 00
- (b) 0x6C 69 6F 6E 73 00
- (c) 0x54 6F 20 74 68 65 20 72 65 73 63 75 65 21 00

Exercise 6.8


Little-Endian Memory

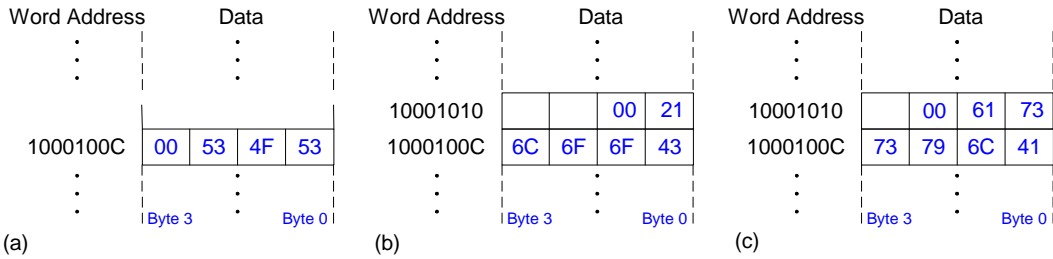

Big-Endian Memory

 

Exercise 6.9

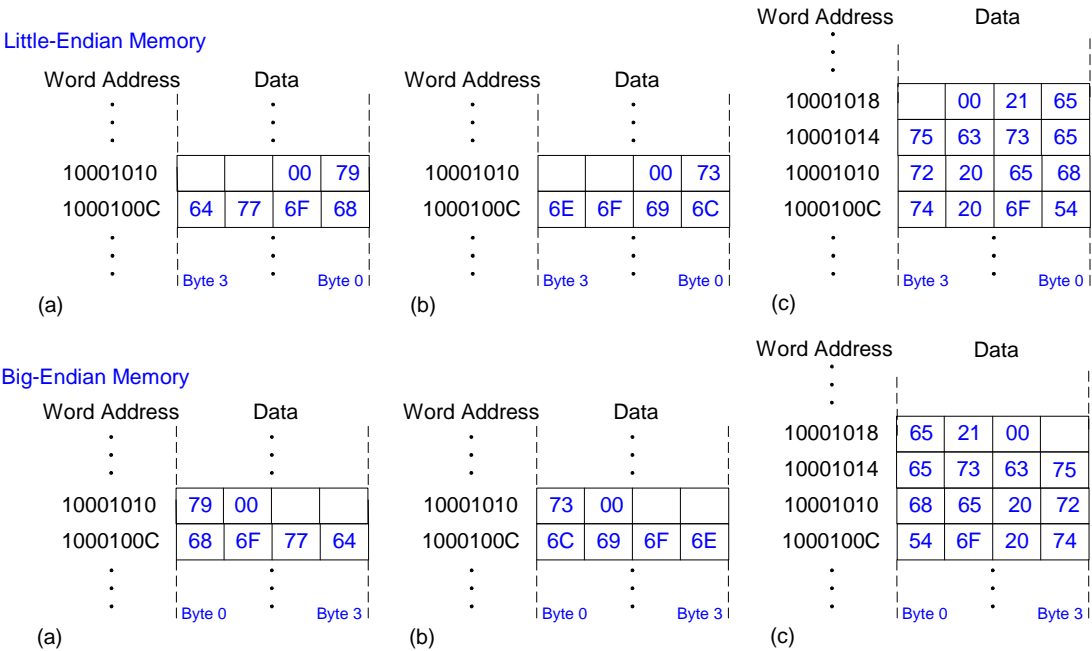

Exercise 6.10

0x02114020
0x8de80020
0x2010fff6

Exercise 6.11

0x20100049
0xad49fff9
0x02f24822

Exercise 6.12

(a)
lw \$t0, 0x20(\$t7)
addi \$s0, \$0, -10
(b)
0x8de80020 (lw)
0x2010fff6 (addi)

Exercise 6.13

(a)
addi \$s0, \$0, 73
sw \$t1, -7(\$t2)

(b)
0x20100049 (addi)
0xad49fff9 (sw)

Exercise 6.14

The program is:

| | | | |
|--------------|------------|---------|-----------------------|
| [0x00400000] | 0x20080000 | | addi \$t0, \$0, 0 |
| [0x00400004] | 0x20090001 | | addi \$t1, \$0, 1 |
| [0x00400008] | 0x0089502a | loop: | slt \$t2, \$a0, \$t1 |
| [0x0040000c] | 0x15400003 | | bne \$t2, \$0, finish |
| [0x00400010] | 0x01094020 | | add \$t0, \$t0, \$t1 |
| [0x00400014] | 0x21290002 | | addi \$t1, \$t1, 2 |
| [0x00400018] | 0x08100002 | | j loop |
| [0x0040001c] | 0x01001020 | finish: | add \$v0, \$t0, \$0 |

An equivalent C program would be (assuming temp = \$t0, i = \$t1, n = \$a0, result = \$v0):

```
temp = 0;
for (i = 1; i <= n; i = i+2)
    temp = temp + i;

result = temp;
```

This program sums the odd integers up to n and places the result in the return register, \$v0.

Exercise 6.15

```
addi $t0, $0, 31
L1:
srlv $t1, $a0, $t0
andi $t1, $t1, 1
slt $t1, $0, $t1
```

```
sb $t1, 0($a1)
addi $a1, $a1, 1
addi $t0, $t0, -1
bgez $t0, L1
jr $ra
```

(a) This program converts a number (\$a0) from decimal to binary and stores it in an array pointed to by \$a1.

```
void convert2bin(int num, char binarray[])
{
    int i;
    char tmp, val = 31;

    for (i=0; i<32; i++) {
        tmp = (num >> val) & 1;
        binarray[i] = tmp;
        val--;
    }
}
```

Exercise 6.16

```
ori $t0, $t1, 0xF234
nor $t0, $t0, $0
```

Exercise 6.17

(a)

```
# $s0=g, $s1=h
slt $t0, $s1, $s0      # if h < g, $t0 = 1
beq $t0, $0, else      # if $t0 == 0, do else
add $s0, $s0, $s1      # g = g + h
j done                 # jump past else block
else:sub $s0, $s0, $s1  # g = g - h
done:
```

(b)

```
slt $t0, $s0, $s1      # if g < h, $t0 = 1
bne $t0, $0, else      # if $t0 != 0, do else
addi $s0, $s0, 1        # g = g + 1
j done                 # jump past else block
else: addi $s1, $s1, -1  # h = h - 1
done:
```

```
(c)
slt $t0, $s1, $s0 # if h < g, $t0 = 1
bne $t0, $0, else # if $t0 != 0, do else
add $s0, $0, $0   # g = 0
j  done           # jump past else block
else:  sub $s1, $0, $0 # h = 0
done:
```

Exercise 6.18

```
int find42( int array[], int size)
{
    int i;        // index into array

    for (i = 0; i < size; i = i+1)
        if (array[i] == 42)
            return i;

    return -1;
}
```

Exercise 6.19

```
(a)
# MIPS assembly code
# base address of array dst = $a0
# base address of array src = $a1
# i = $s0


strcpy:
    addi $sp, $sp, -4
    sw   $s0, 0($sp) # save $s0 on the stack
    add  $s0, $0, $0 # i = 0

loop:
    add  $t1, $a1, $s0 # $t1 = address of src[i]
    lb   $t2, 0($t1)   # $t2 = src[i]
    add  $t3, $a0, $s0 # $t3 = address of dst[i]
    sb   $t2, 0($t3)   # dst[i] = src[i]
    beq  $t2, $0, done # check for null character
```

```
addi $s0, $s0, 1    # i++
j     loop

done:
    lw  $s0, 0($sp)   # restore $s0 from stack
    addi $sp, $sp, 4  # restore stack pointer
    jr  $ra           # return
```

(b) The stack (i) before, (ii) during, and (iii) after the strcpy procedure call.

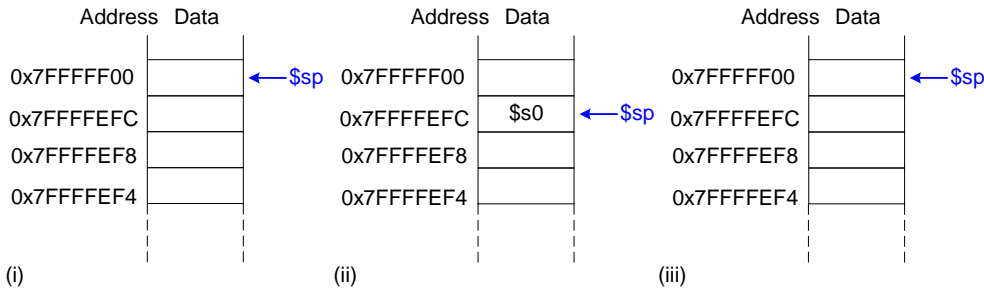

Exercise 6.20


```
find42: addi $t0, $0, 0    # $t0 = i = 0
        addi $t1, $0, 42   # $t1 = 42
loop:   slt  $t3, $t0, $a1  # $t3 = 1 if i < size (not at end of array)
        beq  $t3, $0, exit  # if reached end of array, return -1
        sll  $t2, $t0, 2    # $t2 = i*4
        add  $t2, $t2, $a0  # $t2 = address of array[i]
        lw   $t2, 0($t2)    # $t2 = array[i]
        beq  $t2, $t1, done  # $t2 == 42?
        addi $t0, $t0, 1    # i = i + 1
        j    loop
done:   add  $v0, $t0, $0    # $v0 = i
        jr   $ra
exit:   addi $v0, $0, -1    # $v0 = -1
        jr   $ra
```

Exercise 6.21

(a) The stack frames of each procedure are:
proc1: 3 words deep (for \$s0 - \$s1, \$ra)
proc2: 7 words deep (for \$s2 - \$s7, \$ra)
proc3: 4 words deep (for \$s1 - \$s3, \$ra)

proc4: 0 words deep (doesn't use any saved registers or call other procedures)

(b) Note: we arbitrarily chose to make the initial value of the stack pointer 0x7FFFFFF04 just before the procedure calls.

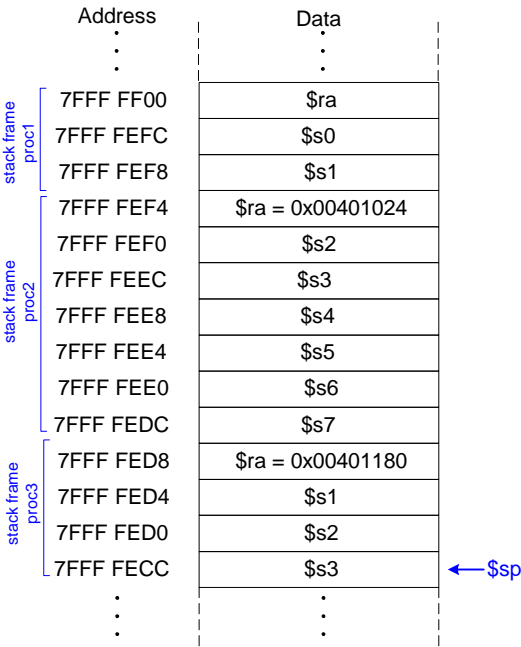

Exercise 6.22

(a)
fib(0) = 0
fib(-1) = 1

```
(b)
int fib(int n)
{
    int prevresult = 1;           // fib(n-1)
    int result = 0;               // fib(n)

    while (n != 0) {              // calculate new fibonacci number
        result = result + prevresult; // fib(n) = fib(n-1) + fib(n-2)
        prevresult = result - prevresult; // fib(n-1) = fib(n) - fib(n-2)
        n = n - 1;
    }
    return result;
}
```

(c)

```
# fib.asm
# 2/21/07 Sarah Harris (Sarah_Harris@hmc.edu)
#
# The fib() procedure computes the nth Fibonacci number.
# n is passed to fib() in $a0, and fib() returns the result in $v0.

main:  addi $a0,$0,9      # initialize procedure argument: n = 9
       jal  fib          # call fibonacci procedure
       ...              # more code
fib:   addi $t0,$0,1      # $t0 = fib(n-1) = fib(-1) = 1
       addi $t1,$0,0      # $t1 = fib(n) = fib(0) = 0
loop:  beq  $a0,$0, end   # done?
       add  $t1,$t1,$t0    # Compute next Fib #, fib(n)
       sub  $t0,$t1,$t0    # Update fib(n-1)
       addi $a0,$a0,-1     # decrement n
       j    loop          # Repeat
end:   add  $v0,$t1,$0     # Put result in $v0
       jr   $ra           # return result
```

Exercise 6.23

(a) 120

(b) 2

(c)

(i) 3 - returned value is 1

(ii) 2 (depending on what's stored on the stack frame of the callee's stack)

(iii) 4

Exercise 6.24

(a) \$v0 ends with 19, as desired.

(b) The program will (2) crash. The jump register instruction (`jr $ra`) at instruction address 0x0040004c will return to the most recent value of `$ra` (0x00400030). It will then repeatedly restore values from the stack and increment the stack pointer. Eventually the stack shrinks beyond the dynamic data segment and the program crashes.

(c)

i: The program will (3) produce an incorrect value in `$v0`. `a` (`$a0`) is not restored, but instead holds the value 3 passed to `f2`. So `f` computes

$$j + a + f2(b) = 5 + 3 + 3 \cdot 3 = 17$$

ii: The program will (4) run correctly despite the deleted lines. `b` is not restored, but is never used again.

iii: (4) `$s0` is not restored. This could corrupt a calling procedure that depended on `$s0` being saved, but does not directly corrupt the result of `f`.

iv: (1) Now `f2` does not move and restore the stack pointer, so values saved to the stack get overwritten. When `f2` tries to return, it always finds `$ra`

pointing to 0x04000078. Therefore, we enter an infinite loop from 0x04000078 to 0x0400008c

v: (3) \$s0 is overwritten with the value 3 in f2 and not restored. Thus, when we return to f1, j=3 instead of the desired 5. So $j + a + f2(b) = 3 + 5 + 3*3 = 17$

vi: (2) As in case iv, \$ra is left pointing to 0x04000078 rather than 0x04000030 when we are all done with the recursion on f2. Therefore, we get in an infinite loop from 0x04000078 to 0x0400008c. However, on each loop \$sp is incremented by 12. Eventually it points to an illegal memory location and the program crashes.

vii: (4) x is not restored in f2 after it recursively calls itself. But x is not used after the recursive call, so the program still produces the correct answer.

Exercise 6.25

- (a) 000100 01000 10001 0000 0000 0000 0010
 = **0x11110002**
- (b) 000100 01111 10100 0000 0100 0000 1111
 = **0x11F4040F**
- (c) 000100 11001 10111 1111 1000 0100 0010
 = **0x1337F842**
- (d) 000011 0000 0100 0001 0001 0100 0111 11
 = **0x0C10451F**
- (e) 000010 00 0001 0000 0000 1100 0000 0001
 = **0x08100C01**

Exercise 6.26

- (a)
- | | | | |
|------------|------------|-----------------|--------------|
| 0x00400028 | add | \$a0, \$a1, \$0 | # 0x00a02020 |
| 0x0040002c | jal | f2 | # 0x0C10000D |
| 0x00400030 | f1: jr | \$ra | # 0x03e00008 |
| 0x00400034 | f2: sw | \$s0, 0(\$s2) | # 0xae500000 |
| 0x00400038 | bne | \$a0, \$0, else | # 0x14800001 |
| 0x0040003c | j | f1 | # 0x0810000C |
| 0x00400040 | else: addi | \$a0, \$a0, -1 | # 0x2084FFFF |
| 0x00400044 | j | f2 | # 0x0810000D |
-
- (b)
- | | | | |
|------------|------------|-----------------|-------------------|
| 0x00400028 | add | \$a0, \$a1, \$0 | # register only |
| 0x0040002c | jal | f2 | # pseudo-direct |
| 0x00400030 | f1: jr | \$ra | # register only |
| 0x00400034 | f2: sw | \$s0, 0(\$s2) | # base addressing |
| 0x00400038 | bne | \$a0, \$0, else | # PC-relative |
| 0x0040003c | j | f1 | # pseudo-direct |
| 0x00400040 | else: addi | \$a0, \$a0, -1 | # immediate |
| 0x00400044 | j | f2 | # pseudo-direct |

Exercise 6.27

(a)

```

set_array:  addi $sp,$sp,-52    # move stack pointer
            sw  $ra,48($sp)    # save return address
            sw  $s0,44($sp)    # save $s0
            sw  $s1,40($sp)    # save $s1


            add  $s0,$0,$0      # i = 0
            addi $s1,$0,10      # max iterations = 10
loop:       add  $a1,$s0,$0      # pass i as parameter
            jal  compare        # call compare(num, i)
            sll  $t1,$s0,2       # $t1 = i*4
            add  $t2,$sp,$t1     # $t2 = address of array[i]
            sw   $v0,0($t2)      # array[i] = compare(num, i);
            addi $s0,$s0,1       # i++
            bne  $s0,$s1,loop    # if i<10, goto loop

            lw   $s1,40($sp)     # restore $s1
            lw   $s0,44($sp)     # restore $s0
            lw   $ra,48($sp)     # restore return address
            addi $sp,$sp,52      # restore stack pointer
            jr   $ra            # return to point of call

compare:    addi $sp,$sp,-4      # move stack pointer
            sw   $ra,0($sp)      # save return address on the stack
            jal  subtract        # input parameters already in $a0,$a1
            slt  $v0,$v0,$0      # $v0=1 if sub(a,b) < 0 (return 0)
            slti $v0,$v0,1       # $v0=1 if sub(a,b)>=0, else $v0 = 0
            lw   $ra,0($sp)      # restore return address
            addi $sp,$sp,4       # restore stack pointer
            jr   $ra            # return to point of call

subtract:   sub  $v0,$a0,$a1     # return a-b
            jr   $ra            # return to point of call
    
```

6.27 (b)

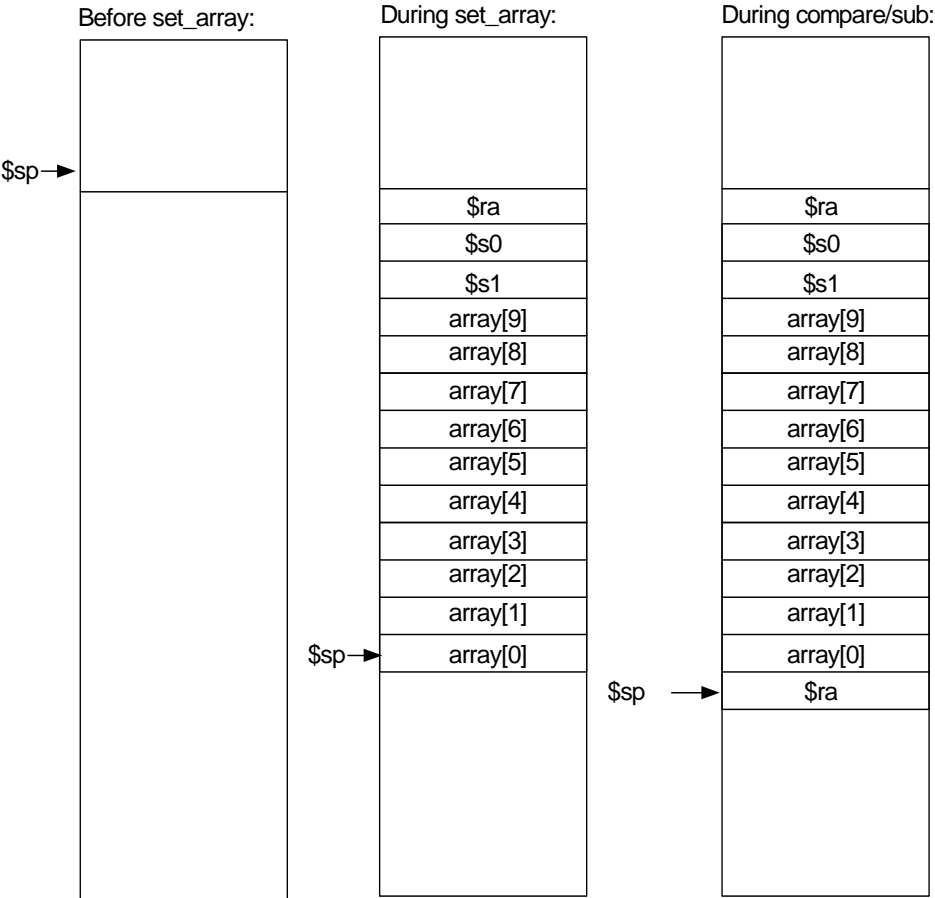

(c) If `$ra` were never stored on the stack, the compare function would return to the instruction after the call to subtract (`slt $v0, $v0, $0`) instead of returning to the `set_array` function. The program would enter an infinite loop in the compare function between `jr $ra` and `slt $v0, $v0, $0`. It would increment the stack during that loop until the stack space was exceeded and the program would likely crash.

Exercise 6.28

(a)


```
# MIPS assembly code
0x400100 f:      addi $sp, $sp, -16 # decrement stack
```

```
0x400104      sw    $a0, 0xc($sp) # save registers on stack
0x400108      sw    $a1, 0x8($sp)
0x40010C      sw    $ra, 0x4($sp)
0x400110      sw    $s0, 0x0($sp)
0x400114      addi  $s0, $a1, 2    # b = k + 2
0x400118      bne  $a0, $0, else   # if (n!=0) do else block
0x40011C      addi  $s0, $0, 10    # b = 10
0x400120      j     done

0x400124 else: addi  $a0, $a0, -1   # update arguments
0x400128      addi  $a1, $a1, 1
0x40012C      jal   f              # call f()
0x400130      lw    $a0, 0xc($sp)  # restore arguments
0x400134      lw    $a1, 0x8($sp)
0x400138      mult  $a0, $a0       # {[hi],[lo]} = n*n
0x40013C      mflo  $t0            # $t0 = lo (assuming 32-bit result)
0x400140      add  $s0, $s0, $t0   # b = b + n*n
0x400144      add  $s0, $s0, $v0   # b = b + n*n + f(n-1,k+1)

0x400148 done: mult  $s0, $a1      # {[hi],[lo]} = b * k
0x40014C      mflo  $v0            # $v0 = lo (assuming 32-bit result)
0x400150      lw    $ra, 0x4($sp)  # restore registers
0x400154      lw    $s0, 0x0($sp)
0x400158      addi  $sp, $sp, 16    # restore stack pointer
0x40015C      jr    $ra           # return
```

6.28 (b) The stack (i) after the last recursive call, and (ii) after return. The final value of `$v0` is 1400.

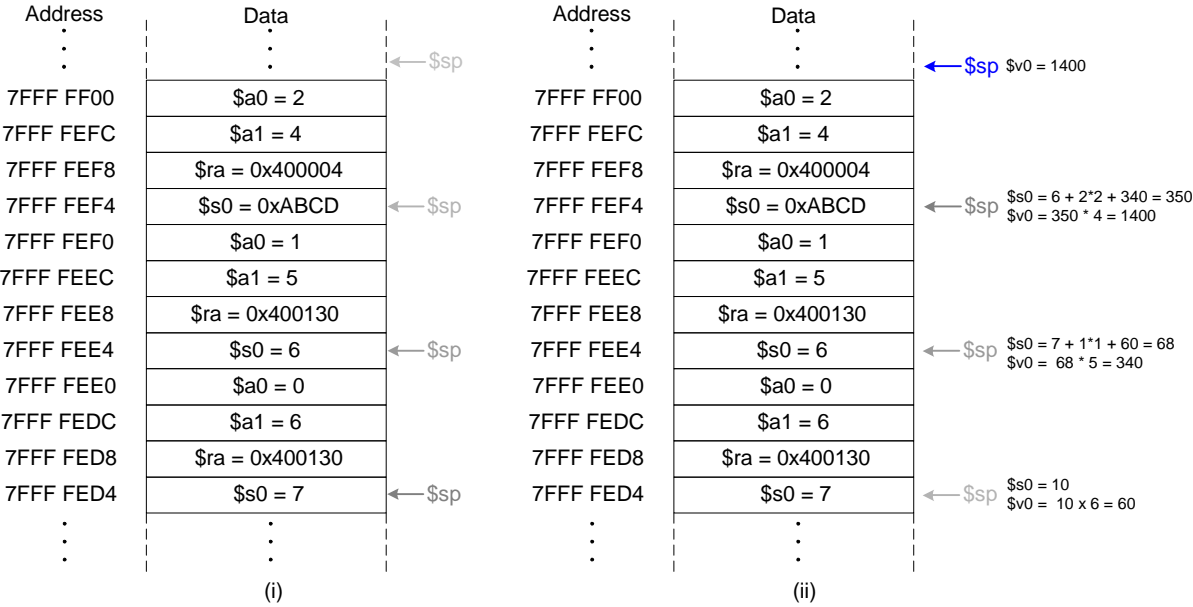

Exercise 6.29

Instructions (32 K - 1) words before the branch to instructions 32 K words after the branch instruction.

Exercise 6.30

(a) In the worst case, a jump instruction can only jump one instruction forward. For example, the following code is impossible. The jump instruction (`j loop`) below can only jump forward to `0x0FFFFFFC` (at most).

```
0x0FFFFFF8      j    loop
0x0FFFFFFC
0x10000000 loop:  ...
```

(b) In the best case, a jump instruction can jump forward 2^{26} instructions. For example,

```
0x0FFFFFFC      j    loop
0x10000000      ...
0x1FFFFFFC loop:  ...
```

(c)

In the worst case, a jump instruction cannot jump backward. For example, the following code is impossible. Because the jump instruction appends the four most significant bits of `PC + 4`, this jump instruction cannot even jump to itself, let alone further backwards.

```
0x0FFFFFFC loop: j    loop
0x10000000      ...
```

(d) In the best case, a jump instruction can jump backward at most $2^{26} - 2$ instructions. For example,

```
0x10000000 loop: ...
...          ...
0x1FFFFFF8      j    loop
```

Exercise 6.31

It is advantageous to have a large address field in the machine format for jump instructions to increase the range of instruction addresses to which the instruction can jump.

Exercise 6.32

```
0x00400000          j Loop1
...
0x0FFFFFFC    Loop1:  j Loop2
...
0x10400000    Loop2:  ...
```

Another option:

```
0x00400000    lui $t1, 0x1040
0x00400004    jr  $t1
```

Exercise 6.33

```
# high-level code
void little2big(int[] array)
{
    int i;

    for (i = 0; i < 10; i = i + 1) {
        array[i] = ((array[i] & 0xFF) << 24) ||
                    (array[i] & 0xFF00) << 8) ||
                    (array[i] & 0xFF0000) >> 8) ||
                    ((array[i] >> 24) & 0xFF));
    }
}

# MIPS assembly code
# $a0 = base address of array
little2big:
    addi $t5, $0, 10    # $t5 = i = 10 (loop counter)
loop:   lb  $t0, 0($a0)  # $t0 = array[i] byte 0
        lb  $t1, 1($a0)  # $t1 = array[i] byte 1
        lb  $t2, 2($a0)  # $t2 = array[i] byte 2
        lb  $t3, 3($a0)  # $t3 = array[i] byte 3
        sb  $t3, 0($a0)  # array[i] byte 0 = previous byte 3
        sb  $t2, 1($a0)  # array[i] byte 1 = previous byte 2
        sb  $t1, 2($a0)  # array[i] byte 2 = previous byte 1
        sb  $t0, 3($a0)  # array[i] byte 3 = previous byte 0
        addi $a0, $a0, 4  # increment index into array
        addi $t5, $t5, -1 # decrement loop counter
        beq  $t5, $0, done
        j    loop
done:
```

Exercise 6.34

(a)

```
void concat(char[] string1, char[] string2, char[] stringconcat)
{
    int i, j;
    i = 0;
    j = 0;

    while (string1[i] != 0) {
        stringconcat[i] = string1[i];
        i = i + 1;
    }
    while (string2[j] != 0) {
        stringconcat[i] = string2[j];
        i = i + 1;
        j = j + 1;
    }
    stringconcat[i] = 0; // append null at end of string
}
```

(b)

```
concat: lb    $t0, 0($a0)      # $t0 = string1[i]
        beq   $t0, $0, string2 # if end of string1, go to string2
        sb    $t0, 0($a2)      # stringconcat[i] = string1[i]
        addi  $a0, $a0, 1      # increment index into string1
        addi  $a2, $a2, 1      # increment index into stringconcat
        j     concat          # loop back
string2: lb    $t0, 0($a1)      # $t0 = string2[j]
        beq   $t0, $0, done     # if end of string2, return
        sb    $t0, 0($a2)      # stringconcat[j] = string2[j]
        addi  $a1, $a1, 1      # increment index into string2
        addi  $a2, $a2, 1      # increment index into stringconcat
        j     string2         # loop back
done:   sb    $0, 0($a2)       # append null to end of string
        jr    $ra
```

Exercise 6.35

```
# define the masks in the global data segment
.data
mmask: .word 0x007FFFFFFF
emask: .word 0x7F800000
ibit:  .word 0x00800000
obit:  .word 0x01000000

.text

flpadd: lw $t4,mmask          # load mantissa mask
        and $t0,$s0,$t4       # extract mantissa from $s0 (a)
        and $t1,$s1,$t4       # extract mantissa from $s1 (b)
        lw $t4,ibit          # load implicit leading 1
        or  $t0,$t0,$t4       # add the implicit leading 1 to mantissa
        or  $t1,$t1,$t4       # add the implicit leading 1 to mantissa
        lw $t4,emask         # load exponent mask
        and $t2,$s0,$t4       # extract exponent from $s0 (a)
        srl $t2,$t2,23        # shift exponent right
        and $t3,$s1,$t4       # extract exponent from $s1 (b)
        srl $t3,$t3,23        # shift exponent right
match:  beq $t2,$t3,addsig     # check whether the exponents match
        bgeu $t2,$t3,shiftb    # determine which exponent is larger
```

```

shifta: sub $t4,$t3,$t2      # calculate difference in exponents
        srav $t0,$t0,$t4     # shift a by calculated difference
        add $t2,$t2,$t4      # update a's exponent
        j addsig             # skip to the add
shiftb: sub $t4,$t2,$t3      # calculate difference in exponents
        srav $t1,$t1,$t4     # shift b by calculated difference
        add $t3,$t3,$t4      # update b's exponent (not necessary)
addsig: add $t5,$t0,$t1      # add the mantissas
norm:   lw $t4,obit          # load mask for bit 24 (overflow bit)
        and $t4,$t5,$t4      # mask bit 24
        beq $t4,$0,done      # right shift not needed because bit 24=0
        srl $t5,$t5,1        # shift right once by 1 bit
        addi $t2,$t2,1       # increment exponent
done:   lw $t4,mmask          # load mask
        and $t5,$t5,$t4      # mask mantissa
        sll $t2,$t2,23       # shift exponent into place
        lw $t4,emask         # load mask
        and $t2,$t2,$t4      # mask exponent
        or $v0,$t5,$t2       # place mantissa and exponent into $v0
        jr $ra               # return to caller

```

Exercise 6.36

(a)

```

0x00400000  main:  addi $sp, $sp, -4
0x00400004          sw  $ra, 0($sp)
0x00400008          lw  $a0, x
0x0040000C          lw  $a1, y
0x00400010          jal  diff
0x00400014          lw  $ra, 0($sp)
0x00400018          addi $sp, $sp, 4
0x0040001C          jr   $ra

0x00400020  diff:  sub  $v0, $a0, $a1
0x00400024          jr   $ra

```

(b)

| symbol | address |
|--------|------------|
| x | 0x10000000 |
| y | 0x10000004 |
| main | 0x00400000 |
| diff | 0x00400020 |

TABLE 6.1 Symbol table


(c)

| Executable file header | Text Size | Data Size |
|------------------------|-----------------|---------------|
| | 0x28 (40 bytes) | 0x8 (8 bytes) |
| Text segment | Address | Instruction |
| | 0x00400000 | 0x23BDFFFC |
| | 0x00400004 | 0xAFBF0000 |
| | 0x00400008 | 0x8F848000 |
| | 0x0040000C | 0x8F858004 |
| | 0x00400010 | 0x0C100008 |
| | 0x00400014 | 0x8FBF0000 |
| | 0x00400018 | 0x23BD0004 |
| | 0x0040001C | 0x03E00008 |
| | 0x00400020 | 0x00851022 |
| | 0x00400024 | 0x03E00008 |
| Data segment | Address | Data |
| | 0x10000000 | x |
| | 0x10000004 | y |

```
addi $sp, $sp, -4
sw   $ra, 0($sp)
lw   $a0, 0x8000($gp)
lw   $a1, 0x8004($gp)
jal  diff
lw   $ra, 0($sp)
addi $sp, $sp, 4
jr   $ra
sub  $v0, $a0, $a1
jr   $ra
```

(d)
The data segment is 8 bytes and the text segment is 40 (0x28) bytes.

(e)

 

Exercise 6.37

```
(a)
0x00400000 main:    addi $sp, $sp, -4
0x00400004          sw  $ra, 0($sp)
0x00400008          addi $t0, $0, 15
0x0040000C          sw  $t0, 0x8000($gp)
0x00400010          addi $a1, $0, 27
0x00400014          sw  $a1, 0x8004($gp)
0x00400018          lw  $a0, 0x8000($gp)
0x0040001C          jal  greater
0x00400020          lw  $ra, 0($sp)
0x00400024          addi $sp, $sp, 4
0x00400028          jr   $ra

0x0040002C greater: slt  $v0, $a1, $a0
0x00400030          jr   $ra
```

(b)

| symbol | address |
|---------|------------|
| a | 0x10000000 |
| b | 0x10000004 |
| main | 0x00400000 |
| greater | 0x0040002C |

TABLE 6.2 Symbol table

(c)


| Executable file header | Text Size | Data Size |
|------------------------|-----------------|---------------|
| | 0x34 (52 bytes) | 0x8 (8 bytes) |
| Text segment | Address | Instruction |
| | 0x00400000 | 0x23BDDFFC |
| | 0x00400004 | 0xAFBF0000 |
| | 0x00400008 | 0x2008000F |
| | 0x0040000C | 0xAF888000 |
| | 0x00400010 | 0x2005001B |
| | 0x00400014 | 0xAF858004 |
| | 0x00400018 | 0x8F848000 |
| | 0x0040001C | 0x0C10000B |
| | 0x00400020 | 0x8FBF0000 |
| | 0x00400024 | 0x23BD0004 |
| | 0x00400028 | 0x03E00008 |
| | 0x0040002C | 0x00A4102A |
| | 0x00400030 | 0x03E00008 |
| Data segment | Address | Data |
| | 0x10000000 | a |
| | 0x10000004 | b |

```
addi $sp, $sp, -4
sw  $ra, 0($sp)
addi $t0, $0, 15
sw  $t0, 0x8000($gp)
addi $a1, $0, 27
sw  $a1, 0x8004($gp)
lw  $a0, 0x8000($gp)
jal  greater
lw  $ra, 0($sp)
addi $sp, $sp, 4
jr  $ra
slt  $v0, $a1, $a0
jr  $ra
```

(d)

The data segment is 8 bytes and the text segment is 52 (0x34) bytes.

(e)

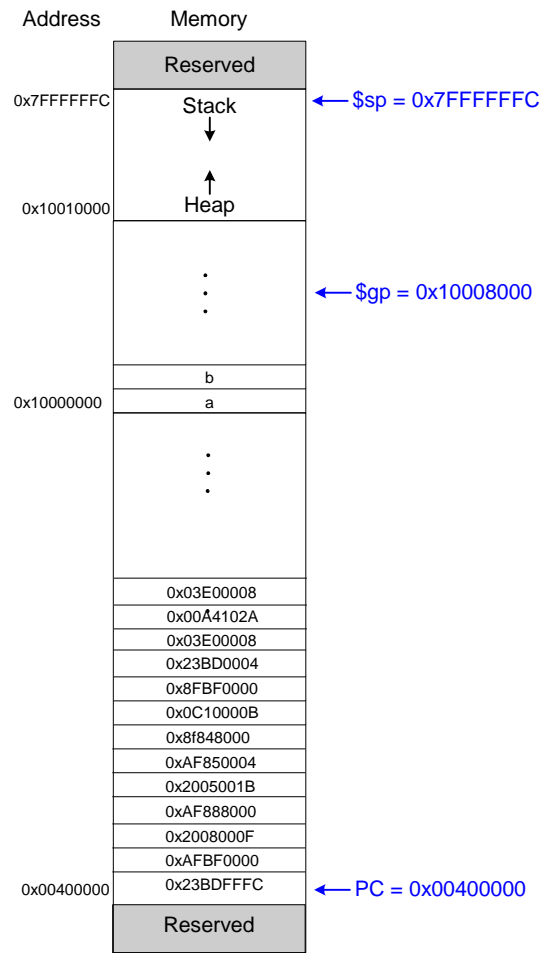

Exercise 6.38

(a)
note: this is not actually a pseudo instruction supplied by MIPS
but the functionality can be implemented as shown below
addi \$t0, \$2, imm31:0

lui \$at, imm31:16
ori \$at, \$at, imm15:0
add \$t0, \$2, \$at

(b)
lw \$t5, imm31:0(\$s0)

```
lui $at, imm31:16
ori $at, $at, imm15:0
add $at, $at, $s0
lw $t5, 0($at)
```

(c)

```
rol $t0, $t1, 5
```

```
srl $at, $t1, 27
sll $t0, $t1, 5
or $t0, $t0, $at
```

(d)

```
ror $s4, $t6, 31
```

```
sll $at, $t6, 1
srl $s4, $t6, 31
or $s4, $s4, $at
```

Exercise 6.39

(a)

```
beq $t1, imm31:0, L
```

```
lui $at, imm31:16
ori $at, $at, imm15:0
beq $t1, $at, L
```

(b)

```
ble $t3, $t5, L
```

```
slt $at, $t5, $t3
beq $at, $0, L
```

(c)

```
bgt $t3, $t5, L
```

```
slt $at, $t5, $t3
bne $at, $0, L
```

(d)

```
bge $t3, $t5, L
```

```
slt $at, $t3, $t5
beq $at, $0, L
```

Question 6.1

```
xor $t0, $t0, $t1 # $t0 = $t0 XOR $t1
xor $t1, $t0, $t1 # $t1 = original value of $t0
xor $t0, $t0, $t1 # $t0 = original value of $t1
```

Question 6.2

High-Level Code

```
// algorithm for finding subset of array with
// largest sum

max = -2,147,483,648; // -2^31
start = 0;
end = 0;

for (i=0; i<length; i=i+1) {

    sum = 0;

    for (j=i; j<length; j=j+1) {

        sum = sum + array[j];

        if (sum > max) {
            max = sum;
            start = i;
            end = j;
        }
    }
}

count = 0;
for ( i = start; i <= end; i=i+1) {
    array2[count] = array[i];
    count = count + 1;
}
```

MIPS Assembly Code

```
# $a0 = base address of array, $a1 = length of array
# $t0 = max, $t1 = start, $t2 = end
# $t3 = i, $t4 = j, $t5 = sum

        li    $t0, 0x80000000 # $t0 = large neg #
        addi  $t1, $0, 0      # start = 0
        addi  $t2, $0, 0      # end = 0
        addi  $t3, $0, -4     # i = -4
        sll   $a1, $a1, 2     # length = length*4

loop1:   addi  $t3, $t3, 4      # i = i+4
        slt   $t6, $t3, $a1    # i<length?
        beq   $t6, $0, finish  # branch if not
        addi  $t5, $0, 0       # reset sum
        addi  $t4, $t3, -4     # j = i-4
loop2:   addi  $t4, $t4, 4      # j = j+4
        slt   $t6, $t4, $a1    # j<length?
        beq   $t6, $0, loop1   # branch if not
        add   $t6, $a0, $t4    # $t6 = &array[j]
        lw    $t6, 0($t6)      # $t6 = array[j]
        add   $t5, $t5, $t6    # sum = sum + $t6
        slt   $t6, $t0, $t5    # max < sum?
        beq   $t6, $0, loop2   # branch if not
        add   $t0, $t5, $0     # max = sum
        add   $t1, $t3, $0     # start = i
        add   $t2, $t4, $0     # end = j
        j     loop2

finish:  addi  $t3, $t1, -4     # i = start - 4
loop3:   add   $t3, $t3, 4      # i = i + 4
        slt   $t6, $t2, $t3    # end < i?
        bne   $t6, $0, return  # if yes, return
        add   $t6, $t3, $a0    # $t6 = &array[i]
        lw    $t6, 0($t6)      # $t6 = array[i]
        sw    $t6, 0($a2)      # array2[count] = array[i]
        add   $a2, $a2, 4      # increment count
        j     loop3

return:  jr    $ra
```

Question 6.3

High-Level Code

```
// high-level algorithm
void reversewords(char[] array) {
    int i, j, length;

    // find length of string
    for (i = 0; array[i] != 0; i = i + 1) ;

    length = i;

    // reverse characters in string
    reverse(array, length-1, 0);

    // reverse words in string
    i = 0; j = 0;

    // check for spaces
    while (i <= length) {
        if ( (i != length) || (array[i] != 0x20) ) {
            i = i + 1;

        } else {
            reverse(array, i-1, j);
            i = i + 1; // j and i at start of next word
            j = i;
        }
    }
}

void reverse(char[] array, int i, int j)
{
    char tmp;
    while (i > j) {
        tmp = array[i];
        array[i] = array[j];
        array[j] = tmp;
        i = i-1;
        j = j+1;
    }
}
```

MIPS Assembly Code

```
# $s2 = i, $s3 = j, $s1 = length
reversewords:
    addi $sp, $sp, -16 # make room on stack
    sw   $ra, 12($sp) # store regs on stack
    sw   $s1, 8($sp)
    sw   $s2, 4($sp)
    sw   $s3, 0($sp)

    addi $s2, $0, 0 # i = 0
length: add  $t4, $a0, $s2 # $t4 = &array[i]
    lb   $t3, 0($t4) # $t3 = array[i]
    beq  $t3, $0, done # end of string?
    addi $s2, $s2, 1 # i++
    j    length

done: addi $s1, $s2, 0 # length = i
    addi $a1, $s1, -1 # $a1 = length - 1
    addi $a2, $0, 0 # $a2 = 0
    jal  reverse # call reverse

    addi $s2, $0, 0 # i = 0
    addi $s3, $0, 0 # j = 0
    addi $t5, $0, 0x20 # $t5 = "space"
word:  slt  $t4, $s1, $s2 # $t4 = 1 if length<i
    bne  $t4, $0, return # return if length<i
    beq  $s2, $s1, else # if i==length, else
    add  $t4, $a0, $s2 # $t4 = &array[i]
    lb   $t4, 0($t4) # $t4 = array[i]
    beq  $t4, $t5, else # if $t4==0x20,else
    addi $s2, $s2, 1 # i = i + 1
    j    word
else:  addi $a1, $s2, -1 # $a1 = i - 1
    addi $a2, $s3, 0 # $a2 = j
    jal  reverse
    addi $s2, $s2, 1 # i = i + 1
    addi $s3, $s2, 0 # j = i
    j    word

return: lw   $ra, 12($sp) # restore regs
    lw   $s1, 8($sp)
    lw   $s2, 4($sp)
    lw   $s3, 0($sp)
    addi $sp, $sp, 16 # restore $sp
    jr   $ra # return

reverse:
    slt  $t0, $a2, $a1 # $t0 = 1 if j < i
    beq  $t0, $0, exit # if j < i, return
    add  $t1, $a0, $a1 # $t1 = &array[i]
    lb   $t2, 0($t1) # $t2 = array[i]
    add  $t3, $a0, $a2 # $t3 = &array[j]
    lb   $t4, 0($t3) # $t4 = array[j]
    sb   $t4, 0($t1) # array[i] =array[j]
    sb   $t2, 0($t3) # array[j] =array[i]
    addi $a1, $a1, -1 # i = i-1
    addi $a2, $a2, 1 # j = j+1
    j    reverse
exit:  jr   $ra
```

Question 6.4

High-Level Code

```
int count = 0;

while (num != 0) {
    if (num && 0x1) // if num AND 0x1
        count = count + 1;

    num = num >> 1;
}
```

MIPS Assembly Code

```
# $a0 = num, $v0 = count
add $v0, $0, $0    # count = 0

count: beq $a0, $0, done # if num == 0, done
       andi $t0, $a0, 0x1 # $t0 = num AND 0x1
       beq $t0, $0, shift # if 0, only shift
       addi $v0, $v0, 1    # count = count + 1
shift: srl $a0, $a0, 1     # num = num >> 1
       j count

done:
```

Question 6.5

High-Level Code

```
num = swap(num, 1, 0x55555555); // swap bits
num = swap(num, 2, 0x33333333); // swap pairs
num = swap(num, 4, 0x0F0F0F0F); // swap nibbles
num = swap(num, 8, 0x00FF00FF); // swap bytes
num = swap(num, 16, 0xFFFFFFFF); // swap halves

// swap masked bits
int swap(int num, int shamt, unsigned int mask) {
    return ((num >> shamt) & mask) |
        ((num & mask) << shamt);
}
```

MIPS Assembly Code

```
# $t3 = num
addi $a0, $t3, 0      # set up args
addi $a1, $0, 1
li $a2, 0x55555555
jal swap              # swap bits
addi $a0, $v0, 0      # num = return value

addi $a1, $0, 2      # set up args
li $a2, 0x33333333
jal swap              # swap pairs
addi $a0, $v0, 0      # num = return value

addi $a1, $0, 4      # set up args
li $a2, 0x0F0F0F0F
jal swap              # swap nibbles
addi $a0, $v0, 0      # num = return value

addi $a1, $0, 8      # set up args
li $a2, 0x00FF00FF
jal swap              # swap bytes
addi $a0, $v0, 0      # num = return value

addi $a1, $0, 16     # set up args
li $a2, 0xFFFFFFFF
jal swap              # swap halves
addi $t3, $v0, 0      # num = return value

done: j done

swap:
    srlv $v0, $a0, $a1 # $v0 = num >> shamt
    and $v0, $v0, $a2  # $v0 = $v0 & mask
    and $t0, $a0, $a2  # $t0 = num & mask
    sllv $t0, $t0, $a1 # $t0 = $t0 << shamt
    or $v0, $v0, $t0   # $v0 = $v0 | $t0
    jr $ra             # return
```

Question 6.6

```
addu $t4, $t2, $t3
xor $t5, $t2, $t3      # compare sign bits
srl $t5, $t5, 31        # $t5 = 1 if sign bits different
bne $t5, $0, nooverflow
xor $t5, $t4, $t3      # compare with result sign bit
srl $t5, $t5, 31        # $t5 = 0 if sign bits same
beq $t5, $0, nooverflow
overflow:

nooverflow:
```


Question 6.7

High-Level Code

```
bool palindrome(char* array) {
    int i, j; // array indices
    // find length of string
    for (j = 0; array[j] != 0; j=j+1) ;

    j = j-1; // j is index of last char

    int i = 0;
    while (j > i) {
        tmp = array[i];
        if (array[i] != array[j])
            return false;
        j = j-1;
        i = i+1;
    }

    return true;
}
```

MIPS Assembly Code

```
# $t0 = j, $t1 = i, $a0 = base address of string
palindrome:
    addi $t0, $0, 0      # j = 0
length:   add $t2, $a0, $t0 # $t2 = &array[j]
          lb  $t2, 0($t2)  # $t2 = array[j]
          beq $t2, $0, done # end of string?
          addi $t0, $t0, 1  # j = j+1
          j   length
done:     addi $t0, $t0, -1 # j = j-1

          addi $t1, $0, 0   # i = 0
loop:     slt  $t2, $t1, $t0 # $t2 = 1 if i < j
          beq  $t2, $0, yes  # if !(i < j) return
          add  $t2, $a0, $t1 # $t2 = &array[i]
          lb  $t2, 0($t2)   # $t2 = array[i]
          add  $t3, $a0, $t0 # $t3 = &array[j]
          lb  $t3, 0($t3)   # $t3 = array[j]
          bne  $t2, $t3, no  # is palindrome?
          addi $t0, $t0, -1  # j = j-1
          addi $t1, $t1, 1   # i = i+1
          j   loop

yes:      # yes a palindrome
          addi $v0, $0, 1
          j   yes
          jr  $ra

no:       # not a palindrome
          addi $v0, $0, 0
          j   no
          jr  $ra
```


CHAPTER 7

Exercise 7.1

- (a) R-type, lw, addi
- (b) R-type
- (c) sw

Exercise 7.2

- (a) sw, beq, j
- (b) lw, sw, beq, addi
- (c) R-type, lw, beq, addi, j

Exercise 7.3

(a) sll

First, we modify the ALU.

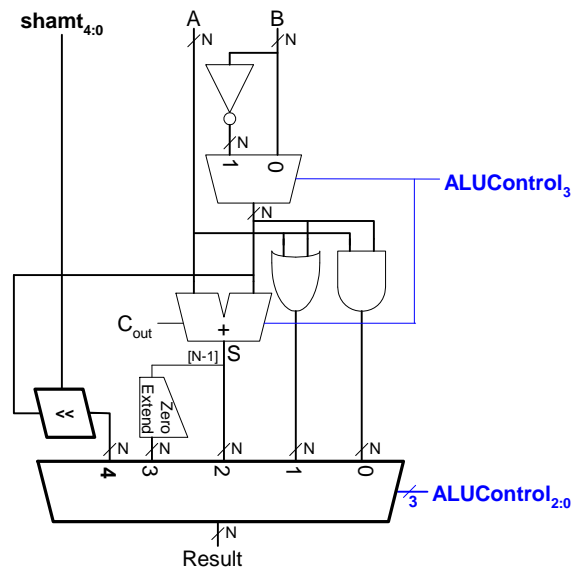


FIGURE 7.1 Modified ALU to support sll

| ALUControl _{3:0} | Function |
|---------------------------|----------------------|
| 0000 | A AND B |
| 0001 | A OR B |
| 0010 | A + B |
| 0011 | not used |
| 1000 | A AND \overline{B} |
| 1001 | A OR \overline{B} |
| 1010 | A - B |
| 1011 | SLT |
| 0100 | SLL |

TABLE 7.1 Modified ALU operations to support sll

| ALUOp | Funct | ALUControl |
|-------|--------------|---------------------------|
| 00 | X | 0010 (add) |
| X1 | X | 1010 (subtract) |
| 1X | 100000 (add) | 0010 (add) |
| 1X | 100010 (sub) | 1010 (subtract) |
| 1X | 100100 (and) | 0000 (and) |
| 1X | 100101 (or) | 0001 (or) |
| 1X | 101010 (slt) | 1011 (set less than) |
| 1X | 000000 (sll) | 0100 (shift left logical) |

TABLE 7.2 ALU decoder truth table

Then we modify the datapath.

 


FIGURE 7.2 Modified single-cycle MIPS processor extended to run sll

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp |
|-------------|---------------|----------|----------|-----------|----------|----------|----------|-----------|
| R-type | 000000 | 1 | 1 | 00 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 0 | 01 | 0 | 0 | 1 | 00 |
| sw | 101011 | 0 | X | 01 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | X | 00 | 1 | 0 | X | 01 |
| lui | 001111 | 1 | 0 | 10 | 0 | 0 | 0 | 00 |

[illegible]

FIGURE 7.3 Modified single-cycle datapath to support `lui`

7.3 (c) `slti`

The datapath doesn't change. Only the controller changes, as shown in Table 7.4 and Table 7.5.

| ALUOp | Funct | ALUControl |
|-------|--------------|---------------------|
| 00 | X | 010 (add) |
| 01 | X | 110 (subtract) |
| 10 | 100000 (add) | 010 (add) |
| 10 | 100010 (sub) | 110 (subtract) |
| 10 | 100100 (and) | 000 (and) |
| 10 | 100101 (or) | 001 (or) |
| 10 | 101010 (slt) | 111 (set less than) |
| 11 | X | 111 (set less than) |


TABLE 7.4 ALU decoder truth table

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp |
|-------------|---------------|----------|----------|----------|----------|----------|----------|-----------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 |
| slti | 001010 | 1 | 0 | 1 | 0 | 0 | 0 | 11 |

TABLE 7.5 Main decoder truth table enhanced to support `slti`

7.3 (d) blez

First, we modify the ALU

 

Then, we modify the datapath




| | | | | | | | | | |
|--------|--------|---|---|---|---|---|---|----|---|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |
| blez | 000110 | 0 | X | 0 | 0 | 0 | X | 01 | 1 |

TABLE 7.6 Main decoder truth table enhanced to support `blez`

Exercise 7.4

(a) jal

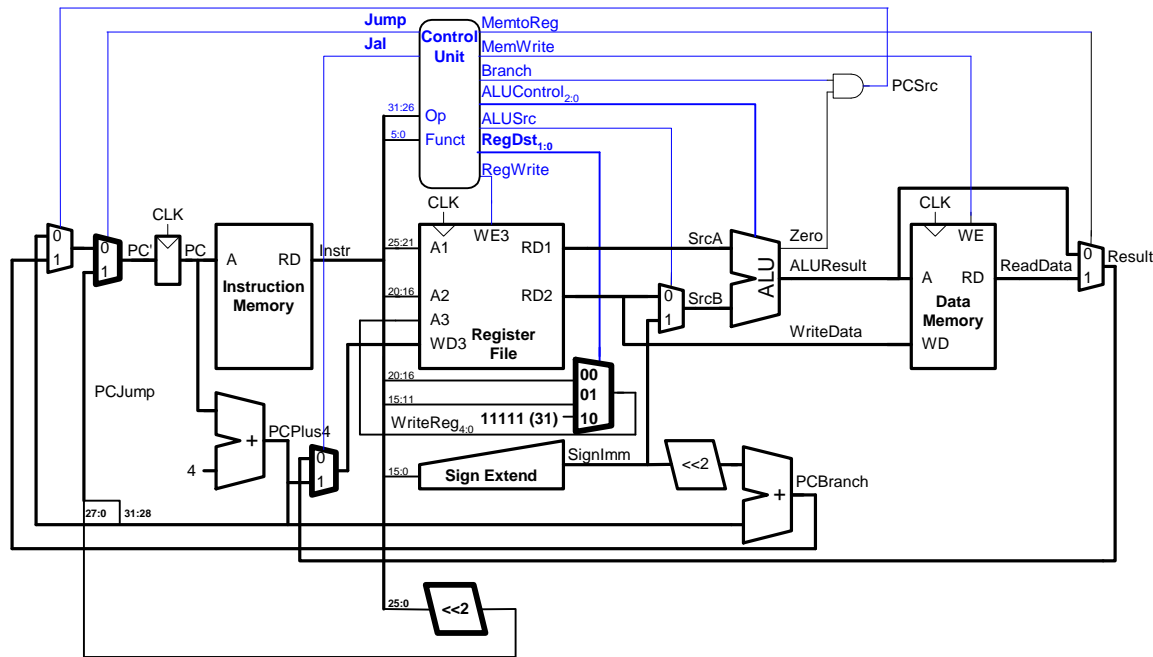

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp | Jump | Jal |
|-------------|--------|----------|--------|--------|--------|----------|----------|-------|------|-----|
| R-type | 000000 | 1 | 01 | 0 | 0 | 0 | 0 | 10 | 0 | 0 |
| lw | 100011 | 1 | 00 | 1 | 0 | 0 | 1 | 00 | 0 | 0 |
| sw | 101011 | 0 | XX | 1 | 0 | 1 | X | 00 | 0 | 0 |
| beq | 000100 | 0 | XX | 0 | 1 | 0 | X | 01 | 0 | 0 |
| addi | 001000 | 1 | 00 | 1 | 0 | 0 | 0 | 00 | 0 | 0 |
| j | 000010 | 0 | XX | X | X | 0 | X | XX | 1 | 0 |
| jal | 000011 | 1 | 10 | X | X | 0 | X | XX | 1 | 1 |

TABLE 7.7 Main decoder truth table enhanced to support `jal`

7.4 (b) lh

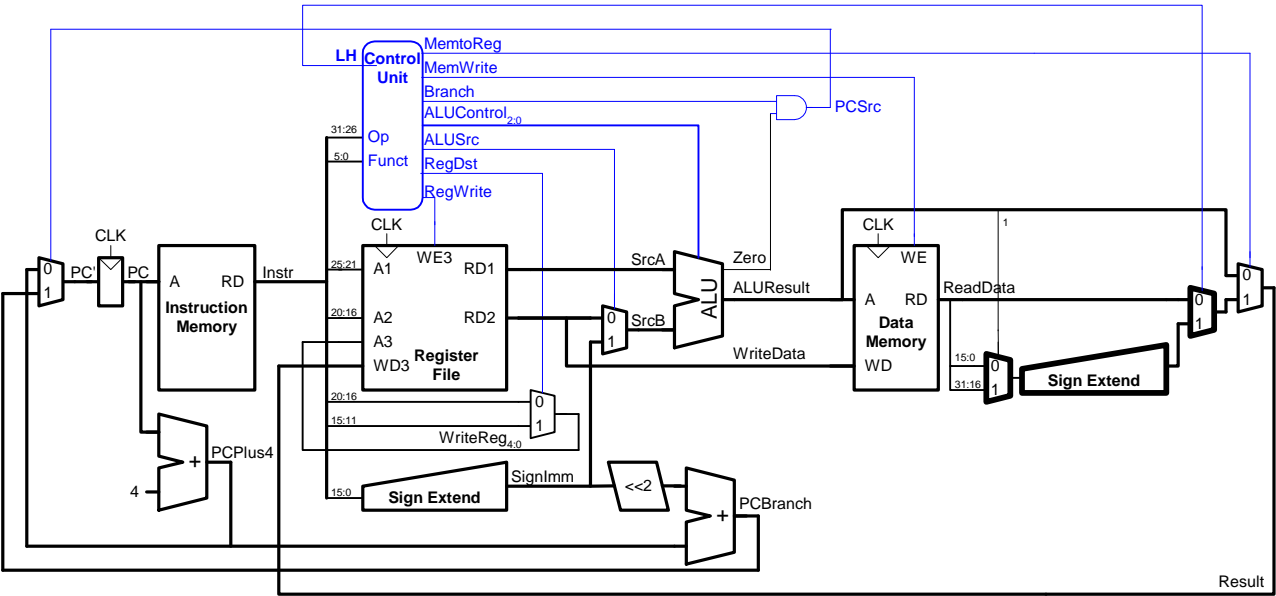


FIGURE 7.4 Modified single-cycle datapath to support `lh`

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp | LH |
|-------------|--------|----------|--------|--------|--------|----------|----------|-------|----|
| R-type | 000000 | 1 | 01 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 00 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | XX | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | XX | 0 | 1 | 0 | X | 01 | 0 |
| lh | 100001 | 1 | 00 | 1 | 0 | 0 | 1 | 00 | 1 |

TABLE 7.8 Main decoder truth table enhanced to support `lh`

7.4 (c) jr

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp |
|-------------|--------|----------|--------|--------|--------|----------|----------|-------|
| R-type | 000000 | 1 | 01 | 0 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 00 | 1 | 0 | 0 | 1 | 00 |
| sw | 101011 | 0 | XX | 1 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | XX | 0 | 1 | 0 | X | 01 |

TABLE 7.9 Main decoder truth table enhanced to support j_r - no changes

| ALUOp | Funct | ALUControl | JR |
|-------|--------------|----------------|----|
| 00 | X | 010 (add) | 0 |
| 01 | X | 110 (subtract) | 0 |
| 10 | 100000 (add) | 010 (add) | 0 |

TABLE 7.10 ALU decoder truth table

| ALUOp | Funct | ALUControl | JR |
|-----------|--------------------|---------------------|----------|
| 10 | 100010 (sub) | 110 (subtract) | 0 |
| 10 | 100100 (and) | 000 (and) | 0 |
| 10 | 100101 (or) | 001 (or) | 0 |
| 10 | 101010 (slt) | 111 (set less than) | 0 |
| 10 | 001000 (jr) | XXX | 1 |

TABLE 7.10 ALU decoder truth table

7.4 (d) srl

6First we modify the ALU

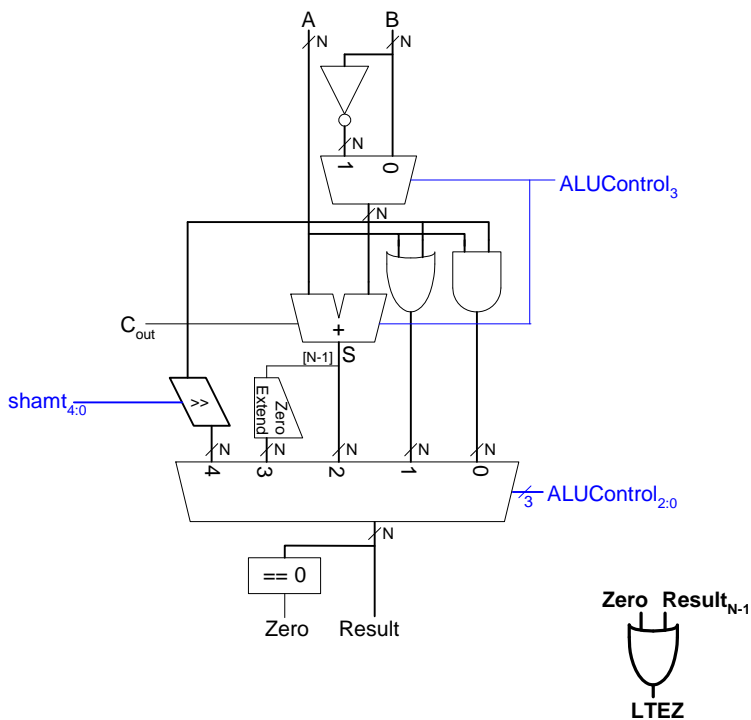


FIGURE 7.6 Modified ALU to support srl


| ALUControl _{3:0} | Function |
|---------------------------|----------------------|
| 0000 | A AND B |
| 0001 | A OR B |
| 0010 | A + B |
| 0011 | not used |
| 1000 | A AND \overline{B} |
| 1001 | A OR \overline{B} |
| 1010 | A - B |
| 1011 | SLT |
| 0100 | SRL |

FIGURE 7.7 Modified ALU operations to support srl

| ALUOp | Funct | ALUControl |
|-------|--------------|-------------------------------------|
| 00 | X | 0010 (add) |
| X1 | X | 1010 (subtract) |
| 1X | 100000 (add) | 0010 (add) |
| 1X | 100010 (sub) | 1010 (subtract) |
| 1X | 100100 (and) | 0000 (and) |
| 1X | 100101 (or) | 0001 (or) |
| 1X | 101010 (slt) | 1011 (set less than) |
| 1X | 000010 (srl) | 0100 (shift right logical variable) |

TABLE 7.11 ALU decoder truth table

FIGURE 7.8 Modified single-cycle datapath to support srl

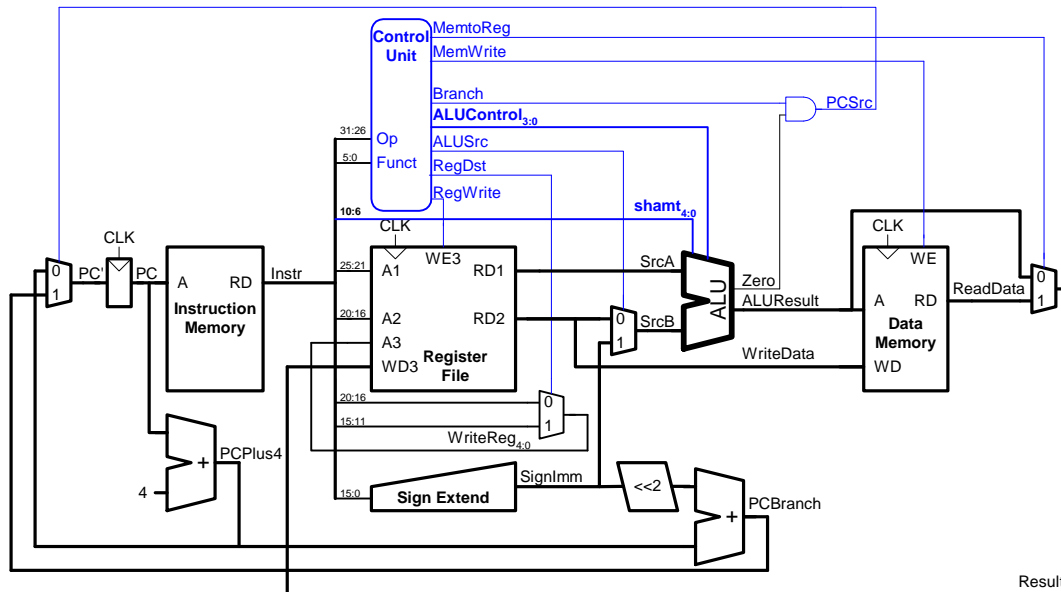

Exercise 7.5

It is not possible to implement this instruction without either modifying the register file (adding another write port) or making the instruction take two cycles to execute.

We modify the register file and datapath as shown in Figure 7.9.


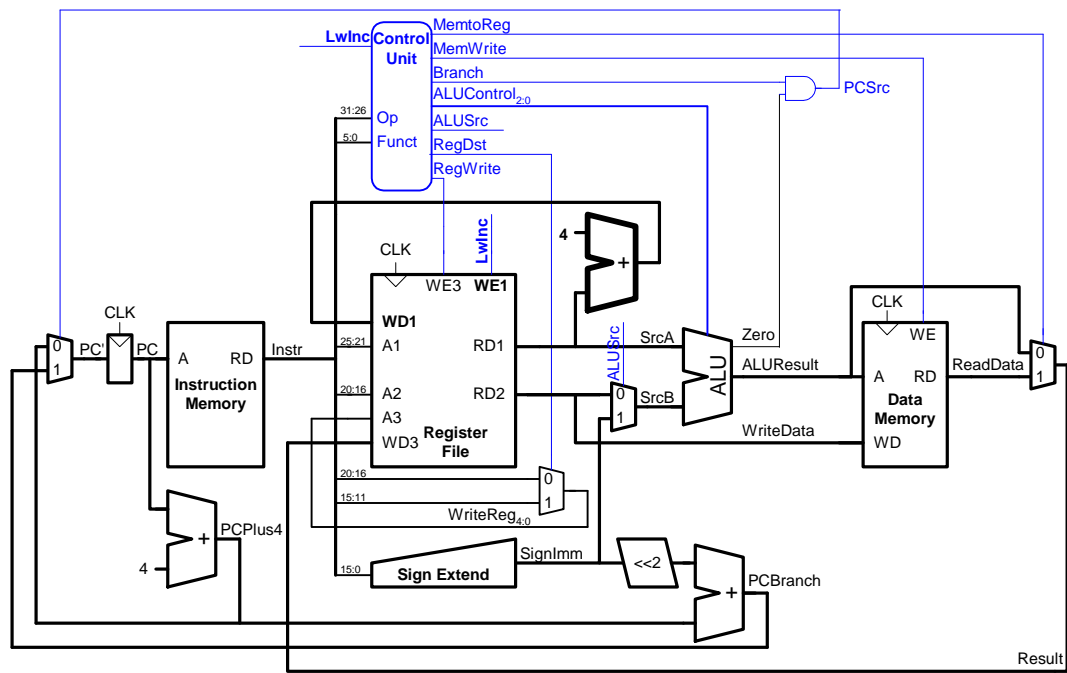


FIGURE 7.9 Modified datapath

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp | Lwinc |
|-------------|--------|----------|--------|--------|--------|----------|----------|-------|-------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |
| lwinc | | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 1 |

TABLE 7.12 Main decoder truth table enhanced to support lwinc

Exercise 7.6

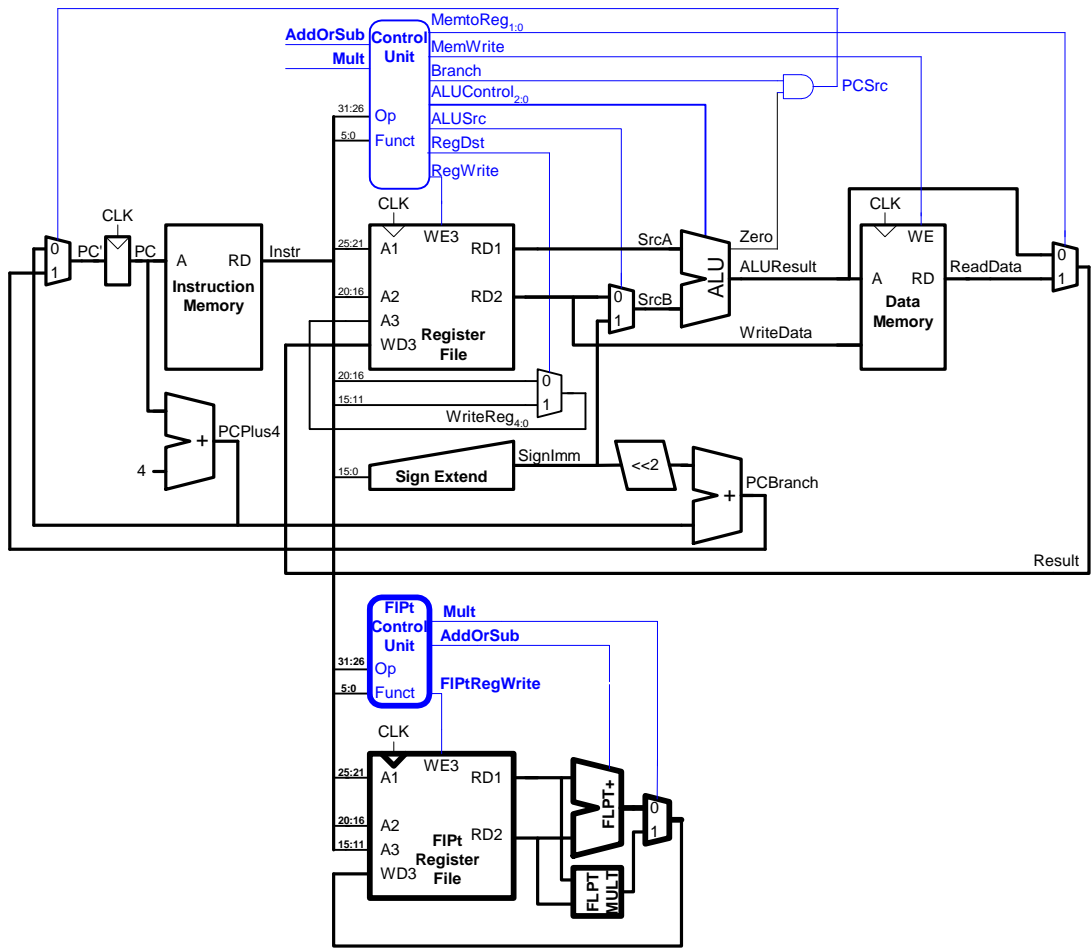

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp |
|-------------|--------|----------|--------|--------|--------|----------|----------|-------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 00 | 10 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 01 | 00 |

TABLE 7.13 Main decoder truth table enhanced to support add.s, sub.s, and mult.s

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp |
|---------------|---------------|----------|----------|----------|----------|----------|-----------|-----------|
| sw | 101011 | 0 | X | 1 | 0 | 1 | XX | 00 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | XX | 01 |
| f-type | 010001 | 0 | X | X | 0 | 0 | XX | XX |

TABLE 7.13 Main decoder truth table enhanced to support add . s, sub . s, and mult . s

| Instruction | opcode | FltPtRegWrite |
|---------------|---------------|---------------|
| f-type | 010001 | 1 |
| others | | 0 |

TABLE 7.14 Floating point main decoder truth table enhanced to support add . s, sub . s, and mult . s

| Funct | Mult | AddOrSub |
|----------------------|----------|----------|
| 000000 (add) | 0 | 1 |
| 000001 (sub) | 0 | 0 |
| 000010 (mult) | 1 | X |

TABLE 7.15 Adder/subtractor decoder truth table

Exercise 7.7

Before the enhancement (see Equation 7.3, page 380 in the text, also Errata):

$$T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$$
$$= 30 + 2(250) + 150 + 25 + 200 + 20 = \mathbf{925ps}$$

The unit that your friend could speed up that would make the largest reduction in cycle time would be the memory unit. So tmem_new = 125ps, and the new cycle time is:

$$T_c = \mathbf{675\ ps}$$

Exercise 7.8

From Equation 7.3, page 380 in the text (see Errata):

$$T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$$

$$= 30 + 2(250) + 150 + 25 + 180 + 20 = \mathbf{905ps}$$

It would take **90.5 seconds** to execute 100 billion instructions.

Exercise 7.9

- (a) lw
- (b) beq
- (c) beq, j

Exercise 7.10

- (a) R-type, addi
- (b) lw, sw, addi, R-type
- (c) all instructions

Exercise 7.11

SystemVerilog

```
module top(input  logic      clk, reset,
           output logic [31:0] writedata, dataadr,
           output logic      memwrite);

    logic [31:0] pc, instr, readdata;

    // instantiate processor and memories
    mips mips(clk, reset, pc, instr, memwrite, dataadr,
              writedata, readdata);
    imem imem(pc[7:2], instr);
    dmem dmem(clk, memwrite, dataadr, writedata, readdata);
endmodule

module dmem(input  logic      clk, we,
            input  logic [31:0] a, wd,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];
```

```
        assign rd = RAM[a[31:2]]; // word aligned

        always_ff @(posedge clk)
            if (we) RAM[a[31:2]] <= wd;
    endmodule

module imem(input  logic [5:0] a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    initial
        $readmemh("memfile.dat",RAM);

    assign rd = RAM[a]; // word aligned
endmodule

module mipssingle(input  logic      clk, reset,
                  output logic [31:0] pc,
                  input  logic [31:0] instr,
                  output logic      memwrite,
                  output logic [31:0] aluresult,
                              writedata,
                  input  logic [31:0] readdata);

    logic      memtoreg;
    logic [1:0] alusrc; // LUI
    logic      regdst;
    logic      regwrite, jump, pcsrc, zero;
    logic [3:0] alucontrol; // SLL
    logic      ltez; // BLEZ

    controller c(instr[31:26], instr[5:0], zero,
                memtoreg, memwrite, pcsrc,
                alusrc, regdst, regwrite, jump,
                alucontrol,
                ltez); // BLEZ

    datapath dp(clk, reset, memtoreg, pcsrc,
                alusrc, regdst, regwrite, jump,
                alucontrol,
                zero, pc, instr,
                aluresult, writedata, readdata,
                ltez); // BLEZ
endmodule

module controller(input  logic [5:0] op, funct,
                  input  logic      zero,
                  output logic      memtoreg, memwrite,
                  output logic      pcsrc,
```

```

        output logic [1:0] alusrc,          // LUI
        output logic      regdst,
        output logic      regwrite,
        output logic      jump,
        output logic [3:0] alucontrol,    // SLL
        input  logic      ltez);          // BLEZ

    logic [1:0] aluop;
    logic      branch;
    logic      blez; // BLEZ

    maindec md(op, memtoreg, memwrite, branch,
               alusrc, regdst, regwrite, jump,
               aluop, blez); // BLEZ
    aludec ad(funct, aluop, alucontrol);

    // BLEZ
    assign pcsrc = (branch & zero) | (blez & ltez);

endmodule

module maindec(input  logic [5:0] op,
               output logic      memtoreg, memwrite,
               output logic      branch,
               output logic [1:0] alusrc, // LUI
               output logic      regdst,
               output logic      regwrite,
               output logic      jump,
               output logic [1:0] aluop,
               output logic      blez);    // BLEZ

    // increase control width for LUI, BLEZ
    logic [10:0] controls;

    assign {regwrite, regdst, alusrc, branch, memwrite,
            memtoreg, aluop, jump, blez} = controls;

    always_comb
    case(op)
        6'b000000: controls = 11'b11000001000; //Rtype
        6'b100011: controls = 11'b10010010000; //LW
        6'b101011: controls = 11'b00010100000; //SW
        6'b000100: controls = 11'b00001000100; //BEQ
        6'b001000: controls = 11'b10010000000; //ADDI
        6'b000010: controls = 11'b00000000010; //J
        6'b001010: controls = 11'b10010001100; //SLTI
        6'b001111: controls = 11'b10100000000; //LUI
        6'b000110: controls = 11'b00000000101; //BLEZ
        default:   controls = 11'bxxxxxxxxxxx; //???
    endcase
endmodule

module aludec(input  logic [5:0] funct,
```

```

        input  logic [1:0] aluop,
        output logic [3:0] alucontrol);
        // increase to 4 bits for SLL

always_comb
case(aluop)
    2'b00: alucontrol = 4'b0010; // add
    2'b01: alucontrol = 4'b1010; // sub
    2'b11: alucontrol = 4'b1011; // slt
    default: case(funcnt) // RTYPE
        6'b100000: alucontrol = 4'b0010; // ADD
        6'b100010: alucontrol = 4'b1010; // SUB
        6'b100100: alucontrol = 4'b0000; // AND
        6'b100101: alucontrol = 4'b0001; // OR
        6'b101010: alucontrol = 4'b1011; // SLT
        6'b000000: alucontrol = 4'b0100; // SLL
        default: alucontrol = 4'bxxxx; // ???
    endcase
endcase
endmodule

module datapath(input  logic      clk, reset,
               input  logic      memtoreg, pcsrc,
               input  logic [1:0] alusrc, // LUI
               input  logic      regdst,
               input  logic      regwrite, jump,
               input  logic [3:0] alucontrol, // SLL
               output logic      zero,
               output logic [31:0] pc,
               input  logic [31:0] instr,
               output logic [31:0] aluresult, writedata,
               input  logic [31:0] readdata,
               output logic      ltez); // LTEZ

logic [4:0] writereg;
logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
logic [31:0] signimm, signimmsh;
logic [31:0] upperimm; // LUI
logic [31:0] srca, srcb;
logic [31:0] result;
logic [31:0] memdata;

// next PC logic
flopr #(32) pcreg(clk, reset, pcnext, pc);
adder      pcadd1(pc, 32'b100, pcplus4);
sl2        immsh(signimm, signimmsh);
adder      pcadd2(pcplus4, signimmsh, pcbranch);
mux2 #(32) pbrmux(pcplus4, pcbranch, pcsrc,
                 pcnextbr);
mux2 #(32) pcmux(pcnextbr, {pcplus4[31:28],
                           instr[25:0], 2'b00},
                 jump, pcnext);

```

```
// register file logic
regfile      rf(clk, regwrite, instr[25:21],
               instr[20:16], writereg,
               writeresult, srca, writedata);

mux2 #(5)     wrmux(instr[20:16], instr[15:11],
                  regdst, writereg);

signext       se(instr[15:0], signimm);
upimm         ui(instr[15:0], upperimm); // LUI

// ALU logic
mux3 #(32)     srcbmux(writedata, signimm,
                     upperimm, alusrc,
                     srcb); // LUI
alu           alu(srca, srcb, alucontrol,
                 instr[10:6], // SLL
                 aluresult, zero,
                 ltez); // BLEZ
mux2 #(32)     rdmux(aluresult, readdata,
                  memtoreg, result);

endmodule

// upimm module needed for LUI
module upimm(input  logic [15:0] a,
             output logic [31:0] y);

    assign y = {a, 16'b0};
endmodule

// mux3 needed for LUI
module mux3 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1, d2,
     input  logic [1:0]      s,
     output logic [WIDTH-1:0] y);

    assign #1 y = s[1] ? d2 : (s[0] ? d1 : d0);
endmodule

module alu(input  logic [31:0] A, B,
          input  logic [3:0] F,
          input  logic [4:0] shamt, // SLL
          output logic [31:0] Y,
          output logic      Zero,
          output logic      ltez); // BLEZ

    logic [31:0] S, Bout;

    assign Bout = F[3] ? ~B : B;
    assign S = A + Bout + F[3]; // SLL
endmodule
```

```

always_comb
case (F[2:0])
  3'b000: Y = A & Bout;
  3'b001: Y = A | Bout;
  3'b010: Y = S;
  3'b011: Y = S[31];
  3'b100: Y = (Bout << shamt); // SLL
endcase

assign Zero = (Y == 32'b0);
assign ltez = Zero | S[31]; // BLEZ

endmodule

module regfile(input  logic      clk,
               input  logic      we3,
               input  logic [4:0] ra1, ra2, wa3,
               input  logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

  logic [31:0] rf[31:0];

  // three ported register file
  // read two ports combinationaly
  // write third port on rising edge of clk
  // register 0 hardwired to 0
  always_ff @(posedge clk)
    if (we3) rf[wa3] <= wd3;

  assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
  assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule

module adder(input  logic [31:0] a, b,
             output logic [31:0] y);

  assign y = a + b;
endmodule

module sl2(input  logic [31:0] a,
           output logic [31:0] y);

  // shift left by 2
  assign y = {a[29:0], 2'b00};
endmodule

module signext(input  logic [15:0] a,
               output logic [31:0] y);

  assign y = {{16{a[15]}}, a};
endmodule

```



```

module flopr #(parameter WIDTH = 8)
    (input  logic          clk, reset,
     input  logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1,
     input  logic          s,
     output logic [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule

```

VHDL

```

-- mips.vhd

library IEEE;
use IEEE.STD_LOGIC_1164.all;    use IEEE.NUMERIC_STD_UN-
SIGNED.all;

entity testbench is
end;

architecture test of testbench is
    component top
        port(clk, reset:          in  STD_LOGIC;
              writedata, dataadr:  out STD_LOGIC_VECTOR(31 downto 0);
              memwrite:           out STD_LOGIC);
    end component;
    signal writedata, dataadr:  STD_LOGIC_VECTOR(31 downto 0);
    signal clk, reset, memwrite: STD_LOGIC;
begin

    -- instantiate device to be tested
    dut: top port map(clk, reset, writedata, dataadr, memwrite);

    -- Generate clock with 10 ns period
    process begin
        clk <= '1';
        wait for 5 ns;
        clk <= '0';
        wait for 5 ns;
    end process;

    -- Generate reset for first two clock cycles

```

```

process begin
    reset <= '1';
    wait for 22 ns;
    reset <= '0';
    wait;
end process;

-- check that 7 gets written to address 84 at end of program
process (clk) begin
    if (clk'event and clk = '0' and memwrite = '1') then
        if (to_integer(dataadr) = 84 and to_integer(writedata) =
7) then
            report "NO ERRORS: Simulation succeeded" severity fail-
ure;
        elsif (dataadr /= 80) then
            report "Simulation failed" severity failure;
        end if;
    end if;
end process;
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;      use IEEE.NUMERIC_STD_UN-
SIGNED.all;

entity top is -- top-level design for testing
    port(clk, reset:          in      STD_LOGIC;
          writedata, dataadr:  buffer STD_LOGIC_VECTOR(31 downto
0);
          memwrite:           buffer STD_LOGIC);
end;

architecture test of top is
    component mips
        port(clk, reset:          in      STD_LOGIC;
              pc:                 out     STD_LOGIC_VECTOR(31 downto 0);
              instr:              in      STD_LOGIC_VECTOR(31 downto 0);
              memwrite:           out     STD_LOGIC;
              aluresult:          out     STD_LOGIC_VECTOR(31 downto 0);
              writedata:          out     STD_LOGIC_VECTOR(31 downto 0);
              readdata:           in      STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component imem
        port(a: in STD_LOGIC_VECTOR(5 downto 0);
              rd: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component dmem
        port(clk, we: in STD_LOGIC;
              a, wd: in STD_LOGIC_VECTOR(31 downto 0);
              rd: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    signal pc, instr,
          readdata: STD_LOGIC_VECTOR(31 downto 0);

```

```
begin
  -- instantiate processor and memories
  mips1: mips port map(clk, reset, pc, instr, memwrite, dataadr,
                      writedata, readdata);
  imem1: imem port map(pc(7 downto 2), instr);
  dmem1: dmem port map(clk, memwrite, dataadr, writedata, re-
addata);
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all; use STD.TEXTIO.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;

entity dmem is -- data memory
  port(clk, we: in STD_LOGIC;
        a, wd: in STD_LOGIC_VECTOR(31 downto 0);
        rd: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of dmem is
begin
  process is
    type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31
downto 0);
    variable mem: ramtype;
  begin
    -- read or write memory
    loop
      if clk'event and clk = '1' then
        if (we = '1') then mem(to_integer(a(7 downto 2))) := wd;
          end if;
        end if;
        rd <= mem(to_integer(a(7 downto 2)));
        wait on clk, a;
      end loop;
    end process;
  end;

  library IEEE;
  use IEEE.STD_LOGIC_1164.all; use STD.TEXTIO.all;
  use IEEE.NUMERIC_STD_UNSIGNED.all;

  entity imem is -- instruction memory
    port(a: in STD_LOGIC_VECTOR(5 downto 0);
          rd: out STD_LOGIC_VECTOR(31 downto 0));
  end;

  architecture behave of imem is
  begin
    process is
      file mem_file: TEXT;
      variable L: line;
```

```

        variable ch: character;
        variable i, index, result: integer;
        type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31
downto 0);
        variable mem: ramtype;
    begin
        -- initialize memory from file
        for i in 0 to 63 loop -- set all contents low
            mem(i) := (others => '0');
        end loop;
        index := 0;
        FILE_OPEN(mem_file, "C:/docs/DDCA2e/hdl/memfile.dat",
READ_MODE);
        while not endfile(mem_file) loop
            readline(mem_file, L);
            result := 0;
            for i in 1 to 8 loop
                read(L, ch);
                if '0' <= ch and ch <= '9' then
                    result := character'pos(ch) - character'pos('0');
                elsif 'a' <= ch and ch <= 'f' then
                    result := character'pos(ch) - character'pos('a')+10;
                else report "Format error on line " & integer'image(in-
dex)
                    severity error;
                end if;
                mem(index)(35-i*4 downto 32-i*4) :=to_std_logic_vec-
tor(result,4);
            end loop;
            index := index + 1;
        end loop;

        -- read memory
        loop
            rd <= mem(to_integer(a));
            wait on a;
        end loop;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mips is -- single cycle MIPS processor
    port(clk, reset:          in  STD_LOGIC;
         pc:                  out STD_LOGIC_VECTOR(31 downto 0);
         instr:               in  STD_LOGIC_VECTOR(31 downto 0);
         memwrite:            out STD_LOGIC;
         alurestult:          out STD_LOGIC_VECTOR(31 downto 0);
         writedata:           out STD_LOGIC_VECTOR(31 downto 0);
         readdata:            in  STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of mips is

```

```

component controller
  port(op, funct:          in STD_LOGIC_VECTOR(5 downto 0);
        zero:              in STD_LOGIC;
        memtoereg, memwrite: out STD_LOGIC;
        psrc:              out STD_LOGIC;
        alusrc:            out STD_LOGIC_VECTOR(1 downto 0); -- LUI
        regdst, regwrite:  out STD_LOGIC;
        jump:              out STD_LOGIC;
        alucontrol:        out STD_LOGIC_VECTOR(3 downto 0); --
- SLL
        ltez:              out STD_LOGIC); -- BLEZ
end component;
component datapath
  port(clk, reset:        in STD_LOGIC;
        memtoereg, psrc:  in STD_LOGIC;
        alusrc, regdst:   in STD_LOGIC;
        regwrite, jump:   in STD_LOGIC;
        alucontrol:       in STD_LOGIC_VECTOR(2 downto 0);
        zero:             out STD_LOGIC;
        pc:               buffer STD_LOGIC_VECTOR(31 downto 0);
        instr:            in STD_LOGIC_VECTOR(31 downto 0);
        aluresult:        buffer STD_LOGIC_VECTOR(31 downto 0);
        writedata:        buffer STD_LOGIC_VECTOR(31 downto 0);
        readdata:         in STD_LOGIC_VECTOR(31 downto 0));
end component;
signal memtoereg: STD_LOGIC;
signal alusrc: STD_LOGIC_VECTOR(1 downto 0); -- LUI
signal regdst, regwrite, jump, psrc: STD_LOGIC;
signal zero: STD_LOGIC;
signal alucontrol: STD_LOGIC_VECTOR(3 downto 0); -- SLL
signal ltez: STD_LOGIC; -- BLEZ
begin
  cont: controller port map(instr(31 downto 26), instr(5 downto
0),
                        zero, memtoereg, memwrite, psrc, alusrc,
                        regdst, regwrite, jump, alucontrol,
                        ltez); -- BLEZ
  dp: datapath port map(clk, reset, memtoereg, psrc, alusrc,
regdst,
                        regwrite, jump, alucontrol, zero, pc, instr,
                        aluresult, writedata, readdata,
                        ltez); -- BLEZ
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity controller is -- single cycle control decoder
  port(op, funct:          in STD_LOGIC_VECTOR(5 downto 0);
        zero:              in STD_LOGIC;
        memtoereg, memwrite: out STD_LOGIC;
        psrc:              out STD_LOGIC;
        alusrc:            out STD_LOGIC_VECTOR(1 downto 0); -- LUI
        regdst, regwrite:  out STD_LOGIC;

```

```

        jump:                out STD_LOGIC;
        alucontrol:          out STD_LOGIC_VECTOR(3 downto 0);  -
- SLL
        ltez:                out STD_LOGIC);                    -- BLEZ
    end;

    architecture struct of controller is
    component maindec
        port(op:              in  STD_LOGIC_VECTOR(5 downto 0);
              memtoreg, memwrite: out STD_LOGIC;
              branch:         out STD_LOGIC;
              alusrc:         out STD_LOGIC_VECTOR(1 downto 0);
-- LUI
              regdst, regwrite: out STD_LOGIC;
              jump:          out STD_LOGIC;
              aluop:         out STD_LOGIC_VECTOR(1 downto 0);
              blez:          out STD_LOGIC);
    end component;
    component aludec
        port(funcnt:         in  STD_LOGIC_VECTOR(5 downto 0);
              aluop:         in  STD_LOGIC_VECTOR(1 downto 0);
              alucontrol: out STD_LOGIC_VECTOR(3 downto 0)); -- SLL
    end component;
    signal aluop: STD_LOGIC_VECTOR(1 downto 0);
    signal branch: STD_LOGIC;
    signal blez: STD_LOGIC; --BLEZ
    begin
        md: maindec port map(op, memtoreg, memwrite, branch,
                             alusrc, regdst, regwrite, jump, aluop, blez);
        ad: aludec port map(funcnt, aluop, alucontrol);

        --BLEZ
        pcsrc <= (branch and zero) or (blez and ltez);
    end;

    library IEEE; use IEEE.STD_LOGIC_1164.all;

    entity maindec is -- main control decoder
        port(op:              in  STD_LOGIC_VECTOR(5 downto 0);
              memtoreg, memwrite: out STD_LOGIC;
              branch:         out STD_LOGIC;
              alusrc:         out STD_LOGIC_VECTOR(1 downto 0); -- LUI
              regdst, regwrite: out STD_LOGIC;
              jump:          out STD_LOGIC;
              aluop:         out STD_LOGIC_VECTOR(1 downto 0);
              blez:          out STD_LOGIC);
    end;

    architecture behave of maindec is
        signal controls: STD_LOGIC_VECTOR(10 downto 0);
    begin
        process(all) begin
            case op is

```

```

        when "000000" => controls <= "11000001000"; -- RTYPE
        when "100011" => controls <= "10010010000"; -- LW
        when "101011" => controls <= "00010100000"; -- SW
        when "000100" => controls <= "00001000100"; -- BEQ
        when "001000" => controls <= "10010000000"; -- ADDI
        when "000010" => controls <= "00000000010"; -- J
        when "001010" => controls <= "10010001100"; -- SLTI
        when "001111" => controls <= "10100000000"; -- LUI
        when "000110" => controls <= "00000000101"; -- BLEZ
        when others    => controls <= "-----"; -- illegal op
    end case;
end process;

    (regwrite, regdst, alusrc, branch, memwrite,
     memtoreg, aluop(1 downto 0), jump, blez) <= controls;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity aludec is -- ALU control decoder
    port(funct:      in  STD_LOGIC_VECTOR(5 downto 0);
          aluop:     in  STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: out STD_LOGIC_VECTOR(3 downto 0)); -- SLL
end;

architecture behave of aludec is
begin
    process(all) begin
        case aluop is
            when "00" => alucontrol <= "0010"; -- add
            when "01" => alucontrol <= "1010"; -- sub
            when "11" => alucontrol <= "1011"; -- slt
            when others => case funct is -- R-type instructions
                when "100000" => alucontrol <= "0010";
-- add
                when "100010" => alucontrol <= "1010";
-- sub
                when "100100" => alucontrol <= "0000";
-- and
                when "100101" => alucontrol <= "0001"; -- or
                when "101010" => alucontrol <= "1011";
-- slt
                when "000000" => alucontrol <= "0100";
-- sll
                when others    => alucontrol <= "----"; -- ???
            end case;
        end case;
    end process;
end;

    library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOG-
    IC_ARITH.all;

```

```

entity datapath is -- MIPS datapath
    port(clk, reset:      in  STD_LOGIC;
          memtoreg, pcsrc: in  STD_LOGIC;
          alusrc:         in  STD_LOGIC_VECTOR(1 downto 0); -- LUI
          alusrc, regdst:  in  STD_LOGIC;
          regwrite, jump: in  STD_LOGIC;
          alucontrol:      in  STD_LOGIC_VECTOR(3 downto 0); --
- SLL
          zero:           out STD_LOGIC;
          pc:             buffer STD_LOGIC_VECTOR(31 downto 0);
          instr:          in  STD_LOGIC_VECTOR(31 downto 0);
          aluresult:      buffer STD_LOGIC_VECTOR(31 downto 0);
          writedata:      buffer STD_LOGIC_VECTOR(31 downto 0);
          readdata:       in  STD_LOGIC_VECTOR(31 downto 0);
          ltez:           out STD_LOGIC); -- LTEZ
end;

architecture struct of datapath is
    component alu
        port(a, b:      in  STD_LOGIC_VECTOR(31 downto 0);
              alucontrol: in  STD_LOGIC_VECTOR(3 downto 0); --SLL
              shamt:     in  STD_LOGIC_VECTOR(4 downto 0); --SLL
              result:    buffer STD_LOGIC_VECTOR(31 downto 0);
              zero:      buffer STD_LOGIC; --BLEZ
              ltez:      out STD_LOGIC); --BLEZ
    end component;
    component regfile
        port(clk:      in  STD_LOGIC;
              we3:      in  STD_LOGIC;
              ra1, ra2, wa3: in  STD_LOGIC_VECTOR(4 downto 0);
              wd3:      in  STD_LOGIC_VECTOR(31 downto 0);
              rd1, rd2: out  STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component adder
        port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
              y:   out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component sl2
        port(a: in  STD_LOGIC_VECTOR(31 downto 0);
              y: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component signext
        port(a: in  STD_LOGIC_VECTOR(15 downto 0);
              y: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component upimm
        port(a: in  STD_LOGIC_VECTOR(15 downto 0);
              y: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component flopr generic(width: integer);
        port(clk, reset: in  STD_LOGIC;
              d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
              q:         out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;

```


- LUI

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;

entity regfile is -- three-port register file
    port(clk:          in  STD_LOGIC;
          we3:         in  STD_LOGIC;
          ral, ra2, wa3: in  STD_LOGIC_VECTOR(4 downto 0);
          wd3:         in  STD_LOGIC_VECTOR(31 downto 0);
          rd1, rd2:    out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of regfile is
    type ramtype is array (31 downto 0) of STD_LOGIC_VECTOR(31
downto 0);
    signal mem: ramtype;
begin
    -- three-ported register file
    -- read two ports combinationally
    -- write third port on rising edge of clock
    -- register 0 hardwired to 0
    process(clk) begin
        if rising_edge(clk) then
            if we3 = '1' then mem(to_integer(wa3)) <= wd3;
            end if;
        end if;
    end process;
    process(all) begin
        if (to_integer(ral) = 0) then rd1 <= X"00000000"; -- register
0 holds 0
        else rd1 <= mem(to_integer(ral));
        end if;
        if (to_integer(ra2) = 0) then rd2 <= X"00000000";
        else rd2 <= mem(to_integer(ra2));
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;

entity adder is -- adder
    port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
          y:   out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of adder is
begin
    y <= a + b;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
```

```

entity sl2 is -- shift left by 2
    port(a: in  STD_LOGIC_VECTOR(31 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of sl2 is
begin
    y <= a(29 downto 0) & "00";
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity signext is -- sign extender
    port(a: in  STD_LOGIC_VECTOR(15 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of signext is
begin
    y <= X"ffff" & a when a(15) else X"0000" & a;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity upimm is -- create upper immediate for LUI
    port(a: in  STD_LOGIC_VECTOR(15 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of upimm is
begin
    y <= a & X"0000";
end;

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_
IC_ARITH.all;

entity flopr is -- flip-flop with synchronous reset
    generic(width: integer);
    port(clk, reset: in  STD_LOGIC;
          d:             in  STD_LOGIC_VECTOR(width-1 downto 0);
          q:             out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture asynchronous of flopr is
begin
    process(clk, reset) begin
        if reset then q <= (others => '0');
        elsif rising_edge(clk) then
            q <= d;
        end if;
    end process;
end;

```

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux2 is -- two-input multiplexer
  generic(width: integer);
  port(d0, d1: in  STD_LOGIC_VECTOR(width-1 downto 0);
        s:      in  STD_LOGIC;
        y:      out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture behave of mux2 is
begin
  y <= d1 when s else d0;
end;

-- 3:1 mux needed for LUI
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux3 is -- three-input multiplexer
  generic(width: integer);
  port(d0, d1, d2: in  STD_LOGIC_VECTOR(width-1 downto 0);
        s:          in  STD_LOGIC_VECTOR(1 downto 0);
        y:          out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture behave of mux3 is
begin
  y <= d1 when s(1) else (d1 when s(0) else d0);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;

entity alu is
  port(a, b:      in  STD_LOGIC_VECTOR(31 downto 0);
        alucontrol: in  STD_LOGIC_VECTOR(3 downto 0); --SLL
        shamt:    in  STD_LOGIC_VECTOR(4 downto 0);   --SLL
        result:   buffer STD_LOGIC_VECTOR(31 downto 0);
        zero:     buffer STD_LOGIC;                   --BLEZ
        ltez:     out STD_LOGIC;                      --BLEZ
end;

architecture behave of alu is
  signal condinvb, sum: STD_LOGIC_VECTOR(31 downto 0);
begin
  condinvb <= not b when alucontrol(3) else b;
  sum <= a + condinvb + alucontrol(3);

  process(all) begin
    case alucontrol(2 downto 0) is
      when "000" => result <= a and b;
      when "001" => result <= a or b;
      when "010" => result <= sum;
      when "011" => result <= (0 => sum(31), others => '0');
```

```
        when "100"    => result <= (condinvb << shamt);    --SLL
        when others => result <= (others => 'X');
    end case;
end process;

zero <= '1' when result = X"00000000" else '0';
ltez <= zero or sum(31);
end;
```

Exercise 7.12

We modify the HDL for the single-cycle MIPS processor to include all instructions from Exercise 7.4.

SystemVerilog

```
module mipssingle(input  logic      clk, reset,
                  output logic [31:0] pc,
                  input  logic [31:0] instr,
                  output logic      memwrite,
                  output logic [31:0] alurestult,
                           writedata,
                  input  logic [31:0] readdata);

    logic      memtoreg;
    logic      alusrc;
    logic [1:0] regdst;      // JAL
    logic      regwrite, jump, pcsrc, zero;
    logic [3:0] alucontrol; // SRL
    logic      jal;          // JAL
    logic      lh, jr;       // LH, JR

    controller c(instr[31:26], instr[5:0], zero,
                 memtoreg, memwrite, pcsrc,
                 alusrc, regdst, regwrite, jump,
                 alucontrol,
                 jal, // JAL
                 lh, jr); // LH, JR
    datapath dp(clk, reset, memtoreg, pcsrc,
                alusrc, regdst, regwrite, jump,
                alucontrol,
                zero, pc, instr,
                alurestult, writedata, readdata,
                jal, // JAL
                lh, jr); // LH, JR
endmodule

module controller(input logic [5:0] op, funct,
                  input logic      zero,
```

```

        output logic      memtoreg, memwrite,
        output logic      pcsrc,
        output logic      alusrc,
        output logic [1:0] regdst,      // JAL
        output logic      regwrite,
        output logic      jump,
        output logic [3:0] alucontrol,  // SRL
        output logic      jal,          // JAL
        output logic      lh, jr);      // LH, JR

logic [1:0] aluop;
logic      branch;

maindec md(op, memtoreg, memwrite, branch,
           alusrc, regdst, regwrite, jump,
           aluop, jal, lh); // JAL, LH
aludec ad(funcnt, aluop, alucontrol, jr);

assign pcsrc = (branch & zero);

endmodule

module maindec(input  logic [5:0] op,
               output logic      memtoreg, memwrite,
               output logic      branch,
               output logic      alusrc,
               output logic [1:0] regdst, // JAL
               output logic      regwrite,
               output logic      jump,
               output logic [1:0] aluop,
               output logic      jal,    // JAL
               output logic      lh);    // LH

logic [11:0] controls;

assign {regwrite, regdst, alusrc, branch, memwrite,
       memtoreg, aluop, jump, jal, lh} = controls;

always_comb
case(op)
6'b000000: controls = 12'b101000010000; //Rtype
6'b100011: controls = 12'b100100100000; //LW
6'b101011: controls = 12'b000101000000; //SW
6'b000100: controls = 12'b000010001000; //BEQ
6'b001000: controls = 12'b100100000000; //ADDI
6'b000010: controls = 12'b000000000100; //J
6'b000011: controls = 12'b110000000110; //JAL
6'b100001: controls = 12'b100100100001; //LH
default:   controls = 12'bxxxxxxxxxxxx; //???
endcase
endmodule

module aludec(input  logic [5:0] funcnt,
```

```

        input logic [1:0] aluop,
        output logic [3:0] alucontrol, //increase to 4
bits for SRL
        output logic      jr); // JR

always_comb
case(aluop)
    2'b00: alucontrol = 4'b0010; // add
    2'b01: alucontrol = 4'b1010; // sub
    2'b11: alucontrol = 4'b1011; // slt
    default: case(funcnt) // RTYPE
        6'b100000: alucontrol = 4'b0010; // ADD
        6'b100010: alucontrol = 4'b1010; // SUB
        6'b100100: alucontrol = 4'b0000; // AND
        6'b100101: alucontrol = 4'b0001; // OR
        6'b101010: alucontrol = 4'b1011; // SLT
        6'b000000: alucontrol = 4'b0100; // SRL
        6'b001000: alucontrol = 4'b0000; // JR
        default: alucontrol = 4'bxxxx; // ???
    endcase
endcase

assign jr = (funcnt == 6'b001000); // JR
endmodule

module datapath(input logic      clk, reset,
                input logic      memtoreg, pcsrc,
                input logic      alusrc,
                input logic [1:0] regdst, // JAL
                input logic      regwrite, jump,
                input logic [3:0] alucontrol, // SRL
                output logic      zero,
                output logic [31:0] pc,
                input logic [31:0] instr,
                output logic [31:0] aluresult, writedata,
                input logic [31:0] readdata,
                input logic      jal, // JAL
                input logic      lh, // LH
                input logic      jr); // JR

logic [4:0] writereg;
logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
logic [31:0] signimm, signimmsh;
logic [31:0] srca, srcb;
logic [31:0] result;
logic [31:0] writeresult; // JAL
logic [15:0] half; // LH
logic [31:0] signhalf, memdata; // LH

// next PC logic
flopr #(32) pcreg(clk, reset, pcnext, pc);
adder      pcadd1(pc, 32'b100, pcplus4);
s12        immsh(signimm, signimmsh);

```

```

    adder      pcadd2(pcplus4, signimmsh, pcbranch);
    mux2 #(32) pcbrmux(pcplus4, pcbranch, pcsrc,
                      pcnextbr);
    mux3 #(32) pcmux(pcnextbr, {pcplus4[31:28],
                               instr[25:0], 2'b00}, srca,
                      {jr, jump}, pcnext);

    // register file logic
    regfile    rf(clk, regwrite, instr[25:21],
                  instr[20:16], writereg,
                  writeresult,
                  srca, writedata);

    mux2 #(32) wamux(result, pcplus4, jal,
                    writeresult); // JAL
    mux3 #(5)  wrmux(instr[20:16], instr[15:11], 5'd31,
                    regdst, writereg); // JAL

    // hardware to support LH
    mux2 #(16) lhmux1(readdata[15:0],
                     readdata[31:16],
                     aluresult[1], half); // LH
    signext    lhse(half, signhalf);      // LH
    mux2 #(32) lhmux2(readdata, signhalf, lh,
                     memdata); // LH

    mux2 #(32) resmux(aluresult, memdata, memtoreg,
                     result);
    signext    se(instr[15:0], signimm);

    // ALU logic
    mux2 #(32) srcbmux(writedata, signimm,
                      alusrc, srcb);
    alu        alu(srca, srcb, alucontrol,
                  instr[10:6], // SRL
                  aluresult, zero);
endmodule

// mux3 needed for JR
module mux3 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1, d2,
     input  logic [1:0]      s,
     output logic [WIDTH-1:0] y);

    assign #1 y = s[1] ? d2 : (s[0] ? d1 : d0);
endmodule

module alu(input  logic [31:0] A, B,
          input  logic [3:0]  F,
          input  logic [4:0]  shamt, // SRL
          output logic [31:0] Y,
          output logic        Zero);

```



```

logic [31:0] S, Bout;

assign Bout = F[3] ? ~B : B;
assign S = A + Bout + F[3]; // SRL

always_comb
    case (F[2:0])
        3'b000: Y = A & Bout;
        3'b001: Y = A | Bout;
        3'b010: Y = S;
        3'b011: Y = S[31];
        3'b100: Y = (Bout >> shamt); // SRL
    endcase

assign Zero = (Y == 32'b0);

endmodule

module regfile(input logic clk,
               input logic we3,
               input logic [4:0] ra1, ra2, wa3,
               input logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

    logic [31:0] rf[31:0];

    // three ported register file
    // read two ports combinationaly
    // write third port on rising edge of clk
    // register 0 hardwired to 0
    always_ff @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
    assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule

module adder(input logic [31:0] a, b,
             output logic [31:0] y);

    assign y = a + b;
endmodule

module sl2(input logic [31:0] a,
           output logic [31:0] y);

    // shift left by 2
    assign y = {a[29:0], 2'b00};
endmodule

module signext(input logic [15:0] a,
               output logic [31:0] y);

```

```

    assign y = {{16{a[15]}}, a};
endmodule

module flopr #(parameter WIDTH = 8)
    (input  logic          clk, reset,
     input  logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1,
     input  logic             s,
     output logic [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mips is -- single cycle MIPS processor
    port(clk, reset:      in  STD_LOGIC;
          pc:             out STD_LOGIC_VECTOR(31 downto 0);
          instr:          in  STD_LOGIC_VECTOR(31 downto 0);
          memwrite:       out STD_LOGIC;
          alurestult:     out STD_LOGIC_VECTOR(31 downto 0);
          writedata:      out STD_LOGIC_VECTOR(31 downto 0);
          readdata:       in  STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of mips is
    port(op, funct:      in  STD_LOGIC_VECTOR(5 downto 0);
          zero:          in  STD_LOGIC;
          memtoreg, memwrite: out STD_LOGIC;
          pcsrc:         out STD_LOGIC;
          alusrc:        out STD_LOGIC;
          regdst:        out STD_LOGIC_VECTOR(1 downto 0); --JAL
          regwrite:      out STD_LOGIC;
          jump:          out STD_LOGIC;
          alucontrol:    out STD_LOGIC_VECTOR(3 downto 0); -- SRL
          jal, lh, jr:   out STD_LOGIC); --
JAL, LH, JR

    component controller
        port(op, funct:      in  STD_LOGIC_VECTOR(5 downto 0);
              zero:          in  STD_LOGIC;
              memtoreg, memwrite: out STD_LOGIC;
              pcsrc:         out STD_LOGIC;

```

```

        alusrc:          out STD_LOGIC;
    regdst:             out STD_LOGIC_VECTOR(1 downto 0); --JAL
        regwrite:       out STD_LOGIC;
        jump:           out STD_LOGIC;
        alucontrol:     out STD_LOGIC_VECTOR(3 downto 0);
-- SRL
        jal, lh, jr:    out STD_LOGIC);
- JAL, LH
    end component;
    component datapath
        port(clk, reset:      in  STD_LOGIC;
            memtoereg, psrc:   in  STD_LOGIC;
            alusrc:           in  STD_LOGIC;
            alusrc:           in  STD_LOGIC;
            regdst:           in  STD_LOGIC_VECTOR(1 downto 0);
-- JAL
            regwrite, jump:    in  STD_LOGIC;
            alucontrol:       in  STD_LOGIC_VECTOR(3 downto 0);
-- SRL
            zero:             out STD_LOGIC;
            pc:               buffer STD_LOGIC_VECTOR(31 downto 0);
            instr:            in  STD_LOGIC_VECTOR(31 downto 0);
            aluresult:        buffer STD_LOGIC_VECTOR(31 downto 0);
            writedata:        buffer STD_LOGIC_VECTOR(31 downto 0);
            readdata:         in  STD_LOGIC_VECTOR(31 downto 0);
            jal, lh, jr:      out STD_LOGIC);
-- JAL, LH, JR
    end component;
    signal memtoereg: STD_LOGIC;
    signal alusrc: STD_LOGIC;
    signal regdst: STD_LOGIC_VECTOR(1 downto 0); --JAL
    signal regwrite, jump, psrc: STD_LOGIC;
    signal zero: STD_LOGIC;
    signal alucontrol: STD_LOGIC_VECTOR(3 downto 0); -- SRL
    signal jal, lh, jr: STD_LOGIC; -- JAL, LH, JR
begin
    cont: controller port map(instr(31 downto 26), instr(5 downto
0),
                                zero, memtoereg, memwrite, psrc, alusrc,
                                regdst, regwrite, jump, alucontrol,
                                jal, lh, jr); -- JAL, LH, JR
    dp: datapath port map(clk, reset, memtoereg, psrc, alusrc,
regdst,
                                regwrite, jump, alucontrol, zero, pc, instr,
                                aluresult, writedata, readdata,
                                jal, lh, jr); -- JAL, LH, JR
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity controller is -- single cycle control decoder
    port(op, funct:      in  STD_LOGIC_VECTOR(5 downto 0);
        zero:           in  STD_LOGIC;

```

```

        memtoreg, memwrite: out STD_LOGIC;
        pcsrc:               out STD_LOGIC;
        alusrc:              out STD_LOGIC;
        regdst:              out STD_LOGIC_VECTOR(1 downto 0); --JAL
        regwrite:            out STD_LOGIC;
        jump:                out STD_LOGIC;
        alucontrol:          out STD_LOGIC_VECTOR(3 downto 0); -- SRL
        jal, lh, jr:         out STD_LOGIC);          --
JAL, LH, JR
    end;

    architecture struct of controller is
    component maindec
        port(op:              in  STD_LOGIC_VECTOR(5 downto 0);
              memtoreg, memwrite: out STD_LOGIC;
              branch:         out STD_LOGIC;
              alusrc:         out STD_LOGIC;
              regdst:         out STD_LOGIC_VECTOR(1 downto 0);
--JAL
              regwrite:       out STD_LOGIC;
              jump:           out STD_LOGIC;
              aluop:          out STD_LOGIC_VECTOR(1 downto 0);
              jal, lh:        out STD_LOGIC); --JAL, LH
        end component;
    component aludec
        port(funcnt:         in  STD_LOGIC_VECTOR(5 downto 0);
              aluop:         in  STD_LOGIC_VECTOR(1 downto 0);
              alucontrol:    out STD_LOGIC_VECTOR(3 downto 0); -- SRL
              jr:            out STD_LOGIC); -- JR
        end component;
    signal aluop: STD_LOGIC_VECTOR(1 downto 0);
    signal branch: STD_LOGIC;
    begin
        md: maindec port map(op, memtoreg, memwrite, branch,
                              alusrc, regdst, regwrite, jump, aluop,
                              jal, lh); --JAL, LH
        ad: aludec port map(funcnt, aluop, alucontrol, jr); --JR

        pcsrc <= (branch and zero);
    end;

    library IEEE; use IEEE.STD_LOGIC_1164.all;

    entity maindec is -- main control decoder
        port(op:              in  STD_LOGIC_VECTOR(5 downto 0);
              memtoreg, memwrite: out STD_LOGIC;
              branch:         out STD_LOGIC;
              alusrc:         out STD_LOGIC;
              regdst:         out STD_LOGIC_VECTOR(1 downto 0); --JAL
              regwrite:       out STD_LOGIC;
              jump:           out STD_LOGIC;
              aluop:          out STD_LOGIC_VECTOR(1 downto 0);
              jal, lh:        out STD_LOGIC); --JAL, LH
    end entity;

```

```

end;

architecture behave of maindec is
    signal controls: STD_LOGIC_VECTOR(11 downto 0);
begin
    process(all) begin
        case op is
            when "000000" => controls <= "101000010000"; -- RTYPE
            when "100011" => controls <= "100100100000"; -- LW
            when "101011" => controls <= "000101000000"; -- SW
            when "000100" => controls <= "000010001000"; -- BEQ
            when "001000" => controls <= "100100000000"; -- ADDI
            when "000010" => controls <= "000000000100"; -- J
            when "000011" => controls <= "110000000110"; -- JAL
            when "100001" => controls <= "100100100001"; -- LH
            when others => controls <= "-----"; -- illegal op
        end case;
    end process;

    (regwrite, regdst, alusrc, branch, memwrite,
     memtoreg, aluop(1 downto 0), jump, jal, lh) <= controls;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity aludec is -- ALU control decoder
    port(funcnt:      in  STD_LOGIC_VECTOR(5 downto 0);
          aluop:      in  STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: out STD_LOGIC_VECTOR(3 downto 0); -- SRL
          jr:         out STD_LOGIC); -- JR
end;

architecture behave of aludec is
begin
    process(all) begin
        case aluop is
            when "00" => alucontrol <= "0010"; -- add
            when "01" => alucontrol <= "1010"; -- sub
            when "11" => alucontrol <= "1011"; -- slt
            when others => case funcnt is -- R-type instructions
                when "100000" => alucontrol <= "0010";
                when "100010" => alucontrol <= "1010";
                when "100100" => alucontrol <= "0000";
                when "100101" => alucontrol <= "0001"; -- or
                when "101010" => alucontrol <= "1011";
                when "000000" => alucontrol <= "0100";
                when "001000" => alucontrol <= "0000"; -- jr
                when others => alucontrol <= "----"; -- ???
            end case;
        end case;
    end process;
end;

```

```

                                end case;
                                end case;
                                end process;

                                jr <= '1' when (funct = "001000"); --JR
                                end;

                                library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOG-
                                IC_ARITH.all;

                                entity datapath is -- MIPS datapath
                                port(clk, reset:          in  STD_LOGIC;
                                    memtoreg, pcsrc:      in  STD_LOGIC;
                                    alusrc:               in  STD_LOGIC;
                                    alusrc:               in  STD_LOGIC;
                                    regdst:               in  STD_LOGIC_VECTOR(1 downto 0); -- JAL
                                    regwrite, jump:      in  STD_LOGIC;
                                    alucontrol:           in  STD_LOGIC_VECTOR(3 downto 0); --
                                - SRL
                                    zero:                out STD_LOGIC;
                                    pc:                  buffer STD_LOGIC_VECTOR(31 downto 0);
                                    instr:               in  STD_LOGIC_VECTOR(31 downto 0);
                                    aluresult:           buffer STD_LOGIC_VECTOR(31 downto 0);
                                    writedata:           buffer STD_LOGIC_VECTOR(31 downto 0);
                                    readdata:            in  STD_LOGIC_VECTOR(31 downto 0);
                                    jal, lh, jr:          out STD_LOGIC); --
                                JAL, LH, JR
                                end;

                                architecture struct of datapath is
                                component alu
                                port(a, b:              in  STD_LOGIC_VECTOR(31 downto 0);
                                    alucontrol: in  STD_LOGIC_VECTOR(3 downto 0); --SRL
                                    shamt:          in  STD_LOGIC_VECTOR(4 downto 0); --SRL
                                    result:        buffer STD_LOGIC_VECTOR(31 downto 0);
                                    zero:          buffer STD_LOGIC);
                                end component;
                                component regfile
                                port(clk:              in  STD_LOGIC;
                                    we3:               in  STD_LOGIC;
                                    ra1, ra2, wa3: in  STD_LOGIC_VECTOR(4 downto 0);
                                    wd3:               in  STD_LOGIC_VECTOR(31 downto 0);
                                    rd1, rd2:          out STD_LOGIC_VECTOR(31 downto 0));
                                end component;
                                component adder
                                port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
                                    y:      out STD_LOGIC_VECTOR(31 downto 0));
                                end component;
                                component sl2
                                port(a: in  STD_LOGIC_VECTOR(31 downto 0);
                                    y: out STD_LOGIC_VECTOR(31 downto 0));
                                end component;
                                component signext

```

[illegible]

-LH

```

signal jumpsel:          STD_LOGIC_VECTOR(1 downto 0);    --JR
begin
    -- next PC logic
    pcjump <= pcplus4(31 downto 28) & instr(25 downto 0) & "00";
    jumpsel <= jr & jump;
    pcreg: flopr generic map(32) port map(clk, reset, pcnext, pc);
    pcadd1: adder port map(pc, X"00000004", pcplus4);
    immsh: sl2 port map(signimm, signimmsh);
    pcadd2: adder port map(pcplus4, signimmsh, pcbranch);
    pcbrmux: mux2 generic map(32) port map(pcplus4, pcbranch,
                                             pcsrc, pcnextbr);
    pcmux: mux3 generic map(32) port map(pcnextbr, pcjump, srca,
    jumpsel, pcnext);

    -- register file logic
    rf: regfile port map(clk, regwrite, instr(25 downto 21),
                         instr(20 downto 16), writereg, result, srca,
    writedata);
    wrmux: mux2 generic map(5) port map(instr(20 downto 16),
    instr(15 downto 11),

```

```

regdst, writereg);

-- hardware to support LH
lhmux1: mux2 generic map(16) port map(readdata(15 downto 0),
readdata(31 downto 16), aluresult(1), half);
lhse: signext port map(half, signhalf);
lhmux2: mux2 generic map(32) port map(readdata, signhalf, lh,
memdata);

resmux: mux2 generic map(32) port map(aluresult, readdata,
memtoreg, result);
se: signext port map(instr(15 downto 0), signimm);
-- ALU logic
srcbmux: mux2 generic map(32) port map(writedata, signimm,
alusrc, srcb);
mainalu: alu port map(srca, srcb, alucontrol, instr(10 downto
6), --SRL
aluresult, zero);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;

entity regfile is -- three-port register file
    port(clk:          in  STD_LOGIC;
          we3:          in  STD_LOGIC;
          ral, ra2, wa3: in  STD_LOGIC_VECTOR(4 downto 0);
          wd3:          in  STD_LOGIC_VECTOR(31 downto 0);
          rd1, rd2:     out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of regfile is
    type ramtype is array (31 downto 0) of STD_LOGIC_VECTOR(31
downto 0);
    signal mem: ramtype;
begin
    -- three-ported register file
    -- read two ports combinatorially
    -- write third port on rising edge of clock
    -- register 0 hardwired to 0
    process(clk) begin
        if rising_edge(clk) then
            if we3 = '1' then mem(to_integer(wa3)) <= wd3;
            end if;
        end if;
    end process;
    process(all) begin
        if (to_integer(ral) = 0) then rd1 <= X"00000000"; -- register
0 holds 0
        else rd1 <= mem(to_integer(ral));
        end if;
    end process;
end;

```



```

        if (to_integer(ra2) = 0) then rd2 <= X"00000000";
        else rd2 <= mem(to_integer(ra2));
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD_UNSIGNED.all;

entity adder is -- adder
    port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
          y:      out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of adder is
begin
    y <= a + b;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity sl2 is -- shift left by 2
    port(a: in  STD_LOGIC_VECTOR(31 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of sl2 is
begin
    y <= a(29 downto 0) & "00";
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity signext is -- sign extender
    port(a: in  STD_LOGIC_VECTOR(15 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of signext is
begin
    y <= X"ffff" & a when a(15) else X"0000" & a;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity upimm is -- create upper immediate for LUI
    port(a: in  STD_LOGIC_VECTOR(15 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of upimm is
begin

```

```
        y <= a & X"0000";
    end;

    library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOG-
    IC_ARITH.all;

    entity flopr is -- flip-flop with synchronous reset
        generic(width: integer);
        port(clk, reset: in STD_LOGIC;
            d:          in STD_LOGIC_VECTOR(width-1 downto 0);
            q:          out STD_LOGIC_VECTOR(width-1 downto 0));
    end;

    architecture asynchronous of flopr is
    begin
        process(clk, reset) begin
            if reset then q <= (others => '0');
            elsif rising_edge(clk) then
                q <= d;
            end if;
        end process;
    end;

    library IEEE; use IEEE.STD_LOGIC_1164.all;
    entity mux2 is -- two-input multiplexer
        generic(width: integer);
        port(d0, d1: in STD_LOGIC_VECTOR(width-1 downto 0);
            s:      in STD_LOGIC;
            y:      out STD_LOGIC_VECTOR(width-1 downto 0));
    end;

    architecture behave of mux2 is
    begin
        y <= d1 when s else d0;
    end;

    -- 3:1 mux needed for LUI
    library IEEE; use IEEE.STD_LOGIC_1164.all;
    entity mux3 is -- three-input multiplexer
        generic(width: integer);
        port(d0, d1, d2: in STD_LOGIC_VECTOR(width-1 downto 0);
            s:          in STD_LOGIC_VECTOR(1 downto 0);
            y:          out STD_LOGIC_VECTOR(width-1 downto 0));
    end;

    architecture behave of mux3 is
    begin
        y <= d1 when s(1) else (d1 when s(0) else d0);
    end;

    library IEEE; use IEEE.STD_LOGIC_1164.all;
    use IEEE.NUMERIC_STD_UNSIGNED.all;
```

```

entity alu is
  port(a, b:          in  STD_LOGIC_VECTOR(31 downto 0);
        alucontrol: in  STD_LOGIC_VECTOR(3 downto 0);    --SRL
        shamt:        in  STD_LOGIC_VECTOR(4 downto 0);    --SRL
        result:        buffer STD_LOGIC_VECTOR(31 downto 0);
        zero:          buffer STD_LOGIC);
end;

architecture behave of alu is
  signal condinvb, sum: STD_LOGIC_VECTOR(31 downto 0);
begin
  condinvb <= not b when alucontrol(3) else b;
  sum <= a + condinvb + alucontrol(3);

  process(all) begin
    case alucontrol(2 downto 0) is
      when "000" => result <= a and b;
      when "001" => result <= a or b;
      when "010" => result <= sum;
      when "011" => result <= (0 => sum(31), others => '0');
      when "100" => result <= (condinvb >> shamt);    --SRL
      when others => result <= (others => 'X');
    end case;
  end process;

  zero <= '1' when result = X"00000000" else '0';
end;

```

We modify the test code to include the extended instructions.

```

# mipstest.asm
# Sarah_Harris@hmc.edu 20 February 2012
#
# Test the MIPS processor.
# add, sub, and, or, slt, addi, lw, sw, beq, j
# If successful, it should write the value 4135 to address 92

#      Assembly      Description      Address Machine
main:  addi $2, $0, 5      # initialize $2 = 5      0      20020005
      lui  $2, 0xEFE      # $2 = 0xEFE00000      4      3C020efe
      sll  $2, $2, 4      # $2 = 0xEFE00000      8      00021100
      jal  forward
      addi $3, $0, 14      # not executed        10     2263000e
back:  blez $2, here      # should be taken     14     18400002
forward: addi $3, $ra, -4  # $3 <= $ra - 4 = 12   18     23e3fffc
      j    back          1c     08000005
here:  addi $7, $3, -9      # initialize $7 = 3    20     2067fff7
      addi $6, $0, 5      # initialize $6 = 5    24     20060005
      or   $4, $7, $6      # $4 <= 3 or 5 = 7     28     00e62025
      and  $5, $3, $4      # $5 <= 12 and 3 = 4   2c     00642824
      add  $5, $5, $4      # $5 = 4 + 7 = 11     30     00a42820
      beq  $5, $7, end     # shouldn't be taken   34     10a7000c
      slti $4, $3, 7      # $4 = 12 < 7 = 0     38     28640007
      beq  $4, $0, around  # should be taken     3c     10800001
      addi $5, $0, 0      # shouldn't happen     40     20050000
around: slti $4, $7, 5     # $4 = 3 < 5 = 1     44     28e40005

```

| | | | | | |
|------|------|---------------|----------------------------|----|----------|
| | add | \$7, \$4, \$5 | # \$7 = 1 + 11 = 12 | 48 | 00853820 |
| | sub | \$7, \$7, \$6 | # \$7 = 12 - 5 = 7 | 4c | 00e63822 |
| | sw | \$7, 68(\$3) | # [68+12] = [80] = 7 | 50 | ac670044 |
| | sw | \$2, 88(\$0) | # [88] = 0xEFE00000 | 54 | ac020058 |
| | lw | \$2, 80(\$0) | # \$2 = [80] = 7 | 58 | 8c020050 |
| | lh | \$3, 90(\$0) | # \$2 = 0xFFFFEFE0 | 5c | 8403005a |
| | j | end | # should be taken | 60 | 0800001a |
| | addi | \$2, \$0, 1 | # shouldn't happen | 64 | 20020001 |
| end: | sub | \$8, \$2, \$3 | # \$8 = 7 - (-4128) = 4135 | 68 | 00434022 |
| | sw | \$8, 92(\$0) | # [92] = 4135 | 6c | ac08005c |

FIGURE 7.10 Assembly and machine code for MIPS test program

Modified Testbench

SystemVerilog

```
module testbench();

    logic        clk;
    logic        reset;

    logic [31:0] aluout, writedata, readdata;
    logic memwrite;

    // instantiate unit to be tested
    topsingle uut(clk, reset, readdata, writedata,
                  aluout, memwrite);

    // initialize test
    initial
    begin
        reset <= 1; # 22; reset <= 0;
    end

    // generate clock to sequence tests
    always
    begin
        clk <= 1; # 5; clk <= 0; # 5;
    end

    // check results
    always @(negedge clk)
    begin
        if(memwrite & aluout == 92) begin
            if(writedata == 4135)
                $display("Simulation succeeded");
            else begin
                $display("Simulation failed");
            end
            $stop;
        end
    end
endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_UNSIGNED.all;
entity testbench is
end;

architecture test of testbench is
    component top
        port(clk, reset:          in   STD_LOGIC;
              readdata:           inout STD_LOGIC_VECTOR(31 downto 0);
              writedata, dataadr:  inout STD_LOGIC_VECTOR(31 downto 0);
              memwrite:           inout STD_LOGIC);
    end component;
    signal readdata, writedata, dataadr:
        STD_LOGIC_VECTOR(31 downto 0);
    signal clk, reset, memwrite: STD_LOGIC;
begin
    -- instantiate device to be tested
    dut: top port map(clk, reset, readdata, writedata, dataadr, memwrite);

    -- Generate clock with 10 ns period
    process begin
        clk <= '1';
        wait for 5 ns;
        clk <= '0';
        wait for 5 ns;
    end process;

    -- Generate reset for first two clock cycles
    process begin
        reset <= '1';
        wait for 22 ns;
        reset <= '0';
        wait;
    end process;

    -- check that 4135 gets written to address 92
    -- at end of program
    process (clk) begin
        if (clk'event and clk = '0' and memwrite = '1' and
            (conv_integer(dataadr) = 92)) then
            if (conv_integer(writedata) = 4135) then
                report "Just kidding: Simulation succeeded"
                    severity failure;
            else
                report "Simulation failed"
                    severity failure;
            end if;
        end if;
    end process;
end;
```

(a) srlv

First, we show the modifications to the ALU.

 


FIGURE 7.11 Modified ALU to support srlv

Next, we show the modifications to the ALU decoder.

| ALUControl _{3:0} | Function |
|---------------------------|----------------------|
| 0000 | A AND B |
| 0001 | A OR B |
| 0010 | A + B |
| 0011 | not used |
| 1000 | A AND \overline{B} |
| 1001 | A OR \overline{B} |
| 1010 | A - B |
| 1011 | SLT |
| 0100 | SRLV |

FIGURE 7.12 Modified ALU operations to support srlv

| ALUOp | Funct | ALUControl |
|-------|---------------|-------------------------------------|
| 00 | X | 0010 (add) |
| X1 | X | 1010 (subtract) |
| 1X | 100000 (add) | 0010 (add) |
| 1X | 100010 (sub) | 1010 (subtract) |
| 1X | 100100 (and) | 0000 (and) |
| 1X | 100101 (or) | 0001 (or) |
| 1X | 101010 (slt) | 1011 (set less than) |
| 1X | 000110 (srlv) | 0100 (shift right logical variable) |

TABLE 7.16 ALU decoder truth table

Next, we show the changes to the datapath. The only modification is the width of *ALUControl*. No changes are made to the datapath main control FSM.

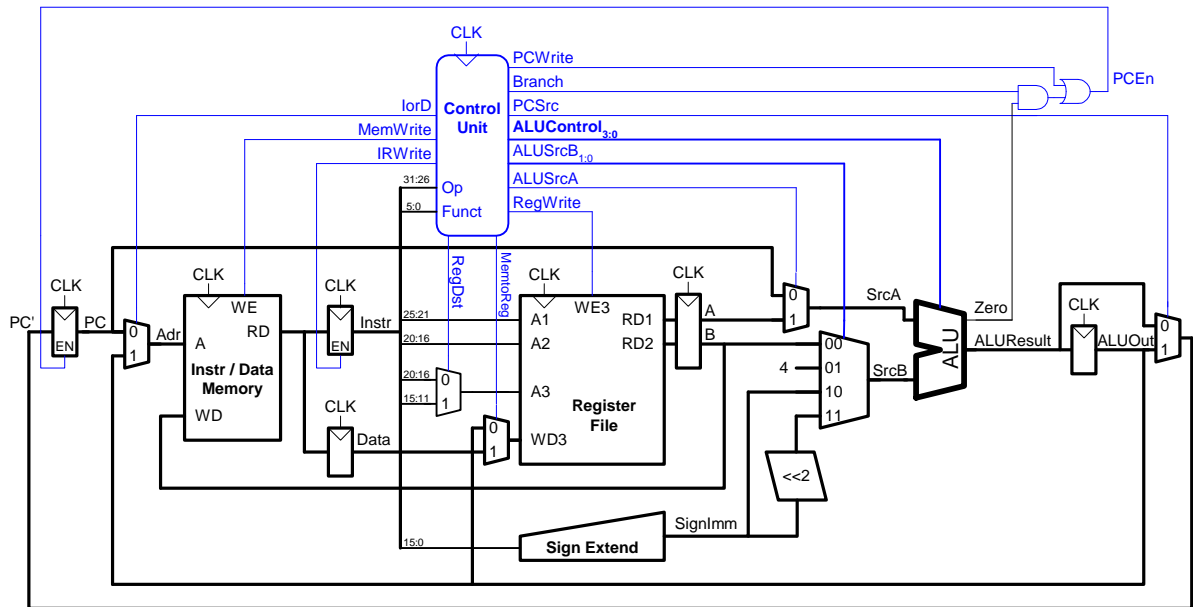


FIGURE 7.13 Modified multicycle MIPS datapath to support `sll`

(b) `ori`

We add a zero extension unit to the datapath, extend the *ALUSrcB* signal from 2 bits to 3 bits, and extend the SrcB multiplexer from 4 inputs to 5 inputs. We also modify the ALU decoder and main control FSM.

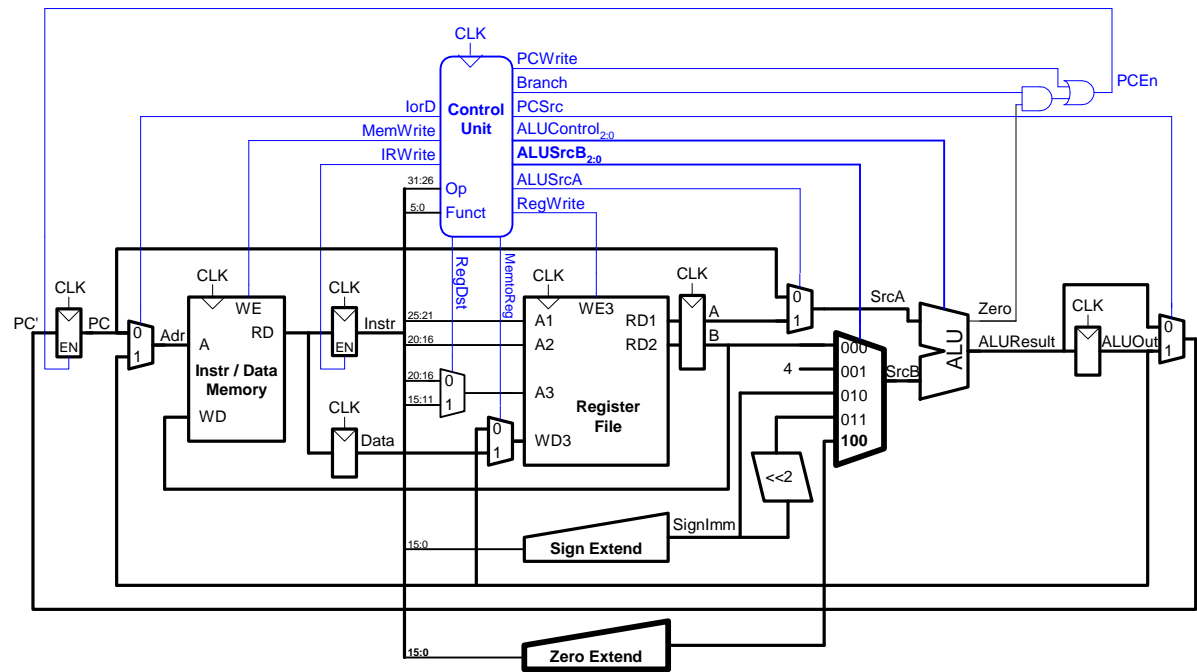



FIGURE 7.14 Modified datapath for *ori*

| ALUOp | Funct | ALUControl |
|-----------|--------------|-----------------|
| 00 | X | 010 (add) |
| 01 | X | 110 (subtract) |
| 11 | X | 001 (or) |
| 10 | 100000 (add) | 010 (add) |
| 10 | 100010 (sub) | 110 (subtract) |
| 10 | 100100 (and) | 000 (and) |

TABLE 7.17 ALU decoder truth table


| ALUOp | Funct | ALUControl |
|-------|--------------|---------------------|
| 10 | 100101 (or) | 001 (or) |
| 10 | 101010 (slt) | 111 (set less than) |

TABLE 7.17 ALU decoder truth table

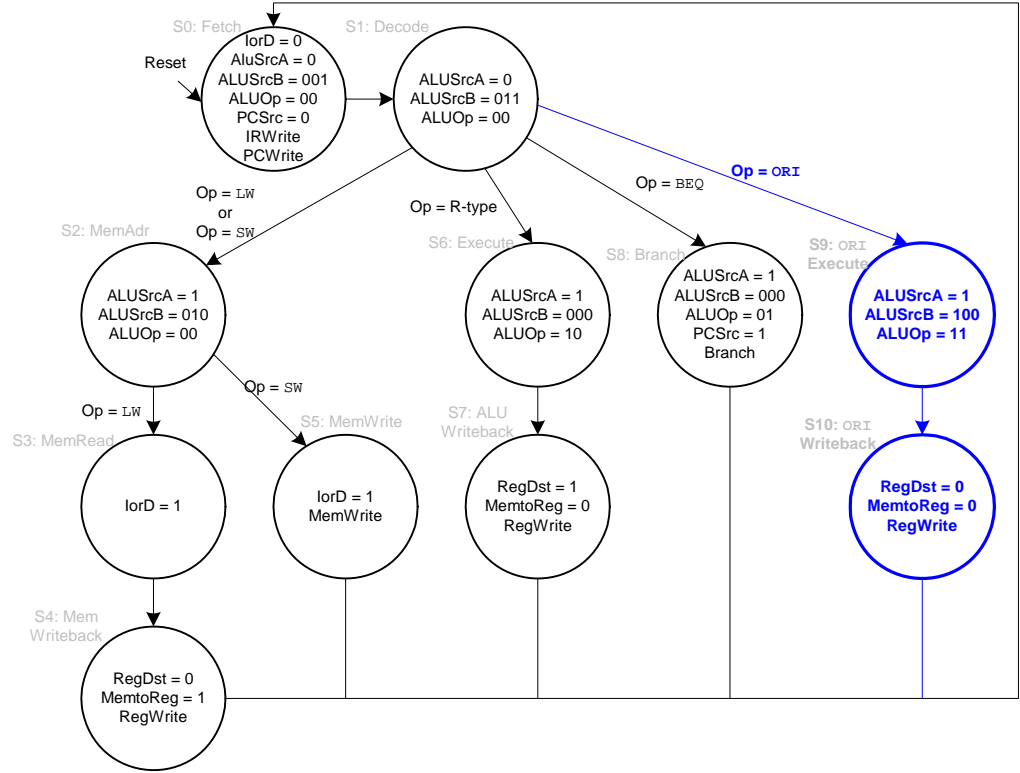

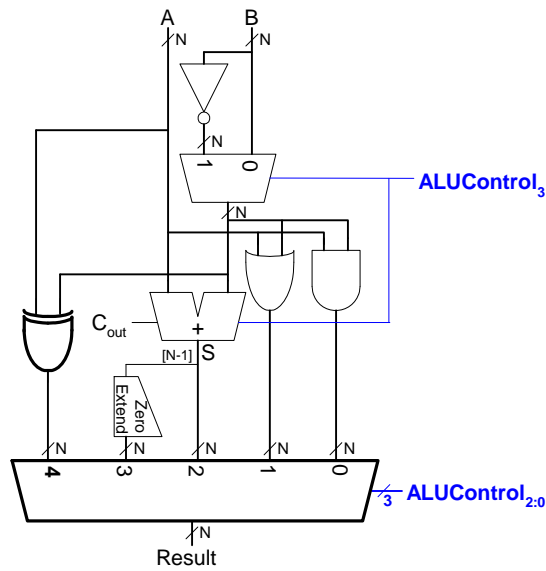(c) xori

First, we modify the ALU and the ALU decoder.




1

| ALUControl _{3:0} | Function |
|---------------------------|----------------------|
| 0000 | A AND B |
| 0001 | A OR B |
| 0010 | A + B |
| 0011 | not used |
| 1000 | A AND \overline{B} |
| 1001 | A OR \overline{B} |
| 1010 | A - B |
| 1011 | SLT |
| 0100 | A XOR B |

| ALUOp | Funct | ALUControl |
|-----------|--------------|----------------------|
| 00 | X | 0010 (add) |
| 01 | X | 1010 (subtract) |
| 11 | X | 0100 (xor) |
| 10 | 100000 (add) | 0010 (add) |
| 10 | 100010 (sub) | 1010 (subtract) |
| 10 | 100100 (and) | 0000 (and) |
| 10 | 100101 (or) | 0001 (or) |
| 10 | 101010 (slt) | 1011 (set less than) |

TABLE 7.18 ALU decoder truth table for `xori`

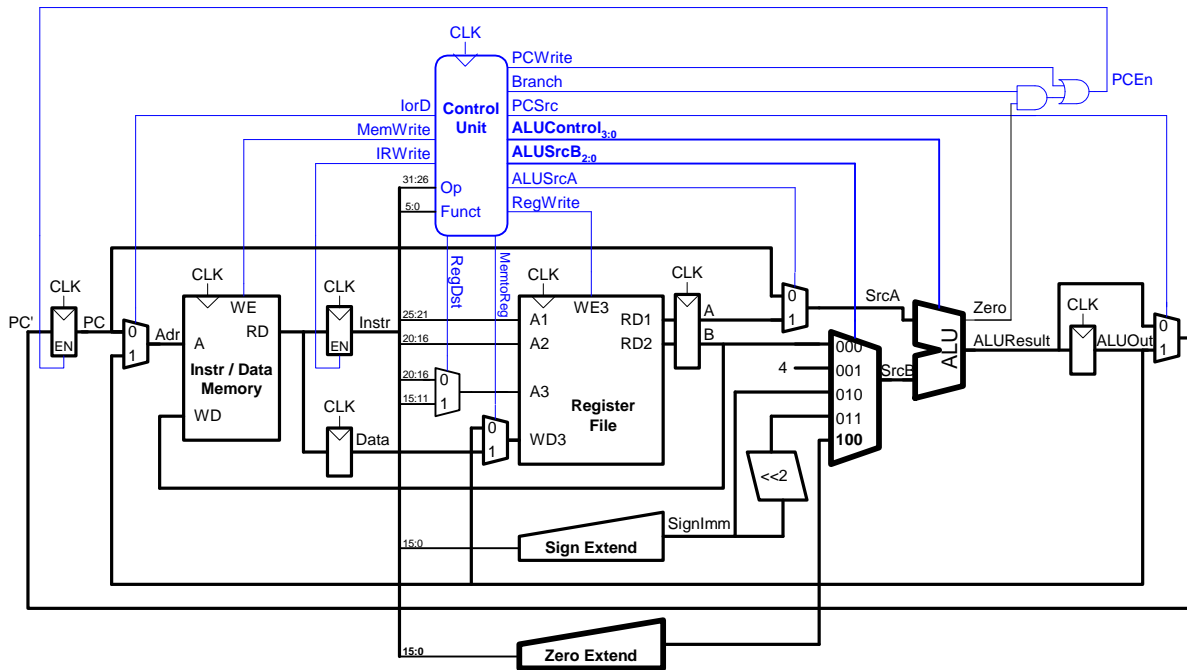Next, we modify the datapath. We change the buswidth of the *ALUControl* signal from 3 bits to 4 bits and the *ALUSrcB* signal from 2 bits to 3 bits. We also extend the SrcB mux and add a zero-extension unit.






First, we extend the ALU Decoder for jr.

TABLE 7.19 ALU decoder truth table with j_r

| ALUOp | Funct | ALUControl |
|-------|--------------|---------------------|
| 1X | 101010 (slt) | 111 (set less than) |
| 1X | 001000 (jr) | 010 (add) |

TABLE 7.19 ALU decoder truth table with jr

Next, we modify the main controller. The datapath requires no modification.

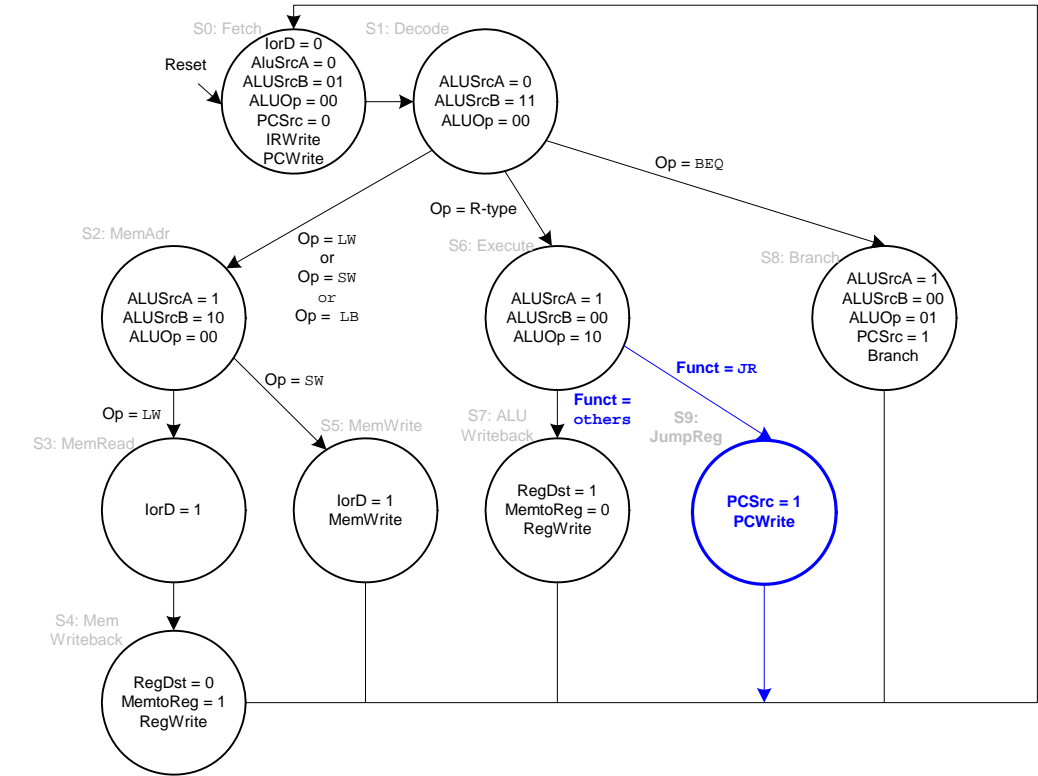

Exercise 7.14

(a) bne

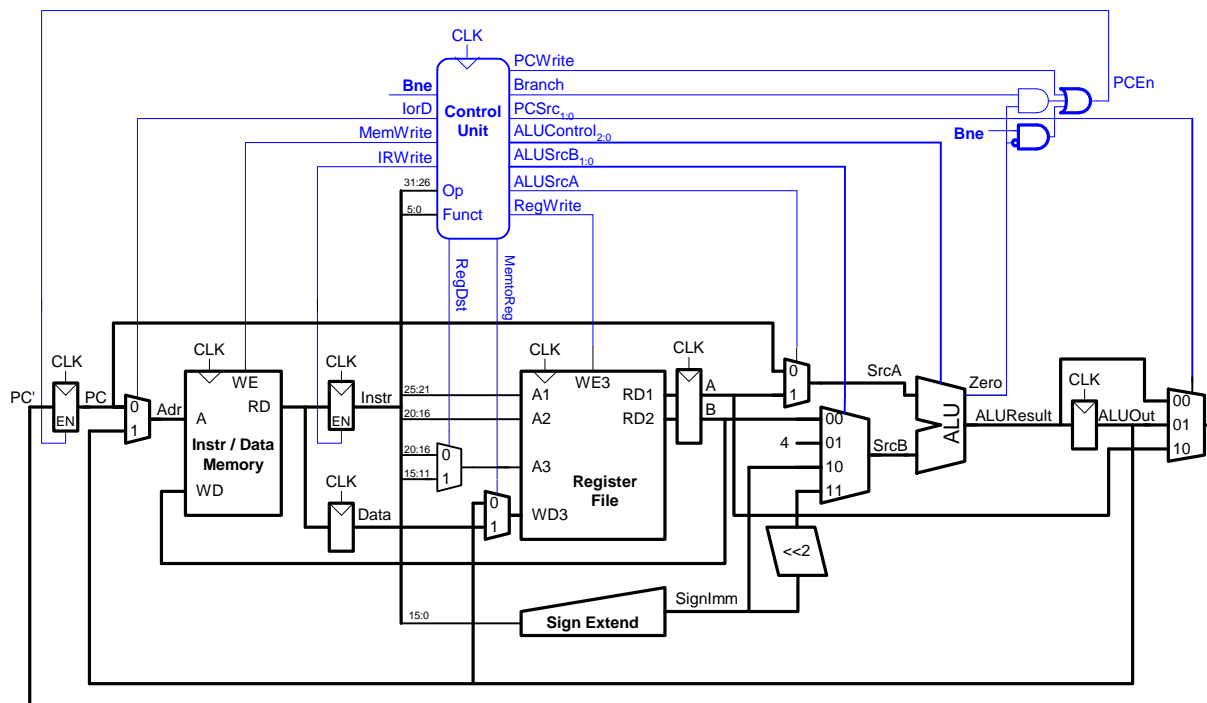


FIGURE 7.15 Modified datapath for bne



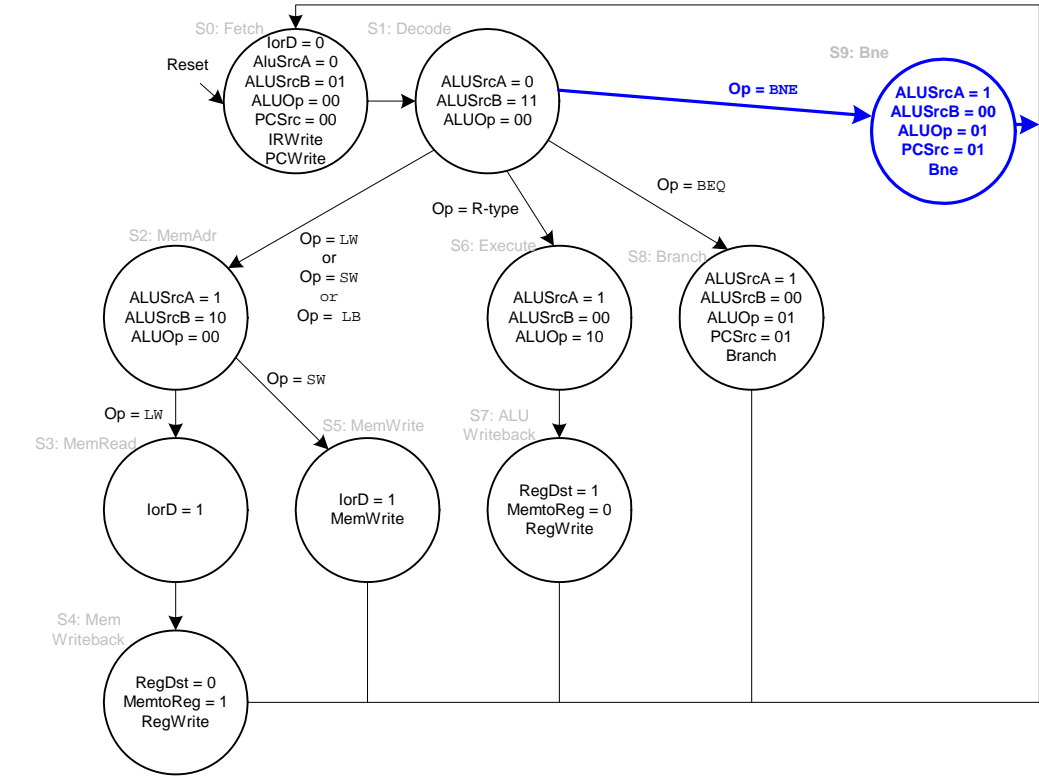


FIGURE 7.16 Modified FSM for `bne`


7.14 (b) 1b

 


* The SE unit is a sign extension unit.

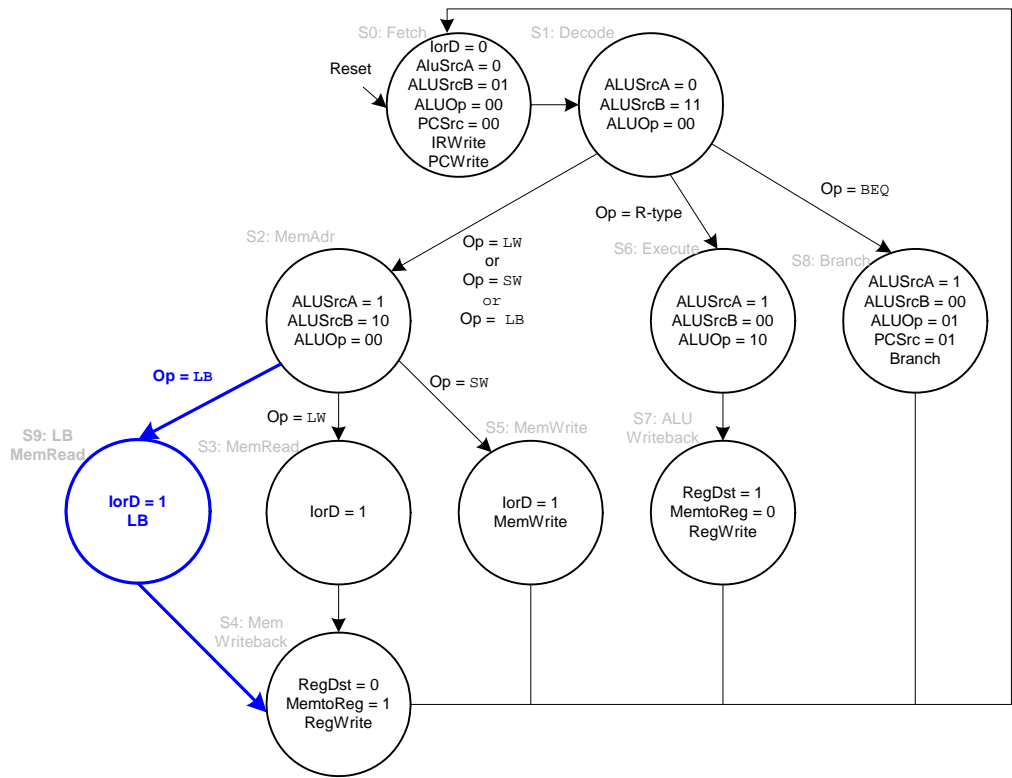

7.14 (c) lbu

 

* The ZE unit is a zero extension unit.

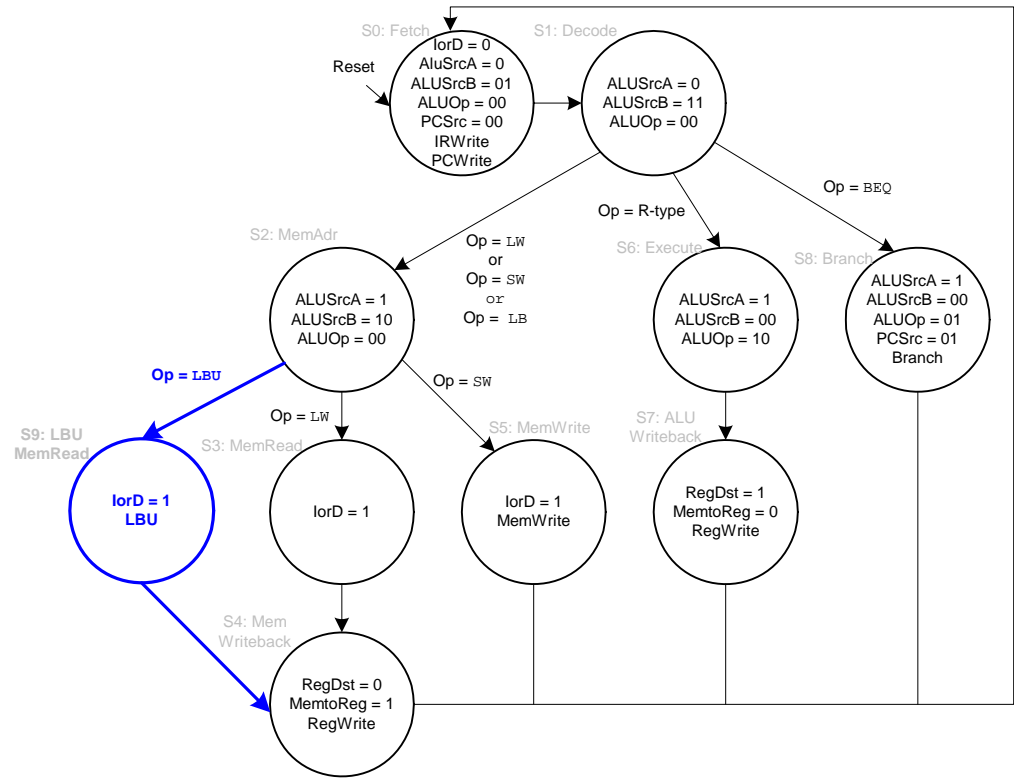

7.14 (d) and i


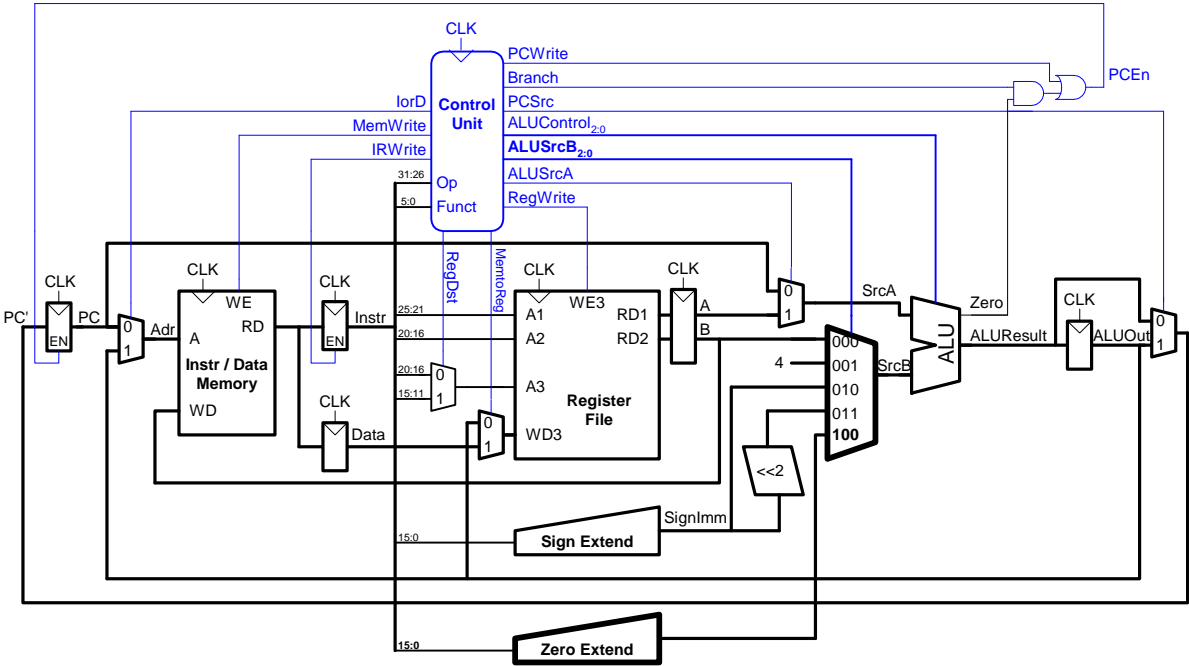


FIGURE 7.17 Modified datapath for andi


| ALUOp | Funct | ALUControl |
|-------|--------------|---------------------|
| 00 | X | 010 (add) |
| 01 | X | 110 (subtract) |
| 11 | X | 000 (and) |
| 10 | 100000 (add) | 010 (add) |
| 10 | 100010 (sub) | 110 (subtract) |
| 10 | 100100 (and) | 000 (and) |
| 10 | 100101 (or) | 001 (or) |
| 10 | 101010 (slt) | 111 (set less than) |

TABLE 7.20 ALU decoder truth table

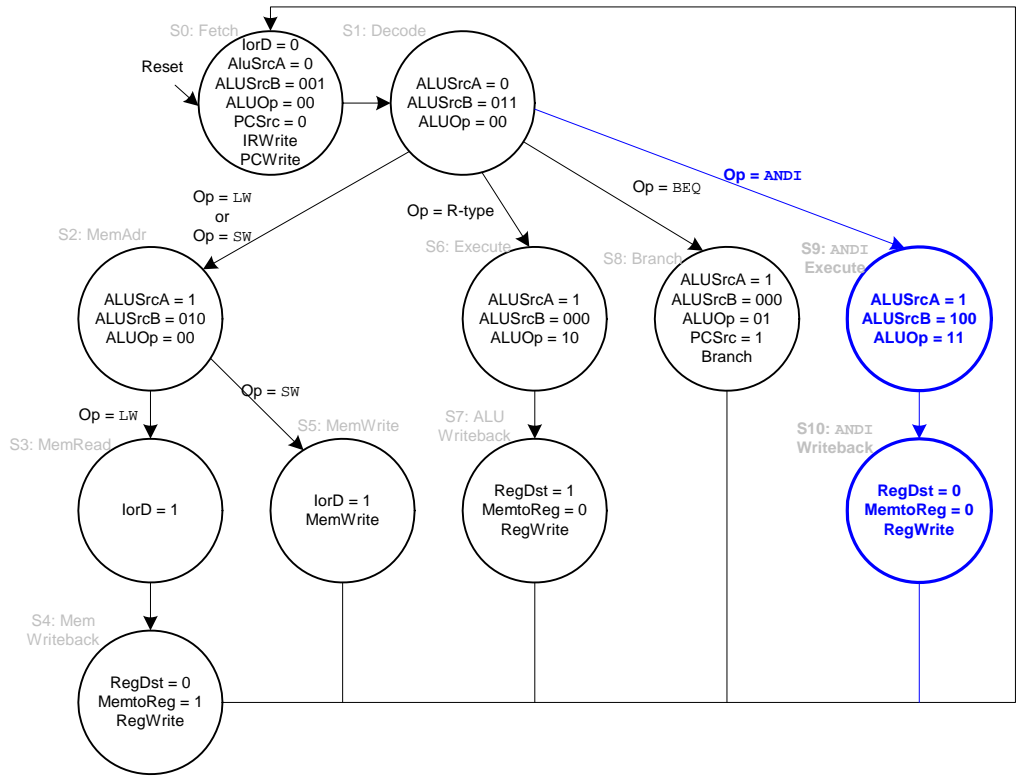


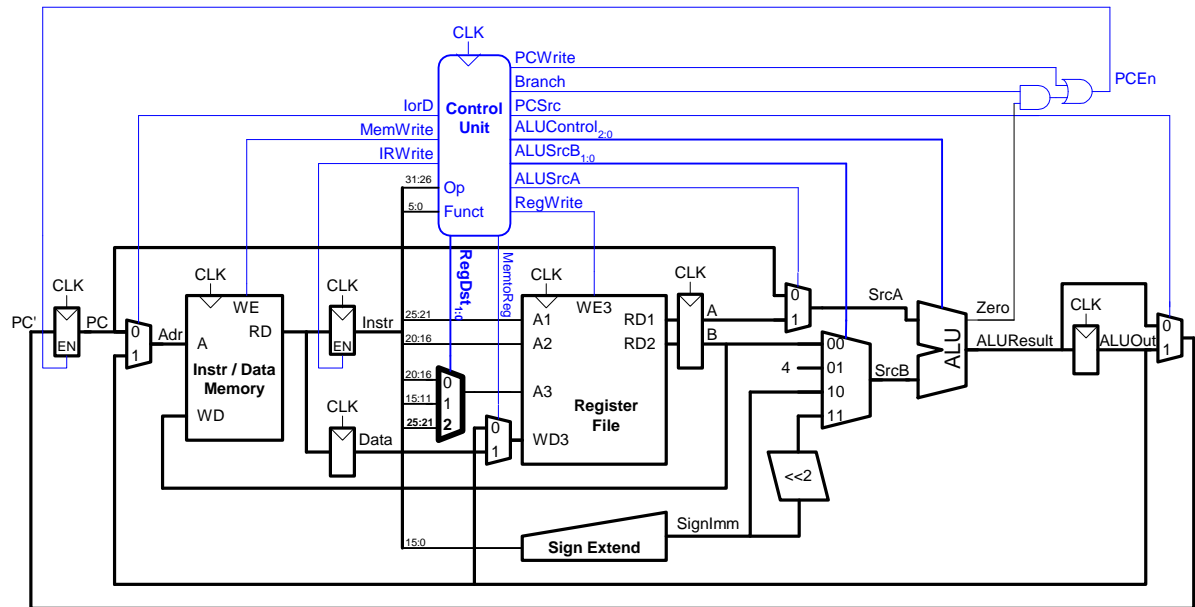Exercise 7.15


Yes, it is possible to add this instruction without modifying the register file. First we show the modifications to the datapath. The only modification is adding the `rs` field of the instruction (*Instruction*_{25:21}) to the input of the write address mux of the register file. *RegDst* must be expanded to two bits.




The finite state machine requires another state to write the *rs* register. If execution time is critical, another adder could be placed just after the A/B register to add 4 to A. Then in State 3, as memory is read, the register file could be written back with the incremented *rs*. In that case, *lwinc* would require the same number of cycles as *lw*. The penalty, however, would be chip area, and thus power and cost.

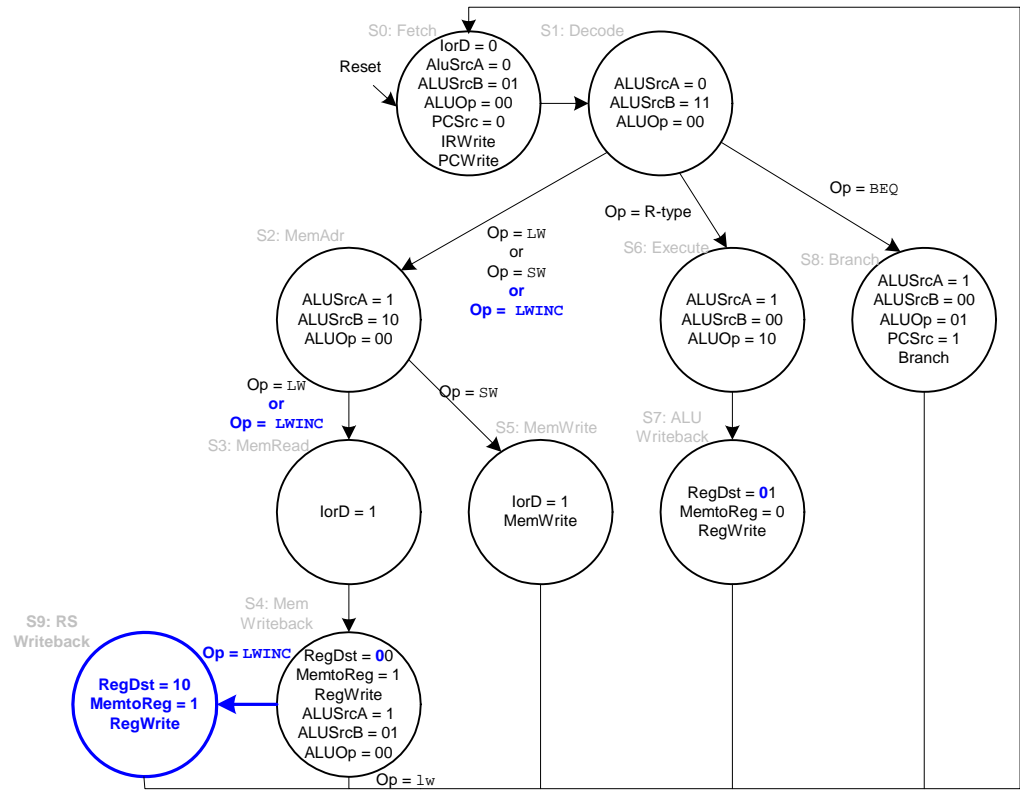

Exercise 7.16

 

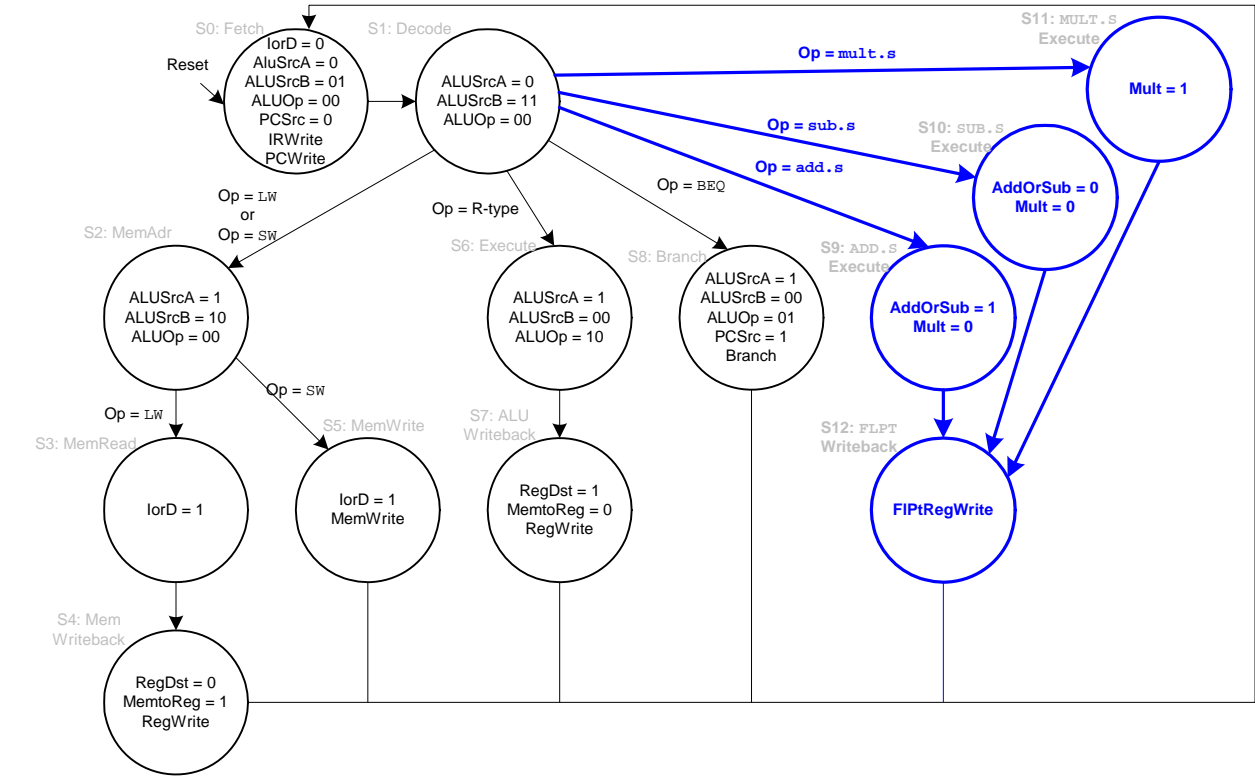

Exercise 7.17


The diagram illustrates the MIPS architecture, divided into two main functional blocks: the main processor (top) and the Floating-Point Processor (FPU, bottom).

Main Processor Block:

- Program Counter (PC):** Receives `PCWrite` and `PCEn` signals. Its output is `PC`, which is used to address `Instr / Data Memory`.
- Instruction / Data Memory:** Has `Adr` (address) and `Data` (data) ports. It is controlled by `WE` (write enable) and `RD` (read enable) signals. It receives `MemWrite` and `IRWrite` control signals.
- Register File:** Contains registers `A1, A2, A3` and write data `WD3`. It is controlled by `WE3` (write enable) and `RD1, RD2` (read enables). It receives `RegDst` and `MemtoReg` control signals.
- ALU (Arithmetic Logic Unit):** Takes `SrcA` and `SrcB` as inputs. It performs operations based on `Op` and `Funct` control signals. It also receives `ALUSrcA` and `ALUSrcB1:0` control signals. The output is `ALUResult`.
- Sign Extend:** Takes a 16-bit input and extends it to 32 bits. It receives a `<<2` shift control signal.
- Control Unit:** Receives `CLK` and `Op` signals. It generates control signals for the other components: `PCWrite`, `Branch`, `PCSrc`, `ALUSrcA`, `ALUSrcB1:0`, `RegWrite`, `MemWrite`, `IRWrite`, `RegDst`, and `MemtoReg`.

Floating-Point Processor (FPU) Block:

- FIPT Control Unit:** Receives `CLK` and `Op` signals. It generates control signals: `FIPTEn`, `Mult`, `AddOrSub`, and `FIPTRegWrite`.
- FIPT Register File:** Contains registers `A1, A2, A3` and write data `WD3`. It is controlled by `WE3` (write enable) and `RD1, RD2` (read enables). It receives `FIPTRegWrite` control signal.
- FIPT ALU:** Takes `A` and `B` as inputs. It performs floating-point operations based on `FIPTEn`, `Mult`, and `AddOrSub` control signals. The output is `FLPT`.

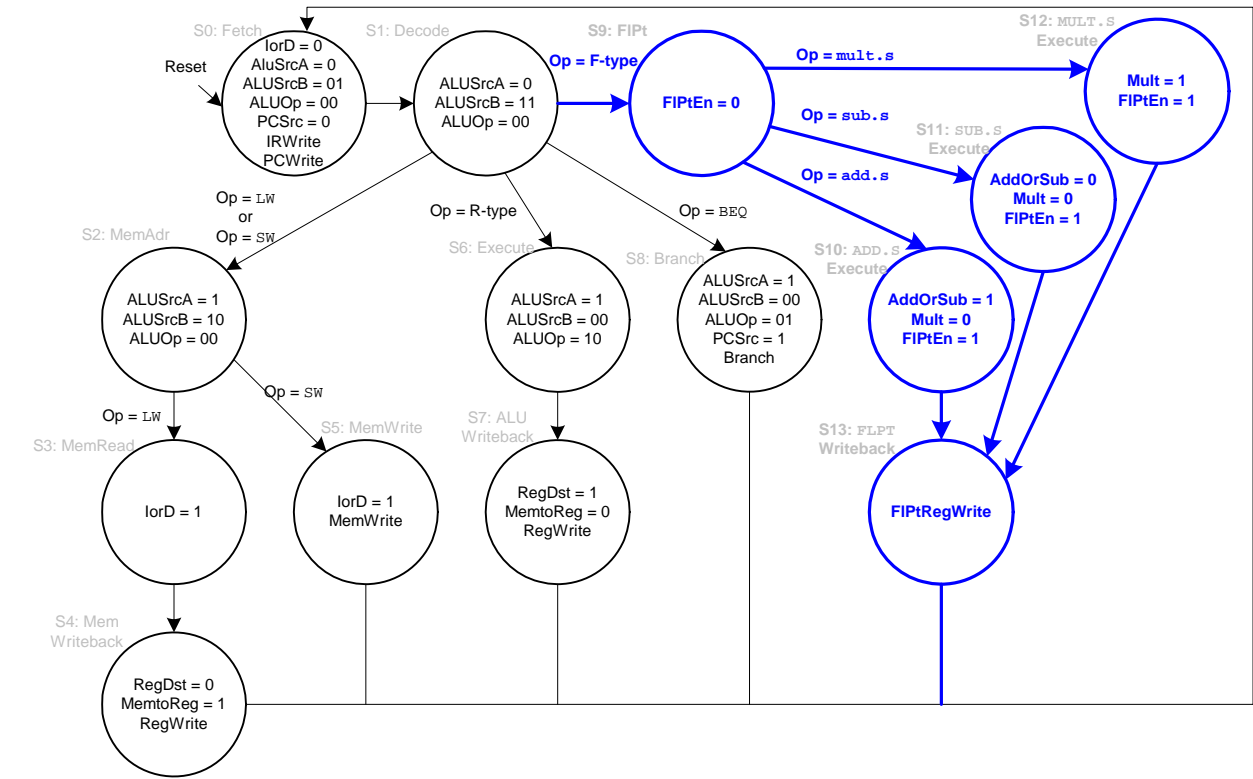

Exercise 7.18

Your friend should work on the memory unit. It should have a delay of 225ps to equal the delay of the ALU plus multiplexer. The cycle time is now 300 ps.

Exercise 7.19

Because the ALU is not on the critical path, the speedup in performance of the ALU does not affect the cycle time. Thus, the cycle time, given in Example 7.8, is still 325 ps. Given the instruction mix in Example 7.7, the overall execution time for 100 billion instructions is still 133.9 seconds.

Exercise 7.20


No, Alyssa should not switch to the slower but lower power register file for her multicycle processor design.


Doubling the delay of the register file puts it on the critical path. (2×150 ps = 300 ps for a read). The critical path is:

$$T_c = t_{pcq} + \max(t_{\text{RRead}}, t_{\text{mux}} + t_{\text{mem}}) + t_{\text{setup}}$$

Because t_{RRead} (300 ps) is larger than $t_{\text{mux}} + t_{\text{mem}}$ ($25 + 250 = 275$ ps), the cycle time would increase by 25 ps with the slower but lower power register file.

Exercise 7.21

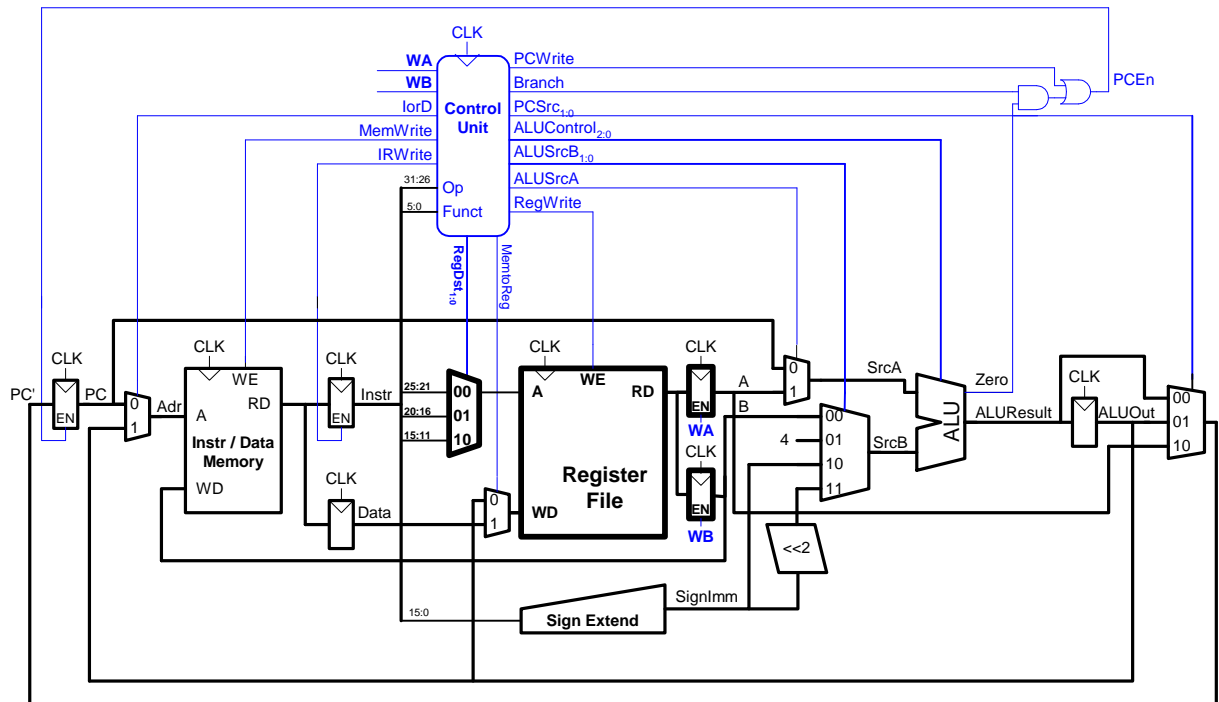

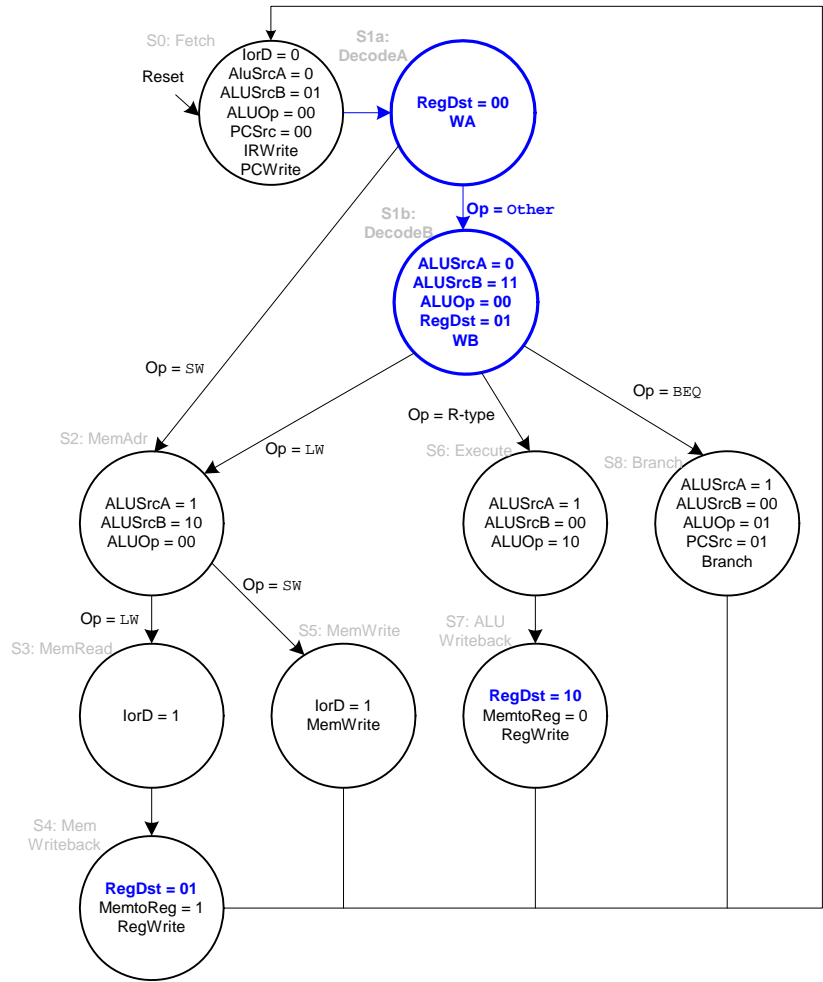

Exercise 7.22

$$\text{Average CPI} = (0.25)(6) + (0.52)(5) + (0.1 + 0.11)(4) + (0.02)(3) = 5$$

Exercise 7.23

$$4 + (3 + 4 + 3) \times 5 + 3 = \mathbf{57 \text{ clock cycles}}$$

The number of instructions executed is $1 + (3 \times 5) + 1 = 17$. Thus, the CPI
= 57 clock cycles / 17 instructions = **3.35 CPI**

Exercise 7.24

$(4 \times 3) + (4 + 3 + 4 + 4 + 3) \times 10 + (4 + 3) = 199$ clock cycles

The number of instructions executed is $3 + (5 \times 10) + 2 = 55$. Thus, the CPI
= 199 clock cycles / 55 instructions = **3.62 CPI**.

Exercise 7.25

MIPS Multicycle Processor

SystemVerilog

```
module mips(input  logic      clk, reset,
           output logic [31:0] adr, writedata,
           output logic      memwrite,
           input  logic [31:0] readdata);

    logic      zero, pcen, irwrite, regwrite,
               alusrc, iord, memtoreg, regdst;
    logic [1:0] alusrcb, pcsrc;
    logic [2:0] alucontrol;
    logic [5:0] op, funct;

    controller c(clk, reset, op, funct, zero,
                 pcen, memwrite, irwrite, regwrite,
                 alusrc, iord, memtoreg, regdst,
                 alusrcb, pcsrc, alucontrol);
    datapath dp(clk, reset,
                pcen, irwrite, regwrite,
                alusrc, iord, memtoreg, regdst,
                alusrcb, pcsrc, alucontrol,
                op, funct, zero,
                adr, writedata, readdata);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mips is -- multicycle MIPS processor
    port(clk, reset:    in  STD_LOGIC;
          adr:          out STD_LOGIC_VECTOR(31 downto 0);
          writedata:    inout STD_LOGIC_VECTOR(31 downto 0);
          memwrite:     out  STD_LOGIC;
          readdata:     in  STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of mips is
    component controller
        port(clk, reset:    in  STD_LOGIC;
              op, funct:    in  STD_LOGIC_VECTOR(5 downto 0);
              zero:         in  STD_LOGIC;
              pcen, memwrite: out STD_LOGIC;
              irwrite, regwrite: out STD_LOGIC;
              alusrc, iord:   out STD_LOGIC;
              memtoreg, regdst: out STD_LOGIC;
              alusrcb, pcsrc: out STD_LOGIC_VECTOR(1 downto 0);
              alucontrol:    out STD_LOGIC_VECTOR(2 downto 0));
    end component;
    component datapath
        port(clk, reset:    in  STD_LOGIC;
              pcen, irwrite: in  STD_LOGIC;
              regwrite, alusrc: in  STD_LOGIC;
              iord, memtoreg: in  STD_LOGIC;
              regdst:        in  STD_LOGIC;
              alusrcb, pcsrc: in  STD_LOGIC_VECTOR(1 downto 0);
              alucontrol:    in  STD_LOGIC_VECTOR(2 downto 0);
              readdata:      in  STD_LOGIC_VECTOR(31 downto 0);
              op, funct:     out STD_LOGIC_VECTOR(5 downto 0);
              zero:          out STD_LOGIC;
              adr:           out STD_LOGIC_VECTOR(31 downto 0);
              writedata:     inout STD_LOGIC_VECTOR(31 downto 0));
    end component;
    signal zero, pcen, irwrite, regwrite, alusrc, iord, memtoreg,
           regdst: STD_LOGIC;
    signal alusrcb, pcsrc: STD_LOGIC_VECTOR(1 downto 0);
    signal alucontrol: STD_LOGIC_VECTOR(2 downto 0);
    signal op, funct: STD_LOGIC_VECTOR(5 downto 0);
begin
    c: controller port map(clk, reset, op, funct, zero,
                          pcen, memwrite, irwrite, regwrite,
                          alusrc, iord, memtoreg, regdst,
                          alusrcb, pcsrc, alucontrol);
    dp: datapath port map(clk, reset,
                        pcen, irwrite, regwrite,
                        alusrc, iord, memtoreg, regdst,
                        alusrcb, pcsrc, alucontrol,
                        readdata, op, funct, zero,
                        adr, writedata);
end;
```

MIPS Multicycle Control

SystemVerilog

```
module controller(input logic clk, reset,
                 input logic [5:0] op, funct,
                 input logic zero,
                 output logic pcen, memwrite,
                 irwrite, regwrite,
                 output logic alusrca, iord,
                 memtoreg, regdst,
                 output logic [1:0] alusrcb, pcsrc,
                 output logic [2:0] alucontrol);

    logic [1:0] aluop;
    logic branch, pcwrite;

    // Main Decoder and ALU Decoder subunits.
    maindec md(clk, reset, op,
               pcwrite, memwrite, irwrite, regwrite,
               alusrca, branch, iord, memtoreg, regdst,
               alusrcb, pcsrc, aluop);
    aludec ad(funct, aluop, alucontrol);

    assign pcen = pcwrite | (branch & zero);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity controller is -- multicycle control decoder
    port(clk, reset: in STD_LOGIC;
          op, funct: in STD_LOGIC_VECTOR(5 downto 0);
          zero: in STD_LOGIC;
          pcen, memwrite: out STD_LOGIC;
          irwrite, regwrite: out STD_LOGIC;
          alusrca, iord: out STD_LOGIC;
          memtoreg, regdst: out STD_LOGIC;
          alusrcb, pcsrc: out STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture struct of controller is
    component maindec
        port(clk, reset: in STD_LOGIC;
              op: in STD_LOGIC_VECTOR(5 downto 0);
              pcwrite, memwrite: out STD_LOGIC;
              irwrite, regwrite: out STD_LOGIC;
              alusrca, branch: out STD_LOGIC;
              iord, memtoreg: out STD_LOGIC;
              regdst: out STD_LOGIC;
              alusrcb, pcsrc: out STD_LOGIC_VECTOR(1 downto 0);
              aluop: out STD_LOGIC_VECTOR(1 downto 0));
    end component;
    component aludec
        port(funct: in STD_LOGIC_VECTOR(5 downto 0);
              aluop: in STD_LOGIC_VECTOR(1 downto 0);
              alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
    end component;
    signal aluop: STD_LOGIC_VECTOR(1 downto 0);
    signal branch, pcwrite: STD_LOGIC;
begin
    md: maindec port map(clk, reset, op,
                        pcwrite, memwrite, irwrite, regwrite,
                        alusrca, branch, iord, memtoreg, regdst,
                        alusrcb, pcsrc, aluop);
    ad: aludec port map(funct, aluop, alucontrol);

    pcen <= pcwrite or (branch and zero);
end;
```


MIPS Multicycle Main Decoder FSM SystemVerilog

```
module maindec(input logic clk, reset,
               input logic [5:0] op,
               output logic pcwrite, memwrite,
                               irwrite, regwrite,
               output logic alusrca, branch, iord,
                               memtoreg, regdst,
               output logic [1:0] alusrcb, pcsrc,
               output logic [1:0] aluop);

typedef enum logic [3:0] {FETCH, DECODE, MEMADR,
                          MEMRD, MEMWB, MEMWR, RTYPEEX,
                          RTYPEWB, BEQEX, ADDIEX,
                          ADDIWB, JEX} statetype;

statetype [3:0] state, nextstate;

parameter LW      = 6'b100011; // Opcode for lw
parameter SW      = 6'b101011; // Opcode for sw
parameter RTYPE   = 6'b000000; // Opcode for R-type
parameter BEQ     = 6'b000100; // Opcode for beq
parameter ADDI    = 6'b001000; // Opcode for addi
parameter J       = 6'b000010; // Opcode for j

reg [3:0] state, nextstate;
reg [14:0] controls;

// state register
always_ff @(posedge clk or posedge reset)
    if (reset) state <= FETCH;
    else state <= nextstate;
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity maindec is -- main control decoder
    port(clk, reset: in STD_LOGIC;
          op: in STD_LOGIC_VECTOR(5 downto 0);
          pcwrite, memwrite: out STD_LOGIC;
          irwrite, regwrite: out STD_LOGIC;
          alusrca, branch: out STD_LOGIC;
          iord, memtoreg: out STD_LOGIC;
          regdst: out STD_LOGIC;
          alusrcb, pcsrc: out STD_LOGIC_VECTOR(1 downto 0);
          aluop: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture behave of maindec is
    type statetype is (FETCH, DECODE, MEMADR, MEMRD, MEMWB, MEMWR,
                      RTYPEEX, RTYPEWB, BEQEX, ADDIEX, ADDIWB, JEX);
    signal state, nextstate: statetype;
    signal controls: STD_LOGIC_VECTOR(14 downto 0);
begin
    --state register
    process(clk, reset) begin
        if reset then state <= FETCH;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when FETCH => nextstate <= DECODE;
            when DECODE =>
                case op is
                    when "100011" => nextstate <= MEMADR;
                    when "101011" => nextstate <= MEMADR;
                    when "000000" => nextstate <= RTYPEEX;
                    when "000100" => nextstate <= BEQEX;
                    when "001000" => nextstate <= ADDIEX;
                    when "000010" => nextstate <= JEX;
                    when others => nextstate <= FETCH; -- should never happen
                end case;
            when MEMADR =>
                case op is
                    when "100011" => nextstate <= MEMRD;
                    when "101011" => nextstate <= MEMWR;
                    when others => nextstate <= FETCH; -- should never happen
                end case;
            when MEMRD => nextstate <= MEMWB;
            when MEMWB => nextstate <= FETCH;
            when MEMWR => nextstate <= FETCH;
            when RTYPEEX => nextstate <= RTYPEWB;
            when RTYPEWB => nextstate <= FETCH;
            when BEQEX => nextstate <= FETCH;
            when ADDIEX => nextstate <= ADDIWB;
            when JEX => nextstate <= FETCH;
            when others => nextstate <= FETCH; -- should never happen
        end case;
    end process;
```

SystemVerilog

```
// next state logic
always_comb
case(state)
  FETCH: nextstate <= DECODE;
  DECODE: case(op)
    LW: nextstate <= MEMADR;
    SW: nextstate <= MEMADR;
    RTYPE: nextstate <= RTYPEEX;
    BEQ: nextstate <= BEQEX;
    ADDI: nextstate <= ADDIEX;
    J: nextstate <= JEX;
    default: nextstate <= FETCH;
    // default should never happen
  endcase
  MEMADR: case(op)
    LW: nextstate <= MEMRD;
    SW: nextstate <= MEMWR;
    default: nextstate <= FETCH;
    // default should never happen
  endcase
  MEMRD: nextstate <= MEMWB;
  MEMWB: nextstate <= FETCH;
  MEMWR: nextstate <= FETCH;
  RTYPEEX: nextstate <= RTYPEWB;
  RTYPEWB: nextstate <= FETCH;
  BEQEX: nextstate <= FETCH;
  ADDIEX: nextstate <= ADDIWB;
  ADDIWB: nextstate <= FETCH;
  JEX: nextstate <= FETCH;
  default: nextstate <= FETCH;
  // default should never happen
endcase

// output logic
assign {pcwrite, memwrite, irwrite, regwrite,
       alusrca, branch, iord, memtoreg, regdst,
       alusrcb, pcsrc, aluop} = controls;

always_comb
case (state)
  FETCH: controls <= 15'b1010_0000_0100_00;
  DECODE: controls <= 15'b0000_0000_1100_00;
  MEMADR: controls <= 15'b0000_1000_1000_00;
  MEMRD: controls <= 15'b0000_0010_0000_00;
  MEMWB: controls <= 15'b0001_0001_0000_00;
  MEMWR: controls <= 15'b0100_0010_0000_00;
  RTYPEEX: controls <= 15'b0000_1000_0000_10;
  RTYPEWB: controls <= 15'b0001_0000_1_0000_00;
  BEQEX: controls <= 15'b0000_1100_0001_01;
  ADDIEX: controls <= 15'b0000_1000_1000_00;
  ADDIWB: controls <= 15'b0001_0000_0000_00;
  JEX: controls <= 15'b1000_0000_0010_00;
  default: controls <= 15'b0000_xxxx_xxxx_xx;
endcase
endmodule
```

VHDL

```
-- output logic
process(all) begin
  case state is
    when FETCH => controls <= "101000000010000";
    when DECODE => controls <= "000000000110000";
    when MEMADR => controls <= "000010000100000";
    when MEMRD => controls <= "000000100000000";
    when MEMWB => controls <= "000100010000000";
    when MEMWR => controls <= "010000100000000";
    when RTYPEEX => controls <= "000010000000010";
    when RTYPEWB => controls <= "000100001000000";
    when BEQEX => controls <= "000011000000101";
    when ADDIEX => controls <= "000010000100000";
    when ADDIWB => controls <= "000100000000000";
    when JEX => controls <= "100000000001000";
    when others => controls <= "-----"; --illegal op
  end case;
end process;

pcwrite <= controls(14);
memwrite <= controls(13);
irwrite <= controls(12);
regwrite <= controls(11);
alusrca <= controls(10);
branch <= controls(9);
iord <= controls(8);
memtoreg <= controls(7);
regdst <= controls(6);
alusrcb <= controls(5 downto 4);
pcsrc <= controls(3 downto 2);
aluop <= controls(1 downto 0);

end;
```

MIPS Multicycle ALU Decoder

SystemVerilog

```
module aludec(input  logic [5:0] funct,
             input  logic [1:0] aluop,
             output logic [2:0] alucontrol);

    always_comb
    case(aluop)
        2'b00: alucontrol <= 3'b010; // add
        2'b01: alucontrol <= 3'b110; // sub
        default: case(funct)           // RTYPE
            6'b100000: alucontrol <= 3'b010; // ADD
            6'b100010: alucontrol <= 3'b110; // SUB
            6'b100100: alucontrol <= 3'b000; // AND
            6'b100101: alucontrol <= 3'b001; // OR
            6'b101010: alucontrol <= 3'b111; // SLT
            default:   alucontrol <= 3'bxxx; // ???
        endcase
    endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity aludec is -- ALU control decoder
    port(funct:   in  STD_LOGIC_VECTOR(5 downto 0);
         aluop:   in  STD_LOGIC_VECTOR(1 downto 0);
         alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture behave of aludec is
begin
    process(all) begin
        case aluop is
            when "00" => alucontrol <= "010"; -- add (for lb/sb/addi)
            when "01" => alucontrol <= "110"; -- sub (for beq)
            when "11" => alucontrol <= "111"; -- slt (for slti)
            when others => case funct is -- R-type instructions
                when "100000" => alucontrol <= "010"; -- add
                when "100010" => alucontrol <= "110"; -- sub
                when "100100" => alucontrol <= "000"; -- and
                when "100101" => alucontrol <= "001"; -- or
                when "101010" => alucontrol <= "111"; -- slt
                when others   => alucontrol <= "---"; -- ???
            end case;
        end case;
    end process;
end;
```

MIPS Multicycle Datapath

SystemVerilog

```
module datapath(input logic      clk, reset,
               input logic      pcen, irwrite,
               input logic      regwrite,
               input logic      alusrc, iord,
                               memtoreg, regdst,
               input logic [1:0] alusrcb, pcsrc,
               input logic [2:0] alucontrol,
               output logic [5:0] op, funct,
               output logic      zero,
               output logic [31:0] adr, writedata,
               input logic [31:0] readdata);

    // Internal signals of the datapath module.

    logic [4:0] writereg;
    logic [31:0] pcnext, pc;
    logic [31:0] instr, data, srca, srcb;
    logic [31:0] a;
    logic [31:0] aluresult, aluout;
    logic [31:0] signimm; // sign-extended immediate
    logic [31:0] signimmsh; // sign-extended immediate
                          // shifted left by 2
    logic [31:0] wd3, rd1, rd2;

    // op and funct fields to controller
    assign op = instr[31:26];
    assign funct = instr[5:0];

    // datapath
    flopenr #(32) pcreg(clk, reset, pcen, pcnext, pc);
    mux2 #(32) adrmux(pc, aluout, iord, adr);
    flopenr #(32) instrreg(clk, reset, irwrite,
                          readdata, instr);
    flopr #(32) datareg(clk, reset, readdata, data);
    mux2 #(5) regdstmux(instr[20:16], instr[15:11],
                       regdst, writereg);
    mux2 #(32) wdmux(aluout, data, memtoreg, wd3);
    regfile rf(clk, regwrite, instr[25:21],
              instr[20:16],
              writereg, wd3, rd1, rd2);
    signext se(instr[15:0], signimm);
    sl2 immsh(signimm, signimmsh);
    flopr #(32) areg(clk, reset, rd1, a);
    flopr #(32) breg(clk, reset, rd2, writedata);
    mux2 #(32) srcamux(pc, a, alusrc, srca);
    mux4 #(32) srcbmux(writedata, 32'b100,
                      signimm, signimmsh,
                      alusrcb, srcb);
    alu alu(srca, srcb, alucontrol,
           aluresult, zero);
    flopr #(32) alureg(clk, reset, aluresult, aluout);
    mux3 #(32) pcmux(aluresult, aluout,
                    {pc[31:28], instr[25:0], 2'b00},
                    pcsrc, pcnext);
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity datapath is -- MIPS datapath
    port(clk, reset: in STD_LOGIC;
          pcen, irwrite: in STD_LOGIC;
          regwrite, alusrc: in STD_LOGIC;
          iord, memtoreg: in STD_LOGIC;
          regdst: in STD_LOGIC;
          alusrcb, pcsrc: in STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: in STD_LOGIC_VECTOR(2 downto 0);
          readdata: in STD_LOGIC_VECTOR(31 downto 0);
          op, funct: out STD_LOGIC_VECTOR(5 downto 0);
          zero: out STD_LOGIC;
          adr: out STD_LOGIC_VECTOR(31 downto 0);
          writedata: inout STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of datapath is
    component alu
        port(A, B: in STD_LOGIC_VECTOR(31 downto 0);
              F: in STD_LOGIC_VECTOR(2 downto 0);
              Y: buffer STD_LOGIC_VECTOR(31 downto 0);
              Zero: out STD_LOGIC);
    end component;
    component regfile
        port(clk: in STD_LOGIC;
              we3: in STD_LOGIC;
              ral, ra2, wa3: in STD_LOGIC_VECTOR(4 downto 0);
              wd3: in STD_LOGIC_VECTOR(31 downto 0);
              rd1, rd2: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component adder
        port(a, b: in STD_LOGIC_VECTOR(31 downto 0);
              y: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component sl2
        port(a: in STD_LOGIC_VECTOR(31 downto 0);
              y: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component signext
        port(a: in STD_LOGIC_VECTOR(15 downto 0);
              y: out STD_LOGIC_VECTOR(31 downto 0));
    end component;
    component flopr generic(width: integer);
        port(clk, reset: in STD_LOGIC;
              d: in STD_LOGIC_VECTOR(width-1 downto 0);
              q: out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    component flopenr generic(width: integer);
        port(clk, reset: in STD_LOGIC;
              en: in STD_LOGIC;
              d: in STD_LOGIC_VECTOR(width-1 downto 0);
              q: out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    component mux2 generic(width: integer);
        port(d0, d1: in STD_LOGIC_VECTOR(width-1 downto 0);
              s: in STD_LOGIC;
              y: out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    component mux3 generic(width: integer);
        port(d0, d1, d2: in STD_LOGIC_VECTOR(width-1 downto 0);
              s: in STD_LOGIC_VECTOR(1 downto 0);
              y: out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    component mux4 generic(width: integer);
        port(d0, d1, d2, d3: in STD_LOGIC_VECTOR(width-1 downto 0);
              s: in STD_LOGIC_VECTOR(1 downto 0);
              y: out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    signal writereg: STD_LOGIC_VECTOR(4 downto 0);
    signal pcnext, pc, instr, data, srca, srcb, a,
           aluresult, aluout, signimm, signimmsh, wd3, rd1, rd2, pcjump:
           STD_LOGIC_VECTOR(31 downto 0);
```

(continued from previous page)

VHDL

[illegible]

The following HDL describes the building blocks that are used in the MIPS multicycle processor that are not found in Section 7.6.2.

MIPS Multicycle Building Blocks

SystemVerilog

```
module flopenr #(parameter WIDTH = 8)
    (input logic clk, reset,
     input logic en,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule

module mux3 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0, d1, d2,
     input logic [1:0] s,
     output logic [WIDTH-1:0] y);

    assign #1 y = s[1] ? d2 : (s[0] ? d1 : d0);
endmodule

module mux4 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0, d1, d2, d3,
     input logic [1:0] s,
     output logic [WIDTH-1:0] y);

    always_comb
        case(s)
            2'b00: y <= d0;
            2'b01: y <= d1;
            2'b10: y <= d2;
            2'b11: y <= d3;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity flopenr is -- flip-flop with asynchronous reset
    generic(width: integer);
    port(clk, reset: in STD_LOGIC;
         en: in STD_LOGIC;
         d: in STD_LOGIC_VECTOR(width-1 downto 0);
         q: out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture asynchronous of flopenr is
begin
    process(clk, reset) begin
        if reset then q <= CONV_STD_LOGIC_VECTOR(0, width);
        elsif rising_edge(clk) and en = '1' then
            q <= d;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux3 is -- three-input multiplexer
    generic(width: integer);
    port(d0, d1, d2: in STD_LOGIC_VECTOR(width-1 downto 0);
         s: in STD_LOGIC_VECTOR(1 downto 0);
         y: out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture behave of mux3 is
begin
    process(all) begin
        case s is
            when "00" => y <= d0;
            when "01" => y <= d1;
            when "10" => y <= d2;
            when others => y <= d0;
        end case;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux4 is -- four-input multiplexer
    generic(width: integer);
    port(d0, d1, d2, d3: in STD_LOGIC_VECTOR(width-1 downto 0);
         s: in STD_LOGIC_VECTOR(1 downto 0);
         y: out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture behave of mux4 is
begin
    process(all) begin
        case s is
            when "00" => y <= d0;
            when "01" => y <= d1;
            when "10" => y <= d2;
            when "11" => y <= d3;
            when others => y <= d0; -- should never happen
        end case;
    end process;
end;
```

Exercise 7.26

We modify the MIPS multicycle processor to implement all instructions from Exercise 7.13.

SystemVerilog

```
module top(input logic clk, reset,
           output logic [31:0] writedata, dataadr,
           output logic memwrite);

    logic [31:0] pc, instr, readdata;

    // instantiate processor and memories
    mips mips(clk, reset, pc, instr, memwrite, dataadr,
              writedata, readdata);
    imem imem(pc[7:2], instr);
    dmem dmem(clk, memwrite, dataadr, writedata, readdata);
endmodule

module dmem(input logic clk, we,
            input logic [31:0] a, wd,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    assign rd = RAM[a[31:2]]; // word aligned

    always_ff @(posedge clk)
        if (we) RAM[a[31:2]] <= wd;
endmodule

module imem(input logic [5:0] a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    initial
        $readmemh("memfile.dat",RAM);

    assign rd = RAM[a]; // word aligned
endmodule

module top(input logic clk, reset,
           output logic [31:0] writedata, adr,
           output logic memwrite);

    logic [31:0] readdata;

    // instantiate processor and memory
    mips mips(clk, reset, adr, writedata, memwrite,
              readdata);
    mem mem(clk, memwrite, adr, writedata,
            readdata);
endmodule
```

```

module mips(input logic      clk, reset,
            output logic [31:0] adr, writedata,
            output logic      memwrite,
            input logic [31:0] readdata);

    logic zero, pcen, irwrite, regwrite,
           alusrca, iord, memtoreg, regdst;
    logic [2:0] alusrcb; // ORI, XORI
    logic [1:0] pcsrc;
    logic [3:0] alucontrol; // SRLV
    logic [5:0] op, funct;

    controller c(clk, reset, op, funct, zero,
                 pcen, memwrite, irwrite, regwrite,
                 alusrca, iord, memtoreg, regdst,
                 alusrcb, pcsrc, alucontrol);
    datapath dp(clk, reset,
                pcen, irwrite, regwrite,
                alusrca, iord, memtoreg, regdst,
                alusrcb, pcsrc, alucontrol,
                op, funct, zero,
                adr, writedata, readdata);
endmodule

module controller(input logic      clk, reset,
                  input logic [5:0] op, funct,
                  input logic      zero,
                  output logic      pcen, memwrite,
                                irwrite, regwrite,
                  output logic      alusrca, iord,
                  output logic      memtoreg, regdst,
                  output logic [2:0] alusrcb,
                                // ORI, XORI
                  output logic [1:0] pcsrc,
                  output logic [3:0] alucontrol); // SRLV

    logic [2:0] aluop; // XORI
    logic      branch, pcwrite;

    // Main Decoder and ALU Decoder subunits.
    maindec md(clk, reset, op,
               pcwrite, memwrite, irwrite, regwrite,
               alusrca, branch, iord, memtoreg, regdst,
               alusrcb, pcsrc, aluop);
    aludec ad(funct, aluop, alucontrol);

    assign pcen = pcwrite | (branch & zero);
endmodule

module maindec(input      clk, reset,
               input [5:0] op,
               output      pcwrite, memwrite,
                                irwrite, regwrite,
               output      alusrca, branch,
                                iord, memtoreg, regdst,
               output [2:0] alusrcb, // ORI, XORI
               output [1:0] pcsrc,
               output [2:0] aluop); // SRLV, XORI

    typedef enum logic [4:0] {FETCH, DECODE, MEMADR,
                              MEMRD, MEMWB, MEMWR, RTYPEEX, RTYPEWB, BEQEX,
                              ADDIEX, ADDIWB, JEX, ORIEX, ORIWB, XORIEX,
                              XORIWB} statetype;
    statetype [4:0] state, nextstate;

```



```

parameter RTYPE = 6'b000000;
parameter LW = 6'b100011;
parameter SW = 6'b101011;
parameter BEQ = 6'b000100;
parameter ADDI = 6'b001000;
parameter J = 6'b000010;
parameter ORI = 6'b001101;
parameter XORI = 6'b001110;

logic [16:0] controls; // ORI, XORI

// state register
always_ff @(posedge clk or posedge reset)
    if(reset) state <= FETCH;
    else state <= nextstate;

// next state logic
always_comb
    case(state)
        FETCH: nextstate <= DECODE;
        DECODE: case(op)
            LW: nextstate <= MEMADR;
            SW: nextstate <= MEMADR;
            RTYPE: nextstate <= RTYPEEX;
            BEQ: nextstate <= BEQEX;
            ADDI: nextstate <= ADDIEX;
            J: nextstate <= JEX;
            ORI: nextstate <= ORIEX; // ORI
            XORI: nextstate <= XORIEX; // XORI
            default: nextstate <= FETCH;
                // should never happen
        endcase
        MEMADR: case(op)
            LW: nextstate <= MEMRD;
            SW: nextstate <= MEMWR;
            default: nextstate <= FETCH;
                // should never happen
        endcase
        MEMRD: nextstate <= MEMWB;
        MEMWB: nextstate <= FETCH;
        MEMWR: nextstate <= FETCH;
        RTYPEEX: nextstate <= RTYPEWB;
        RTYPEWB: nextstate <= FETCH;
        BEQEX: nextstate <= FETCH;
        ADDIEX: nextstate <= ADDIWB;
        ADDIWB: nextstate <= FETCH;
        JEX: nextstate <= FETCH;
        ORIEX: nextstate <= ORIWB; // ORI
        ORIWB: nextstate <= FETCH; // ORI
        XORIEX: nextstate <= XORIWB; // XORI
        XORIWB: nextstate <= FETCH; // XORI
        default: nextstate <= FETCH;
            // should never happen
    endcase

// output logic
assign {pcwrite, memwrite, irwrite, regwrite,
        alusrc, branch, iord, memtoreg, regdst,
        alusrcb, psrc,
        aluop} = controls; // extend aluop to 3 bits // ORI, SRLV

always_comb
    case(state)
        FETCH: controls <= 19'b1010_00000_00100_000;
        DECODE: controls <= 19'b0000_00000_01100_000;
    endcase

```

320 SOLUTIONS chapter 7

```

MEMADR: controls <= 19'b0000_10000_01000_000;
MEMRD:  controls <= 19'b0000_00100_00000_000;
MEMWB:  controls <= 19'b0001_00010_00000_000;
MEMWR:  controls <= 19'b0100_00100_00000_000;
RTYPEEX: controls <= 19'b0000_10000_00000_010;
RTYPEWB: controls <= 19'b0001_00001_00000_000;
BEQEX:  controls <= 19'b0000_11000_00001_001;
ADDIEX: controls <= 19'b0000_10000_01000_000;
ADDIWB: controls <= 19'b0001_00000_00000_000;
JEX:    controls <= 19'b1000_00000_00010_000;
ORIEX:  controls <= 19'b0000_10000_10000_011; // ORI
ORIWB:  controls <= 19'b0001_00000_00000_000; // ORI
XORIEX: controls <= 19'b0000_10000_10000_100; // XORI
XORIWB: controls <= 19'b0001_00000_00000_000; // XORI
default: controls <= 19'b0000_xxxxxx_xxxxx_xxx_x;
           // should never happen
    endcase
endmodule

module aludec(input  logic [5:0] funct,
              input  logic [2:0] aluop,
              output logic [3:0] alucontrol);

    always_comb
    case(aluop)
        3'b000: alucontrol <= 4'b0010; // add
        3'b001: alucontrol <= 4'b1010; // sub
        3'b011: alucontrol <= 4'b0001; // or  // ORI
        3'b100: alucontrol <= 4'b0101; // xor // XORI
        3'b010: case(funct)
            // RTYPE
            6'b100000: alucontrol <= 4'b0010; // ADD
            6'b100010: alucontrol <= 4'b1010; // SUB
            6'b100100: alucontrol <= 4'b0000; // AND
            6'b100101: alucontrol <= 4'b0001; // OR
            6'b101010: alucontrol <= 4'b1011; // SLT
            6'b000110: alucontrol <= 4'b0100; // SRLV
            default:   alucontrol <= 4'bxxxx; // ???
        endcase
        default: alucontrol <= 4'bxxxx; // ???
    endcase
endmodule

module datapath(input  logic      clk, reset,
                input  logic      pcen, irwrite,
                input  logic      regwrite,
                input  logic      alusrca, iord,
                                memtoreg, regdst,
                input  logic [2:0] alusrcb, //ORI, XORI
                input  logic [1:0] pcsrc,
                input  logic [3:0] alucontrol, // SRLV
                output logic [5:0] op, funct,
                output logic      zero,
                output logic [31:0] adr, writedata,
                input  logic [31:0] readdata);

    // Internal signals of the datapath module

    logic [4:0] writereg;
    logic [31:0] pcnext, pc;
    logic [31:0] instr, data, srca, srcb;
    logic [31:0] a;
    logic [31:0] aluresult, aluout;
    logic [31:0] signimm; // the sign-extended imm
    logic [31:0] zeroimm; // the zero-extended imm

```

```

                                // ORI, XORI
logic [31:0] signimmsh; // the sign-extended imm << 2
logic [31:0] wd3, rd1, rd2;

// op and funct fields to controller
assign op = instr[31:26];
assign funct = instr[5:0];

// datapath
flopennr #(32) pcreg(clk, reset, pcen, pcnext, pc);
mux2      #(32) adrmux(pc, aluout, iord, adr);
flopennr #(32) instrreg(clk, reset, irwrite,
                        readdata, instr);

flopennr #(32) datareg(clk, reset, readdata, data);

mux2      #(5) regdstmux(instr[20:16],
                        instr[15:11], regdst, writereg);
mux2      #(32) wdmux(aluout, data, memtoreg, wd3);
regfile   rf(clk, regwrite, instr[25:21],
            instr[20:16],
            writereg, wd3, rd1, rd2);
signext   se(instr[15:0], signimm);
zeroext   ze(instr[15:0], zeroimm); // ORI, XORI
sl2       immsh(signimm, signimmsh);
flopennr #(32) areg(clk, reset, rd1, a);
flopennr #(32) breg(clk, reset, rd2, writedata);
mux2      #(32) srcamux(pc, a, alusrca, srca);
mux5      #(32) srcbmux(writedata, 32'b100,
                        signimm, signimmsh,
                        zeroimm, // ORI, XORI
                        alusrca, srcb);

alu        alu(srca, srcb, alucontrol, rd1[4:0],
              aluresult, zero); // SRLV
flopennr #(32) alureg(clk, reset, aluresult, aluout);
mux3      #(32) pcmux(aluresult, aluout,
                    {pc[31:28], instr[25:0], 2'b00},
                    pcsrc, pcnext);

endmodule

module alu(input logic [31:0] A, B,
           input logic [3:0] F, // SRLV, XORI
           input logic [4:0] shamt, // SRLV
           output logic [31:0] Y, output Zero);

logic [31:0] S, Bout;

assign Bout = F[3] ? ~B : B; // SRLV, XORI
assign S = A + Bout + F[3]; // SRLV, XORI

always_comb
case (F[2:0])
3'b000: Y <= A & Bout;
3'b001: Y <= A | Bout;
3'b010: Y <= S;
3'b011: Y <= S[31];
3'b100: Y <= (Bout >> shamt); // SRLV
3'b101: Y <= A ^ Bout; // XORI
endcase

assign Zero = (Y == 32'b0);
endmodule

```

322 SOLUTIONS chapter 7

```
// mux5 is needed for ORI, XORI
module mux5 #(parameter WIDTH = 8)
    (input    [WIDTH-1:0] d0, d1, d2, d3, d4,
     input    [2:0]      s,
     output reg [WIDTH-1:0] y);

    always_comb
    case(s)
        3'b000: y <= d0;
        3'b001: y <= d1;
        3'b010: y <= d2;
        3'b011: y <= d3;
        3'b100: y <= d4;
    endcase
endmodule

// zeroext is needed for ORI, XORI
module zeroext(input  [15:0] a,
               output [31:0] y);

    assign y = {16'b0, a};
endmodule

// mux3 needed for JR
module mux3 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1, d2,
     input  logic [1:0]      s,
     output logic [WIDTH-1:0] y);

    assign #1 y = s[1] ? d2 : (s[0] ? d1 : d0);
endmodule

module alu(input  logic [31:0] A, B,
           input  logic [3:0]  F,
           input  logic [4:0]  shamt, // SRLV
           output logic [31:0] Y,
           output logic        Zero);

    logic [31:0] S, Bout;

    assign Bout = F[3] ? ~B : B;
    assign S = A + Bout + F[3]; // SRLV

    always_comb
    case (F[2:0])
        3'b000: Y = A & Bout;
        3'b001: Y = A | Bout;
        3'b010: Y = S;
        3'b011: Y = S[31];
        3'b100: Y = (Bout >> shamt); // SRLV
    endcase

    assign Zero = (Y == 32'b0);
endmodule

module regfile(input  logic      clk,
               input  logic      we3,
               input  logic [4:0] ra1, ra2, wa3,
               input  logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

    logic [31:0] rf[31:0];

    // three ported register file
    // read two ports combinationaly
```

```
// write third port on rising edge of clk
// register 0 hardwired to 0
always_ff @(posedge clk)
    if (we3) rf[wa3] <= wd3;

assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule

module adder(input  logic [31:0] a, b,
             output logic [31:0] y);

    assign y = a + b;
endmodule

module sl2(input  logic [31:0] a,
           output logic [31:0] y);

    // shift left by 2
    assign y = {a[29:0], 2'b00};
endmodule

module signext(input  logic [15:0] a,
               output logic [31:0] y);

    assign y = {{16{a[15]}}, a};
endmodule

module flopr #(parameter WIDTH = 8)
    (input  logic          clk, reset,
     input  logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1,
     input  logic          s,
     output logic [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mips is -- multicycle MIPS processor
    port(clk, reset:      in  STD_LOGIC;
          adr:           out STD_LOGIC_VECTOR(31 downto 0);
          writedata:      inout STD_LOGIC_VECTOR(31 downto 0);
          memwrite:       out STD_LOGIC;
          readdata:       in  STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of mips is
    component controller
        port(clk, reset:      in  STD_LOGIC;
              op, funct:      in  STD_LOGIC_VECTOR(5 downto 0);
              zero:           in  STD_LOGIC;
              pcen, memwrite: out STD_LOGIC);
```

```

        irwrite, regwrite: out STD_LOGIC;
        alusrca, iord:      out STD_LOGIC;
        memtoreg, regdst:  out STD_LOGIC;
        alusrcb:           out STD_LOGIC_VECTOR(2 downto 0); --ORI, XORI
        pcsrc:             out STD_LOGIC_VECTOR(1 downto 0);
        alucontrol:        out STD_LOGIC_VECTOR(3 downto 0)); --SRLV
    end component;
    component datapath
    port(clk, reset:      in  STD_LOGIC;
         pcen, irwrite:   in  STD_LOGIC;
         regwrite, alusrca: in STD_LOGIC;
         iord, memtoreg:  in  STD_LOGIC;
         regdst:         in  STD_LOGIC;
         alusrcb, pcsrc:  in  STD_LOGIC_VECTOR(1 downto 0);
         alucontrol:      in  STD_LOGIC_VECTOR(2 downto 0);
         readdata:        in  STD_LOGIC_VECTOR(31 downto 0);
         op, funct:       out STD_LOGIC_VECTOR(5 downto 0);
         zero:            out STD_LOGIC;
         adr:             out STD_LOGIC_VECTOR(31 downto 0);
         writedata:       inout STD_LOGIC_VECTOR(31 downto 0);
         readdata:        in  STD_LOGIC_VECTOR(31 downto 0));
    end component;
    signal zero, pcen, irwrite, regwrite, alusrca, iord, memtoreg,
           regdst: STD_LOGIC;
    signal alusrcb: STD_LOGIC_VECTOR(2 downto 0); -- ORI, XORI
    signal pcsrc:   STD_LOGIC_VECTOR(1 downto 0);
    signal alucontrol: STD_LOGIC_VECTOR(3 downto 0); -- SRLV
    signal op, funct: STD_LOGIC_VECTOR(5 downto 0);
begin
    c: controller port map(clk, reset, op, funct, zero,
                          pcen, memwrite, irwrite, regwrite,
                          alusrca, iord, memtoreg, regdst,
                          alusrcb, pcsrc, alucontrol);
    dp: datapath port map(clk, reset,
                        pcen, irwrite, regwrite,
                        alusrca, iord, memtoreg, regdst,
                        alusrcb, pcsrc, alucontrol,
                        readdata, op, funct, zero,
                        adr, writedata, readdata);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity controller is -- multicycle control decoder
    port(clk, reset:      in  STD_LOGIC;
         op, funct:       in  STD_LOGIC_VECTOR(5 downto 0);
         zero:            in  STD_LOGIC;
         pcen, memwrite:  out STD_LOGIC;
         irwrite, regwrite: out STD_LOGIC;
         alusrca, iord:   out STD_LOGIC;
         memtoreg, regdst: out STD_LOGIC;
         alusrcb:         out STD_LOGIC_VECTOR(2 downto 0); --ORI, XORI
         pcsrc:           out STD_LOGIC_VECTOR(1 downto 0);
         alucontrol:      out STD_LOGIC_VECTOR(3 downto 0)); --SRLV
end;
architecture struct of controller is
    component maindec
    port(clk, reset:      in  STD_LOGIC;
         op:              in  STD_LOGIC_VECTOR(5 downto 0);
         pcwrite, memwrite: out STD_LOGIC;
         irwrite, regwrite: out STD_LOGIC;
         alusrca, branch:  out STD_LOGIC;
         iord, memtoreg:   out STD_LOGIC;
         regdst:          out STD_LOGIC;
         alusrcb:         out STD_LOGIC_VECTOR(2 downto 0); --ORI, XORI
         pcsrc:           out STD_LOGIC_VECTOR(1 downto 0);
    end component;

```

```

    aluop:                out STD_LOGIC_VECTOR(2 downto 0));--SRLV, XORI
end component;
component aludec
    port(funcnt:         in  STD_LOGIC_VECTOR(5 downto 0);
          aluop:         in  STD_LOGIC_VECTOR(1 downto 0);
          alucontrol:    out STD_LOGIC_VECTOR(2 downto 0));
end component;
signal aluop: STD_LOGIC_VECTOR(2 downto 0);  --XORI
signal branch, pcwrite: STD_LOGIC;
begin
    md: maindec port map(clk, reset, op,
                        pcwrite, memwrite, irwrite, regwrite,
                        alusrca, branch, iord, memtoreg, regdst,
                        alusrca, pcsrc, aluop);
    ad: aludec port map(funcnt, aluop, alucontrol);

    pcen <= pcwrite or (branch and zero);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity maindec is -- main control decoder
    port(clk, reset:      in  STD_LOGIC;
          op:             in  STD_LOGIC_VECTOR(5 downto 0);
          pcwrite, memwrite: out STD_LOGIC;
          irwrite, regwrite: out STD_LOGIC;
          alusrca, branch:  out STD_LOGIC;
          iord, memtoreg:   out STD_LOGIC;
          regdst:          out STD_LOGIC;
          alusrca:         out STD_LOGIC_VECTOR(2 downto 0); --ORI, XORI
          pcsrc:           out STD_LOGIC_VECTOR(1 downto 0);
          aluop:           out STD_LOGIC_VECTOR(2 downto 0));--SRLV, XORI
end;

architecture behave of maindec is
    type statetype is (FETCH, DECODE, MEMADR, MEMRD, MEMWB, MEMWR,
                      RTYPEEX, RTYPEWB, BEQEX, ADDIEX, ADDIWB, JEX,
                      ORIEX, ORIWB, XORIEX, XORIWB);
    signal state, nextstate: statetype;
    signal controls: STD_LOGIC_VECTOR(16 downto 0);
begin
    --state register
    process(clk, reset) begin
        if reset then state <= FETCH;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when FETCH =>          nextstate <= DECODE;
            when DECODE =>
                case op is
                    when "100011" => nextstate <= MEMADR; --LW
                    when "101011" => nextstate <= MEMADR; --SW
                    when "000000" => nextstate <= RTYPEEX;--RTYPE
                    when "000100" => nextstate <= BEQEX;  --BEQ
                    when "001000" => nextstate <= ADDIEX; --ADDI
                    when "000010" => nextstate <= JEX;    --J
                    when "001101" => nextstate <= ORIEX;  --ORI
                    when "001110" => nextstate <= XORIEX; --XOR
                    when others => nextstate <= FETCH; -- should never happen
                end case;
            when MEMADR =>

```

```

        case op is
            when "100011" => nextstate <= MEMRD;
            when "101011" => nextstate <= MEMWR;
            when others    => nextstate <= FETCH; -- should never happen
        end case;
    when MEMRD =>          nextstate <= MEMWB;
    when MEMWB =>          nextstate <= FETCH;
    when MEMWR =>          nextstate <= FETCH;
    when RTYPEEX =>        nextstate <= RTYPEWB;
    when RTYPEWB =>        nextstate <= FETCH;
    when BEQEX =>          nextstate <= FETCH;
    when ADDIEX =>          nextstate <= ADDIWB;
    when JEX =>            nextstate <= FETCH;
    when ORIEX =>          nextstate <= ORIWB; // ORI
    when ORIWB =>          nextstate <= FETCH; // ORI
    when XORIEX =>         nextstate <= XORIWB; // XORI
    when XORIWB =>         nextstate <= FETCH; // XORI
    when others =>         nextstate <= FETCH; -- should never happen
end case;
end process;

-- output logic
process(all) begin
    case state is
        when FETCH => controls <= "1010_00000_00100_000";
        when DECODE => controls <= "0000_00000_01100_000";
        when MEMADR => controls <= "0000_10000_01000_000";
        when MEMRD => controls <= "0000_00100_00000_000";
        when MEMWB => controls <= "0001_00010_00000_000";
        when MEMWR => controls <= "0100_00100_00000_000";
        when RTYPEEX => controls <= "0000_10000_00000_010";
        when RTYPEWB => controls <= "0001_00001_00000_000";
        when BEQEX => controls <= "0000_11000_00001_001";
        when ADDIEX => controls <= "0000_10000_01000_000";
        when ADDIWB => controls <= "0001_00000_00000_000";
        when JEX => controls <= "1000_00000_00010_000";
        when ORIEX => controls <= "0000_10000_10000_011";
        when ORIWB => controls <= "0001_00000_00000_000";
        when XORIEX => controls <= "0000_10000_10000_100";
        when XORIWB => controls <= "0001_00000_00000_000";
        when others => controls <= "0000_-----"; --illegal op
    end case;
end process;

pcwrite <= controls(16);
memwrite <= controls(15);
irwrite <= controls(14);
regwrite <= controls(13);
alusrca <= controls(12);
branch <= controls(11);
iord <= controls(10);
memtoreg <= controls(9);
regdst <= controls(8);
alusrcb <= controls(7 downto 5);
pcsrc <= controls(4 downto 3);
aluop <= controls(2 downto 0);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity aludec is -- ALU control decoder
    port(funcnt:      in STD_LOGIC_VECTOR(5 downto 0);
          aluop:      in STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
end;

```



```

architecture behave of aludec is
begin
  process(all) begin
    case aluop is
      when "000" => alucontrol <= "0010"; -- add (for lb/sb/addi)
      when "001" => alucontrol <= "1010"; -- sub (for beq)
      when "011" => alucontrol <= "0001"; -- or (for ori)
      when "100" => alucontrol <= "0101"; -- xor (for xori)
      when others => case funct is
        -- R-type instructions
        when "100000" => alucontrol <= "0010"; -- add
        when "100010" => alucontrol <= "1010"; -- sub
        when "100100" => alucontrol <= "0000"; -- and
        when "100101" => alucontrol <= "0001"; -- or
        when "101010" => alucontrol <= "1011"; -- slt
        when "000110" => alucontrol <= "0100"; -- srlv
        when others => alucontrol <= "----"; -- ???
      end case;
    end case;
  end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity datapath is -- MIPS datapath
  port(clk, reset: in STD_LOGIC;
        pcen, irwrite: in STD_LOGIC;
        regwrite, alusrca: in STD_LOGIC;
        iord, memtoreg: in STD_LOGIC;
        regdst: in STD_LOGIC;
        alusrcb: in STD_LOGIC_VECTOR(2 downto 0); --ori, xori
        pcsrc: in STD_LOGIC_VECTOR(1 downto 0);
        alucontrol: in STD_LOGIC_VECTOR(3 downto 0); --srlv
        readdata: in STD_LOGIC_VECTOR(31 downto 0);
        op, funct: out STD_LOGIC_VECTOR(5 downto 0);
        zero: out STD_LOGIC;
        adr: out STD_LOGIC_VECTOR(31 downto 0);
        writedata: inout STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of datapath is
  component alu
    port(A, B: in STD_LOGIC_VECTOR(31 downto 0);
          F: in STD_LOGIC_VECTOR(3 downto 0); --srlv, xori
          shamt: in STD_LOGIC_VECTOR(4 downto 0); --srlv
          Y: out STD_LOGIC_VECTOR(31 downto 0);
          Zero: out STD_LOGIC);
  end component;
  component regfile
    port(clk: in STD_LOGIC;
          we3: in STD_LOGIC;
          ral, ra2, wa3: in STD_LOGIC_VECTOR(4 downto 0);
          wd3: in STD_LOGIC_VECTOR(31 downto 0);
          rdl, rd2: out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component adder
    port(a, b: in STD_LOGIC_VECTOR(31 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component sl2
    port(a: in STD_LOGIC_VECTOR(31 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component signext
    port(a: in STD_LOGIC_VECTOR(15 downto 0);
          y: out STD_LOGIC_VECTOR(31 downto 0));
  end component;

```

```

end component;
component zeroext
  port(a: in  STD_LOGIC_VECTOR(15 downto 0);
        y: out STD_LOGIC_VECTOR(31 downto 0));
end component;
component flopr generic(width: integer);
  port(clk, reset: in  STD_LOGIC;
        d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
        q:         out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component flopenr generic(width: integer);
  port(clk, reset: in  STD_LOGIC;
        en:       in  STD_LOGIC;
        d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
        q:         out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component mux2 generic(width: integer);
  port(d0, d1: in  STD_LOGIC_VECTOR(width-1 downto 0);
        s:     in  STD_LOGIC;
        y:     out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component mux3 generic(width: integer);
  port(d0, d1, d2: in  STD_LOGIC_VECTOR(width-1 downto 0);
        s:         in  STD_LOGIC_VECTOR(1 downto 0);
        y:         out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component mux4 generic(width: integer);
  port(d0, d1, d2, d3: in  STD_LOGIC_VECTOR(width-1 downto 0);
        s:             in  STD_LOGIC_VECTOR(1 downto 0);
        y:             out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component mux5 generic(width: integer);
  port(d0, d1, d2, d3, d4: in  STD_LOGIC_VECTOR(width-1 downto 0);
        s:                 in  STD_LOGIC_VECTOR(2 downto 0);
        y:                 out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
signal writereg: STD_LOGIC_VECTOR(4 downto 0);
signal pcnext, pc, instr, data, srca, srcb, a,
  aluresult, aluout, signimm, signimmsh, wd3, rd1, rd2, pcjump:
  STD_LOGIC_VECTOR(31 downto 0);

begin
  -- op and funct fields to controller
  op <= instr(31 downto 26);
  funct <= instr(5 downto 0);

  -- datapath
  pcreg: flopenr generic map(32) port map(clk, reset, pcen, pcnext, pc);
  adrmux: mux2 generic map(32) port map(pc, aluout, iord, adr);
  instrreg: flopenr generic map(32) port map(clk, reset, irwrite,
    readdata, instr);
  datareg: flopr generic map(32) port map(clk, reset, readdata, data);
  regdstmux: mux2 generic map(5) port map(instr(20 downto 16),
    instr(15 downto 11),
    regdst, writereg);
  wdmux: mux2 generic map(32) port map(aluout, data, memtoreg, wd3);
  rf: regfile port map(clk, regwrite, instr(25 downto 21),
    instr(20 downto 16),
    writereg, wd3, rd1, rd2);
  se: signext port map(instr(15 downto 0), signimm);
  ze: zeroext port map(instr(15 downto 0), zeroimm); -- ori, xori
  immsh: sl2 port map(signimm, signimmsh);
  areg: flopr generic map(32) port map(clk, reset, rd1, a);
  breg: flopr generic map(32) port map(clk, reset, rd2, writedata);
  srcamux: mux2 generic map(32) port map(pc, a, alusrca, srca);

```

[illegible]

330 SOLUTIONS chapter 7

```

        when "01" =>    y <= d1;
        when "10" =>    y <= d2;
        when "11" =>    y <= d3;
        when others => y <= d0; -- should never happen
    end case;
end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux5 is -- five-input multiplexer
    generic(width: integer);
    port(d0, d1, d2, d3, d4: in  STD_LOGIC_VECTOR(width-1 downto 0);
          s:                    in  STD_LOGIC_VECTOR(2 downto 0);
          y:                    out STD_LOGIC_VECTOR(width-1 downto 0));
end;
architecture behave of mux5 is
begin
    process(all) begin
        case s is
            when "000" =>    y <= d0;
            when "001" =>    y <= d1;
            when "010" =>    y <= d2;
            when "011" =>    y <= d3;
            when "100" =>    y <= d4;
            when others => y <= d0; -- should never happen
        end case;
    end process;
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity alu is
    port(A, B:      in  STD_LOGIC_VECTOR(31 downto 0);
          F:        in  STD_LOGIC_VECTOR(3 downto 0); --srlv, xori
          shamt:    in  STD_LOGIC_VECTOR(4 downto 0); --srlv
          Y:        out STD_LOGIC_VECTOR(31 downto 0);
          Zero:     out STD_LOGIC);
end;

architecture synth of alu is
    signal S, Bout:      STD_LOGIC_VECTOR(31 downto 0);
begin
    Bout <= (not B) when (F(3) = '1') else B;
    S <= A + Bout + F(3);
    Zero <= '1' when (Y = X"00000000") else '0';

    process(all) begin
        case F(2 downto 0) is
            when "000" => Y <= A and Bout;
            when "001" => Y <= A or Bout;
            when "010" => Y <= S;
            when "011" => Y <=
                ("00000000000000000000000000000000" & S(31));
            when "100" => Y <= (Bout >> shamt); --srlv
            when others => Y <= X"00000000";
        end case;
    end process;
end process;

```

```

end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_unsigned.all;

entity signext is
    port(A:      in  STD_LOGIC_VECTOR(15 downto 0);
         Y:      out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture synth of signext is
begin
    Y <= (15 downto 0 => a, others => a(15));
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_unsigned.all;

entity zeroext is
    port(A:      in  STD_LOGIC_VECTOR(15 downto 0);
         Y:      out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture synth of zeroext is
begin
    Y <= (15 downto 0 => a, others => '0');
end;

# mipstest.asm
# Sarah_Harris@hmc.edu 20 February 2012
#
# Test the MIPS multicycle processor.
# add, sub, and, or, slt, addi, lw, sw, beq, j
# extended instructions: srlv, ori, xori, jr

# If successful, it should write the value 0xFE0B to memory address 108

#
# Assembly          Description          Address Machine
main:  addi $2, $0, 5      # initialize $2 = 5      0    20020005
      ori  $3, $2, 0xFEFE # $3 = 0xFEFF          4    3443fefe
      srlv $2, $3, $2     # $2 = $3 >> $2 = 0x7F7  8    00431006
      j    forward       #                    c    08000006
      addi $3, $0, 14     # not executed        10   2263000e
back:  beq  $2, $2, here   # should be taken     14   10420003
forward: addi $3, $3, 12   # $3 <= 0xFF0B        18   2063000c
      addi $31, $0, 0x14  # $31 ($ra) <= 0x14   1c   201f0014
      jr   $ra            # return to address 0x14 20   08000005
here:  addi $7, $3, -9     # $7 <= 0xFF02        24   2067ffff
      xori $6, $7, 0xFF07 # $6 <= 5             28   38e6ff07
      bne  $3, $7, around # should be taken     2c   14670003
      slt  $4, $7, $3     # not executed        30   00e6302a
      beq  $4, $0, around # not executed        34   10800001
      addi $5, $0, 0      # not executed        38   20050000
around: sw  $7, 95($6)    # [95+5] = [100] = 0xFF02 3c   acc7005f
      sw  $2, 104($0)     # [104] = 0x7F7       40   ac020068
      lw  $2, 100($0)     # $2 = [100] = 0xFF02  44   8c020064
      lbu $3, 107($0)    # $3 = 0x000000F7     48   9003006b
      j    end            # should be taken     4c   08000015
      addi $2, $0, 1      # not executed        50   20020001
end:   sub  $8, $2, $3     # $8 = 0xFE0B         54   00434022
      sw  $8, 108($0)    # [108] = 0xFE0B     58   ac08006c

```

FIGURE 7.18 Assembly and machine code for multicycle MIPS test program

MIPS Multicycle Modified Testbench

SystemVerilog

```
module testbench();

    logic        clk;
    logic        reset;

    logic [31:0] writedata, dataadr;
    logic memwrite;

    // keep track of execution status
    logic [31:0] cycle;
    logic        succeed;

    // instantiate device to be tested
    topmulti dut(clk, reset, writedata, dataadr, mem-
write);

    // initialize test
    initial
        begin
            reset <= 1; # 12; reset <= 0;
            cycle <= 1;
            succeed <= 0;
        end

    // generate clock to sequence tests
    always
        begin
            clk <= 1; # 5; clk <= 0; # 5;
            cycle <= cycle + 1;
        end

    // check results
    always @(negedge clk)
        begin
            if(memwrite & dataadr == 108) begin
                if(writedata == 65035) // 65035=0xFE0B
                    $display("Simulation succeeded");
                else begin
                    $display("Simulation failed");
                end
            end
            $stop;
        end
endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_UNSIGNED.all;
entity testbench is
end;

architecture test of testbench is
    component topmulti
        port(clk, reset:          in    STD_LOGIC;
              writedata, dataadr: inout STD_LOGIC_VECTOR(31 downto 0);
              memwrite:          inout STD_LOGIC);
    end component;
    signal readdata, writedata, dataadr:
        STD_LOGIC_VECTOR(31 downto 0);
    signal clk, reset, memwrite: STD_LOGIC;
begin

    -- instantiate device to be tested
    dut: topmulti port map(clk, reset, writedata, dataadr, memwrite);

    -- Generate clock with 10 ns period
    process begin
        clk <= '1';
        wait for 5 ns;
        clk <= '0';
        wait for 5 ns;
    end process;

    -- Generate reset for first two clock cycles
    process begin
        reset <= '1';
        wait for 22 ns;
        reset <= '0';
        wait;
    end process;

    -- check that 65035 gets written to address 108
    -- at end of program
    process (clk) begin
        if (clk'event and clk = '0' and memwrite = '1' and
            conv_integer(dataadr) = 108) then
            if (conv_integer(writedata) = 65035) then
                report "Just kidding: Simulation succeeded"
                    severity failure;
            else
                report "Simulation failed"
                    severity failure;
            end if;
        end if;
    end process;
end;
```

Exercise 7.27

We modify the MIPS multicycle processor to implement all instructions from Exercise 7.14.

SystemVerilog

```

module top(input  logic      clk, reset,
           output logic [31:0] writedata, dataadr,
           output logic      memwrite);

    logic [31:0] pc, instr, readdata;

    // instantiate processor and memories
    mips mips(clk, reset, pc, instr, memwrite, dataadr,
              writedata, readdata);
    imem imem(pc[7:2], instr);
    dmem dmem(clk, memwrite, dataadr, writedata, readdata);
endmodule

module dmem(input  logic      clk, we,
            input  logic [31:0] a, wd,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    assign rd = RAM[a[31:2]]; // word aligned

    always_ff @(posedge clk)
        if (we) RAM[a[31:2]] <= wd;
endmodule

module imem(input  logic [5:0] a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    initial
        $readmemh("memfile.dat",RAM);

    assign rd = RAM[a]; // word aligned
endmodule

module top(input  logic      clk, reset,
           output logic [31:0] writedata, adr,
           output logic      memwrite);

    logic [31:0] readdata;

    // instantiate processor and memory
    mips mips(clk, reset, adr, writedata, memwrite,
              readdata);
    mem mem(clk, memwrite, adr, writedata,
            readdata);
endmodule

module mips(input  logic      clk, reset,
            output logic [31:0] adr, writedata,
            output logic      memwrite,
            input  logic [31:0] readdata);

    logic zero, pcen, irwrite, regwrite,
          alusrc, iord, memtoreg, regdst;
    logic [2:0] alusrcb; // ANDI
    logic [1:0] pcsrc;
    logic [2:0] alucontrol;
    logic [5:0] op, funct;
    logic [1:0] lb;      // LB/LBU

```

334 SOLUTIONS chapter 7

```

    controller c(clk, reset, op, funct, zero,
                pcen, memwrite, irwrite, regwrite,
                alusrca, iord, memtoreg, regdst,
                alusrcb, pcsrc, alucontrol, lb); // LB/LBU
    datapath dp(clk, reset,
                pcen, irwrite, regwrite,
                alusrca, iord, memtoreg, regdst,
                alusrcb, pcsrc, alucontrol,
                lb, // LB/LBU
                op, funct, zero,
                adr, writedata, readdata);
endmodule

module controller(input logic clk, reset,
                  input logic [5:0] op, funct,
                  input logic zero,
                  output logic pcen, memwrite,
                  output logic irwrite, regwrite,
                  output logic alusrca, iord,
                  output logic memtoreg, regdst,
                  output logic [2:0] alusrcb, // ANDI
                  output logic [1:0] pcsrc,
                  output logic [2:0] alucontrol,
                  output logic [1:0] lb); // LB/LBU

    logic [1:0] aluop;
    logic branch, pcwrite;
    logic bne; // BNE

    // Main Decoder and ALU Decoder subunits.
    maindec md(clk, reset, op,
                pcwrite, memwrite, irwrite, regwrite,
                alusrca, branch, iord, memtoreg, regdst,
                alusrcb, pcsrc, aluop, bne, lb); //BNE, LBU
    aludec ad(funct, aluop, alucontrol);

    assign pcen = pcwrite | (branch & zero) |
                (bne & ~zero); // BNE
endmodule

module maindec(input clk, reset,
                input [5:0] op,
                output pcwrite, memwrite,
                output irwrite, regwrite,
                output alusrca, branch,
                output iord, memtoreg, regdst,
                output [2:0] alusrcb, // ANDI
                output [1:0] pcsrc,
                output [1:0] aluop,
                output bne, // BNE
                output [1:0] lb); // LB/LBU

    typedef enum logic [4:0] {FETCH, DECODE, MEMADR,
                              MEMRD, MEMWB, MEMWR, RTYPEEX, RTYPEWB, BEQEX,
                              ADDIEX, ADDIWB, JEX, ANDIEX, ANDIWB,
                              BNEEX, LBRD, LBRD} statetype;
    statetype [4:0] state, nextstate;

    parameter RTYPE = 6'b000000;
    parameter LW = 6'b100011;
    parameter SW = 6'b101011;
    parameter BEQ = 6'b000100;
    parameter ADDI = 6'b001000;
    parameter J = 6'b000010;
    parameter BNE = 6'b000101;

```



```

parameter LBU = 6'b100100;
parameter LB = 6'b100000;
parameter ANDI = 6'b001100;

logic [18:0] controls; // ANDI, BNE, LBU

// state register
always_ff @(posedge clk or posedge reset)
    if(reset) state <= FETCH;
    else state <= nextstate;

// next state logic
always_comb
    case(state)
        FETCH: nextstate <= DECODE;
        DECODE: case(op)
            LW: nextstate <= MEMADR;
            SW: nextstate <= MEMADR;
            LB: nextstate <= MEMADR; // LB
            LBU: nextstate <= MEMADR; // LBU
            RTYPE: nextstate <= RTYPEEX;
            BEQ: nextstate <= BEQEX;
            ADDI: nextstate <= ADDIEX;
            J: nextstate <= JEX;
            BNE: nextstate <= BNEEX; // BNE
            ANDI: nextstate <= ADDIEX; // ANDI
            default: nextstate <= FETCH;
            // should never happen
        endcase
        MEMADR: case(op)
            LW: nextstate <= MEMRD;
            SW: nextstate <= MEMWR;
            LBU: nextstate <= LBURD; // LBU
            LB: nextstate <= LBRD; // LB
            default: nextstate <= FETCH;
            // should never happen
        endcase
        MEMRD: nextstate <= MEMWB;
        MEMWB: nextstate <= FETCH;
        MEMWR: nextstate <= FETCH;
        RTYPEEX: nextstate <= RTYPEWB;
        RTYPEWB: nextstate <= FETCH;
        BEQEX: nextstate <= FETCH;
        ADDIEX: nextstate <= ADDIWB;
        ADDIWB: nextstate <= FETCH;
        JEX: nextstate <= FETCH;
        ANDIEX: nextstate <= ANDIWB; // ANDI
        ANDIWB: nextstate <= FETCH; // ANDI
        BNEEX: nextstate <= FETCH; // BNE
        LBURD: nextstate <= MEMWB; // LBU
        LBRD: nextstate <= MEMWB; // LB
        default: nextstate <= FETCH;
        // should never happen
    endcase

// output logic
assign {pcwrite, memwrite, irwrite, regwrite,
        alusrca, branch, iord, memtoreg, regdst,
        bne, // BNE
        alusrca, pcsrc,
        aluop,
        lb} = controls; // LBU

always_comb
    case(state)

```

```

        FETCH: controls <= 19'b1010_00000_0_00100_00_00;
        DECODE: controls <= 19'b0000_00000_0_01100_00_00;
        MEMADR: controls <= 19'b0000_10000_0_01000_00_00;
        MEMRD: controls <= 19'b0000_00100_0_00000_00_00;
        MEMWB: controls <= 19'b0001_00010_0_00000_00_00;
        MEMWR: controls <= 19'b0100_00100_0_00000_00_00;
        RTYPEEX: controls <= 19'b0000_10000_0_00000_10_00;
        RTYPEWB: controls <= 19'b0001_00001_0_00000_00_00;
        BEQEX: controls <= 19'b0000_11000_0_00001_01_00;
        ADDIEX: controls <= 19'b0000_10000_0_01000_00_00;
        ADDIWB: controls <= 19'b0001_00000_0_00000_00_00;
        JEX: controls <= 19'b1000_00000_0_00010_00_00;
        ANDIEX: controls <= 19'b0000_10000_0_10000_11_00; // ANDI
        ANDIWB: controls <= 19'b0001_00000_0_00000_00_00; // ANDI
        BNEEX: controls <= 19'b0000_10000_1_00001_01_00; // BNE
        LBU: controls <= 19'b0000_00100_0_00000_00_01; // LBU
        LBRD: controls <= 19'b0000_00100_0_00000_00_10; // LB
        default: controls <= 19'b0000_xxxxx_x_xxxxx_xx_xx;
                // should never happen
    endcase
endmodule

module aludec(input logic [5:0] funct,
              input logic [1:0] aluop,
              output logic [2:0] alucontrol);

    always_comb
    case(aluop)
        2'b00: alucontrol <= 3'b010; // add
        2'b01: alucontrol <= 3'b110; // sub
        2'b11: alucontrol <= 3'b000; // and
        2'b10: case(funct)
            6'b100000: alucontrol <= 3'b010; // ADD
            6'b100010: alucontrol <= 3'b110; // SUB
            6'b100100: alucontrol <= 3'b000; // AND
            6'b100101: alucontrol <= 3'b001; // OR
            6'b101010: alucontrol <= 3'b111; // SLT
            default: alucontrol <= 3'bxxx; // ???
        endcase
        default: alucontrol <= 3'bxxx; // ???
    endcase
endmodule

module datapath(input logic clk, reset,
                input logic pcen, irwrite,
                input logic regwrite,
                input logic alusrca, iord,
                memtoreg, regdst,
                input logic [2:0] alusrcb, // ANDI
                input logic [1:0] pcsrc,
                input logic [2:0] alucontrol,
                input logic [1:0] lb, // LB/LBU
                output logic [5:0] op, funct,
                output logic zero,
                output logic [31:0] adr, writedata,
                input logic [31:0] readdata);

    // Internal signals of the datapath module

    logic [4:0] writereg;
    logic [31:0] pcnext, pc;
    logic [31:0] instr, data, srca, srcb;
    logic [31:0] a;
    logic [31:0] aluresult, aluout;
    logic [31:0] signimm; // the sign-extended imm

```

```

logic [31:0] zeroimm;    // the zero-extended imm
                        // ANDI
logic [31:0] signimmsh; // the sign-extended imm << 2
logic [31:0] wd3, rd1, rd2;
logic [31:0] memdata, membytezext, membytesext; // LB / LBU
logic [7:0] membyte; // LB / LBU

// op and funct fields to controller
assign op = instr[31:26];
assign funct = instr[5:0];

// datapath
flopennr #(32) pcreg(clk, reset, pcen, pcnext, pc);
mux2      #(32) adrmux(pc, aluout, iord, adr);
flopennr #(32) instrreg(clk, reset, irwrite,
                        readdata, instr);

// changes for LB / LBU
flopennr #(32) datareg(clk, reset, memdata, data);
mux4      #(8) lbmux(readdata[31:24],
                    readdata[23:16], readdata[15:8],
                    readdata[7:0], aluout[1:0],
                    membyte);
zeroext8_32 lbze(membyte, membytezext);
signext8_32 lbse(membyte, membytesext);
mux3      #(32) datamux(readdata, membytezext, membytesext,
                        lb, memdata);

mux2      #(5) regdstmux(instr[20:16],
                        instr[15:11], regdst, writereg);
mux2      #(32) wdmux(aluout, data, memtoreg, wd3);
regfile   rf(clk, regwrite, instr[25:21],
            instr[20:16],
            writereg, wd3, rd1, rd2);
signext   se(instr[15:0], signimm);
zeroext   ze(instr[15:0], zeroimm); // ANDI
sl2       immsh(signimm, signimmsh);
flopennr #(32) areg(clk, reset, rd1, a);
flopennr #(32) breg(clk, reset, rd2, writedata);
mux2      #(32) srcamux(pc, a, alusrc, src);
mux5      #(32) srcbmux(writedata, 32'b100,
                        signimm, signimmsh,
                        zeroimm, // ANDI
                        alusrcb, srcb);

alu       alu(src, srcb, alucontrol, aluresult, zero);
flopennr #(32) alureg(clk, reset, aluresult, aluout);
mux3      #(32) pcmux(aluresult, aluout,
                    {pc[31:28], instr[25:0], 2'b00},
                    pcsrc, pcnext);

endmodule

module alu(input logic [31:0] A, B,
           input logic [2:0] F,
           output logic [31:0] Y, output Zero);

logic [31:0] S, Bout;

assign Bout = F[2] ? ~B : B;
assign S = A + Bout + F[2];

always_comb
  case (F[1:0])
    3'b00: Y <= A & Bout;
  endcase

```

338 SOLUTIONS chapter 7

```

        3'b01: Y <= A | Bout;
        3'b10: Y <= S;
        3'b11: Y <= S[31];
    endcase

    assign Zero = (Y == 32'b0);
endmodule

// mux5 is needed for ANDI
module mux5 #(parameter WIDTH = 8)
    (input    [WIDTH-1:0] d0, d1, d2, d3, d4,
     input    [2:0]      s,
     output reg [WIDTH-1:0] y);

    always_comb
        case(s)
            3'b000: y <= d0;
            3'b001: y <= d1;
            3'b010: y <= d2;
            3'b011: y <= d3;
            3'b100: y <= d4;
        endcase
    endmodule

// zeroext is needed for ANDI
module zeroext(input  [15:0] a,
               output [31:0] y);

    assign y = {16'b0, a};
endmodule

// zeroext8_32 is needed for LBU
module zeroext8_32(input  logic [7:0] a,
                   output logic [31:0] y);

    assign y = {24'b0, a};
endmodule

// signext8_32 is needed for LB
module signext8_32(input  logic [7:0] a,
                  output logic [31:0] y);

    assign y = {{24{a[7]}}, a};
endmodule

module alu(input  logic [31:0] A, B,
           input  logic [3:0] F,
           input  logic [4:0] shamt, // SRL
           output logic [31:0] Y,
           output logic      Zero);

    logic [31:0] S, Bout;

    assign Bout = F[3] ? ~B : B;
    assign S = A + Bout + F[3]; // SRL

    always_comb
        case (F[2:0])
            3'b000: Y = A & Bout;
            3'b001: Y = A | Bout;
            3'b010: Y = S;
            3'b011: Y = S[31];
            3'b100: Y = (Bout >> shamt); // SRL
        endcase

```

```
    assign Zero = (Y == 32'b0);

endmodule

module regfile(input  logic      clk,
               input  logic      we3,
               input  logic [4:0] ra1, ra2, wa3,
               input  logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

    logic [31:0] rf[31:0];

    // three ported register file
    // read two ports combinatorially
    // write third port on rising edge of clk
    // register 0 hardwired to 0
    always_ff @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
    assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule

module adder(input  logic [31:0] a, b,
             output logic [31:0] y);

    assign y = a + b;
endmodule

module sl2(input  logic [31:0] a,
           output logic [31:0] y);

    // shift left by 2
    assign y = {a[29:0], 2'b00};
endmodule

module signext(input  logic [15:0] a,
               output logic [31:0] y);

    assign y = {{16{a[15]}}, a};
endmodule

module flopr #(parameter WIDTH = 8)
    (input  logic      clk, reset,
     input  logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1,
     input  logic      s,
     output logic [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mips is -- multicycle MIPS processor
    port(clk, reset:          in  STD_LOGIC;
```

340 SOLUTIONS chapter 7

```

        adr:                out STD_LOGIC_VECTOR(31 downto 0);
    writedata:              inout STD_LOGIC_VECTOR(31 downto 0);
        memwrite:           out STD_LOGIC;
    readdata:               in  STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of mips is
    component controller
        port(clk, reset:      in  STD_LOGIC;
              op, funct:      in  STD_LOGIC_VECTOR(5 downto 0);
              zero:           in  STD_LOGIC;
              pcen, memwrite: out STD_LOGIC;
              irwrite, regwrite: out STD_LOGIC;
              alusrca, iord:   out STD_LOGIC;
              memtoreg, regdst: out STD_LOGIC;
              alusrcb:         out STD_LOGIC_VECTOR(2 downto 0); --andi
              pcsrc:          out STD_LOGIC_VECTOR(1 downto 0);
              alucontrol:      out STD_LOGIC_VECTOR(2 downto 0);
              lb:             out STD_LOGIC_VECTOR(1 downto 0)); --lb, lbu
    end component;
    component datapath
        port(clk, reset:      in  STD_LOGIC;
              pcen, irwrite:   in  STD_LOGIC;
              regwrite, alusrca: in STD_LOGIC;
              iord, memtoreg:   in  STD_LOGIC;
              regdst:          in  STD_LOGIC;
              alusrcb:         in  STD_LOGIC_VECTOR(2 downto 0); --andi
              pcsrc:          in  STD_LOGIC_VECTOR(1 downto 0);
              alucontrol:      in  STD_LOGIC_VECTOR(2 downto 0);
              lb:             in  STD_LOGIC_VECTOR(1 downto 0); --lb / lbu
              readdata:        in  STD_LOGIC_VECTOR(31 downto 0);
              op, funct:       out STD_LOGIC_VECTOR(5 downto 0);
              zero:           out STD_LOGIC;
              adr:            out STD_LOGIC_VECTOR(31 downto 0);
              writedata:       inout STD_LOGIC_VECTOR(31 downto 0));
    end component;
    signal zero, pcen, irwrite, regwrite, alusrca, iord, memtoreg,
           regdst: STD_LOGIC;
    signal alusrcb: STD_LOGIC_VECTOR(2 downto 0); --andi
    signal pcsrc: STD_LOGIC_VECTOR(1 downto 0);
    signal alucontrol: STD_LOGIC_VECTOR(2 downto 0);
    signal op, funct: STD_LOGIC_VECTOR(5 downto 0);
    signal lb: STD_LOGIC_VECTOR(1 downto 0); --lb / lbu
begin
    c: controller port map(clk, reset, op, funct, zero,
                          pcen, memwrite, irwrite, regwrite,
                          alusrca, iord, memtoreg, regdst,
                          alusrcb, pcsrc, alucontrol, lb); --lb / lbu
    dp: datapath port map(clk, reset,
                        pcen, irwrite, regwrite,
                        alusrca, iord, memtoreg, regdst,
                        alusrcb, pcsrc, alucontrol,
                        lb,
                        readdata, op, funct, zero,
                        adr, writedata, readdata);
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity controller is -- multicycle control decoder
    port(clk, reset:      in  STD_LOGIC;
          op, funct:      in  STD_LOGIC_VECTOR(5 downto 0);
          zero:           in  STD_LOGIC;
          pcen, memwrite: out STD_LOGIC;
          irwrite, regwrite: out STD_LOGIC;
          alusrca, iord:   out STD_LOGIC;
    );
end entity;

```

```

    memtoreg, regdst:    out STD_LOGIC;
    alusrcb:             out STD_LOGIC_VECTOR(2 downto 0); --andi
    pcsrc:               out STD_LOGIC_VECTOR(1 downto 0);
    alucontrol:          out STD_LOGIC_VECTOR(2 downto 0);
    lb:                  out STD_LOGIC_VECTOR(1 downto 0)); --lb, lbu
end;
architecture struct of controller is
    component maindec
        port(clk, reset:    in  STD_LOGIC;
              op:           in  STD_LOGIC_VECTOR(5 downto 0);
              pcwrite, memwrite: out STD_LOGIC;
              irwrite, regwrite: out STD_LOGIC;
              alusrca, branch: out STD_LOGIC;
              iord, memtoreg: out STD_LOGIC;
              regdst:       out STD_LOGIC;
              alusrcb:      out STD_LOGIC_VECTOR(2 downto 0); --andi
              pcsrc:       out STD_LOGIC_VECTOR(1 downto 0);
              aluop:       out STD_LOGIC_VECTOR(1 downto 0);
              lb:          out STD_LOGIC_VECTOR(1 downto 0)); --lb / lbu
    end component;
    component aludec
        port(funcnt:    in  STD_LOGIC_VECTOR(5 downto 0);
              aluop:    in  STD_LOGIC_VECTOR(1 downto 0);
              alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
    end component;
    signal aluop: STD_LOGIC_VECTOR(1 downto 0);
    signal branch, pcwrite, bne: STD_LOGIC; --bne
begin
    md: maindec port map(clk, reset, op,
                        pcwrite, memwrite, irwrite, regwrite,
                        alusrca, branch, iord, memtoreg, regdst,
                        alusrcb, pcsrc, aluop, bne, lb); --bne, lb
    ad: aludec port map(funcnt, aluop, alucontrol);

    pcen <= pcwrite or (branch and zero) or (bne and (not zero)); --bne
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity maindec is -- main control decoder
    port(clk, reset:    in  STD_LOGIC;
          op:           in  STD_LOGIC_VECTOR(5 downto 0);
          pcwrite, memwrite: out STD_LOGIC;
          irwrite, regwrite: out STD_LOGIC;
          alusrca, branch: out STD_LOGIC;
          iord, memtoreg: out STD_LOGIC;
          regdst:       out STD_LOGIC;
          alusrcb:      out STD_LOGIC_VECTOR(2 downto 0); --andi
          pcsrc:       out STD_LOGIC_VECTOR(1 downto 0);
          aluop:       out STD_LOGIC_VECTOR(1 downto 0);
          bne:         out STD_LOGIC; --bne
          aluop:       out STD_LOGIC_VECTOR(1 downto 0)); --lb / lbu
    end;

architecture behave of maindec is
    type statetype is (FETCH, DECODE, MEMADR, MEMRD, MEMWB, MEMWR,
                      RTYPEWB, BEQEX, ADDIEX, ADDIWB, JEX,
                      ANDIEX, ANDIWB, BNEEX, LBRD, LBRD);
    signal state, nextstate: statetype;
    signal controls: STD_LOGIC_VECTOR(18 downto 0);
begin
    --state register
    process(clk, reset) begin
        if reset then state <= FETCH;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

```

```

        end if;
    end process;

    -- next state logic
    process(all) begin
        case state is
            when FETCH =>          nextstate <= DECODE;
            when DECODE =>
                case op is
                    when "100011" => nextstate <= MEMADR; --LW
                    when "101011" => nextstate <= MEMADR; --SW
                    when "100000" => nextstate <= MEMADR; --LB
                    when "100100" => nextstate <= MEMADR; --LBU
                    when "000000" => nextstate <= RTYPEEX; --RTYPE
                    when "000100" => nextstate <= BEQEX;  --BEQ
                    when "001000" => nextstate <= ADDIEX; --ADDI
                    when "000010" => nextstate <= JEX;    --J
                    when "000101" => nextstate <= ORIEX;  --BNE
                    when "001100" => nextstate <= ORIEX;  --ANDI
                    when others => nextstate <= FETCH; -- should never happen
                end case;
            when MEMADR =>
                case op is
                    when "100011" => nextstate <= MEMRD;
                    when "101011" => nextstate <= MEMWR;
                    when "100000" => nextstate <= LBRD;  --LB
                    when "100100" => nextstate <= LBRD;  --LBU
                    when others => nextstate <= FETCH; -- should never happen
                end case;
            when MEMRD =>          nextstate <= MEMWB;
            when MEMWB =>          nextstate <= FETCH;
            when MEMWR =>          nextstate <= FETCH;
            when RTYPEEX =>        nextstate <= RTYPEWB;
            when RTYPEWB =>        nextstate <= FETCH;
            when BEQEX =>          nextstate <= FETCH;
            when ADDIEX =>          nextstate <= ADDIWB;
            when JEX =>            nextstate <= FETCH;
            when ANDIEX =>          nextstate <= ANDIWB; // ANDI
            when ANDIWB =>          nextstate <= FETCH; // ANDI
            when BNEEX =>          nextstate <= FETCH; // BNE
            when LBRD =>           nextstate <= MEMWB; // LBU
            when LBRD =>           nextstate <= MEMWB; // LB
            when others =>          nextstate <= FETCH; -- should never happen
        end case;
    end process;

    -- output logic
    process(all) begin
        case state is
            when FETCH => controls <= "1010_00000_0_00100_00_00";
            when DECODE => controls <= "0000_00000_0_01100_00_00";
            when MEMADR => controls <= "0000_10000_0_01000_00_00";
            when MEMRD => controls <= "0000_00100_0_00000_00_00";
            when MEMWB => controls <= "0001_00010_0_00000_00_00";
            when MEMWR => controls <= "0100_00100_0_00000_00_00";
            when RTYPEEX => controls <= "0000_10000_0_00000_10_00";
            when RTYPEWB => controls <= "0001_00001_0_00000_00_00";
            when BEQEX => controls <= "0000_11000_0_00001_01_00";
            when ADDIEX => controls <= "0000_10000_0_01000_00_00";
            when ADDIWB => controls <= "0001_00000_0_00000_00_00";
            when JEX => controls <= "1000_00000_0_00010_00_00";
            when ANDIEX => controls <= "0000_10000_0_10000_11_00";
            when ANDIWB => controls <= "0001_00000_0_00000_00_00";
            when BNEEX => controls <= "0000_10000_1_00001_01_00";
            when LBRD => controls <= "0000_00100_0_00000_00_01";
            when LBRD => controls <= "0000_00100_0_00000_00_10";
        end case;
    end process;

```



```

        when others => controls <= "0000_-----_-----_-----";
                                --illegal op
    end case;
end process;

pcwrite <= controls(18);
memwrite <= controls(17);
irwrite <= controls(16);
regwrite <= controls(15);
alusrca <= controls(14);
branch <= controls(13);
iord <= controls(12);
memtoreg <= controls(11);
regdst <= controls(10);
bne <= controls(9);
alusrcb <= controls(8 downto 6);
pcsrc <= controls(5 downto 4);
aluop <= controls(3 downto 1);
lb <= controls(0);

end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity aludec is -- ALU control decoder
    port(funcnt:      in  STD_LOGIC_VECTOR(5 downto 0);
          aluop:      in  STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture behave of aludec is
begin
    process(all) begin
        case aluop is
            when "00" => alucontrol <= "010"; -- add (for lb/sb/addi)
            when "01" => alucontrol <= "110"; -- sub (for beq)
            when "11" => alucontrol <= "000"; -- and (for andi)
            when others => case funct is
                                -- R-type instructions
                                when "100000" => alucontrol <= "010"; -- add
                                when "100010" => alucontrol <= "110"; -- sub
                                when "100100" => alucontrol <= "000"; -- and
                                when "100101" => alucontrol <= "001"; -- or
                                when "101010" => alucontrol <= "111"; -- slt
                                when others   => alucontrol <= "----"; -- ???
                            end case;
        end case;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity datapath is -- MIPS datapath
    port(clk, reset:      in  STD_LOGIC;
          pcen, irwrite:  in  STD_LOGIC;
          regwrite, alusrca: in STD_LOGIC;
          iord, memtoreg:  in  STD_LOGIC;
          regdst:         in  STD_LOGIC;
          alusrcb:        in  STD_LOGIC_VECTOR(2 downto 0); --andi
          pcsrc:          in  STD_LOGIC_VECTOR(1 downto 0);
          alucontrol:      in  STD_LOGIC_VECTOR(2 downto 0);
          lb:             in  STD_LOGIC_VECTOR(1 downto 0); --lb / lbu
          readdata:        in  STD_LOGIC_VECTOR(31 downto 0);
          op, funct:      out STD_LOGIC_VECTOR(5 downto 0);
          zero:           out STD_LOGIC;
          adr:            out STD_LOGIC_VECTOR(31 downto 0);
          writedata:      inout STD_LOGIC_VECTOR(31 downto 0));

```

```

end;

architecture struct of datapath is
  component alu
    port(A, B:      in  STD_LOGIC_VECTOR(31 downto 0);
         F:         in  STD_LOGIC_VECTOR(2 downto 0);
         Y:         out STD_LOGIC_VECTOR(31 downto 0);
         Zero:      out STD_LOGIC);
  end component;
  component regfile
    port(clk:       in  STD_LOGIC;
         we3:       in  STD_LOGIC;
         ra1, ra2, wa3: in STD_LOGIC_VECTOR(4 downto 0);
         wd3:       in  STD_LOGIC_VECTOR(31 downto 0);
         rd1, rd2:  out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component adder
    port(a, b: in  STD_LOGIC_VECTOR(31 downto 0);
         y:   out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component sl2
    port(a: in  STD_LOGIC_VECTOR(31 downto 0);
         y: out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component signext
    port(a: in  STD_LOGIC_VECTOR(15 downto 0);
         y: out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component zeroext
    port(a: in  STD_LOGIC_VECTOR(15 downto 0);
         y: out STD_LOGIC_VECTOR(31 downto 0));
  end component;
  component flopr generic(width: integer);
    port(clk, reset: in  STD_LOGIC;
         d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
         q:         out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  component flopenr generic(width: integer);
    port(clk, reset: in  STD_LOGIC;
         en:        in  STD_LOGIC;
         d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
         q:         out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  component mux2 generic(width: integer);
    port(d0, d1: in  STD_LOGIC_VECTOR(width-1 downto 0);
         s:      in  STD_LOGIC;
         y:      out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  component mux3 generic(width: integer);
    port(d0, d1, d2: in  STD_LOGIC_VECTOR(width-1 downto 0);
         s:         in  STD_LOGIC_VECTOR(1 downto 0);
         y:         out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  component mux4 generic(width: integer);
    port(d0, d1, d2, d3: in  STD_LOGIC_VECTOR(width-1 downto 0);
         s:             in  STD_LOGIC_VECTOR(1 downto 0);
         y:             out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  component mux5 generic(width: integer);
    port(d0, d1, d2, d3, d4: in  STD_LOGIC_VECTOR(width-1 downto 0);
         s:                 in  STD_LOGIC_VECTOR(2 downto 0);
         y:                 out STD_LOGIC_VECTOR(width-1 downto 0));
  end component;
  -- lb / lbu
  component zeroext8_32
    port(a: in  STD_LOGIC_VECTOR(7 downto 0);

```

[illegible]

```

    port(clk, reset: in  STD_LOGIC;
          en:           in  STD_LOGIC;
          d:             in  STD_LOGIC_VECTOR(width-1 downto 0);
          q:             out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture asynchronous of flopenr is
begin
    process(clk, reset) begin
        if reset then q <= CONV_STD_LOGIC_VECTOR(0, width);
        elsif rising_edge(clk) and en = '1' then
            q <= d;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux3 is -- three-input multiplexer
    generic(width: integer);
    port(d0, d1, d2: in  STD_LOGIC_VECTOR(width-1 downto 0);
          s:           in  STD_LOGIC_VECTOR(1 downto 0);
          y:           out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture behave of mux3 is
begin
    process(all) begin
        case s is
            when "00" => y <= d0;
            when "01" => y <= d1;
            when "10" => y <= d2;
            when others => y <= d0;
        end case;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux4 is -- four-input multiplexer
    generic(width: integer);
    port(d0, d1, d2, d3: in  STD_LOGIC_VECTOR(width-1 downto 0);
          s:             in  STD_LOGIC_VECTOR(1 downto 0);
          y:             out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture behave of mux4 is
begin
    process(all) begin
        case s is
            when "00" => y <= d0;
            when "01" => y <= d1;
            when "10" => y <= d2;
            when "11" => y <= d3;
            when others => y <= d0; -- should never happen
        end case;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mux5 is -- five-input multiplexer
    generic(width: integer);
    port(d0, d1, d2, d3, d4: in  STD_LOGIC_VECTOR(width-1 downto 0);
          s:                 in  STD_LOGIC_VECTOR(2 downto 0);

```

```

        y:                                out STD_LOGIC_VECTOR(width-1 downto 0));
end;
architecture behave of mux5 is
begin
    process(all) begin
        case s is
            when "000" => y <= d0;
            when "001" => y <= d1;
            when "010" => y <= d2;
            when "011" => y <= d3;
            when "100" => y <= d4;
            when others => y <= d0; -- should never happen
        end case;
    end process;
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity alu is
    port(A, B:      in  STD_LOGIC_VECTOR(31 downto 0));
        F:         in  STD_LOGIC_VECTOR(2 downto 0);
        Y:         out STD_LOGIC_VECTOR(31 downto 0);
        Zero:      out STD_LOGIC);
end;

architecture synth of alu is
    signal S, Bout: STD_LOGIC_VECTOR(31 downto 0);
begin
    Bout <= (not B) when (F(3) = '1') else B;
    S <= A + Bout + F(3);
    Zero <= '1' when (Y = X"00000000") else '0';

    process(all) begin
        case F(1 downto 0) is
            when "00" => Y <= A and Bout;
            when "01" => Y <= A or Bout;
            when "10" => Y <= S;
            when "11" => Y <=
                ("00000000000000000000000000000000" & S(31));
            when others => Y <= X"00000000";
        end case;
    end process;
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_unsigned.all;

entity signext is
    port(A:      in  STD_LOGIC_VECTOR(15 downto 0);
        Y:      out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture synth of signext is
begin
    Y <= (15 downto 0 => a, others => a(15));
end;

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_unsigned.all;

```

```
entity zeroext is
  port(A:      in  STD_LOGIC_VECTOR(15 downto 0);
        Y:      out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture synth of zeroext is
begin
  Y <= (15 downto 0 => a, others => '0');
end;

-- for lb / lbu
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_unsigned.all;

entity signext8_32 is
  port(A:      in  STD_LOGIC_VECTOR(7 downto 0);
        Y:      out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture synth of signext8_32 is
begin
  Y <= (7 downto 0 => a, others => a(7));
end;

-- for lb / lbu
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_unsigned.all;

entity zeroext8_32 is
  port(A:      in  STD_LOGIC_VECTOR(7 downto 0);
        Y:      out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture synth of zeroext8_32 is
begin
  Y <= (7 downto 0 => a, others => '0');
end;
```

Exercise 7.28

\$s1 is written, \$t0 is read in cycle 5.

Exercise 7.29

\$s0 is written, \$t4 and \$t5 are read in cycle 5.

Exercise 7.30

 


FIGURE 7.19 Abstract pipeline for Exercise 7.30

Exercise 7.31

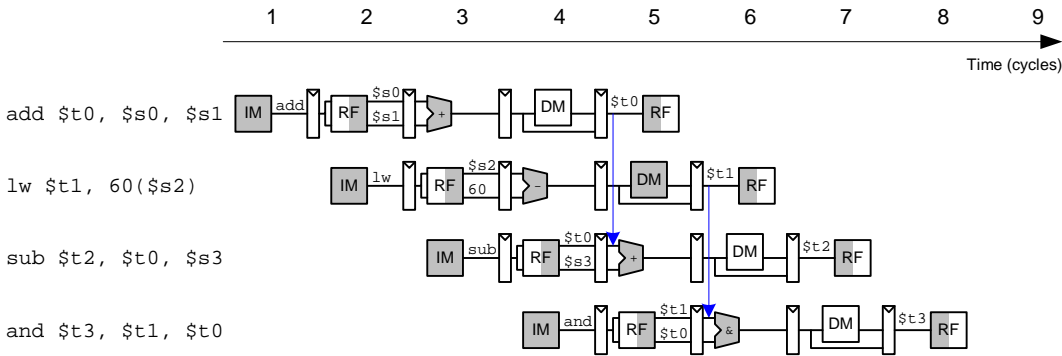


FIGURE 7.20 Abstract pipeline for Exercise 7.31

Exercise 7.32

It takes $1 + 4(5) + 2 = \mathbf{23}$ clock cycles to issue all the instructions.

instructions = $1 + 3(5) + 1 = 17$

CPI = 23 clock cycles / 17 instructions = **1.35**.

Exercise 7.33

It takes $3 + 6(10) + 3 = \mathbf{66 \text{ clock cycles}}$ to issue all the instructions.

instructions = $3 + 5(10) + 2 = 55$

CPI = $66 \text{ clock cycles} / 55 \text{ instructions} = \mathbf{1.2}$.

Exercise 7.34

`addi` requires no additional changes to the datapath, only changes to the control. The main decoder is modified to accommodate `addi` the same as it was for the single-cycle processor (Table 7.4) repeated in Table 7.21 for convenience.

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp |
|-------------|---------------|----------|----------|----------|----------|----------|----------|-----------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 |
| addi | 001000 | 1 | 0 | 1 | 0 | 0 | 0 | 00 |

TABLE 7.21 Main decoder truth table enhanced to support `addi`


Exercise 7.35

| Instruction | opcode | RegWrite | RegDst | ALUSrc | Branch | MemWrite | MemtoReg | ALUOp | JumpD |
|-------------|--------|----------|--------|--------|--------|----------|----------|-------|-------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |
| j | 000010 | 0 | X | X | 0 | 0 | X | XX | 1 |

TABLE 7.22 Main decoder truth table enhanced to support j

We must also write new equations for the flush signal, *FlushE*.
 $FlushE = lwstall \text{ OR } branchstall \text{ OR } JumpD$

Exercise 7.36

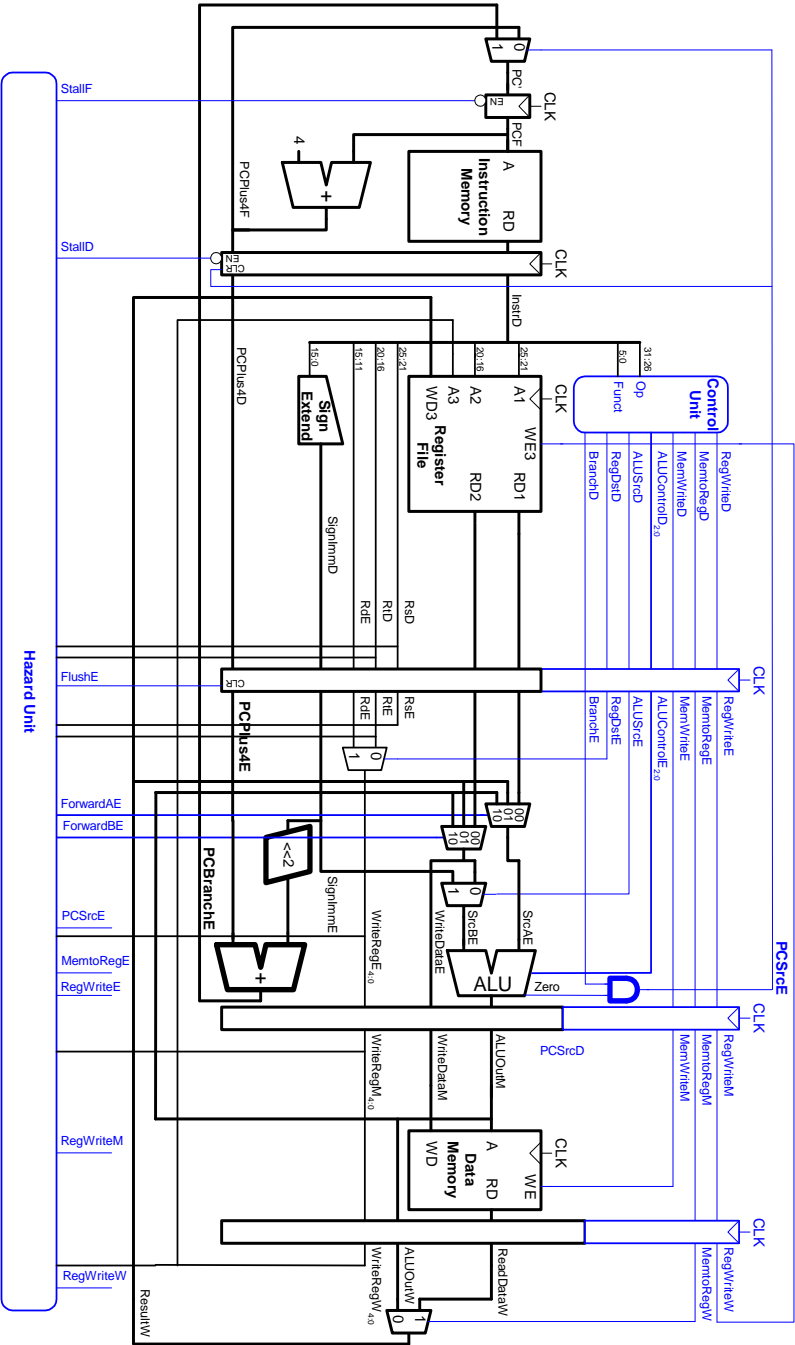

The Hazard Unit must no longer produce the ForwardAD and ForwardBD signals. PCPlus4 must also be passed through the pipeline register to the Execute stage. Also, the FlushE signal requires new hardware, as described by the following Boolean expression:

$$\text{FlushE} = \text{lwstall} \text{ OR } \text{PCSrcE}$$

CPI calculation:

Loads take 1 clock cycle when there is no dependency and 2 when the processor must stall for a dependency, so they have a CPI of $(0.6)(1) + (0.4)(2) = 1.4$. Branches take 1 clock cycle when they are predicted properly and 3 when they are not, so they have a CPI of $(0.75)(1) + (0.25)(3) = 1.5$. Jumps always have a CPI of 2. All other instructions have a CPI of 1. Hence, for this benchmark, Average CPI = $(0.25)(1.4) + (0.1)(1) + (0.11)(1.5) + (0.02)(2) + (0.52)(1) = 1.175$.

Cycle time calculation:

We modify Equation 7.5 to correspond to our new hardware. Only the Decode and Execute stages change.

$$T_c = \max \left(\begin{array}{l} t_{\text{pcq}} + t_{\text{memread}} + t_{\text{setup}} \\ 2(t_{\text{RFread}} + t_{\text{setup}}) \\ t_{\text{pcq}} + t_{\text{mux}} + t_{\text{mux}} + t_{\text{ALU}} + t_{\text{AND}} + t_{\text{mux}} + t_{\text{setup}} \\ t_{\text{pcq}} + t_{\text{memwrite}} + t_{\text{setup}} \\ 2(t_{\text{pcq}} + t_{\text{mux}} + t_{\text{RFwrite}}) \end{array} \right) \left\{ \begin{array}{l} \text{Fetch} \\ \text{Decode} \\ \text{Execute} \\ \text{Memory} \\ \text{Writeback} \end{array} \right.$$

Thus, the cycle time of the pipelined processor is $T_{c,3} = \max(30 + 250 + 20, 2(150 + 20), 30 + 25 + 25 + 200 + 15 + 25 + 20, 30 + 220 + 20, 2(30 + 25 + 100)) = \max(300, 340, 340, 270, 310) = \mathbf{340 \text{ ps}}$. The Decode and Execute stages tie for the critical path.

According to Equation 7.1, the total execution time is $T_3 = (100 \times 10^9 \text{ instructions})(1.175 \text{ cycles / instruction})(340 \times 10^{-12} \text{ s/cycle}) = \mathbf{39.95 \text{ s}}$.

This compares with the execution time of 63.3 s when the branch prediction was performed in the Decode stage (see Example 7.10).

Exercise 7.37

The critical path is the Decode stage, according to Equation 7.5:

$T_{c3} = \max(30 + 250 + 20, 2(150 + 25 + 40 + 15 + 25 + 20), 30 + 25 + 25 + 200 + 20, 30 + 220 + 20, 2(30 + 25 + 100)) = \max(300, 550, 300, 270, 310) = 550$ ps. The next slowest stage is 310 ps for the writeback stage, so it doesn't make sense to make the Decode stage any faster than that.

The slowest unit in the Decode stage is the register file read (150 ps). We need to reduce the cycle time by $550 - 310 = 240$ ps. Thus, we need to reduce the register file read delay by $240/2 = 120$ ps to $(150 - 120) = \mathbf{30}$ ps.

The new cycle time is **310 ps**.

Exercise 7.38

Increasing the ALU delay by 20% (from 200 ps to 240 ps) does not change the critical path (the critical path is the Decode stage in either case, not the Execute stage). Thus, a 20% increase or decrease in delay in the ALU will not affect the cycle time.

Exercise 7.39

$$\text{CPI} = 0.25(1 + 0.5 \cdot 6) + 0.1(1) + 0.11(1 + 0.3 \cdot 1) + 0.02(2) + 0.52(1) = 1.8$$

$$\text{Execution Time} = (100 \times 10^9 \text{ instructions})(1.8 \text{ cycles/instruction})(400 \times 10^{-12} \text{ s/cycle}) = 72\text{s}$$

Exercise 7.40

MIPS Pipelined Processor

SystemVerilog

```
// pipelined MIPS processor
module mips(input logic clk, reset,
            output logic [31:0] pcF,
            input logic [31:0] instrF,
            output logic memwriteM,
            output logic [31:0] aluoutM, writedataM,
            input logic [31:0] readdataM);

    logic [5:0] opD, functD;
    logic regdstE, alusrcE,
          pcsrcD,
          memtoeregE, memtoeregM, memtoeregW,
          regwriteE, regwriteM, regwriteW;

    logic [2:0] alucontrolE;
    logic flushE, equalD;

    controller c(clk, reset, opD, functD, flushE,
                  equalD, memtoeregE, memtoeregM,
                  memtoeregW, memwriteM, pcsrcD,
                  branchD, alusrcE, regdstE, regwriteE,
                  regwriteM, regwriteW, jumpD,
                  alucontrolE);

    datapath dp(clk, reset, memtoeregE, memtoeregM,
                memtoeregW, pcsrcD, branchD,
                alusrcE, regdstE, regwriteE,
                regwriteM, regwriteW, jumpD,
                alucontrolE,
                equalD, pcF, instrF,
                aluoutM, writedataM, readdataM,
                opD, functD, flushE);

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity mips is -- pipelined MIPS processor
    port(clk, reset: in STD_LOGIC;
          pcF: inout STD_LOGIC_VECTOR(31 downto 0);
          instrF: in STD_LOGIC_VECTOR(31 downto 0);
          memwriteM: out STD_LOGIC;
          aluoutM, writedataM: inout STD_LOGIC_VECTOR(31 downto 0);
          readdataM: in STD_LOGIC_VECTOR(31 downto 0));
end;

architecture struct of mips is
    component controller
        port(clk, reset: in STD_LOGIC;
              opD, functD: in STD_LOGIC_VECTOR(5 downto 0);
              flushE, equalD: in STD_LOGIC;
              branchD: inout STD_LOGIC;
              memtoeregE, memtoeregM: inout STD_LOGIC;
              memtoeregW, memwriteM: out STD_LOGIC;
              pcsrcD, alusrcE: out STD_LOGIC;
              regdstE: out STD_LOGIC;
              regwriteE: inout STD_LOGIC;
              regwriteM, regwriteW: inout STD_LOGIC;
              jumpD: out STD_LOGIC;
              alucontrolE: out STD_LOGIC_VECTOR(2 downto 0));
    end component;
    component datapath
        port(clk, reset: in STD_LOGIC;
              memtoeregE, memtoeregM, memtoeregW: in STD_LOGIC;
              pcsrcD, branchD: in STD_LOGIC;
              alusrcE, regdstE: in STD_LOGIC;
              regwriteE, regwriteM, regwriteW: in STD_LOGIC;
              jumpD: in STD_LOGIC;
              alucontrolE: in STD_LOGIC_VECTOR(2 downto 0);
              equalD: out STD_LOGIC;
              pcF: inout STD_LOGIC_VECTOR(31 downto 0);
              instrF: in STD_LOGIC_VECTOR(31 downto 0);
              aluoutM, writedataM: inout STD_LOGIC_VECTOR(31 downto 0);
              readdataM: in STD_LOGIC_VECTOR(31 downto 0);
              opD, functD: out STD_LOGIC_VECTOR(5 downto 0);
              flushE: inout STD_LOGIC);
    end component;

    signal opD, functD: STD_LOGIC_VECTOR(5 downto 0);
    signal regdstE, alusrcE, pcsrcD, memtoeregE, memtoeregM,
          memtoeregW, regwriteE, regwriteM, regwriteW,
          branchD, jumpD: STD_LOGIC;
    signal alucontrolE: STD_LOGIC_VECTOR(2 downto 0);
    signal flushE, equalD: STD_LOGIC;
begin
    c: controller port map(clk, reset, opD, functD, flushE, equalD, branchD,
                          memtoeregE, memtoeregM, memtoeregW, memwriteM, pcsrcD,
                          alusrcE, regdstE, regwriteE, regwriteM, regwriteW, jumpD,
                          alucontrolE);
    dp: datapath port map(clk, reset, memtoeregE, memtoeregM, memtoeregW,
                          pcsrcD, branchD,
                          alusrcE, regdstE, regwriteE, regwriteM, regwriteW, jumpD,
                          alucontrolE,
                          equalD, pcF, instrF,
                          aluoutM, writedataM, readdataM,
                          opD, functD, flushE);
end;
```

MIPS Pipelined Control SystemVerilog

```
module controller(input logic      clk, reset,
                 input logic [5:0] opD, functD,
                 input logic      flushE, equalD,
                 output logic      memtoregE,
                                     memtoregM,
                 output logic      memtoregW,
                                     memwriteM,
                 output logic      pcsrcD,
                                     branchD, alusrcE,
                 output logic      regdstE,
                                     regwriteE,
                 output logic      regwriteM,
                                     regwriteW,
                 output logic      jumpD,
                 output logic [2:0] alucontrolE);

    logic [1:0] aluopD;

    logic      memtoregD, memwriteD, alusrcD,
               regdstD, regwriteD;
    logic [2:0] alucontrolD;
    logic      memwriteE;

    maindec md(opD, memtoregD, memwriteD, branchD,
               alusrcD, regdstD, regwriteD, jumpD,
               aluopD);
    aludec ad(functD, aluopD, alucontrolD);

    assign pcsrcD = branchD & equalD;

    // pipeline registers
    floprc #(8) regE(clk, reset, flushE,
                    {memtoregD, memwriteD, alusrcD,
                     regdstD, regwriteD, alucontrolD},
                    {memtoregE, memwriteE, alusrcE,
                     regdstE, regwriteE, alucontrolE});
    flopr #(3) regM(clk, reset,
                   {memtoregE, memwriteE, regwriteE},
                   {memtoregM, memwriteM, regwriteM});
    flopr #(2) regW(clk, reset,
                   {memtoregM, regwriteM},
                   {memtoregW, regwriteW});
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity controller is -- pipelined control decoder
    port(clk, reset:      in  STD_LOGIC;
          opD, functD:    in  STD_LOGIC_VECTOR(5 downto 0);
          flushE, equalD: in  STD_LOGIC;
          branchD:        in  STD_LOGIC;
          memtoregE, memtoregM: in  STD_LOGIC;
          memtoregW, memwriteM: out STD_LOGIC;
          pcsrcD, alusrcE:  out STD_LOGIC;
          regdstE:        out STD_LOGIC;
          regwriteE:      in  STD_LOGIC;
          regwriteM, regwriteW: in  STD_LOGIC;
          jumpD:          out STD_LOGIC;
          alucontrolE:     out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture struct of controller is
    component maindec
        port(op:      in  STD_LOGIC_VECTOR(5 downto 0);
              memtoreg, memwrite: out STD_LOGIC;
              branch, alusrc:    out STD_LOGIC;
              regdst, regwrite:  out STD_LOGIC;
              jump:            out STD_LOGIC;
              aluop:          out  STD_LOGIC_VECTOR(1 downto 0));
    end component;
    component aludec
        port(funct:    in  STD_LOGIC_VECTOR(5 downto 0);
              aluop:    in  STD_LOGIC_VECTOR(1 downto 0);
              alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
    end component;
    component flopr is generic(width: integer);
        port(clk, reset: in  STD_LOGIC;
              d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
              q:         out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    component floprc generic(width: integer);
        port(clk, reset: in  STD_LOGIC;
              clear:     in  STD_LOGIC;
              d:         in  STD_LOGIC_VECTOR(width-1 downto 0);
              q:         out STD_LOGIC_VECTOR(width-1 downto 0));
    end component;
    signal aluopD: STD_LOGIC_VECTOR(1 downto 0);
    signal memtoregD, memwriteD, alusrcD: STD_LOGIC;
    signal regdstD, regwriteD: STD_LOGIC;
    signal alucontrolD: STD_LOGIC_VECTOR(2 downto 0);
    signal memwriteE: STD_LOGIC;

    -- internal signals
    signal d_regE: STD_LOGIC_VECTOR(7 downto 0);
    signal q_regE: STD_LOGIC_VECTOR(7 downto 0);
    signal d_regM: STD_LOGIC_VECTOR(2 downto 0);
    signal q_regM: STD_LOGIC_VECTOR(2 downto 0);
    signal d_regW: STD_LOGIC_VECTOR(1 downto 0);
    signal q_regW: STD_LOGIC_VECTOR(1 downto 0);
begin
    md: maindec port map(opD, memtoregD, memwriteD, branchD,
                        alusrcD, regdstD, regwriteD, jumpD,
                        aluopD);
    ad: aludec port map(functD, aluopD, alucontrolD);

    pcsrcD <= branchD and equalD;
```

(controller continued from previous page)

VHDL

```
-- pipeline registers
regE: floprc generic map(8) port map (clk, reset, flushE,
    d_regE, q_regE);
regM: floprc generic map(3) port map(clk, reset,
    d_regM, q_regM);
regW: floprc generic map(2) port map(clk, reset,
    d_regW, q_regW);

d_regE <= memtoRegD & memwriteD & aluSrcD & regdstD &
    regwriteD & alucontrolD;
memtoRegE <= q_regE(7);
memwriteE <= q_regE(6);
aluSrcE <= q_regE(5);
regdstE <= q_regE(4);
regwriteE <= q_regE(3);
alucontrolE <= q_regE(2 downto 0);

d_regM <= memtoRegE & memwriteE & regwriteE;
memtoRegM <= q_regM(2);
memwriteM <= q_regM(1);
regwriteM <= q_regM(0);

d_regW <= memtoRegM & regwriteM;
memtoRegW <= q_regW(1);
regwriteW <= q_regW(0);
end;
```

MIPS Pipelined Main Decoder

SystemVerilog

```
module maindec(input  logic [5:0] op,
               output logic   memtoReg, memwrite,
               output logic   branch, aluSrc,
               output logic   regdst, regwrite,
               output logic   jump,
               output logic [1:0] aluop);

    logic [9:0] controls;

    assign {regwrite, regdst, aluSrc,
           branch, memwrite,
           memtoReg, jump, aluop} = controls;

    always_comb
    case(op)
        6'b000000: controls <= 9'b110000010; //Rtype
        6'b100011: controls <= 9'b101001000; //LW
        6'b101011: controls <= 9'b001010000; //SW
        6'b000100: controls <= 9'b000100001; //BEQ
        6'b001000: controls <= 9'b101000000; //ADDI
        6'b000010: controls <= 9'b000000100; //J
        default:   controls <= 9'bxxxxxxx; //???
    endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity maindec is -- main control decoder
    port(op:          in   STD_LOGIC_VECTOR(5 downto 0);
          memtoReg, memwrite: out STD_LOGIC;
          branch, aluSrc:    out STD_LOGIC;
          regdst, regwrite:  out STD_LOGIC;
          jump:              out STD_LOGIC;
          aluop:             out  STD_LOGIC_VECTOR(1 downto 0));
end;

architecture behave of maindec is
    signal controls: STD_LOGIC_VECTOR(8 downto 0);
begin
    process(all) begin
        case op is
            when "000000" => controls <= "110000010"; -- Rtype
            when "100011" => controls <= "101001000"; -- LW
            when "101011" => controls <= "001010000"; -- SW
            when "000100" => controls <= "000100001"; -- BEQ
            when "001000" => controls <= "101000000"; -- ADDI
            when "000010" => controls <= "000000100"; -- J
            when others   => controls <= "-----"; -- illegal op
        end case;
    end process;

    regwrite <= controls(8);
    regdst   <= controls(7);
    aluSrc   <= controls(6);
    branch   <= controls(5);
    memwrite <= controls(4);
    memtoReg <= controls(3);
    jump     <= controls(2);
    aluop    <= controls(1 downto 0);
end;
```


MIPS Pipelined ALU Decoder

SystemVerilog

```
module aludec(input  logic [5:0] funct,
             input  logic [1:0] aluop,
             output logic [2:0] alucontrol);

    always_comb
    case(aluop)
        2'b00: alucontrol <= 3'b010; // add
        2'b01: alucontrol <= 3'b110; // sub
        default: case(funct)           // RTYPE
            6'b100000: alucontrol <= 3'b010; // ADD
            6'b100010: alucontrol <= 3'b110; // SUB
            6'b100100: alucontrol <= 3'b000; // AND
            6'b100101: alucontrol <= 3'b001; // OR
            6'b101010: alucontrol <= 3'b111; // SLT
            default:   alucontrol <= 3'bxxx; // ???
        endcase
    endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity aludec is -- ALU control decoder
    port(funct:   in  STD_LOGIC_VECTOR(5 downto 0);
          aluop:   in  STD_LOGIC_VECTOR(1 downto 0);
          alucontrol: out STD_LOGIC_VECTOR(2 downto 0));
end;

architecture behave of aludec is
begin
    process(all) begin
        case aluop is
            when "00" => alucontrol <= "010"; -- add (for lb/sb/addi)
            when "01" => alucontrol <= "110"; -- sub (for beq)
            when others => case funct is
                                -- R-type instructions
                                when "100000" => alucontrol <= "010"; -- add
                                when "100010" => alucontrol <= "110"; -- sub
                                when "100100" => alucontrol <= "000"; -- and
                                when "100101" => alucontrol <= "001"; -- or
                                when "101010" => alucontrol <= "111"; -- slt
                                when others   => alucontrol <= "---"; -- ???
                            end case;
        end case;
    end process;
end;
```

MIPS Pipelined Datapath

SystemVerilog

VHDL

```

module datapath(input logic clk, reset,
               input logic memtoregE,
               memtoregM,
               memtoregW,
               input logic pcsrD, branchD,
               input logic alusrcE, regdstE,
               input logic regwriteE,
               regwriteM,
               regwriteW,
               input logic jumpD,
               input logic [2:0] alucontrolE,
               output logic equalD,
               output logic [31:0] pcF,
               input logic [31:0] instrF,
               output logic [31:0] aluoutM,
               writedataM,
               input logic [31:0] readdataM,
               output logic [5:0] opD, functD,
               output logic flushE);

logic forwardaD, forwardbD;
logic [1:0] forwardaE, forwardbE;
logic stallF;
logic [4:0] rsD, rtD, rdD, rsE, rtE, rdE;
logic [4:0] writeregE, writeregM, writeregW;
logic flushD;
logic [31:0] pcnextFD, pcnextbbrFD,
pcplus4F, pcbranchD;
logic [31:0] signimmD, signimmE, signimmshD;
logic [31:0] srcaD, srca2D, srcaE, srca2E;
logic [31:0] srcbD, srcb2D, srcbE, srcb2E, srcb3E;
logic [31:0] pcplus4D, instrD;
logic [31:0] aluoutE, aluoutW;
logic [31:0] readdataW, resultW;

// hazard detection
hazard h(rsD, rtD, rsE, rtE, writeregE, writeregM,
        writeregW, regwriteE, regwriteM, regwriteW,
        memtoregE, memtoregM, branchD,
        forwardaD, forwardbD, forwardaE,
        forwardbE,
        stallF, stallD, flushE);

// next PC logic (operates in fetch and decode)
mux2 #(32) pcbrmux(pcplus4F, pcbranchD, pcsrD,
pcnextbbrFD);
mux2 #(32) pcmux(pcnextbbrFD, {pcplus4D[31:28],
instrD[25:0], 2'b00},
jumpD, pcnextFD);

// register file (operates in decode and writeback)
regfile rf(clk, regwriteW, rsD, rtD, writeregW,
resultW, srcaE, srcbD);

// Fetch stage logic
flopennr #(32) pcoreg(clk, reset, ~stallF,
pcnextFD, pcF);
adder pcadd1(pcF, 32'b100, pcplus4F);

```

```

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity datapath is -- MIPS datapath
port(clk, reset: in STD_LOGIC;
      memtoregE, memtoregM, memtoregW: in STD_LOGIC;
      pcsrD, branchD: in STD_LOGIC;
      alusrcE, regdstE: in STD_LOGIC;
      regwriteE, regwriteM, regwriteW: in STD_LOGIC;
      jumpD: in STD_LOGIC;
      alucontrolE: in STD_LOGIC_VECTOR(2 downto 0);
      equalD: out STD_LOGIC;
      pcF: inout STD_LOGIC_VECTOR(31 downto 0);
      instrF: in STD_LOGIC_VECTOR(31 downto 0);
      aluoutM, writedataM: inout STD_LOGIC_VECTOR(31 downto 0);
      readdataM: in STD_LOGIC_VECTOR(31 downto 0);
      opD, functD: out STD_LOGIC_VECTOR(5 downto 0);
      flushE: inout STD_LOGIC);
end;

architecture struct of datapath is
component alu
port(A, B: in STD_LOGIC_VECTOR(31 downto 0);
      F: in STD_LOGIC_VECTOR(2 downto 0);
      Y: buffer STD_LOGIC_VECTOR(31 downto 0);
      Zero: out STD_LOGIC);
end component;
component regfile
port(clk: in STD_LOGIC;
      we3: in STD_LOGIC;
      ra1, ra2, wa3: in STD_LOGIC_VECTOR(4 downto 0);
      wd3: in STD_LOGIC_VECTOR(31 downto 0);
      rd1, rd2: out STD_LOGIC_VECTOR(31 downto 0));
end component;
component adder
port(a, b: in STD_LOGIC_VECTOR(31 downto 0);
      y: out STD_LOGIC_VECTOR(31 downto 0));
end component;
component sl2
port(a: in STD_LOGIC_VECTOR(31 downto 0);
      y: out STD_LOGIC_VECTOR(31 downto 0));
end component;
component signext
port(a: in STD_LOGIC_VECTOR(15 downto 0);
      y: out STD_LOGIC_VECTOR(31 downto 0));
end component;
component flopr generic(width: integer);
port(clk, reset: in STD_LOGIC;
      d: in STD_LOGIC_VECTOR(width-1 downto 0);
      q: out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component flopenr is generic(width: integer);
port(clk, reset: in STD_LOGIC;
      en: in STD_LOGIC;
      d: in STD_LOGIC_VECTOR(width-1 downto 0);
      q: out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component floprc is generic(width: integer);
port(clk, reset: in STD_LOGIC;
      clear: in STD_LOGIC;
      d: in STD_LOGIC_VECTOR(width-1 downto 0);
      q: out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component flopenrc is generic(width: integer);
port(clk, reset: in STD_LOGIC;
      en, clear: in STD_LOGIC;
      d: in STD_LOGIC_VECTOR(width-1 downto 0);
      q: out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component mux2 generic(width: integer);
port(d0, d1: in STD_LOGIC_VECTOR(width-1 downto 0);
      s: in STD_LOGIC;
      y: out STD_LOGIC_VECTOR(width-1 downto 0));
end component;
component mux3 generic(width: integer);
port(d0, d1, d2: in STD_LOGIC_VECTOR(width-1 downto 0);
      s: in STD_LOGIC_VECTOR(1 downto 0);
      y: out STD_LOGIC_VECTOR(width-1 downto 0));
end component;

```

*(continued from previous page)***SystemVerilog**

```

// Decode stage
flopnr # (32) r1D(clk, reset, ~stallD, pcplus4F,
pcplus4D);
flopenrc # (32) r2D(clk, reset, ~stallD, flushD, instrF, instrD);
signext se(instrD[15:0], signimmD);
sl2 immsh(signimmD, signimmshD);
adder pcadd2(pcplus4D, signimmshD, pcbranchD);
mux2 # (32) forwardadmux(srcaD, aluoutM, forwardaD, srca2D);
mux2 # (32) forwardbdmux(srcbD, aluoutM, forwardbD, srcb2D);
eqcmp comp(srca2D, srcb2D, equalD);

assign opD = instrD[31:26];
assign functD = instrD[5:0];
assign rsD = instrD[25:21];
assign rtD = instrD[20:16];
assign rdD = instrD[15:11];

assign flushD = pcsrCD | jumpD;

// Execute stage
floprr # (32) r1E(clk, reset, flushE, srcaD, srcaE);
floprr # (32) r2E(clk, reset, flushE, srcbD, srcbE);
floprr # (32) r3E(clk, reset, flushE, signimmD, signimmeE);
floprr # (5) r4E(clk, reset, flushE, rsD, rsE);
floprr # (5) r5E(clk, reset, flushE, rtD, rtE);
floprr # (5) r6E(clk, reset, flushE, rdD, rdE);
mux3 # (32) forwardaemux(srcaE, resultW, aluoutM, forwardaE, srca2E);
mux3 # (32) forwardbemux(srcbE, resultW, aluoutM, forwardbE, srcb2E);
mux2 # (32) srcbmux(srcb2E, signimmeE, alusrcE, srcb3E);
alu alu(srca2E, srcb3E, alucontrolE, aluoutE);
mux2 # (5) wrmmux(rtE, rdE, regdstE, writeregE);

// Memory stage
floprr # (32) r1M(clk, reset, srcb2E, writedataM);
floprr # (32) r2M(clk, reset, aluoutE, aluoutM);
floprr # (5) r3M(clk, reset, writeregE, writeregM);

// Writeback stage
floprr # (32) r1W(clk, reset, aluoutM, aluoutW);
floprr # (32) r2W(clk, reset, readdataM, readdataW);
floprr # (5) r3W(clk, reset, writeregM, writeregW);
mux2 # (32) resmux(aluoutW, readdataW, memtoregW, resultW);

endmodule

```

VHDL

```

component eqcmp is
port(a, b: in STD_LOGIC_VECTOR(31 downto 0);
y: out STD_LOGIC);
end component;

component hazard
port(rsD, rtD, rsE, rtE: in STD_LOGIC_VECTOR(4 downto 0);
writeregE, writeregM, writeregW: in STD_LOGIC_VECTOR(4 downto 0);
regwriteE, regwriteM, regwriteW: in STD_LOGIC;
memtoregE, memtoregM, branchD: in STD_LOGIC;
forwardaD, forwardbD: out STD_LOGIC;
forwardaE, forwardbE: out STD_LOGIC_VECTOR(1 downto 0);
stallF, flushE: out STD_LOGIC;
stallD: inout STD_LOGIC);
end component;

signal forwardaD, forwardbD: STD_LOGIC;
signal forwardaE, forwardbE: STD_LOGIC_VECTOR(1 downto 0);
signal stallF, stallFbar, stallD, stallDbar: STD_LOGIC;
signal rsD, rtD, rdD, rsE, rtE, rdE: STD_LOGIC_VECTOR(4 downto 0);
signal writeregE, writeregM, writeregW: STD_LOGIC_VECTOR(4 downto 0);
signal flushD: STD_LOGIC;
signal pcnextFD, pcnextbrFD, pcplus4F, pcbranchD: STD_LOGIC_VECTOR(31 downto 0);
signal signimmD, signimmeE, signimmshD: STD_LOGIC_VECTOR(31 downto 0);
signal srcaD, srca2D, srcaE, srca2E: STD_LOGIC_VECTOR(31 downto 0);
signal srcbD, srcb2D, srcbE, srcb2E, srcb3E: STD_LOGIC_VECTOR(31 downto 0);
signal pcplus4D, instrD: STD_LOGIC_VECTOR(31 downto 0);
signal aluoutE, aluoutW: STD_LOGIC_VECTOR(31 downto 0);
signal readdataW, resultW: STD_LOGIC_VECTOR(31 downto 0);
signal d1_pcmmux: STD_LOGIC_VECTOR(31 downto 0);
begin
-- hazard detection
h: hazard port map(rsD, rtD, rsE, rtE, writeregE, writeregM, writeregW,
regwriteE, regwriteM, regwriteW,
memtoregE, memtoregM, branchD,
forwardaD, forwardbD, forwardaE, forwardbE,
stallF, stallD, flushE);

-- next PC logic (operates in fetch and decode)
d1_pcmmux <= pcplus4D(31 downto 28) & instrD(25 downto 0) & "00";
pcbrmmux: mux2 generic map(32) port map(pcplus4F, pcbranchD, pcsrCD,
pcnextbrFD);
pcmmux: mux2 generic map(32) port map(pcnextbrFD, d1_pcmmux,
jumpD, pcnextFD);

-- register file (operates in decode and writeback)
rf: regfile port map(clk, regwriteW, rsD, rtD, writeregW,
resultW, srcaD, srcbD);

-- Fetch stage logic
stallDbar <= (not stallD);
stallFbar <= (not stallF);

pcreg: flopnr generic map(32) port map(clk, reset, stallFbar,
pcnextFD, pcF);
pcaddl: adder port map(pcF, "00000000000000000000000000000000",
pcplus4F);

-- Decode stage
r1D: flopnr generic map(32) port map(clk, reset, stallDbar,
pcplus4F, pcplus4D);
r2D: flopnr generic map(32) port map(clk, reset, stallDbar,
flushD, instrD, instrD);
se: signext port map(instrD(15 downto 0), signimmD);
immsh: sl2 port map(signimmD, signimmshD);
pcadd2: adder port map(pcplus4D, signimmshD, pcbranchD);
forwardadmux: mux2 generic map(32) port map(srcaD, aluoutM,
forwardaD, srca2D);
forwardbdmux: mux2 generic map(32) port map(srcbD, aluoutM,
forwardbD, srcb2D);
comp: eqcmp port map(srca2D, srcb2D, equalD);

opD <= instrD(31 downto 26);
functD <= instrD(5 downto 0);
rsD <= instrD(25 downto 21);
rtD <= instrD(20 downto 16);
rdD <= instrD(15 downto 11);

flushD <= pcsrCD or jumpD;

```

(continued from previous page)

VHDL

```
-- Execute stage
r1E: floprc generic map(32) port map(clk, reset, flushE, srcaD, srcaE);
r2E: floprc generic map(32) port map(clk, reset, flushE, srcbD, srcbE);
r3E: floprc generic map(32) port map(clk, reset, flushE, signimmD,
                                     signimmE);
r4E: floprc generic map(5) port map(clk, reset, flushE, rsD, rsE);
r5E: floprc generic map(5) port map(clk, reset, flushE, rtD, rtE);
r6E: floprc generic map(5) port map(clk, reset, flushE, rdD, rdE);
forwardaemux: mux3 generic map(32) port map(srcaE, resultW, aluoutM,
                                             forwardaE, srca2E);
forwardbemux: mux3 generic map(32) port map(srcbE, resultW, aluoutM,
                                             forwardbE, srcb2E);
srcbmux: mux2 generic map(32) port map(srcb2E, signimmE, alusrcE,
                                       srcb3E);
alul: alu port map(srca2E, srcb3E, alucontrolE, aluoutE);
wrmux: mux2 generic map(5) port map(rtE, rdE, regdstE, writeregE);

-- Memory stage
r1M: flopr generic map(32) port map(clk, reset, srcb2E, writedataM);
r2M: flopr generic map(32) port map(clk, reset, aluoutE, aluoutM);
r3M: flopr generic map(5) port map(clk, reset, writeregE, writeregM);

-- Writeback stage
r1W: flopr generic map(32) port map(clk, reset, aluoutM, aluoutW);
r2W: flopr generic map(32) port map(clk, reset, readdataM, readdataW);
r3W: flopr generic map(5) port map(clk, reset, writeregM, writeregW);
resmux: mux2 generic map(32) port map(aluoutW, readdataW, memtoeregW,
                                       resultW);

end;
```

The following describes the building blocks that are used in the MIPS pipelined processor that are not found in Section 7.6.2.

MIPS Pipelined Processor Hazard Unit

SystemVerilog

```

module hazard(input  logic [4:0] rsD, rtD, rsE, rtE,
              input  logic [4:0] writeregE,
                    writeregM, writeregW,
              input  logic      regwriteE, regwriteM,
                    regwriteW,
              input  logic      memtoregE, memtoregM,
                    branchD,
              output logic      forwardaD,
                    forwardbD,
              output logic [1:0] forwardaE, forwardbE,
              output logic      stallF, stallD,
                    flushE);

    logic lwstallD, branchstallD;

    // forwarding sources to D stage (branch equality)
    assign forwardaD = (rsD != 0 & rsD == writeregM &
                       regwriteM);
    assign forwardbD = (rtD != 0 & rtD == writeregM &
                       regwriteM);

    // forwarding sources to E stage (ALU)
    always_comb
    begin
        forwardaE = 2'b00; forwardbE = 2'b00;
        if (rsE != 0)
            if (rsE == writeregM & regwriteM)
                forwardaE = 2'b10;
            else if (rsE == writeregW & regwriteW)
                forwardaE = 2'b01;
        if (rtE != 0)
            if (rtE == writeregM & regwriteM)
                forwardbE = 2'b10;
            else if (rtE == writeregW & regwriteW)
                forwardbE = 2'b01;
    end

    // stalls
    assign #1 lwstallD = memtoregE &
                       (rtE == rsD | rtE == rtD);
    assign #1 branchstallD = branchD &
                       (regwriteE &
                        (writeregE == rsD | writeregE == rtD) |
                        memtoregM &
                        (writeregM == rsD | writeregM == rtD));

    assign #1 stallD = lwstallD | branchstallD;
    assign #1 stallF = stallD;
    // stalling D stalls all previous stages
    assign #1 flushE = stallD;
    // stalling D flushes next stage

    // Note: not necessary to stall D stage on store
    // if source comes from load;
    // instead, another bypass network could
    // be added from W to M
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity hazard is -- hazard unit
    port(rsD, rtD, rsE, rtE:      in  STD_LOGIC_VECTOR(4 downto 0);
          writeregE, writeregM, writeregW: in  STD_LOGIC_VECTOR(4 downto 0);
          regwriteE, regwriteM, regwriteW: in  STD_LOGIC;
          memtoregE, memtoregM, branchD:  in  STD_LOGIC;
          forwardaD, forwardbD:           out STD_LOGIC;
          forwardaE, forwardbE:           out STD_LOGIC_VECTOR(1 downto 0);
          stallF, flushE:                 out STD_LOGIC;
          stallD:                         inout STD_LOGIC);
end;

architecture behave of hazard is
    signal lwstallD, branchstallD: STD_LOGIC;
begin

    -- forwarding sources to D stage (branch equality)
    forwardaD <= '1' when ((rsD /= "00000") and (rsD = writeregM) and
                          (regwriteM = '1'))
                else '0';
    forwardbD <= '1' when ((rtD /= "00000") and (rtD = writeregM) and
                          (regwriteM = '1'))
                else '0';

    -- forwarding sources to E stage (ALU)
    process(all) begin
        forwardaE <= "00"; forwardbE <= "00";
        if (rsE /= "00000") then
            if ((rsE = writeregM) and (regwriteM = '1')) then
                forwardaE <= "10";
            elsif ((rsE = writeregW) and (regwriteW = '1')) then
                forwardaE <= "01";
            end if;
        end if;
        if (rtE /= "00000") then
            if ((rtE = writeregM) and (regwriteM = '1')) then
                forwardbE <= "10";
            elsif ((rtE = writeregW) and (regwriteW = '1')) then
                forwardbE <= "01";
            end if;
        end if;
    end process;

    -- stalls
    lwstallD <= '1' when ((memtoregE = '1') and ((rtE = rsD) or (rtE = rtD)))
                else '0';
    branchstallD <= '1' when ((branchD = '1') and
                             (((regwriteE = '1') and
                               ((writeregE = rsD) or (writeregE = rtD))) or
                              (memtoregM = '1') and
                              ((writeregM = rsD) or (writeregM = rtD)))))
                else '0';
    stallD <= (lwstallD or branchstallD) after 1 ns;
    stallF <= stallD after 1 ns; -- stalling D stalls all previous stages
    flushE <= stallD after 1 ns; -- stalling D flushes next stage

    -- not necessary to stall D stage on store if source comes from load;
    -- instead, another bypass network could be added from W to M
end;

```

MIPS Pipelined Processor Parts

SystemVerilog

```
module floprc #(parameter WIDTH = 8)
    (input logic          clk, reset,
     input logic          clear,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset)    q <= #1 0;
        else if (clear) q <= #1 0;
        else          q <= #1 d;
endmodule

module flopenrc #(parameter WIDTH = 8)
    (input logic          clk, reset,
     input logic          en, clear,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= #1 0;
        else if (clear) q <= #1 0;
        else if (en) q <= #1 d;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity floprc is -- flip-flop with synchronous reset and clear
    generic(width: integer);
    port(clk, reset: in  STD_LOGIC;
         clear:    in  STD_LOGIC;
         d:        in  STD_LOGIC_VECTOR(width-1 downto 0);
         q:        out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture synchronous of floprc is
begin
    process(clk, reset, clear) begin
        if rising_edge(clk) then
            if reset then q <= CONV_STD_LOGIC_VECTOR(0, width);
            elsif clear then q <= CONV_STD_LOGIC_VECTOR(0, width);
            else q <= d;
            end if;
        end if;
    end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_ARITH.all;
entity flopenrc is -- flip-flop with synchronous reset, enable, and clear
    generic(width: integer);
    port(clk, reset: in  STD_LOGIC;
         en, clear:  in  STD_LOGIC;
         d:          in  STD_LOGIC_VECTOR(width-1 downto 0);
         q:          out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture asynchronous of flopenrc is
begin
    process(clk, reset, clear) begin
        if rising_edge(clk) then
            if reset then q <= CONV_STD_LOGIC_VECTOR(0, width);
            elsif clear then q <= CONV_STD_LOGIC_VECTOR(0, width);
            elsif en then q <= d;
            end if;
        end if;
    end process;
end;
```

MIPS Pipelined Processor Memories

SystemVerilog

```

module imem(input  logic [5:0]  a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    initial
        begin
            $readmemh("memfile.dat",RAM);
        end

    assign rd = RAM[a]; // word aligned
endmodule

module dmem(input  logic      clk, we,
            input  logic [31:0] a, wd,
            output logic [31:0] rd);

    reg [31:0] RAM[63:0];

    initial
        begin
            $readmemh("memfile.dat",RAM);
        end

    assign rd = RAM[a[31:2]]; // word aligned

    always @(posedge clk)
        if (we)
            RAM[a[31:2]] <= wd;
endmodule

```

VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.all; use STD.TEXTIO.all;
use IEEE.STD_LOGIC_UNSIGNED.all; use IEEE.STD_LOGIC_ARITH.all;
entity imem is -- instruction memory
    port(a:  in  STD_LOGIC_VECTOR(5 downto 0);
         rd: out STD_LOGIC_VECTOR(31 downto 0));
end;
architecture behave of imem is
begin
    process is
        file memfile: TEXT;
        variable L: line;
        variable ch: character;
        variable index, result: integer;
        type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31 downto 0);
        variable mem: ramtype;
    begin
        -- initialize memory from file
        for i in 0 to 63 loop -- set all contents low
            mem(conv_integer(i)) := CONV_STD_LOGIC_VECTOR(0, 32);
        end loop;
        index := 0;
        FILE_OPEN(memfile, "memfile.dat", READ_MODE);
        while not endfile(memfile) loop
            readline(memfile, L);
            result := 0;
            for i in 1 to 8 loop
                read(L, ch);
                if '0' <= ch and ch <= '9' then
                    result := result*16 + character'pos(ch) - character'pos('0');
                elsif 'a' <= ch and ch <= 'f' then
                    result := result*16 + character'pos(ch) - character'pos('a')+10;
                else report "Format error on line " & integer'image(index)
                    severity error;
            end if;
        end loop;
        mem(index) := CONV_STD_LOGIC_VECTOR(result, 32);
        index := index + 1;
    end loop;

    -- read memory
    loop
        rd <= mem(CONV_INTEGER(a));
        wait on a;
    end loop;
end process;
end;

library IEEE; use IEEE.STD_LOGIC_1164.all;
use STD.TEXTIO.all;
use IEEE.STD_LOGIC_UNSIGNED.all; use IEEE.STD_LOGIC_ARITH.all;

entity dmem is -- data memory
    port(clk, we:  in  STD_LOGIC;
         a, wd:   in  STD_LOGIC_VECTOR(31 downto 0);
         rd:      out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of dmem is
begin
    process is
        type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31 downto 0);
        variable mem: ramtype;
    begin
        -- read or write memory
        loop
            if clk'event and clk = '1' then
                if (we = '1') then mem(CONV_INTEGER(a(7 downto 2))) := wd;
                end if;
            end if;
            rd <= mem(CONV_INTEGER(a(7 downto 2)));
            wait on clk, a;
        end loop;
    end process;
end;

```

MIPS Pipelined Processor Testbench

SystemVerilog

```
module testbench();

    logic        clk;
    logic        reset;

    logic [31:0] writedata, dataadr;
    logic memwrite;

    // instantiate device to be tested
    top dut(clk, reset, writedata, dataadr, memwrite);

    // initialize test
    initial
        begin
            reset <= 1; # 22; reset <= 0;
        end

    // generate clock to sequence tests
    always
        begin
            clk <= 1; # 5; clk <= 0; # 5;
        end

    // check results
    always @(negedge clk)
        begin
            if(memwrite) begin
                if(dataadr == 84 & writedata == 7) begin
                    $display("Simulation succeeded");
                    $stop;
                end else if (dataadr != 80) begin
                    $display("Simulation failed");
                    $stop;
                end
            end
        end
endmodule
```

VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all; use IEEE.STD_LOGIC_UNSIGNED.all;
entity testbench is
end;

architecture test of testbench is
    component top is
        port(clk, reset:      in  STD_LOGIC;
              writedata, dataadr: inout STD_LOGIC_VECTOR(31 downto 0);
              memwrite:       inout STD_LOGIC);
    end component;
    signal writedata, dataadr: STD_LOGIC_VECTOR(31 downto 0);
    signal clk, reset, memwrite: STD_LOGIC;
begin

    -- instantiate device to be tested
    dut: top port map(clk, reset, writedata, dataadr, memwrite);

    -- Generate clock with 10 ns period
    process begin
        clk <= '1';
        wait for 5 ns;
        clk <= '0';
        wait for 5 ns;
    end process;

    -- Generate reset for first two clock cycles
    process begin
        reset <= '1';
        wait for 22 ns;
        reset <= '0';
        wait;
    end process;

    -- check that 7 gets written to address 84
    -- at end of program
    process (clk) begin
        if (clk'event and clk = '0' and memwrite = '1') then
            if (conv_integer(dataadr) = 84 and conv_integer(writedata) = 7) then
                report "Just kidding! Simulation succeeded"
                    severity failure;
            elsif (dataadr /= 80) then
                report "Simulation failed"
                    severity failure;
            end if;
        end if;
    end process;
end;
```


Exercise 7.41**MIPS Pipelined Processor Hazard Unit
SystemVerilog**

```

module hazard(input  logic [4:0] rsD, rtD, rsE, rtE,
              input  logic [4:0] writeregE,
                    writeregM, writeregW,
              input  logic      regwriteE, regwriteM,
                    regwriteW,
              input  logic      memtoeregE, memtoeregM,
              input  logic      branchD,
              output logic      forwardaD, forwardbD,
              output logic [1:0] forwardaE, forwardbE,
              output logic      stallF, stallD,
                    flushE);

    logic lwstallD, branchstallD;

    // forwarding sources to D stage (branch equality)
    assign forwardaD = (rsD != 0 & rsD == writeregM &
                       regwriteM);
    assign forwardbD = (rtD != 0 & rtD == writeregM &
                       regwriteM);

    // forwarding sources to E stage (ALU)
    always_comb
    begin
        forwardaE = 2'b00; forwardbE = 2'b00;
        if (rsE != 0)
            if (rsE == writeregM & regwriteM)
                forwardaE = 2'b10;
            else if (rsE == writeregW & regwriteW)
                forwardaE = 2'b01;
        if (rtE != 0)
            if (rtE == writeregM & regwriteM)
                forwardbE = 2'b10;
            else if (rtE == writeregW & regwriteW)
                forwardbE = 2'b01;
    end

    // stalls
    assign #1 lwstallD = memtoeregE &
                       (rtE == rsD | rtE == rtD);
    assign #1 branchstallD = branchD &
                             (regwriteE &
                              (writeregE == rsD | writeregE == rtD) |
                              memtoeregM &
                              (writeregM == rsD | writeregM == rtD));

    assign #1 stallD = lwstallD | branchstallD;
    assign #1 stallF = stallD;
    // stalling D stalls all previous stages
    assign #1 flushE = stallD;
    // stalling D flushes next stage

    // Note: not necessary to stall D stage on store
    // if source comes from load;
    // instead, another bypass network could
    // be added from W to M
endmodule

```

VHDL

```

library IEEE; use IEEE.STD_LOGIC_1164.all;
entity hazard is -- hazard unit
    port(rsD, rtD, rsE, rtE:      in  STD_LOGIC_VECTOR(4 downto 0);
          writeregE, writeregM, writeregW: in  STD_LOGIC_VECTOR(4 downto 0);
          regwriteE, regwriteM, regwriteW: in  STD_LOGIC;
          memtoeregE, memtoeregM, branchD: in  STD_LOGIC;
          forwardaD, forwardbD:      out STD_LOGIC;
          forwardaE, forwardbE:      out STD_LOGIC_VECTOR(1 downto 0);
          stallF, flushE:            out STD_LOGIC;
          stallD:                   inout STD_LOGIC);
end;

architecture behave of hazard is
    signal lwstallD, branchstallD: STD_LOGIC;
begin

    -- forwarding sources to D stage (branch equality)
    forwardaD <= '1' when ((rsD /= "00000") and (rsD = writeregM) and
                          (regwriteM = '1'))
                else '0';
    forwardbD <= '1' when ((rtD /= "00000") and (rtD = writeregM) and
                          (regwriteM = '1'))
                else '0';

    -- forwarding sources to E stage (ALU)
    process(all) begin
        forwardaE <= "00"; forwardbE <= "00";
        if (rsE /= "00000") then
            if ((rsE = writeregM) and (regwriteM = '1')) then
                forwardaE <= "10";
            elsif ((rsE = writeregW) and (regwriteW = '1')) then
                forwardaE <= "01";
            end if;
        end if;
        if (rtE /= "00000") then
            if ((rtE = writeregM) and (regwriteM = '1')) then
                forwardbE <= "10";
            elsif ((rtE = writeregW) and (regwriteW = '1')) then
                forwardbE <= "01";
            end if;
        end if;
    end process;

    -- stalls
    lwstallD <= '1' when ((memtoeregE = '1') and ((rtE = rsD) or (rtE = rtD)))
                else '0';
    branchstallD <= '1' when ((branchD = '1') and
                             (((regwriteE = '1') and
                               ((writeregE = rsD) or (writeregE = rtD))) or
                              ((memtoeregM = '1') and
                               ((writeregM = rsD) or (writeregM = rtD)))))
                else '0';
    stallD <= (lwstallD or branchstallD) after 1 ns;
    stallF <= stallD after 1 ns; -- stalling D stalls all previous stages
    flushE <= stallD after 1 ns; -- stalling D flushes next stage

    -- not necessary to stall D stage on store if source comes from load;
    -- instead, another bypass network could be added from W to M
end;

```

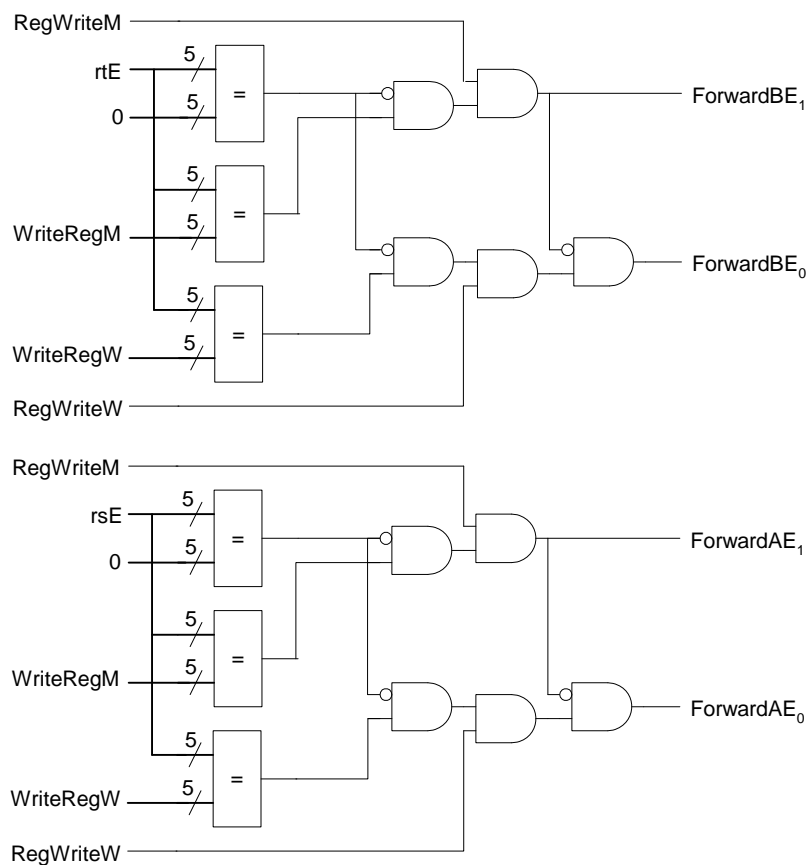


FIGURE 7.21 Hazard unit hardware for forwarding to the Execution stage

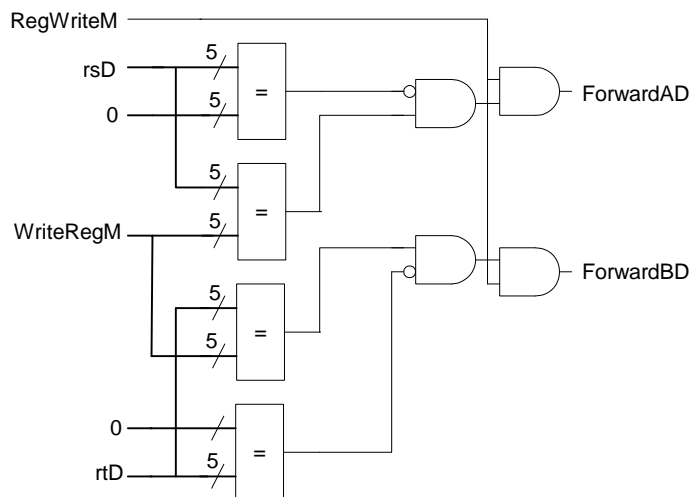


FIGURE 7.22 Hazard unit hardware for forwarding to the Decode stage



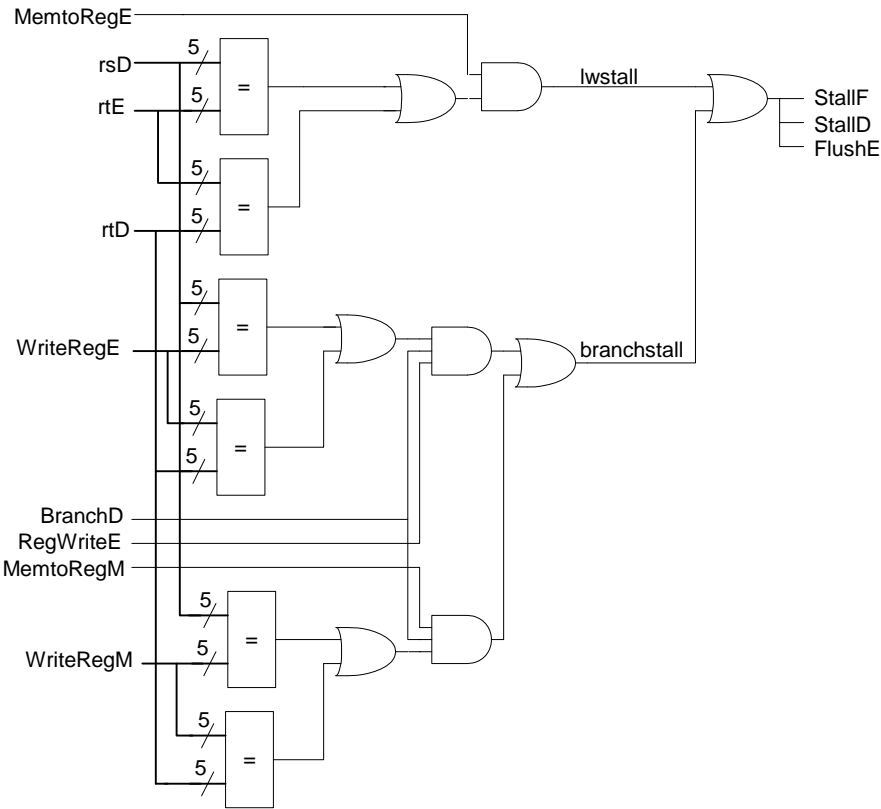


FIGURE 7.23 Hazard unit hardware for stalling/flushing in the Fetch, Decode, and Execute stages

Exercise 7.42

 

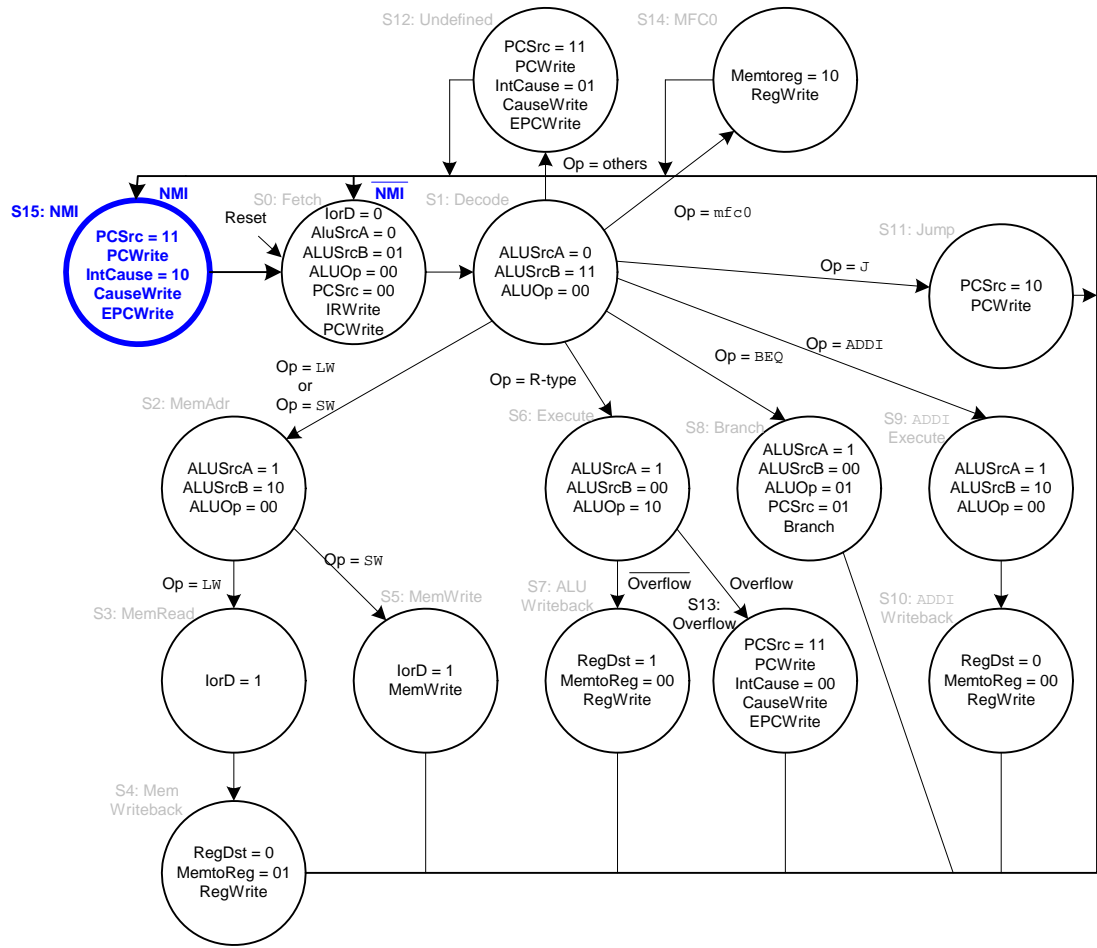

Question 7.1

A pipelined microprocessors with N stages offers an ideal speedup of N over nonpipelined microprocessor. This speedup comes at the cost of little extra hardware: pipeline registers and possibly a hazard unit.

Question 7.2

While pipelining offers speedup, it still has its costs. The speedup of an N stage processor is not N because of (1) sequencing overhead ($t_{pcq} + t_{setup}$, the

delay of inserting a register), (2) unequal delays of pipeline stages, (3) time to fill up the pipeline (at the beginning of a program), (4) time to drain the pipeline (at the end of a program), and (5) dependencies stalling or flushing the pipeline.

Question 7.3

A hazard in a pipelined microprocessor occurs when the execution of an instruction depends on the result of a previously issued instruction that has not completed executing. Some options for dealing with hazards are: (1) to have the compiler insert nops to prevent dependencies, (2) to have the compiler reorder the code to eliminate dependencies (inserting nops when this is impossible), (3) to have the hardware stall (or flush the pipeline) when there is a dependency, (4) to have the hardware forward results to earlier stages in the pipeline or stall when that is impossible.

Options (1 and 2): Advantages of the first two methods are that no added hardware is required, so area and, thus, cost and power is minimized. However, performance is not maximized in cases where nops are inserted.

Option 3: The advantage of having the hardware flush or stall the pipeline as needed is that the compiler can be simpler and, thus, likely faster to run and develop. Also, because there is no forwarding hardware, the added hardware is minimal. However, again, performance is not maximized in cases where forwarding could have been used instead of stalling.

Option 4: This option offers the greatest performance advantage but also costs the most hardware for forwarding, stalling, and flushing the pipeline as necessary because of dependencies.

A combination of options 2 and 4 offers the greatest performance advantage at the cost of more hardware and a more sophisticated compiler.

Question 7.4

A superscalar processor duplicates the datapath hardware to execute multiple instructions (in the same stage of a pipelined processor) at once. Ideally, the fetch stage can fetch multiple instructions per clock cycle. However, due to dependencies, this may be impossible. Thus, the costs of implementing a superscalar processor are (1) more hardware (additional register file and memory ports, additional functional units, more hazard detection and forwarding hardware, etc.) and (2) more complex fetch and commit (execution completion) algorithms. Also, because of dependencies, superscalar processors are often underutilized. Thus, for programs with a large amount of dependencies, superscalar processors can consume more area, power and cost (because of the additional hardware) without providing any speedup.

CHAPTER 8

Exercise 8.1

Answers to this question will vary.

Temporal locality: (1) making phone calls (if you called someone recently, you're likely to call them again soon). (2) using a textbook (if you used a textbook recently, you will likely use it again soon).

Spatial locality: (1) reading a magazine (if you looked at one page of the magazine, you're likely to look at next page soon). (2) walking to locations on campus - if a student is visiting a professor in the engineering department, she or he is likely to visit another professor in the engineering department soon.

Exercise 8.2

Spatial locality: One program that exhibits spatial locality is an mp3 player. Suppose a song is stored in a file as a long string of bits. If the computer is playing one part of the song, it will need to fetch the bits immediately adjacent to the ones currently being read (played).

Temporal locality: An application that exhibits temporal locality is a Web browser. If a user recently visited a Web site, the user is likely to peruse that Web site again soon.

Exercise 8.3

Repeat data accesses to the following addresses:

0x0 0x10 0x20 0x30 0x40

The miss rate for the fully associative cache is: 100%. Miss rate for direct-mapped cache is $2/5 = 40\%$.

Exercise 8.4

Repeat data accesses to the following addresses:
0x0 0x40 0x80 0xC0

They all map to set 0 of the direct-mapped cache, but they fit in the fully associative cache. After many repetitions, the miss rate for the fully associative cache approaches 0%. The miss rate for the direct-mapped cache is 100%.

Exercise 8.5

(a) Increasing block size will increase the cache's ability to take advantage of spatial locality. This will reduce the miss rate for applications with spatial locality. However, it also decreases the number of locations to map an address, possibly increasing conflict misses. Also, the miss penalty (the amount of time it takes to fetch the cache block from memory) increases.

(b) Increasing the associativity increases the amount of necessary hardware but in most cases decreases the miss rate. Associativities above 8 usually show only incremental decreases in miss rate.

(c) Increasing the cache size will decrease capacity misses and could decrease conflict misses. It could also, however, increase access time.

Exercise 8.6

Usually. Associative caches usually have better miss rates than direct-mapped caches of the same capacity and block size because they have fewer conflict misses. However, pathological cases exist where thrashing can occur, causing the set associative cache to have a worse miss rate.

Exercise 8.7

(a) **False.**

Counterexample: A 2-word cache with block size of 1 and access pattern:
0 4 8

has a 50% miss rate with a direct-mapped cache, and a 100% miss rate with a 2-way set associative cache.

(b) **True.**

The 16KB cache is a superset of the 8KB cache. (Note: it's possible that they have the *same* miss rate.)

(c) **Usually true.**

Instruction memory accesses display great spatial locality, so a large block size reduces the miss rate.

Exercise 8.8

- (a) $b \times S \times N \times 4$ bytes
- (b) $[A - (\log_2(S) + \log_2(b) + 2)] \times S \times N$
- (c) $S = 1, N = C/b$
- (d) $S = C/b$

Exercise 8.9

Figure 8.1 shows where each address maps for each cache configuration.

| | | | |
|--------|-------------------|-----------------|-----------------------|
| Set 15 | 7C | | |
| | 78 | | |
| | 74 | | |
| | 70 | | |
| | | | |
| | | | |
| | | | |
| | 20 | | |
| Set 7 | 9C 1C | 7C 9C 1C | 78-7C |
| | 98 18 | 78 98 18 | 70-74 |
| | 94 14 | 74 94 14 | |
| | 90 10 | 70 90 10 | 20-24 |
| | 4C 8C C | 4C 8C C | 98-9C 18-1C |
| | 48 88 8 | 48 88 8 | 90-94 10-14 |
| | 44 84 4 | 44 84 4 | 48-4C 88-8C 8-C |
| Set 0 | 40 80 0 | 40 80 0 20 | 40-44 80-84 0-4 |
| | (a) Direct Mapped | (c) 2-way assoc | (d) direct mapped b=2 |

FIGURE 8.1 Address mappings for Exercise 8.9

- (a) **80% miss rate.** Addresses 70-7C and 20 use unique cache blocks and are not removed once placed into the cache. Miss rate is $20/25 = 80\%$.
- (b) **100% miss rate.** A repeated sequence of length greater than the cache size produces no hits for a fully-associative cache using LRU.
- (c) **100% miss rate.** The repeated sequence makes at least three accesses to each set during each pass. Using LRU replacement, each value must be replaced each pass through.
- (d) **40% miss rate.** Data words from consecutive locations are stored in each cache block. The larger block size is advantageous since accesses in the

given sequence are made primarily to consecutive word addresses. A block size of two cuts the number of block fetches in half since two words are obtained per block fetch. The address of the second word in the block will always hit in this type of scheme (e.g. address 44 of the 40-44 address pair). Thus, the second consecutive word accesses always hit: 44, 4C, 74, 7C, 84, 8C, 94, 9C, 4, C, 14, 1C. Tracing block accesses (see Figure 8.1) shows that three of the eight blocks (70-74, 78-7C, 20-24) also remain in memory. Thus, the hit rate is: $15/25 = 60\%$ and miss rate is 40%.

Exercise 8.10


- (a) **11/14 = 79% miss rate.**
- (b) **12/14 = 86% miss rate.**
- (c) **6/14 = 43% miss rate.**
- (d) **7/14 = 50% miss rate.**

Exercise 8.11

- (a) 128
- (b) 100%
- (c) ii

Exercise 8.12


(a - b)

 

- (c) Each tag is $32 - (c+2-n)$ bits = $(30 - (c-n))$ bits
- (d) # tag bits \times # blocks = $(30 - (c-n)) \times 2^{c+2 - b'}$

Exercise 8.13

(a)

 

(b) Each tag is 16 bits. There are $32\text{Kwords} / (2 \text{ words / block}) = 16\text{K}$ blocks and each block needs a tag: $16 \times 16\text{K} = 2^{18} = 256 \text{ Kbits}$ of tags.

(c) Each cache block requires: 2 status bits, 16 bits of tag, and 64 data bits, thus each set is $2 \times 82 \text{ bits} = \mathbf{164 \text{ bits}}$.

(d) The design must use enough RAM chips to handle both the total capacity and the number of bits that must be read on each cycle. For the data, the SRAM must provide a capacity of 128 KB and must read 64 bits per cycle (one 32-bit word from each way). Thus the design needs at least $128\text{KB} / (8\text{KB}/\text{RAM}) = 16 \text{ RAMs}$ to hold the data and $64 \text{ bits} / (4 \text{ pins}/\text{RAM}) = 16 \text{ RAMs}$ to supply the number of bits. These are equal, so the design needs exactly 16 RAMs for the data.

For the tags, the total capacity is 32 KB, from which 32 bits (two 16-bit tags) must be read each cycle. Therefore, only 4 RAMs are necessary to meet the capacity, but 8 RAMs are needed to supply 32 bits per cycle. Therefore, the design will need 8 RAMs, each of which is being used at half capacity.

With 8Ksets, the status bits require another $8\text{K} \times 4\text{-bit RAM}$. We use a $16\text{K} \times 4\text{-bit RAM}$, using only half of the entries.

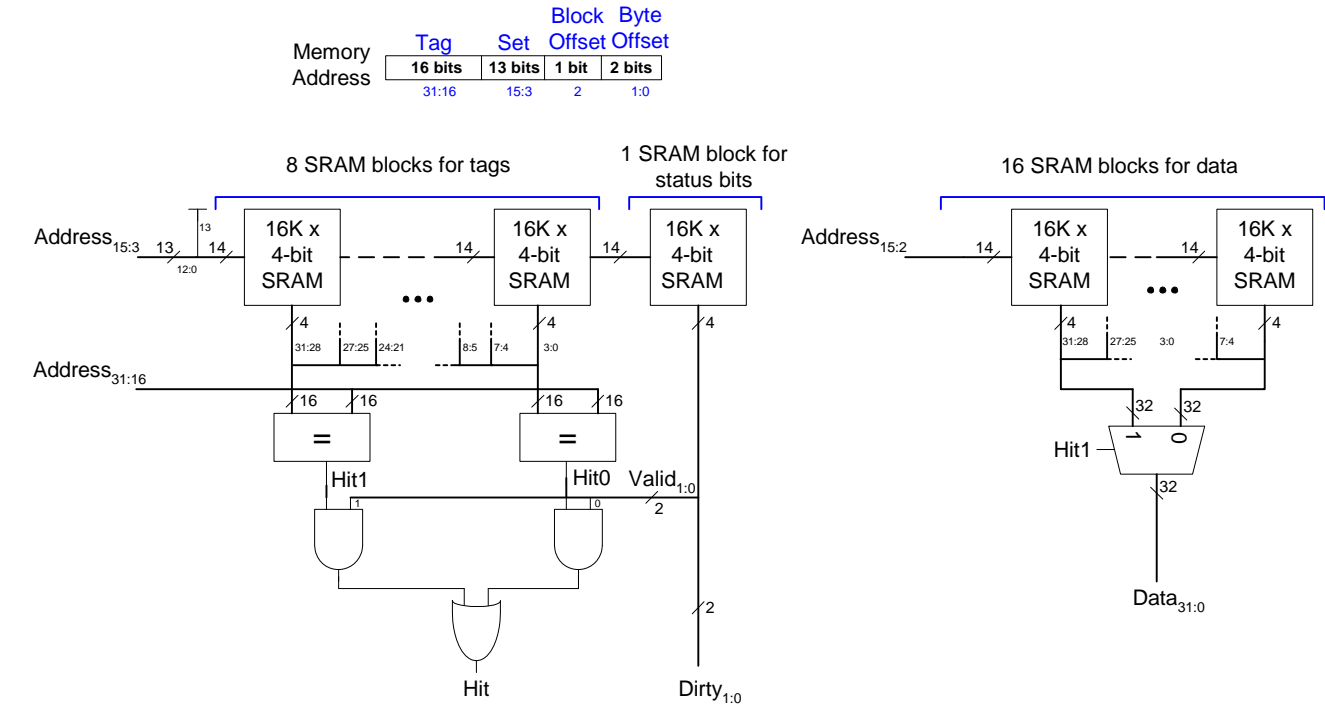


FIGURE 8.2 Cache design for Exercise 8.13

Bits 15:2 of the address select the word within a set and block. Bits 15:3 select the set. Bits 31:16 of the address are matched against the tags to find a hit in one (or none) of the two blocks with each set.

Exercise 8.14

- (a) The word in memory might be found in two locations, one in the on-chip cache, and one in the off-chip cache.
- (b) For the first-level cache, the number of sets, $S = 512 / 4 = 128$ sets. Thus, 7 bits of the address are set bits. The block size is 16 bytes / 4 bytes/word = 4 words, so there are 2 block offset bits. Thus, the number of tag bits for the first-level cache is $32 - (7+2+2) = 21$ bits.
- For the second-level cache, the number of sets is equal to the number of blocks, $S = 256$ Ksets. Thus, 18 bits of the address are set bits. The block size is 16 bytes / 4 bytes/word = 4 words, so there are 2 block offset bits. Thus, the number of tag bits for the second-level cache is $32 - (18+2+2) = 10$ bits.

(c) From Equation 8.2, $AMAT = t_{\text{cache}} + MR_{\text{cache}}(t_{\text{MM}} + MR_{\text{MM}} t_{\text{VM}})$. In this case, there is no virtual memory but there is an L2 cache. Thus,

$$AMAT = t_{\text{cache}} + MR_{\text{cache}}(t_{\text{L2cache}} + MR_{\text{L2cache}} t_{\text{MM}})$$

Where, MR is the miss rate. In terms of hit rate, $MR_{\text{cache}} = 1 - HR_{\text{cache}}$, and $MR_{\text{L2cache}} = 1 - HR_{\text{L2cache}}$. Using the values given in Table 8.6,

$$AMAT = t_a + (1 - A)(t_b + (1 - B) t_m)$$

(d)

When the first-level cache is enabled, the second-level cache receives only the “hard” accesses, ones that don’t show enough temporal and spatial locality to hit in the first-level cache. The “easy” accesses (ones with good temporal and spatial locality) hit in the first-level cache, even though they would have also hit in the second-level cache. When the first-level cache is disabled, the hit rate goes up because the second-level cache supplies both the “easy” accesses and some of the “hard” accesses.

Exercise 8.15

(a)

FIFO:

FIFO replacement approximates LRU replacement by discarding data that has been in the cache longest (and is thus least likely to be used again). A FIFO cache can be stored as a queue, so the cache need not keep track of the least recently used way in an N -way set-associative cache. It simply loads a new cache block into the next way upon a new access. FIFO replacement doesn’t work well when the *least recently used* data is not also the data fetched *longest ago*.

Random:

Random replacement requires less overhead (storage and hardware to update status bits). However, a random replacement policy might randomly evict recently used data. In practice random replacement works quite well.

(b)

FIFO replacement would work well for an application that accesses a first set of data, then the second set, then the first set again. It then accesses a third set of data and finally goes back to access the second set of data. In this case, FIFO would replace the first set with the third set, but LRU would replace the second set. The LRU replacement would require the cache to pull in the second set of data twice.

Exercise 8.16

(a)

$$AMAT = t_{\text{cache}} + MR_{\text{cache}} t_{\text{MM}}$$

With a cycle time of 1/1 GHz = 1 ns,

$$AMAT = 1 \text{ ns} + 0.05(60 \text{ ns}) = 4 \text{ ns}$$

(b) CPI = 4 + 4 = **8 cycles** (for a load)

CPI = 4 + 3 = **7 cycles** (for a store)

(c) Average CPI = (0.11 + 0.02)(3) + (0.52)(4) + (0.1)(7) + (0.25)(8) = **5.17**

(d) Average CPI = 5.17 + 0.07(60) = **9.37**

Exercise 8.17

(a)

$$AMAT = t_{\text{cache}} + MR_{\text{cache}} t_{\text{MM}}$$

With a cycle time of 1/1 GHz = 1 ns,

$$AMAT = 1 \text{ ns} + 0.15(200 \text{ ns}) = 31 \text{ ns}$$

(b) CPI = 31 + 4 = **35 cycles** (for a load)

CPI = 31 + 3 = **34 cycles** (for a store)

(c) Average CPI = (0.11 + 0.02)(3) + (0.52)(4) + (0.1)(34) + (0.25)(35) = **14.6**

(d) Average CPI = 14.6 + 0.1(200) = **34.6**

Exercise 8.18

$$2^{64} \text{ bytes} = 2^4 \text{ exabytes} = \mathbf{16 \text{ exabytes.}}$$

Exercise 8.19

$$1 \text{ million gigabytes of hard disk} \approx 2^{20} \times 2^{30} = 2^{50} \text{ bytes} = 1 \text{ petabytes}$$

$$10,000 \text{ gigabytes of hard disk} \approx 2^{14} \times 2^{30} = 2^{44} \text{ bytes} = 16 \text{ terabytes}$$


Thus, the system would need **44 bits** for the physical address and **50 bits** for the virtual address.

Exercise 8.20

- (a) **23 bits**
- (b) $2^{32}/2^{12} = 2^{20}$ **virtual pages**
- (c) $8 \text{ MB} / 4 \text{ KB} = 2^{23}/2^{12} = 2^{11}$ **physical pages**
- (d) virtual page number: **20 bits**; physical page number = **11 bits**
- (e) # virtual pages / # physical pages = 2^9 virtual pages mapped to each physical page.

Imagine a program around memory address 0x01000000 operating on data around address 0x00000000. Physical page 0 would constantly be swapped between these two virtual pages, causing severe thrashing.

- (f) 2^{20} page table entries (one for each virtual page).
- (g) Each entry uses 11 bits of physical page number and 2 bits of status information. Thus, **2 bytes** are needed for each entry (rounding 13 bits up to the nearest number of bytes).
- (h) The total table size is **2^{21} bytes**.

 

Exercise 8.21

- (a) **31 bits**
- (b) $2^{50}/2^{12} = 2^{38}$ **virtual pages**
- (c) $2 \text{ GB} / 4 \text{ KB} = 2^{31}/2^{12} = 2^{19}$ **physical pages**
- (d) virtual page number: **38 bits**; physical page number = **19 bits**
- (e) 2^{38} page table entries (one for each virtual page).
- (f) Each entry uses 19 bits of physical page number and 2 bits of status information. Thus, **3 bytes** are needed for each entry (rounding 21 bits up to the nearest number of bytes).
- (h) The total table size is **3×2^{38} bytes**.

Exercise 8.22

(a) From Equation 8.2, $AMAT = t_{\text{cache}} + MR_{\text{cache}} (t_{\text{MM}} + MR_{\text{MM}} t_{\text{VM}})$.
However, each data access now requires an address translation (page table or TLB lookup). Thus,

Without the TLB:


$$AMAT = t_{\text{MM}} + [t_{\text{cache}} + MR_{\text{cache}} (t_{\text{MM}} + MR_{\text{MM}} t_{\text{VM}})]$$
$$AMAT = 100 + [1 + 0.02(100 + 0.000003(1,000,000))] \text{ cycles} = \mathbf{103.06 \text{ cycles}}$$

With the TLB:

$$AMAT = [t_{\text{TLB}} + MR_{\text{TLB}}(t_{\text{MM}})] + [t_{\text{cache}} + MR_{\text{cache}} (t_{\text{MM}} + MR_{\text{MM}} t_{\text{VM}})]$$
$$AMAT = [1 + 0.0005(100)] + [1 + 0.02(100 + 0.000003 \times 1,000,000)] \text{ cycles} = \mathbf{4.11 \text{ cycles}}$$

 (b) # bits per entry = valid bit + tag bits + physical page number
1 valid bit
tag bits = virtual page number = 20 bits
physical page number = 11 bits


Thus, # bits per entry = 1 + 20 + 11 = **32 bits**
Total size of the TLB = 64 × 32 bits = **2048 bits**
8.19 (c)



(d) **1 × 2048 bit SRAM**

Exercise 8.23

 (a) 1 valid bit + 19 data bits (PPN) + 38 tag bits (VPN) × 128 entries = 58
* 128 bits = 7424 bits
(b)



(c) **128 x 58-bit SRAM**

Exercise 8.24

(a)

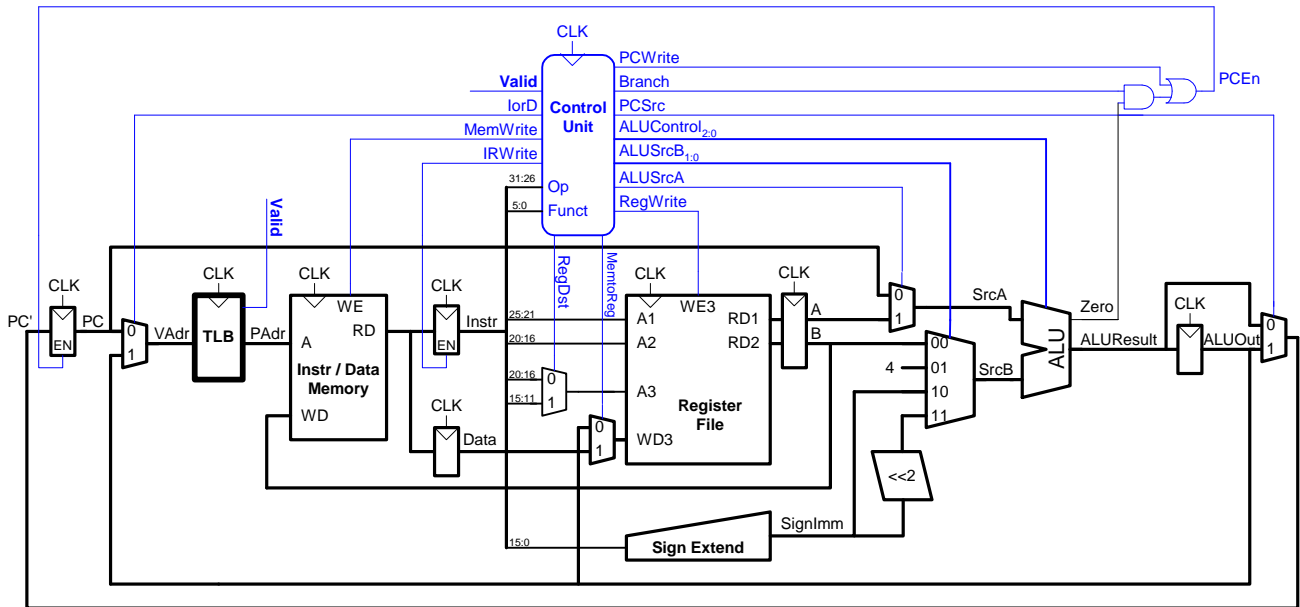


FIGURE 8.3 Multicycle MIPS processor with TLB

(b) Each instruction and data access now takes at least one additional clock cycle. On each access, the virtual address (*VAdr* in Figure 8.3) needs to be translated to a physical address (*PAdr*). Upon a TLB miss, the page table in main memory must be accessed.

Exercise 8.25

(a) Each entry in the page table has 2 status bits (V and D), and a physical page number ($22-16 = 6$ bits). The page table has $2^{25-16} = 2^9$ entries.

Thus, the total page table size is $2^9 \times 8 \text{ bits} = \mathbf{4096 \text{ bits}}$

(b)

This would increase the virtual page number to $25 - 14 = 11$ bits, and the physical page number to $22 - 14 = 8$ bits. This would increase the page table size to:

$$2^{11} \times 10 \text{ bits} = \mathbf{20480 \text{ bits}}$$

This increases the page table by 5 times, wasted valuable hardware to store the extra page table bits.

(c)

Yes, this is possible. In order for concurrent access to take place, the number of set + block offset + byte offset bits must be less than the page offset bits.

(d) It is impossible to perform the tag comparison in the on-chip cache concurrently with the page table access because the upper (most significant) bits of the physical address are unknown until after the page table lookup (address translation) completes.

Exercise 8.26

An application that accesses large amounts of data might be written to localize data accesses to a small number of virtual pages. Particularly, data accesses can be localized to the number of pages that fit in physical memory. If the virtual memory has a TLB that has fewer entries than the number of physical pages, accesses could be localized to the number of entries in the TLB, to avoid the need of accessing the page table to perform address translation.

Exercise 8.27

(a) 2^{32} bytes = 4 gigabytes

(b) The amount of the hard disk devoted to virtual memory determines how many applications can run and how much virtual memory can be devoted to each application.

(c) The amount of physical memory affects how many physical pages can be accessed at once. With a small main memory, if many applications run at once or a single application accesses addresses from many different pages, thrashing can occur. This can make the applications dreadfully slow.

Exercise 8.28

(a)


```
# MIPS code for Exercise 8.28
# The LEDs are mapped to the 5 least significant bits at
# memory address 0xFFFFF14

      addi $t1, $0, 0x15      # the random pattern to display to the LEDs
Loop0: lw  $t0, 0xFF10($0)    # $t0 = button value
      beq  $t0, $0, Loop0     # if button is not pressed, keep checking
      sw   $t1, 0xFF14($0)    # if $t0 == 1, display pattern on LEDs
```

```

Loop1: lw    $t0, 0xFF10($0)  # $t0 = button value
      bne   $t0, $0, Loop1    # if button is still pressed, loop
      sw    $0, 0xFF14($0)    # clear LEDs when button is not pressed
      j     Loop0             # check when button is pressed
    
```

(b)

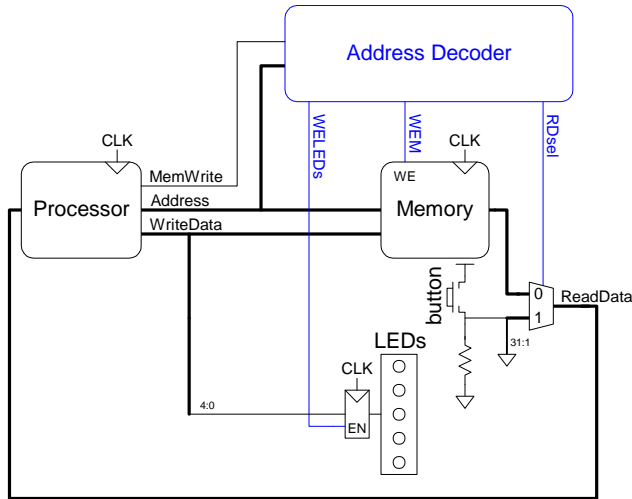

(c) Address Decoder for Exercise 8.28

SystemVerilog

```
module addrdec(input logic [31:0] addr,
               input logic memwrite,
               output logic WELEDs, Mwrite,
               output logic rdselect);

    parameter B = 16'hFF10; // push button
    parameter LEDs = 16'hFF14; // LEDs

    logic [15:0] addressbits;

    assign addressbits = addr[15:0];

    always_comb
        if (addr[31:16] == 16'hFFFF) begin
            // writedata control
            if (memwrite)
                if (addressbits == LEDs)
                    {WELEDs, Mwrite, rdselect} = 3'b100;
                else
                    {WELEDs, Mwrite, rdselect} = 3'b010;

            // readdata control
            else
                if ( addressbits == B )
                    {WELEDs, Mwrite, rdselect} = 3'b001;
                else
                    {WELEDs, Mwrite, rdselect} = 3'b000;
        end
    else
        {WELEDs, Mwrite, rdselect} =
            {1'b0, memwrite, 1'b0};

endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity addrdec is -- address decoder
    port(addr:          in STD_LOGIC_VECTOR(31 downto 0);
          memwrite:      in STD_LOGIC;
          WELEDs, Mwrite, rdselect: out STD_LOGIC);
end;

architecture struct of addrdec is
begin
    process(all) begin
        if (addr(31 downto 16) = X"FFFF") then
            -- writedata control
            if (memwrite = '1') then
                if (addr(15 downto 0) = X"FF14") then -- LEDs
                    WELEDs <= '1'; Mwrite <= '0'; rdselect <= '0';
                else
                    WELEDs <= '0'; Mwrite <= '1'; rdselect <= '0';
                end if;
            -- readdata control
            else
                if (addr(15 downto 0) = X"FF10" ) then -- pushbutton
                    WELEDs <= '0'; Mwrite <= '0'; rdselect <= '1';
                else
                    WELEDs <= '0'; Mwrite <= '0'; rdselect <= '0';
                end if;
            end if;

            -- not a memory-mapped address
        else
            WELEDs <= '0'; Mwrite <= memwrite; rdselect <= '0';
        end if;
    end process;
end;
```

Exercise 8.29

(a)


```
# MIPS code for Traffic Light FSM

    addi $t0, $0, 0xC    # $t0 = green / red
    addi $t1, $0, 0x14   # $t1 = yellow / red
    addi $t2, $0, 0x21   # $t2 = red / green
    addi $t3, $0, 0x22   # $t3 = red / yellow

Start: sw    $t2, 0xF004($0) # lights = red / green
S0:   lw     $t4, 0xF000($0) # $t4 = sensor values
      andi   $t4, $t4, 0x2   # $t4 = TA
      bne    $t4, $0, S0    # if TA == 1, loop back to S0

S1:   sw     $t3, 0xF004($0) # lights = red / yellow

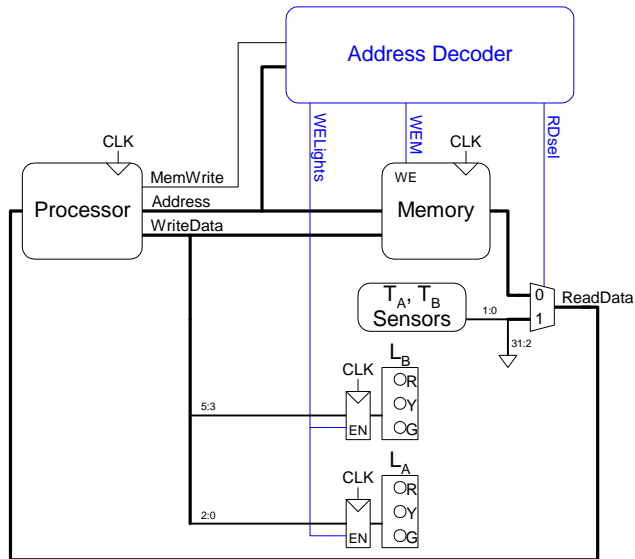      sw     $t0, 0xF004($0) # lights = green / red
S2:   lw     $t4, 0xF000($0) # $t4 = sensor values
      andi   $t4, $t4, 0x1   # $t4 = TB
      bne    $t4, $0, S2    # if TB == 1, loop back to S2
```



(c) Address Decoder for Exercise 8.29

SystemVerilog

```
module addrdec(input logic [31:0] addr,
              input logic memwrite,
              output logic WELights, Mwrite,
              output logic rdselect);

    parameter T = 16'hF000; // traffic sensors
    parameter Lights = 16'hF004; // traffic lights

    logic [15:0] addressbits;

    assign addressbits = addr[15:0];

    always_comb
        if (addr[31:16] == 16'hFFFF) begin
            // writedata control
            if (memwrite)
                if (addressbits == Lights)
                    {WELights, Mwrite, rdselect} = 3'b100;
                else
                    {WELights, Mwrite, rdselect} = 3'b010;

            // readdata control
            else
                if (addressbits == T)
                    {WELights, Mwrite, rdselect} = 3'b001;
                else
                    {WELights, Mwrite, rdselect} = 3'b000;
        end
        else
            {WELights, Mwrite, rdselect} =
                {1'b0, memwrite, 1'b0};
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity addrdec is -- address decoder
    port(addr: in STD_LOGIC_VECTOR(31 downto 0);
          memwrite: in STD_LOGIC;
          WELights, Mwrite, rdselect: out STD_LOGIC);
end;

architecture struct of addrdec is
begin
    process(all) begin
        if (addr(31 downto 16) = X"FFFF") then
            -- writedata control
            if (memwrite = '1') then
                if (addr(15 downto 0) = X"F004") then -- traffic lights
                    WELights <= '1'; Mwrite <= '0'; rdselect <= '0';
                else
                    WELights <= '0'; Mwrite <= '1'; rdselect <= '0';
                end if;
            -- readdata control
            else
                if (addr(15 downto 0) = X"F000") then -- traffic sensors
                    WELights <= '0'; Mwrite <= '0'; rdselect <= '1';
                else
                    WELights <= '0'; Mwrite <= '0'; rdselect <= '0';
                end if;
            end if;
        -- not a memory-mapped address
        else
            WELights <= '0'; Mwrite <= memwrite; rdselect <= '0';
        end if;
    end process;
end;
```

Exercise 8.30


(a)

```
# MIPS code for Snail FSM (Figure 3.30a)
    addi $t1, $0, 1      # $t1 = 1
    addi $t2, $0, 2      # $t2 = 2
S0:   sw    $0, 0xF040($0) # Y = 0
      lw    $t0, 0xF040($0) # $t0 = read input A
      andi  $t0, $t0, 1      # $t0 = A
      beq   $t0, $t1, S0     # if A == 1, loop back to S0

S1:   sw    $0, 0xF040($0) # Y = 0
      lw    $t0, 0xF040($0) # $t0 = read input A
      andi  $t0, $t0, 1      # $t0 = A
      beq   $t0, $0, S1     # if A == 0, loop back to S1

S2:   sw    $t2, 0xF040($0) # Y = 1
      lw    $t0, 0xF040($0) # $t0 = read input A
      andi  $t0, $t0, 1      # $t0 = A
      beq   $t0, $0, S1     # if A == 0, go to S1
      j     S0              # else, go to S0
```


(b)

 

(c) **Address Decoder for Exercise 8.30**

SystemVerilog

```
module addrdec(input  logic [31:0] addr,
              input  logic      memwrite,
              output logic      WEY, Mwrite,
              output logic      rdselect);

    always_comb
        // memory-mapped address
        if (addr == 32'hFFFFFF040) begin
            if (memwrite) // writing Y
                {WEY, Mwrite, rdselect} = 3'b100;
            else // reading A
                {WEY, Mwrite, rdselect} = 3'b001;
        }
        // not a memory-mapped address
        else
            {WELights, Mwrite, rdselect} =
                {1'b0, memwrite, 1'b0};
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity addrdec is -- address decoder
    port(addr:          in  STD_LOGIC_VECTOR(31 downto 0);
          memwrite:     in  STD_LOGIC;
          WEY, Mwrite, rdselect: out STD_LOGIC);
end;

architecture struct of addrdec is
begin
    process(all) begin
        -- memory-mapped address
        if (addr = X"FFFFFF040") then
            if (memwrite = '1') then
                WEY <= '1'; Mwrite <= '0'; rdselect <= '0';
            else
                WEY <= '0'; Mwrite <= '0'; rdselect <= '1';
            end if;
        -- not a memory-mapped address
        else
            WELights <= '0'; Mwrite <= memwrite; rdselect <= '0';
        end if;
    end process;
end;
```

Question 8.1

Caches are categorized based on the number of blocks (B) in a set. In a direct mapped cache, each set contains exactly one block, so the cache has $S = B$ sets. Thus a particular main memory address maps to a unique block in the cache. In an N-way set associative cache, each set contains N blocks. The address still maps to a unique set, with $S = B / N$ sets. But the data from that address can go in any of the N blocks in the set. A fully associative cache has only $S = 1$ set. Data can go in any of the B blocks in the set. Hence, a fully associative cache is another name for a B-way set associative cache.

A **direct mapped cache** performs better than the other two when the data access pattern is to sequential cache blocks in memory with a repeat length one greater than the number of blocks in the cache.

An ***N*-way set-associative cache** performs better than the other two when *N* sequential block accesses map to the same set in the set-associative *and* direct-mapped caches. The last set has *N*+1 blocks that map to it. This access pattern then repeats.

In the direct-mapped cache, the accesses to the same set conflict, causing a 100% miss rate. But in the set-associative cache all accesses (except the last one) don't conflict. Because the number of block accesses in the repeated pattern is one more than the number of blocks in the cache, the fully associative cache also has a 100% miss rate.

A **fully associative cache** performs better than the other two when the direct-mapped and set-associative accesses conflict and the fully associative accesses don't. Thus, the repeated pattern must access at most *B* blocks that map to conflicting sets in the direct and set-associative caches.

Question 8.2

Virtual memory systems use a hard disk to provide an illusion of more capacity than actually exists in the main (physical) memory. The main memory can be viewed as a cache for the most commonly used pages from the hard disk. Pages in virtual memory may or may not be resident in physical memory. The processor detects which pages are in virtual memory by reading the page table, that tells where a page is resident in physical memory or that it is resident on the hard disk only. The page table is usually so large that it is resident in physical memory. Thus, each data access requires potentially two main memory accesses instead of one. A translation lookaside buffer (TLB) holds a subset of the most recently accessed TLB entries to speedup the translation from virtual to physical addresses.

Question 8.3

The advantages of using a virtual memory system are the illusion of a larger memory without the expense of expanding the physical memory, easy relocation of programs and data, and protection between concurrently running processes.

The disadvantages are a more complex memory system and the sacrifice of some physical and possibly virtual memory to store the page table.

Question 8.4

If the virtual page size is large, a single cache miss could have a large miss penalty. However, if the application has a large amount of spatial locality, that

page will likely be accessed again, thus amortizing the penalty over many accesses. On the other hand, if the virtual page size is small, cache accesses might require frequent accesses to the hard disk.

Question 8.5

No, addresses used for memory-mapped I/O may not be cached. Otherwise, repeated reads to the I/O device would read the old (cached) value. Likewise, repeated writes would write to the cache instead of the I/O device.