 


Lecture 2: Continuation of SystemVerilog

Adder Examples

```
module fulladder(input logic a, b, cin,  
                 output logic s, cout);  
    logic p, g;    // internal nodes  
  
    assign p = a ^ b;  
    assign g = a & b;  
  
    assign s = p ^ cin;  
    assign cout = g | (p & cin);  
endmodule
```




Adder Examples

```
/* hierarchical 4-bit adder */
module h4ba(input logic [3:0] A, B,
           input logic carry_in,
           output logic [3:0] sum,
           output logic carry_out);

    logic carry_out_0, carry_out_1, carry_out_2; // internal signals

    fulladder fa0 (A[0], B[0], carry_in, sum[0], carry_out_0);
    fulladder fa1 (A[1], B[1], carry_out_0, sum[1], carry_out_1);
    fulladder fa2 (A[2], B[2], carry_out_1, sum[2], carry_out_2);
    fulladder fa3 (A[3], B[3], carry_out_2, sum[3], carry_out);

endmodule
```

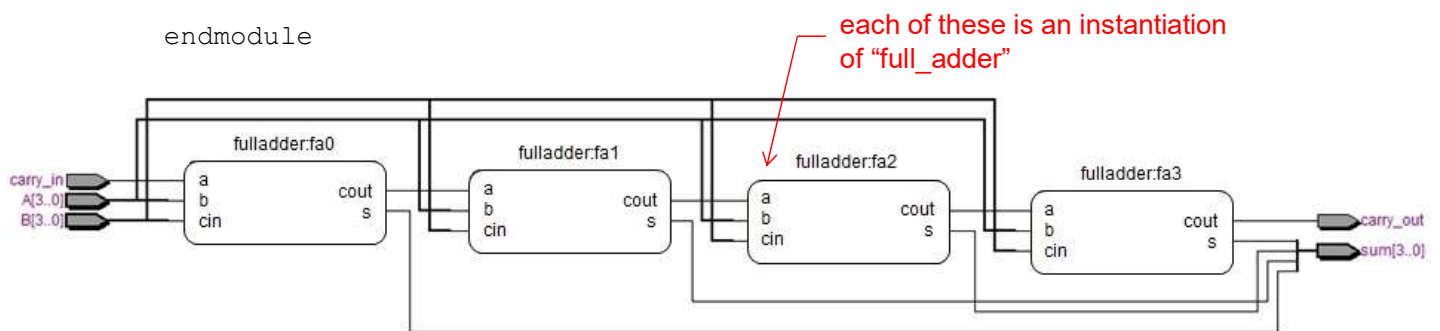


3

Adder Examples

```
module add4(input logic [3:0] A, B,
            output logic [3:0] sum);
    assign sum = A + B;
endmodule
```

 Verilog compilers will replace arithmetic operators with default logic implementations (e.g. ripple carry adder)



4

Numbers

Format: N'Bvalue

N = number of bits, **B** = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	unsized	decimal	42	00...0101010

Slide derived from slides by Harris & Harris from their book

5

Bit Manipulations: Example 1

```
assign y = {a[2:1], {3{b[0]}}}, a[0], 6'b100_010};
```

```
// if y is a 12-bit signal, the above statement produces:
```

```
// y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0
```

```
// underscores (_) are used for formatting only to make
```

```
// it easier to read. SystemVerilog ignores them.
```


Slide derived from slides by Harris & Harris from their book

6

Bit Manipulations: Example 2

```
module mux2_8(input  logic [7:0] d0, d1,
              input  logic      s,
              output logic [7:0] y);

     mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule
```



Slide derived from slides by Harris & Harris from their book

7

More Examples

```
module ex1(input logic [3:0] X, Y, Z,
           input logic a, cin,
           output logic [3:0] R1, R2, R3, Q1, Q2,
           output logic [7:0] P1, P2,
           output logic t, cout);
```

assign R1 = X | (Y & ~Z); ← use of bitwise Boolean operators

assign t = &X; ← example reduction operator

assign R2 = (a == 1'b0) ? X : Y; ← conditional operator

assign P1 = 8'hff; ← example constants

assign P2 = {4{a}, X[3:2], Y[1:0]}; ← replication, same as {a, a, a, a}

← example concatenation

assign {cout, R3} = X + Y + cin;

assign Q1 = X << 2; ← bit shift operator

assign Q2 = {X[1], X[0], 1'b0, 1'b0}; ← equivalent bit shift
endmodule

8

Combinational logic using always

```
module ex2(input logic a, b, c,  
           output logic f);
```

```
    logic t; // internal signal
```

```
    always_comb
```

```
    begin
```

```
        t = a & b;
```


```
        f = t | c;
```

```
    end
```

should use "=" (called "**blocking**" assignment) in comb. logic always statements. RHS just takes output from the previous equation.

The order of statements matters!

```
endmodule
```

 

9

Combinational logic using always

```
module ex3(input logic [3:0] d0, d1,  
           input logic s,  
           output logic [3:0] y);
```

```
    always_comb
```

```
    begin
```

```
        if (s)
```

```
            y = d1;
```


```
        else
```

```
            y = d0;
```

```
    end
```

```
endmodule
```

 If-then-else translates into a 2:1 multiplexor



Combinational logic using always

```
/* behavioral description of a 4-bit adder */
```

```
module p4ba(input logic [3:0] A, B,
           input logic carry_in,
           output logic [3:0] sum,
           output logic carry_out);
```

```
    logic [4:0] carry; // internal signal
```

```
    always_comb
```

```
    begin
```

```
        carry[0] = carry_in;
```

```
        for (int i = 0; i < 4; i++) begin
```

```
            sum[i] = A[i] ^ B[i] ^ carry[i];
```

```
            carry[i+1] = A[i] & B[i] |
                        A[i] & carry[i] |
                        B[i] & carry[i];
```

```
        end
```

```
        carry_out = carry[4];
```

```
    end
```

```
endmodule
```

entire **"always_comb"** block is called an **"always statement"** for combianational logic


for loops must have a specified range. simply interpreted as **"replication"**.

Note we can declare the loop control variable within the for loop

Verilog calls the use of **"="** inside an always statement as a **"blocking"** assignment. all it means is that the Verilog will **"parse"** the lines of code inside the always block in **"sequential"** order in the generation of logic. (will make more sense later when we discuss **"non-blocking"** assignments.)

11

Combinational logic using always

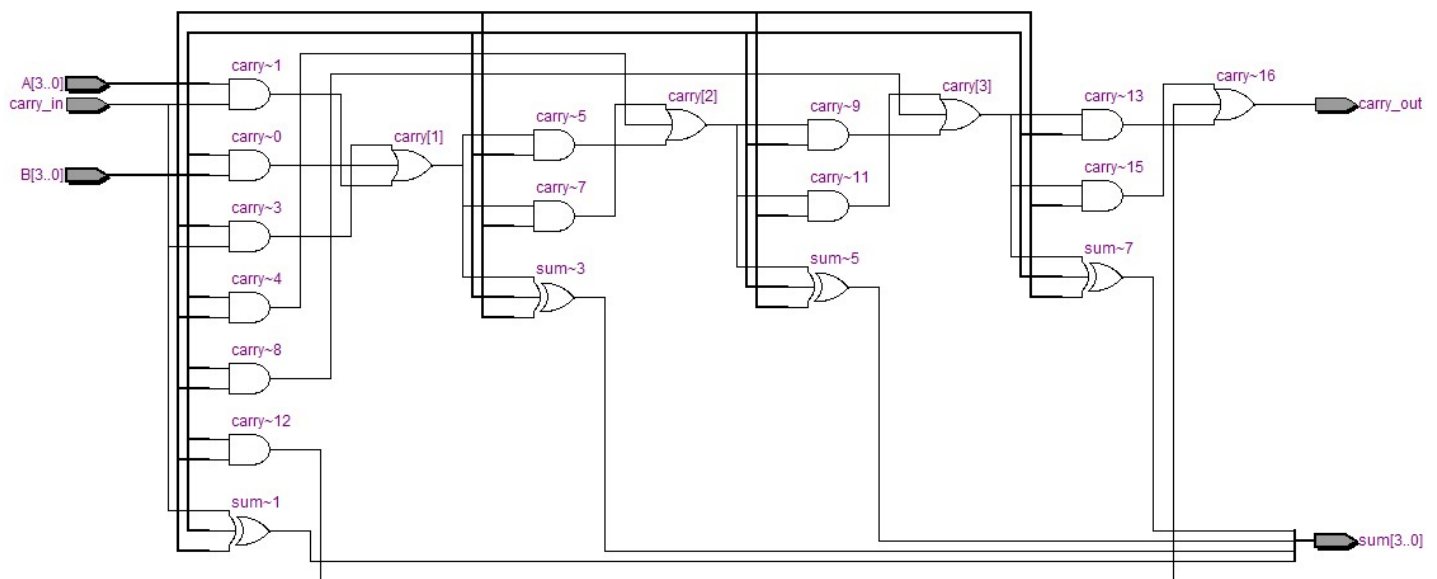

12

Combinational logic using case

```
module sevenseg(input  logic [3:0] data,
                output logic [6:0] segments);

  always_comb
  case (data)
    //                                abc_defg
    0: segments = 7'b111_1110;
    1: segments = 7'b011_0000;
    2: segments = 7'b110_1101;
    3: segments = 7'b111_1001;
    4: segments = 7'b011_0011;
    5: segments = 7'b101_1011;
    6: segments = 7'b101_1111;
    7: segments = 7'b111_0000;
    8: segments = 7'b111_1111;
    9: segments = 7'b111_0011;
    default: segments = 7'b000_0000; // required
  endcase
endmodule
```

case statement
translates into a more
complex “multiplexor”
similar to if-then-else

Slide derived from slides by Harris & Harris from their book

13

Combinational logic using case

- **case** statement implies combinational logic **only if** all possible input combinations described
- Remember to use **default** statement
- Otherwise, compiler will create an “asynchronous latch” to remember previous value: **bad** because this is not intended!


Slide derived from slides by Harris & Harris from their book

14

Combinational logic using casez

```
module priority_casez(input  logic [3:0] a,
                     output logic [3:0] y);

   always_comb
    casez(a)
      4'b1???: y = 4'b1000; // ? = don't care
      4'b01??: y = 4'b0100;
      4'b001?: y = 4'b0010;
      4'b0001: y = 4'b0001;
      default: y = 4'b0000;
    endcase
endmodule
```



Slide derived from slides by Harris & Harris from their book

15

Nesting

- In general, for loop, if-then-else, and case statements can be “nested”. e.g.,

```
for (...)
  if (...)
    case (...)
      ...
    endcase
  else
    ...
```

- Compiler will compile from the “inner-most” scope outwards: i.e., it will first produce multiplexor logic for “case” statement, then produce multiplexor logic for the “if-then-else” part, then replicate all that logic based on the number of iterations in the “for loop”.

16

Functions

```
/* adder subtractor */
module add_sub(input logic op,
               input logic [3:0] A, B,
               input logic carry_in,
               output logic [3:0] sum,
               output logic carry_out);
    function logic [4:0] adder(input logic [3:0] x, y,
                              input logic cin);
        logic [3:0] s; // internal signals
        logic c;

        c = cin;
        for (int i = 0; i < 4; i++) begin
            s[i] = x[i] ^ y[i] ^ c;
            c = (x[i] & y[i]) | (c & x[i]) | (c & y[i]);
        end
        adder = {c, s};
    endfunction

    always_comb
        if (op) // subtraction
            {carry_out, sum} = adder(A, ~B, 1);
        else
            {carry_out, sum} = adder(A, B, 0);
endmodule
```

function is like a comb. always statement, but can be called (instantiated) later.