 


Lecture 4: Continuation of SystemVerilog

Last Lecture: Divide by 3 FSM


- Output should be “1” every 3 clock cycles



The double circle indicates the reset state

Finite State Machines (FSMs)

 - A simple Moore machine looks like the following



Slide derived from slides by Harris & Harris from their book

3

FSM Example in SystemVerilog

```
module divideby3FSM (input logic clk, reset_n,
                    output logic q);

    enum logic [1:0] {S0=2'b00, S1=2'b01, S2=2'b10} state; // declare states as enum

    // next state logic and state register
    always_ff @(posedge clk, negedge reset_n)
    begin
        if (!reset_n)
            state <= S0;
        else begin
            case (state)
                S0: state <= S1;
                S1: state <= S2;
                S2: state <= S0;
            endcase
        end
    end

    // output logic
    assign q = (state == S0);
endmodule
```

state transition graph is the same thing as a state transition table, which can be specify as a case statement

← output is "1" every clock cycles when we are in state S0

4

FSM Example in SystemVerilog

```
module divideby3FSM (input logic clk, reset_n,  
                    output logic q);
```


```
    enum logic [1:0] {S0=2'b00, S1=2'b01, S2=2'b10} state; // declare states as enum
```

```
    // next state logic and state register  
    always_ff @(posedge clk, negedge reset_n)  
    begin  
        if (!reset_n)  
            state <= S0;  
        else begin  
            case (state)  
                S0: state <= S1;  
                S1: state <= S2;  
                S2: state <= S0;  
            endcase  
        end  
    end
```

```
    // output logic  
    assign q = (state == S0);  
endmodule
```

compiler recognizes this “template” should use positive edge-triggered flip-flops w/ negative edge asynchronous reset should be used.

 
compiler knows this “if” part defines the reset values for flip-flops.



5

What asynchronous reset means

 - “Negative-edge asynchronous reset” means the following:



6

Continuing with the FSM Example

- What if we want to design the “Divide by 3 FSM” example with just one “always_ff” statement (no separate “assign” statement)?
- Let’s assume we still want “q” to be “1” when we are in state “S0”.
- Can we put the logic for “q” instead the “always_ff” statement?
- Yes, but a flip-flop will be created for “q”!

7

FSM Example in SystemVerilog

```
module fsm2 (input logic clk, reset_n, output logic q);
    enum logic [1:0] {S0=2'b00, S1=2'b01, S2=2'b10} state; // declare states as enum

    always_ff @(posedge clk, negedge reset_n)
    begin
        if (!reset_n) begin
            state <= S0;
            q <= 1;
        end else begin
            case (state)
                S0: begin
                    state <= S1;
                    q <= 0;
                end
                S1: begin
                    state <= S2;
                    q <= 0;
                end
                S2: begin
                    state <= S0;
                    q <= 1;
                end
            endcase
        end
    end
endmodule
```

} synthesis will generate D-FFs for both “state” and “q”

} in order to have the output “q” = 1 when “state” is in S0, have to set the D-FF for “q” in S2 so that the output “q” = 1 when “state” gets to S0.


8

FSM Example in SystemVerilog

```
module fsm2 (input logic clk, reset_n, output logic q);
    enum logic [1:0] {S0=2'b00, S1=2'b01, S2=2'b10} state; // declare states as enum
```

```
always_ff @(posedge clk, negedge reset_n)
begin
    if (!reset_n) begin
        state <= S0;
        q <= 1;
    end else begin
        case (state)
            S0: begin
                state <= S1;
                q <= 0;
            end
            S1: begin
                state <= S2;
                q <= 0;
            end
            S2: begin
                state <= S0;
                q <= 1;
            end
        endcase
    end
end
```

 compiler knows this “if” part defines the reset values for flip-flops.



```
endmodule
```

9

RTL Example

```
module rtl_example (input logic clk, reset_n,
    input logic [7:0] a, b,
    output logic [7:0] f, count);

    // default encoding: s0=2'b00, s1=2'b01, s2=2'b10
    enum logic [1:0] {s0, s1, s2} state;
    logic [7:0] c, t;


    function logic [7:0] myinc(input logic [7:0] x);
        logic [7:0] sum;
        logic c; // this is an internal c
        begin
            c = 1;
            for (int i = 0; i < 8; i++) begin
                sum[i] = x[i] ^ c;
                c = c & x[i];
            end
            myinc = sum;
        end
    endfunction

    always_comb
    begin
        t = c << 1;
        f = t + 1;
    end
```

```
always_ff@(posedge clk, negedge reset_n)
if (!reset_n) begin
    count <= 0;
    c <= 0; // this c is different than function
    state <= s0;
end else begin
    case (state)
        s0: begin
            count <= 0;
            c <= 0;
            state <= s1;
        end
        s1: begin
            count <= count + 1;
            c <= a + b;
            state <= s2;
        end
        s2: begin
            count <= myinc(count);
            c <= a - b;
            state <= s0;
        end
    endcase
end
```

```
endmodule
```

RTL Example

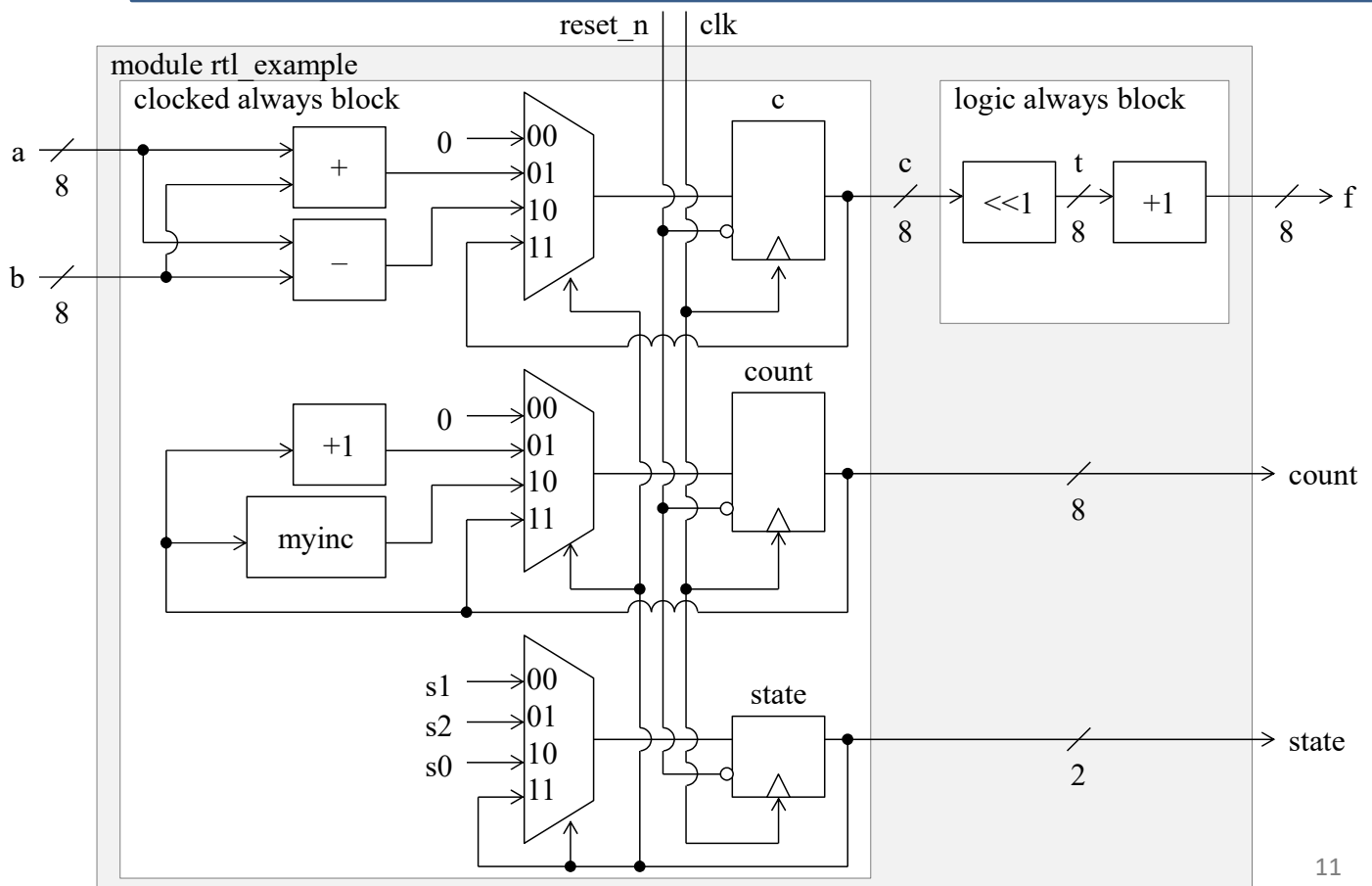

11

Fibonacci Calculator

- $F(0) = 0, F(1) = 1$
- $F(n) = F(n - 1) + F(n - 2)$, when $n > 1$
- Examples:


F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9
0	1	1	2	3	5	8	13	21	34

Fibonacci Calculator

- Design a FSM with the interface below.
- `input_s` is “n”, and `fibonacci_out` is “F(n)”.
- Wait in IDLE state until `begin_fibo`.
- When testbench sees `done==1`, it will check if `fibonacci_out==F(input_s)`.

```
module fibonacci_calculator (input logic clk, reset_n,  
                             input logic [4:0] input_s,  
                             input logic begin_fibo,  
                             output logic [15:0] fibo_out,  
                             output logic done);
```
 
```
...  
always_ff @(posedge clk, negedge reset_n)  
begin  
    ...  
end  
endmodule
```



13

Fibonacci Calculator

- Basic idea is to introduce 3 registers:

```
logic [4:0] counter;  
logic [15:0] R0, R1;
```
- Set loop counter to “n”

```
counter <= input_s;
```
- Repeat as long as counter is greater than 1 since we already know what `F(0)` and `F(1)` are:

```
counter <= counter - 1;  
R0 <= R0 + R1;  
R1 <= R0;
```
- Finally, set output to “F(n)”

```
done <= 1;  
fibo_out <= R0;
```

Fibonacci Calculator

```
module fibonacci_calculator (input logic clk, reset_n,  
                             input logic [4:0] input_s,  
                             input logic begin_fibo,  
                             output logic [15:0] fibo_out,  
                             output logic done);  
  
    enum logic [1:0] {IDLE=2'b00, COMPUTE=2'b01, DONE=2'b10} state;  
  
    logic [4:0] count;  
    logic [15:0] R0, R1;  
  
    always_ff @(posedge clk, negedge reset_n)  
    begin  
        if (!reset_n) begin  
            state <= IDLE;  
            done <= 0;  
        end else  
            case (state)  
                IDLE:  
                    if (begin_fibo) begin  
                        count <= input_s;  
                        R0 <= 1;  
                        R1 <= 0;  
                        state <= COMPUTE;  
                    end  
                COMPUTE:  
                    if (count > 1) begin  
                        count <= count - 1;  
                        R0 <= R0 + R1;  
                        R1 <= R0;  
                    end else begin  
                        state <= DONE;  
                        done <= 1;  
                        fibo_out <= R0;  
                    end  
                DONE:  
                    state <= IDLE;  
            endcase  
        end  
    end  
endmodule
```

in clocked always stmts,
D-FFs keep track of
previous value, so the
missing “else” part will
just keep “state” at
IDLE.

15

Fibonacci Calculator

- A three state solution is provided.
- Design it using only 2 states (or fewer) w/o creating flip-flops for `fibo_out` or `done`, and should work for $n \geq 1$. Hint: use “assign” statements for `fibo_out` and `done`.
- Use provided “tb_fibonacci_calculator.sv” to verify your design using ModelSim.
- Synthesize your 2-state “fibonacci_calculator.sv” design using Quartus.

16

Fibonacci Calculator: 2 States

```
module fibonacci_calculator (...);

    enum logic {IDLE=1'b0, COMPUTE=1'b1} state;

    logic [4:0] count;
    logic [15:0] R0, R1;

    assign done = ...; // no FF will be generated
    assign fibo_out = ...; // no FF will be generated

    // just update count, R0, R1, state in always_ff
    always_ff @(posedge clk, negedge reset_n)
    begin
        if (!reset_n)
            ...
        else case (state)
            IDLE:
                ...
            COMPUTE:
                ...
        endcase
    end
endmodule
```