

# Lecture 3: Continuation of SystemVerilog

## Last Lecture

- Talked about combinational logic always statements. e.g.,

```
module ex2(input logic a, b, c,  
          output logic f);
```

```
    logic t; // internal signal
```

```
    always_comb
```

```
    begin
```

```
        t = a & b;
```

```
        f = t | c;
```

```
    end
```

```
endmodule
```

should use “=” (called “**blocking**” assignment) in comb. logic always statements. RHS just takes output from the previous equation.

The order of statements matters!

# This Lecture

- Talk about “**clocked always statements**”, which generate combinational logic gates **and flip-flops**
- Unfortunately, SystemVerilog **does not** have well-defined semantics for describing flip-flops and finite state machines (FSMs)
- Instead, SystemVerilog relies on **idioms** to describe flip-flops and FSMs (i.e., the use of coding templates that synthesis tools will interpret to mean flip-flops and FSMs)
- If you do not follow these “templates”, your code may still simulate correctly, but may produce incorrect hardware

3

## D Flip-Flop

```
module flop(input logic      clk,  
            input logic [3:0] d,  
            output logic [3:0] q);
```

```
    always_ff @(posedge clk)
```

```
        q <= d;                                // pronounced “q gets d”
```

```
endmodule
```

- Verilog calls “<=” a “**non-blocking**” assignment.
- It means “**wait until next clk tick**” **before** updating “q”
- This is why synthesis will produce a positive edge-triggered D-FF
- “always\_ff” indicates that this is a “clocked always statement”



# Resettable D Flip-Flop

```
module flopr(input  logic      clk,
             input  logic      reset,
             input  logic [3:0] d,
             output logic [3:0] q);
```


```
// synchronous reset
```

```
always_ff @(posedge clk)
  if (reset) q <= 4'b0;
  else      q <= d;
```

```
endmodule
```

- Using this “template”, the “if” part specifies the “reset” condition, and the “else” part specifies what gets stored “q” after next clk tick

 - Synthesis tools will recognize this “template”



Slide derived from slides by Harris & Harris from their book

5

# Resettable D Flip-Flop


```
module flopr(input  logic      clk,
             input  logic      reset,
             input  logic [3:0] d,
             output logic [3:0] q);
```

```
// asynchronous reset
```

```
always_ff @(posedge clk, posedge reset)
  if (reset) q <= 4'b0;
  else      q <= d;
```

```
endmodule
```

 - By specifying the “reset” signal here, synthesis tools will understand the **if-then-else** template matches to an asynchronously resettable D-FF



- Again this works because synthesis tools recognize this template.

Slide derived from slides by Harris & Harris from their book

6

# Resettable D Flip-Flop

```
module flopr_n(input  logic      clk,
               input  logic      reset_n,
               input  logic [3:0] d,
               output logic [3:0] q);
```


```
    // asynchronous reset
```

```
    always_ff @(posedge clk, negedge reset_n)
```

```
        if (!reset_n) q <= 4'b0;
```

```
        else          q <= d;
```

```
endmodule
```

 

- By specifying the “negedge reset\_n” signal here, synthesis tools will asynchronously resettable D-FFs that are reset on the “falling” edge of reset\_n

- The template requires the if-then-else to use

if (!reset\_n) ... else ....

Slide derived from slides by Harris & Harris from their book

7

# Creating logic gates + FFs

```
module ex4(input  logic clk,
           input  logic t, c,
           output logic f);
```

```
    always_ff @(posedge clk)
```


```
    begin
```

```
        f <= t & c;
```

```
    end
```

```
endmodule
```

 - Positive edge triggered register (D-FF) produced for “f”.
- “<=” means LHS stores “new” value after next clk tick.




8

# Clocked always statements

```
module ex5(input  logic clk,
           input  logic a, b, c,
           output logic f);
```

```
    logic t;
    always_ff @(posedge clk)
    begin
```
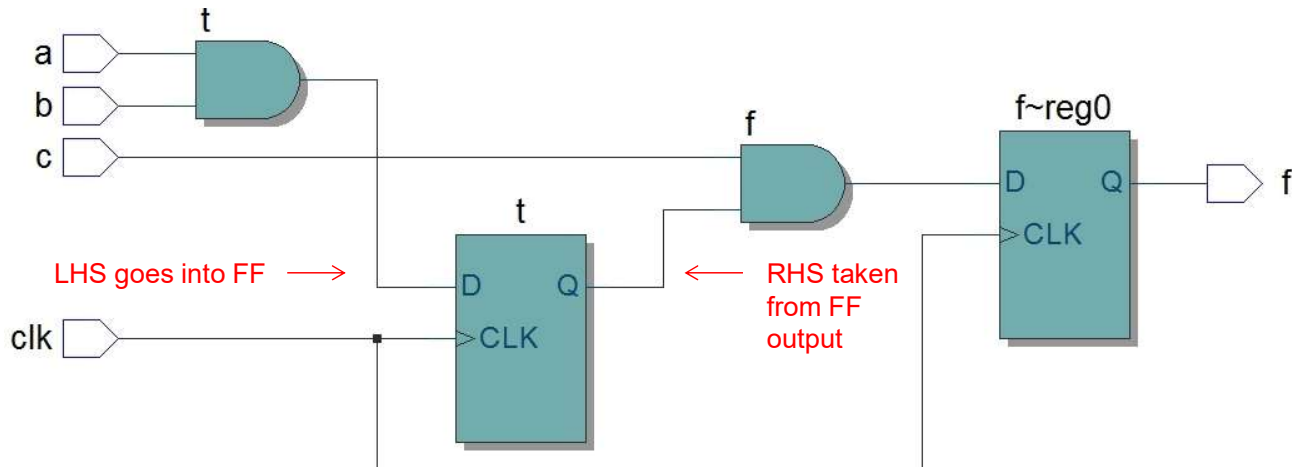
```
        t <= a & b;  ← LHS stores output of AND-gate to "t" register
        f <= t & c;  ← RHS reads from "t" register
    end
endmodule
```



9

# Clocked always statements

```
module ex6(input  logic clk, reset_n, a, b, c,
           output logic f);
```

```
    logic t;
    always_ff @ (posedge clk, negedge reset_n)
    begin
```


```
        if (!reset_n) begin
            t <= 0;
            f <= 0;
        end else begin
            t <= a & b;
            f <= t & c;
        end
    end
endmodule
```

this if part specifies how registers should be initialized

Template specifies async reset edge-triggered D-FFs

**Positive** edge-triggered on "clk"

 Async reset **negative** edge on "reset\_n"



10

# Clocked always statements


```

module ex7 (input logic      clk, reset_n, op,
            input logic [3:0] x,
            output logic [3:0] dataout);
    always_ff @ (posedge clk, negedge reset_n)
    begin
        if (!reset_n)
            dataout <= 4'b0000;
        else
            if (op)
                dataout <= dataout + x;
            else
                dataout <= dataout - x;
    end
endmodule

```

this if part specifies how registers should be initialized

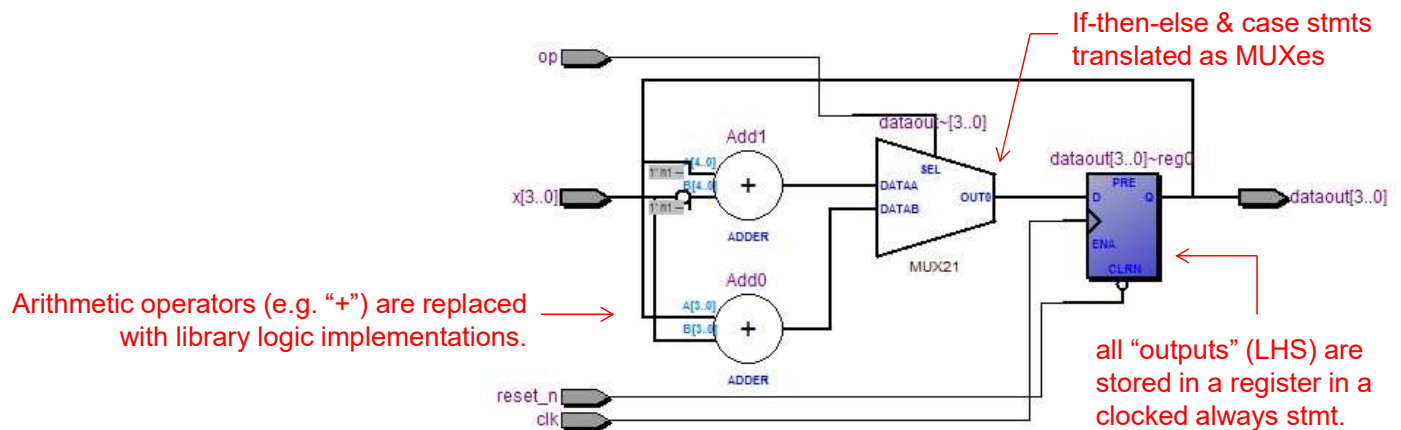- this else part specifies how registers should be updated at each cycle.
- all "outputs" (LHS) are stored in a register in a clocked always stmt. LHS specifies "new" value that will be stored after next clk tick.
- should use "<=" instead of "=", which means on the RHS, the value is the "current" value of the register.



# Clocked always statements

```

module ex8 (input logic clk, reset_n, op,
            input logic [3:0] x,
            output logic [3:0] dataout);
    logic [3:0] y, z;

```

```

    always_ff@(posedge clk,negedge reset_n)
    begin
        if (!reset_n)
            y <= 4'b0000;
        else
            if (op)
                y <= y + x;
            else
                y <= y - x;
    end

```


1<sup>st</sup> always stmt

```

    always_ff@(posedge clk,negedge reset_n)
    if (!reset_n) begin
        dataout <= 4'b0000;
        z <= 4'b0000;
    end else begin
        z <= y + 1;
        dataout <= dataout + z;
    end
endmodule

```

2<sup>nd</sup> always stmt

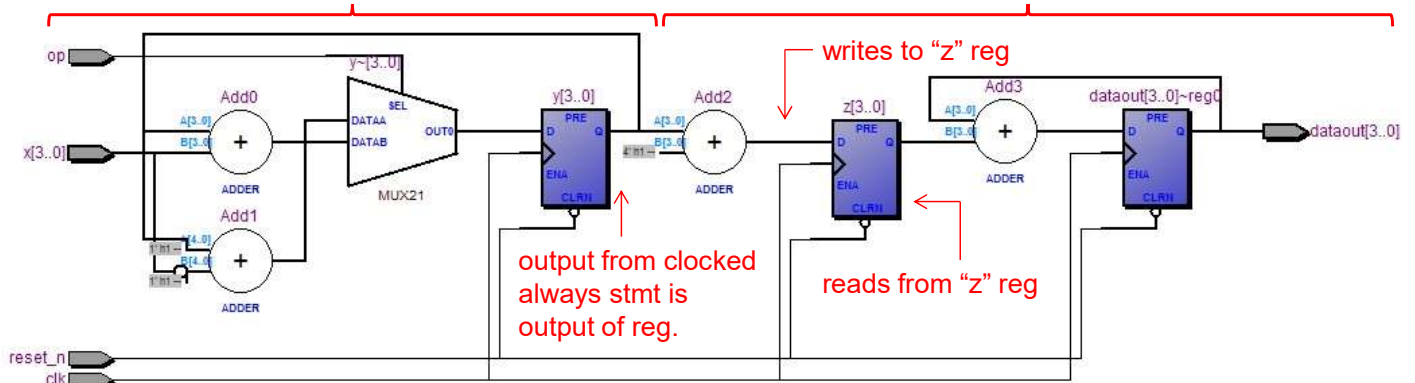

# Mixing statements


```

module ex9 (input logic clk, reset_n, op,
            input logic [3:0] x,
            output logic [3:0] dataout);
    logic [3:0] y, z;

    assign z = y + 1;
    assign dataout = z + 1;

    always_ff@(posedge clk, negedge reset_n)
    begin
        if (!reset_n)
            y <= 4'b0000;
        else
            if (op)
                y <= y + x;
            else
                y <= y - x;
        end
    end
endmodule

```

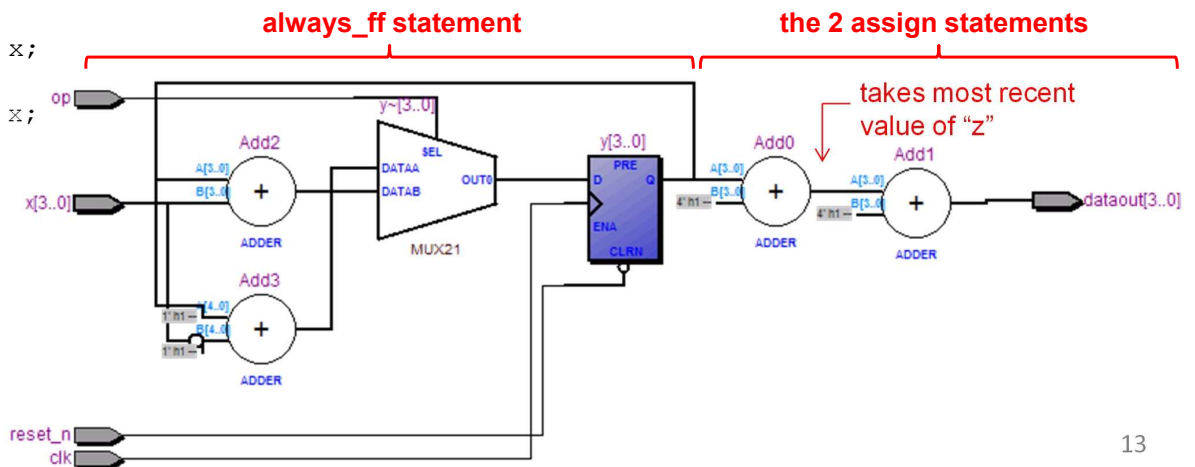

13

# Mixing statements

```

module ex10 (input logic clk, reset_n, op,
              input logic [3:0] x,
              output logic [3:0] dataout);
    logic [3:0] y, z;

```

same behavior as ex9, but using always\_comb instead of 2 assign statements

```

    always_comb
    begin
        z = y + 1;
        dataout = z + 1;
    end
endmodule


```

should use "=" in comb. logic always stmts. no reg. RHS just takes output from the previous eqn.

```

    always_ff@(posedge clk, negedge reset_n)
    begin
        if (!reset_n)
            y <= 4'b0000;
        else
            if (op)
                y <= y + x;
            else
                y <= y - x;
        end
    end
endmodule


```

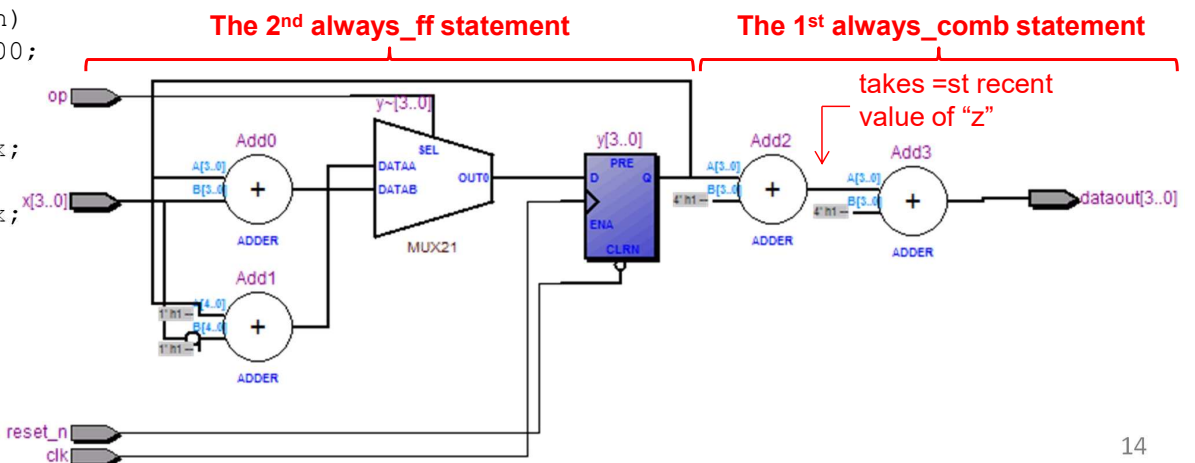

14
 
# Last Lecture: Divide by 3 FSM

- Output should be “1” every 3 clock cycles




The double circle indicates the reset state

Slide derived from slides by Harris & Harris from their book

15
 
## Finite State Machines (FSMs)

- A simple Moore machine looks like the following



Slide derived from slides by Harris & Harris from their book

16



# FSM Example in SystemVerilog

```
module divideby3FSM (input logic clk, reset_n,  
                    output logic q);  
  
    enum logic [1:0] {S0=2'b00, S1=2'b01, S2=2'b10} state; // declare states as enum  
  
    // next state logic and state register  
    always_ff @(posedge clk, negedge reset_n)  
    begin  
        if (!reset_n)  
            state <= S0;  
        else begin  
            case (state)  
                S0: state <= S1;  
                S1: state <= S2;  
                S2: state <= S0;  
            endcase  
        end  
    end  
  
    // output logic  
    assign q = (state == S0);  
endmodule
```

state transition graph is the same  
thing as a state transition table, which  
can be specify as a case statement

← output is "1" every clock cycles when we are in state S0